 


unsigned binary range: 0 to  $(2^n)-1$ ; 1's Complement: pos is 0 to  $2^{(n-1)}$  and to get neg is invert bits of pos 2's Complement range:  $-2^{(n-1)}$  to  $2^{(n-1)}-1$ ; **CMOS** uses both pMOS and nMOS; **NOT** gate: 2 transistors (pMOS on top, nMOS on bottom) → **AND/OR**: 6 transistors; **Two Level Logic**: **Sum of Products (Disjunctive) and Product of Sums (Conjunctive)**; **Boolean Algebra Properties**: Associative;  $(a \cdot b) \cdot c = a \cdot (b \cdot c)$ ,  $(a+b)+c=a+(b+c)$ ; Commutative:  $a \cdot b=b \cdot a$ ,  $a+b=b+a$ ; Distributive:  $a \cdot (b+c)=(a \cdot b)+(a \cdot c)$ ,  $a+(b \cdot c)=(a+b) \cdot (a+c)$ ; Identity:  $a \cdot 1=a$ ,  $a+0=a$ ; Complement:  $a \cdot a'=0$ ,  $a+a'=1$ ; Uniting Theorem:  $ab+a'b=b$ ,  $(a'+b)(a+b)=b$ ; Absorption Theorem:  $a+ab=a$ ,  $a(1+b)=a$ ; If we can prove a statement using laws of Boolean algebra true, then the dual of the statement is also true: swap  $(+, \cdot)$  and complement all 0's and 1's; Distributive OR:  $X + YZ \rightarrow (X+Y)(X+Z)$ ; Distributive AND:  $X \cdot YZ \rightarrow (X \cdot Y)(X \cdot Z)$ ; # of literals counts number of unique occurrences of variable **and** complement, # of variables is number of occurrences of literal, # pins = total # of input + output

**Complement**: variable with a "BAR" over it or ' after it  $\Rightarrow A'$ ; **Literal**: variable or its complement; **Implicant**: product of literals  $\Rightarrow ABC$ ; **Implicate**: sum of literals  $\Rightarrow (A+B+C)$ ; **Minterm/Maxterm**: implicant/implicate that **includes all the inputs**  $\Rightarrow f(A, B, C, D)=ABCD/(A'+B+C+D)$ ; **maxterm** is sum when 0, **minterm** is product when 1; SOP/POS minimizes number of implicants; **Canonical POS/SOP Form**: each term in SOP is minterm, each term in POS is maxterm → to turn canonical, for product multiple by 1 and add missing variable as  $(A+A')$  and for sum add 0 and add in missing variable as  $AA'$

**(UP) NAND; Consensus Theorem**: Given a pair of terms where one the variables appears as a true and complement, the consensus is formed by ANDing (or ORing) the remaining terms together  $(AB+A'C+BC \text{ and } (A+B)(A'+C)(B+C))$ : WORKS FOR GROUPS OF VARIABLES; USEFUL:  $A + A'B = A + B \Rightarrow$  you can show that adding the consensus term is equivalent to the original through boolean algebra, venn diagrams, or truth tables

Show  $AB + A'C + BC == AB + A'C$   
 $AB + A'C + BC$   
 $AB + A'C + 1BC$   
 $AB + A'C + (A+A')BC$   
 $AB + A'C + ABC + A'BC$




**Bubble Pushing**: pushing bubbles backward (from the output) or forward (from the inputs) changes the body of the gate from AND to OR or vice versa; **Shannon's**:  $f(x, \dots) = x \cdot f(1, \dots) + x' \cdot f(0, \dots) = (x+f(0, \dots))(x'+f(1, \dots)) \rightarrow$  can apply recursively to more than one term  $(f(x, y, \dots) = x \cdot y \cdot f(1, 1, \dots) + x' \cdot y \cdot f(0, 1, \dots) + x \cdot y' \cdot f(1, 0, \dots) + x' \cdot y' \cdot f(0, 0, \dots))$   
**NOR; Incompletely Specified Function**: Output does not matter in certain input cases  $\Rightarrow \Sigma m(1, 3, 4, 7) + \Sigma d(2, 5)$  means minterms 1, 3, 4, 7 are 1 and 2, 5 are X and rest are 0 while  $\Pi M(0, 6) \Pi d(2, 5)$  means maxterms 0, 6 are 0 and 2, 5 are X and the rest are 1 → if no unspecified, then sum of all minterms is logically equivalent to prod of all maxterms; **Minimal Two Level Logic**: For all expressions with minimum # of implicants/implicates, find the solution

with the minimum # of literals; **Karnaugh Map**  $\Rightarrow$  **Covers**: a term covers a minterm if that term evaluates to "1" when the minterms it covers evaluate to 1 (ab covers  $abc+abc'$ ); **prime implicant/implicate** - the largest implicant/implicate that covers a region of 1's; **essential prime implicant/implicate** - a prime implicant/implicate that is only prime implicant that includes at least one of its 1's; **Universal Gates**: any row on a truth table can be expressed with two logical operations, and/or with not and the entire truth table can be expressed with three logic operations: and, not or;  $\text{NOT}(A) = \text{NAND}(A, A) = \text{NOR}(A, A)$ ,  $\text{AND}(A, B) = \text{NAND}(\text{NAND}(A, B), \text{NAND}(A, B)) = \text{NOR}(\text{NOR}(A, A), \text{NOR}(B, B))$ ,  $\text{OR}(A, B) = \text{NAND}(\text{NAND}(A, A), \text{NAND}(B, B)) = \text{NOR}(\text{NOR}(A, B), \text{NOR}(A, B))$ ; **Bubble Pushing**: 1) to convert to NAND network: replace all AND gates with NAND (bubble output) and replace all OR gates with NAND (bubble inputs) and if bubble output drives bubble input, DONE else add inverter 2) to convert to NOR network: replace all OR gates with NOR (bubble output) and replace all AND gates with NOR (bubble input) and if bubble output drives bubble input, DONE else add inverter;

**Numbering K-map Example:**

abcd	00	01	11	10
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

**5 Variable K-map:**

 

**Multi-Output:**

$F_1 = \sum m(11, 12, 13, 14, 15) \quad F_2 = \sum m(3, 7, 11, 12, 13, 15) \quad F_3 = \sum m(3, 7, 12, 13, 14, 15)$

$F_1 = AB + ACD$

$F_2 = ABC' + CD$

$F_3 = AB + A'CD$

9 gates

$F_1 = ABC' + ACD + ABC \quad F_2 = ABC' + ACD + A'CD \quad F_3 = ABC' + A'CD + ABC$

7 gates

# Quine-McCluskey:

- cd' covers 2, 6, 10, 14

$$f(a,b,c,d) = \sum m(0,1,2,5,6,7,8,9,10,14)$$

0	0000	✓
1	0001	✓
2	0010	✓
8	1000	✓
5	0101	✓
6	0110	✓
9	1001	✓
10	1010	✓
7	0111	✓
14	1110	✓

		0	1	2	5	6	7	8	9	10	14
0,1,8,9	b'c'	x	x					x	x		
0,2,8,10	b'd'	x		x				x		x	
2,6,10,14	cd'			x		x				x	x
1,5	a'c'd		x		x						
5,7	a'bd				x	x					
6,7	a'bc					x	x				

$$a'c'd (5) \parallel a'bd (7) \\ a'bc (7)$$

If given POS and want to find minimal two level, apply negate on whole thing, do Quine on SOP, then negate that result

XOR – eXclusive OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

$A \oplus B$   
 $A \otimes B$   
 $\Rightarrow A \wedge B$

XNOR – eXclusive NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$M \times x$   
 $o x p r$

Multiplexer

S	A	B	Y
0	0	?	0
0	1	?	1
1	?	0	0
1	?	1	1

$Y = S ? B : A$

Tri State

E	A	Y
0	0	z
1	0	0
1	1	1

$Y = E ? A : z$

XOR from 2:1 MUX

Start with TT

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Write the equation

$y =$

Convert to Gates

# of transistors 10

$s = A$

$B$

$i1$

$i0$

$Y$

Pass Transistor Logic

- Use transistor to pass a value instead of a "1" (Vdd) or "0" (Vss).
- NMOS good at passing 0V, bad at passing Vdd
- PMOS good as passing Vdd, bad at passing 0V

10 transistors

Combine NMOS and PMOS

Buffer/Inverter at Output (Why?)

$V_{dd}$

$0V$

$V_{dd} - V_t$

$0V + V_t$

DECODER

E	i1	i0	o0	o1	o2	o3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

$i[0]$

$i[1]$

$E$

$q[0]$

$q[1]$

$q[2]$

$q[3]$

ENCODER

i0	i1	i2	i3	o1	o0
0	0	0	0	x	x
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$i[0]$

$i[1]$

$i[2]$

$i[3]$

$q[0]$

$q[1]$

XOR can be used for parity check and detect odd number of bit errors

Noise Margin

High noise margin :  $V_{oh} - V_{ih}$

Low noise margin :  $V_{il} - V_{ol}$

If  $V_{oh}$  falls below  $V_{ih}$  then reliable sampling of "H" is in doubt

If  $V_{ol}$  rises above  $V_{il}$  then reliable sampling of "L" is in doubt

$t_{cd} = 2.0 + 3 = 2.3$

$t_{pd} = 2.0 + 2.0 + 3 = 4.3$

A. 2.3, 3.8

B. 2.3, 4.3

C. 1.5, 4.0

D. 2.3, 5.0

E. None of the above

Gate	Max Tpd (FO4 INV delays)
ND2	1.5
ND3	2.0
NR2	2.0