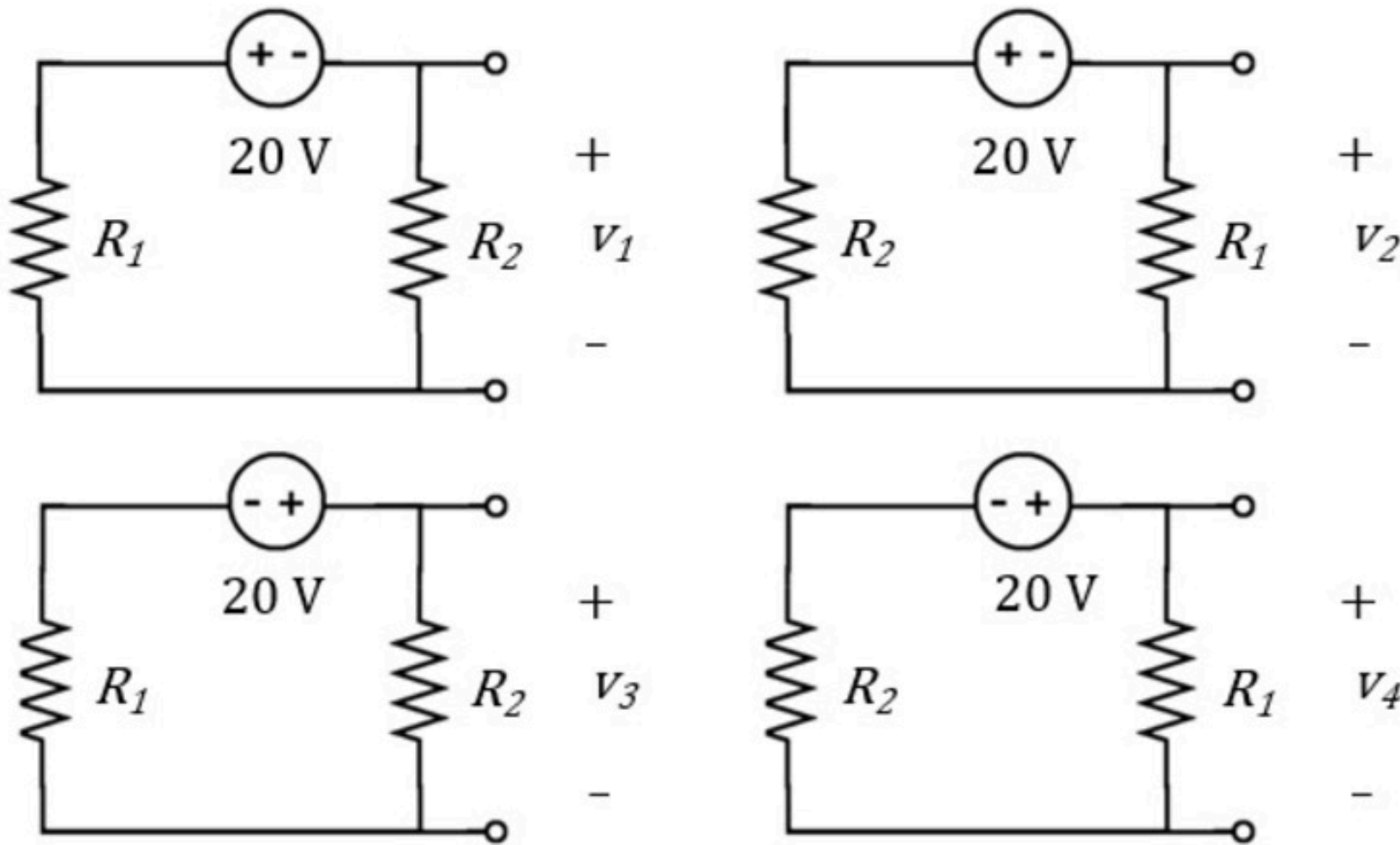


Basic analysis 004

Problem has been graded.

Determine the voltages v_1 , v_2 , v_3 and v_4



Given Variables:

R_1 : 4 ohm

R_2 : 6 ohm

Calculate the following:

v_1 (V) :

v_2 (V) :

v_3 (V) :

v_4 (V) :

Hint: Voltage divider and mind the signs.