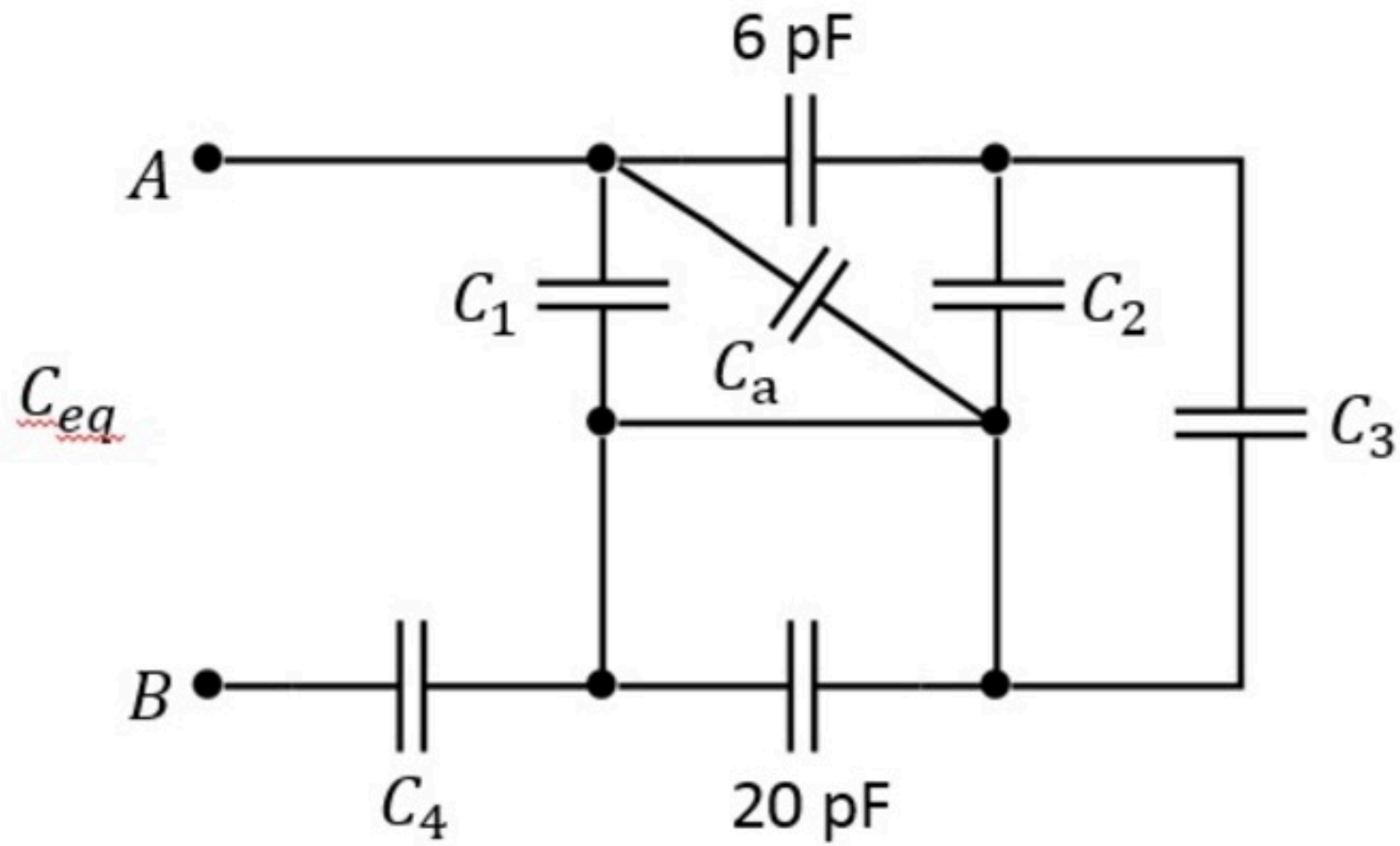


Capacitors Inductors 002

Problem has been graded.

Given C_{eq} between points A and B , what is C_a ?



Given Variables:

C_1 : 2 pF

C_2 : 2 pF

C_3 : 4 pF



C_4 : 6 pF

C_{eq} : 3 pF

Calculate the following:

C_a (pF) :

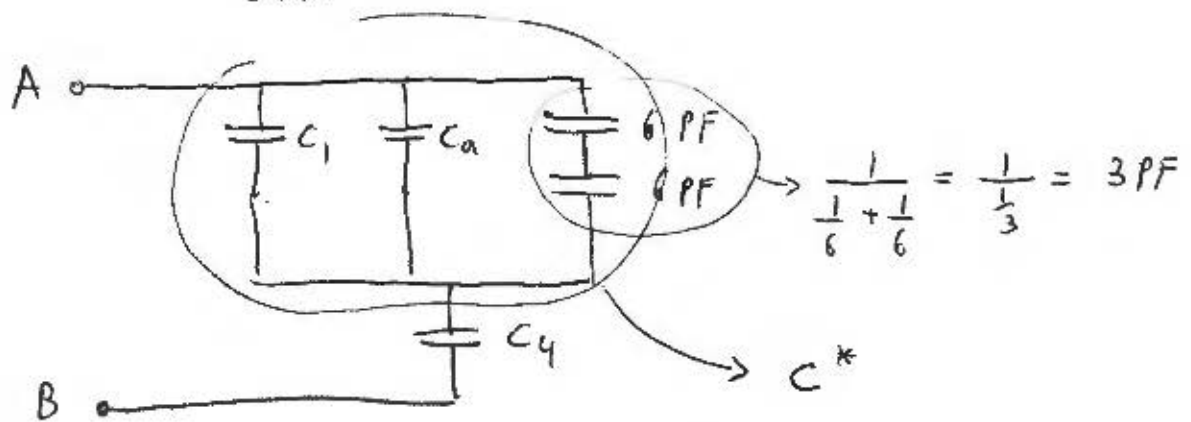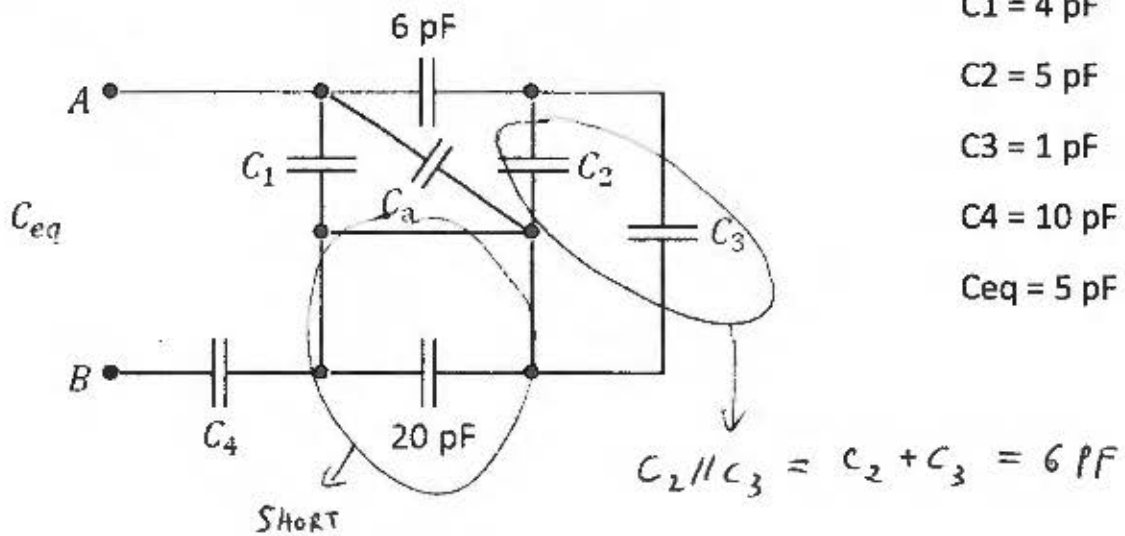Given C_{eq} between points A and B, what is C_a ?



$$\frac{1}{C_{eq}} = \frac{1}{C_4} + \frac{1}{C^*} \Rightarrow \frac{1}{C^*} = \frac{1}{5} - \frac{1}{10} = \frac{1}{10} \Rightarrow C^* = 10 \text{ pF}$$

$$C^* = C_1 + C_a + 3 \Rightarrow C_a = 10 - 4 - 3 = 3 \text{ pF}$$

$$\boxed{C_a = 3 \text{ pF}}$$