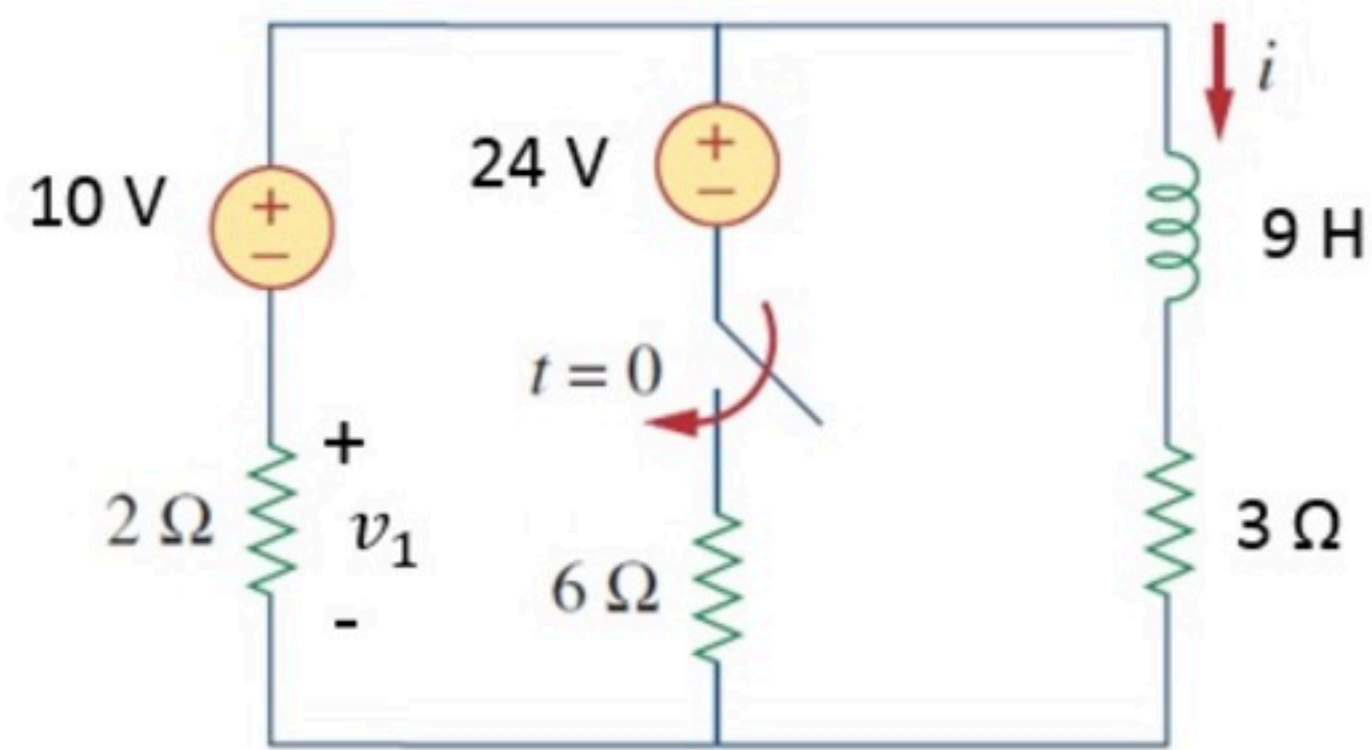


# PP First order circuits 007

Unlimited Attempts.

The switch has been open for a long time.  
At time  $t = 0$ , the switch is closed.

Find  $v_1(t) = D$  for  $t = 0^-$   
 $= A \cdot e^{-t/\tau} + B$  for  $t > 0$



Given Variables:

...

Calculate the following:

D (V) :

-4



A (V) :

1.5



B (V) :

-1



$\tau$  (s) :

2



Hint: First find the inductor current just before the switch opens.