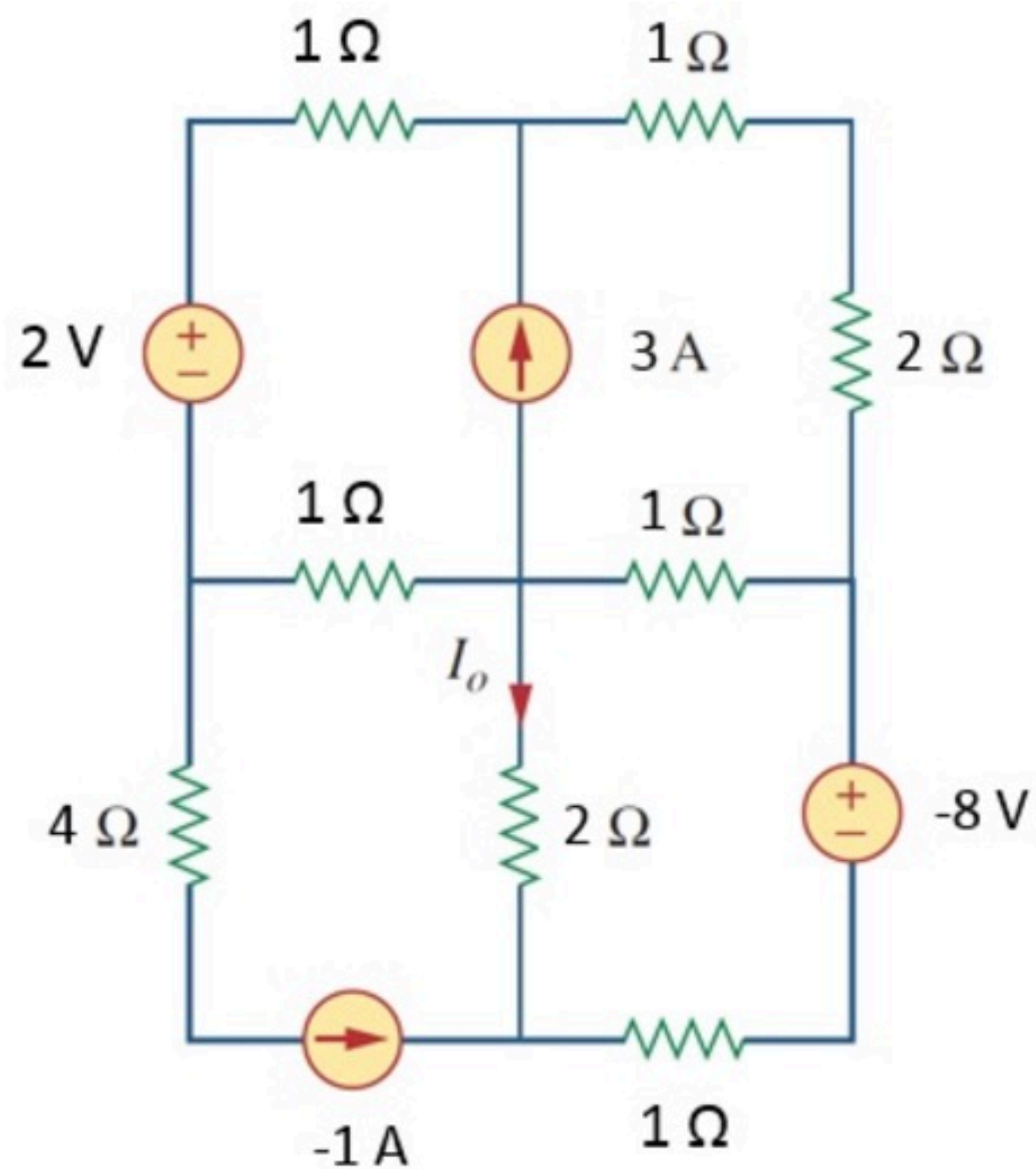


PP Nodal Mesh 013

Unlimited Attempts.

Find the current I_o . Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

I_o (A) :

-2

Hint: Use a supermesh

