

Name

PID

UNIVERSITY OF CALIFORNIA, SAN DIEGO

Electrical and Computer Engineering Department

ECE 65 – Fall 2022

Components and Circuits lab

Midterm Exam *Solutions*

Closed books, one one-sided cheat sheet, and calculators are allowed

Electronic devices are not allowed.

Please put all answers in the provided sheets.

Be sure to write your name and PID on **all pages**.

Please do not begin until told.

Show your work.

Good luck.

Problem 1. (12 points)

You will use the last digit of your PID to answer this question.

$V_1 = -1 \times$ the last digit of your PID. (The unit is Volts)

$V_2 = -2 \times$ the last digit of your PID. (The unit is Volts)

For example, if your PID is A14126523, solve this problem with $V_1 = -3 \text{ V}$, and $V_2 = -6 \text{ V}$.

If the last digit of your PID is zero, solve this problem with $V_1 = -2 \text{ V}$, and $V_2 = -4 \text{ V}$.

- a) Design a diode waveform shaping circuit such that the amplitude of its output voltage signal is always between V_1 and V_2 . This means

$$V_2 \leq \text{amplitude of output voltage} \leq V_1$$


- b) Parametrically solve your designed circuit.

- Find the transfer function of the circuit.
- Draw the transfer function graph.

Assume you have access to regular PN junction diodes ($V_{D0} = 0.7 \text{ V}$), Zener diodes (any desired V_Z), and other circuit elements.

You must use Zener diode(s) in your design.

Show your work.

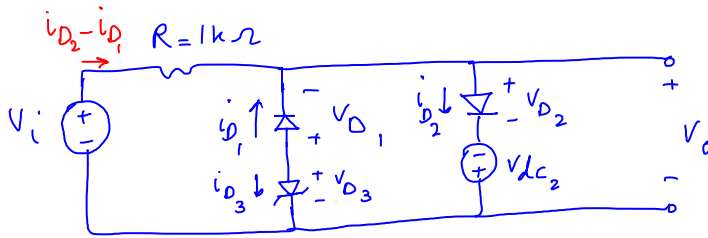

$$V_1 = -1V, V_2 = -2V$$

$$V_i = (i_{D2} - i_{D1}) \times 1k\Omega - V_{D1} + V_{D3}$$

$$V_o = -V_{D1} + V_{D3}$$

$$\text{Also, } V_i = (i_{D2} - i_{D1}) \times 1k\Omega + V_{D2} - V_{dc2}$$

$$\text{Also, } V_o = V_{D2} - V_{dc2}$$

Case 1: D_1 is ON and D_2 off and D_3 in Zener

$$V_{D1} = V_{D0} = 0.7V, \quad i_{D1} \geq 0, \quad V_{D2} < V_{D0}, \quad i_{D2} = 0$$


$$V_{D3} = -V_Z, \quad i_{D3} \leq 0$$

We want $V_o = -2V$ when D_1 conducts.

$$V_o = -0.7V - V_{Z1} = -2 \rightarrow V_{Z1} = 1.3V$$

$$V_i = -i_{D1} \times 1k\Omega - 0.7V - 1.3$$
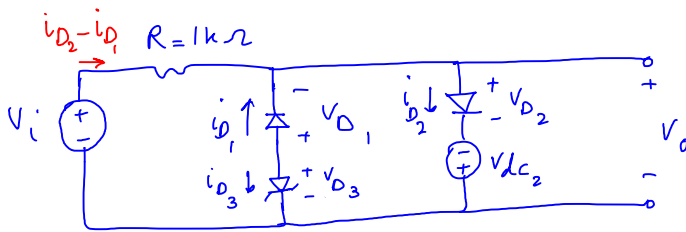
$$i_{D1} = \frac{-V_i - 0.7 - 1.3}{1k\Omega} \geq 0 \rightarrow V_i \leq -2V$$



$$V_i = (i_{D_2} - i_{D_1}) \times 1k\Omega - V_{D_1} + V_{D_3}$$

$$V_o = -V_{D_1} + V_{D_3}$$

$$\text{Also, } V_i = (i_{D_2} - i_{D_1}) \times 1k\Omega + V_{D_2} - V_{dc_2}$$

$$\text{Also, } V_o = V_{D_2} - V_{dc_2}$$

Case 2 D_1 and D_3 are off and D_2 is ON

$$V_{D_2} = V_{D_0} = 0.7V, \quad i_{D_2} \geq 0, \quad V_{D_1} < V_{D_0}, \quad i_{D_1} = 0$$

$$-V_{D_2} < V_{D_3} < V_{D_0}, \quad i_{D_3} = 0$$

We want $V_o = -1$ when D_2 conducts.

$$V_o = V_{D_0} - V_{dc_2} = 0.7 - V_{dc_2} = -1V$$

$$\Rightarrow V_{dc_2} = 1.7V$$


$$V_i = 1k\Omega \times i_{D_2} + V_{D_2} - V_{dc_2}$$

$$V_i = 1k\Omega \times i_{D_2} + 0.7V - 1.7V$$

$$i_{D_2} = \frac{V_i + 1V}{1k\Omega} \geq 0 \rightarrow V_i \geq -1V$$

Name

PID

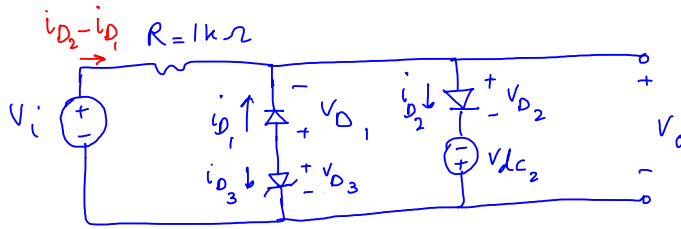

$$V_1 = -1 \text{ V}, \quad V_2 = -2 \text{ V}$$

$$V_i = (i_{D2} - i_{D1}) \times 1k\Omega - V_{D1} + V_{D3}$$

$$V_o = -V_{D1} + V_{D3}$$

$$\text{Also, } V_i = (i_{D2} - i_{D1}) \times 1k\Omega + V_{D2} - V_{dc2}$$

$$\text{Also, } V_o = V_{D2} - V_{dc2}$$

Case 3 D_1 and D_2 and D_3 are off

$$V_{D2} < 0.7 \text{ V}, \quad i_{D2} = 0, \quad V_{D1} < V_{D0}, \quad i_{D1} = 0, \quad -V_2 < V_{D3} < V_{D0}, \quad i_{D3} = 0$$

$$V_i = (i_{D2} - i_{D1}) \times 1k\Omega - V_{D1} + V_{D3} = -V_{D1} + V_{D3}$$

$$-\infty < V_{D1} < 0.7 \rightarrow -0.7 < -V_{D1} < \infty$$

$$-V_2 < V_{D3} < 0.7$$


$$-V_2 - 0.7 < V_{D3} - V_{D1} < \infty \rightarrow V_i = V_{D3} - V_{D1} > -V_2 - 0.7 \text{ V}$$

We need $V_i > -2 \text{ V}$ for this case \Rightarrow

$$-V_2 - 0.7 = -2 \rightarrow V_2 = 1.3 \text{ V}$$

Name

PID

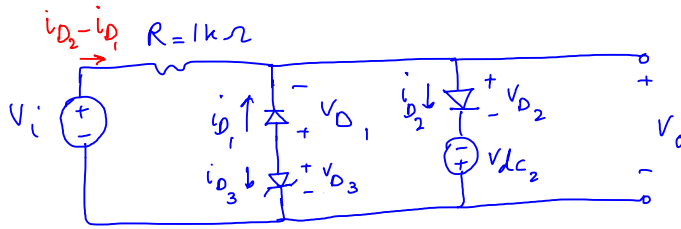

$$V_1 = -1 \text{ V}, \quad V_2 = -2 \text{ V}$$

Case 3

$$V_i > -2 \text{ V} \quad \text{and}$$


$$V_i = (i_{D2} - i_{D1}) \times 1 \text{ k}\Omega + V_{D2} - V_{dc2} = V_{D2} - 1.7 \text{ V}$$

$$V_{D2} = V_i + 1.7 \text{ V} < 0.7 \quad \rightarrow \quad V_i < -1 \text{ V}$$

$$V_i < -1 \text{ V} \quad \text{and} \quad V_i > -2 \text{ V} \quad \rightarrow \quad -2 < V_i < -1$$


$$V_o = V_i$$

$$\left\{ \begin{array}{ll} V_i \geq -1 \text{ V} & V_o = -1 \\ -2 < V_i < -1 & V_o = V_i \\ V_i \leq -2 \text{ V} & V_o = -2 \text{ V} \end{array} \right.$$

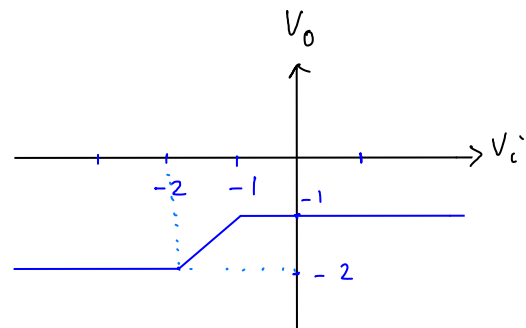

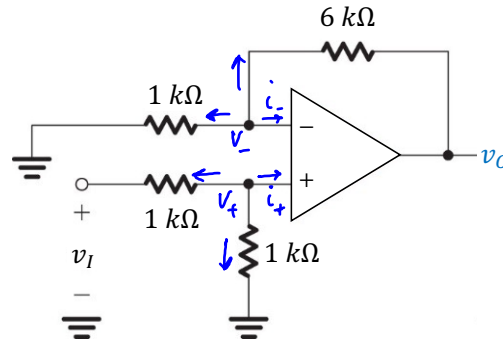Problem 2. (5 points)

Assuming an ideal op-amp with $V_{sat} = \pm 15V$ in the below circuit, find (derive) an expression for the voltage gain.



Show your work.

ideal op-amp and negative feedback : $V_+ = V_-$

also $i_+ = i_- = 0$

KCL at the + input terminal:

$$\frac{V_+}{1k\Omega} + \frac{V_+ - V_I}{1k\Omega} + i_+ = 0 \quad \rightarrow \quad \frac{2V_+}{1k\Omega} = \frac{V_I}{1k\Omega} \quad \rightarrow \quad V_+ = \frac{1}{2} V_I$$

KCL at the - input terminal:

$$\frac{V_-}{1k\Omega} + \frac{V_- - V_O}{6k\Omega} + i_- = 0 \quad \rightarrow \quad \frac{V_-}{1k\Omega} + \frac{V_-}{6k\Omega} - \frac{V_O}{6k\Omega} = 0$$

$$6V_- + V_- = V_O \quad \rightarrow \quad 7V_- = V_O$$

$$\rightarrow V_- = \frac{1}{7} V_O$$

Name

PID

$$\left\{ \begin{array}{l} V_+ = V_- \\ V_+ = \frac{1}{2} V_I \\ V_- = \frac{1}{7} V_o \end{array} \right. \Rightarrow \frac{1}{7} V_o = \frac{1}{2} V_I \Rightarrow V_o = \frac{7}{2} V_I$$

Name

PID