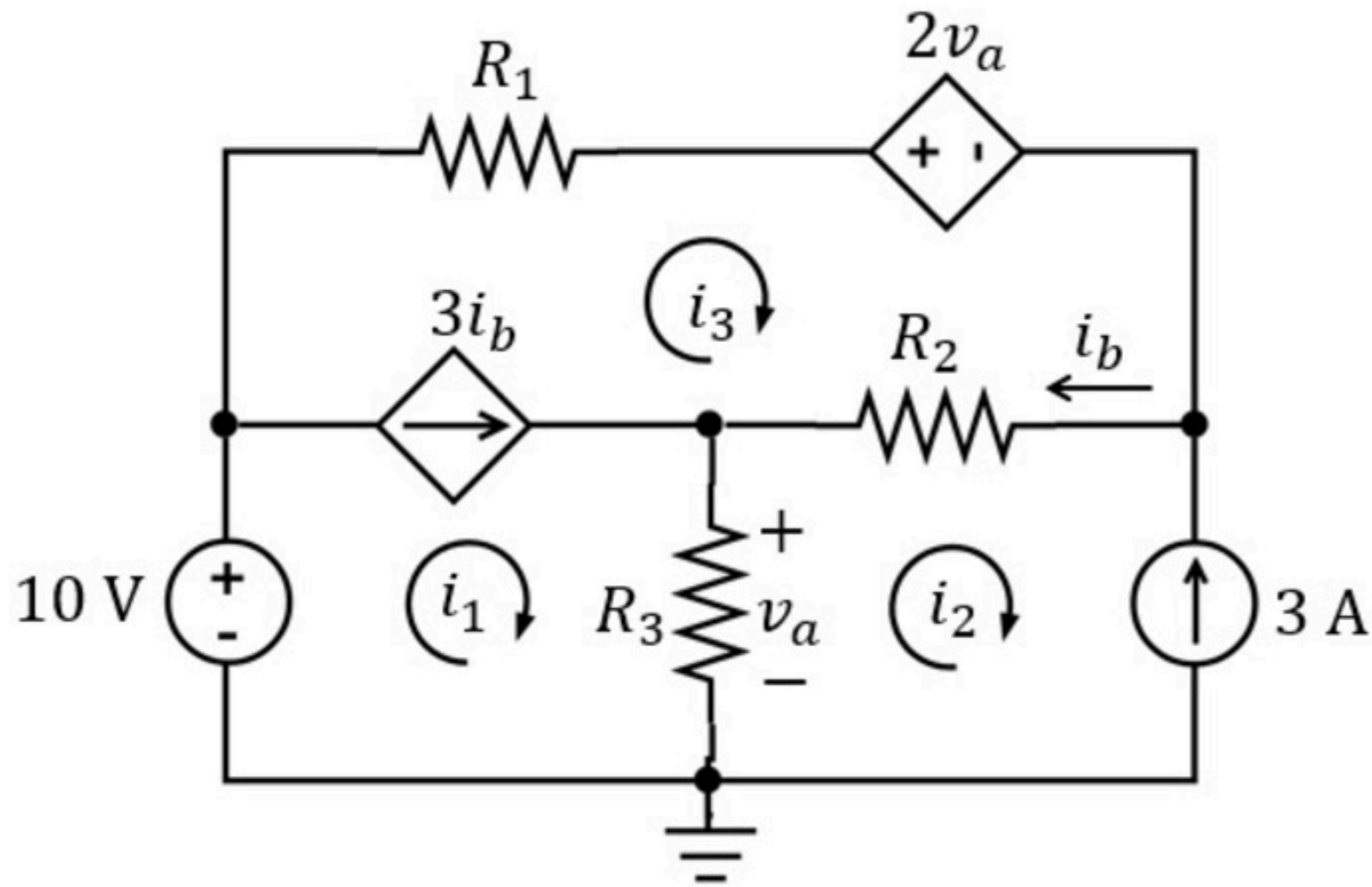


Nodal Mesh 010

Problem has been graded.

Find the mesh currents i_1 , i_2 , and i_3 .



Given Variables:

R_1 : 8 ohm

R_2 : 2 ohm

R_3 : 2 ohm

Calculate the following:

i_1 (A) :

i_2 (A) :

i_3 (A) :
