


PP Capacitors Inductors 003

Unlimited Attempts.

Below is the voltage across a 4 H inductor. The current through the inductor at time $t = 1$ s is -1 A.

What is the current i_1 through the inductor at time $t = 3$ s?

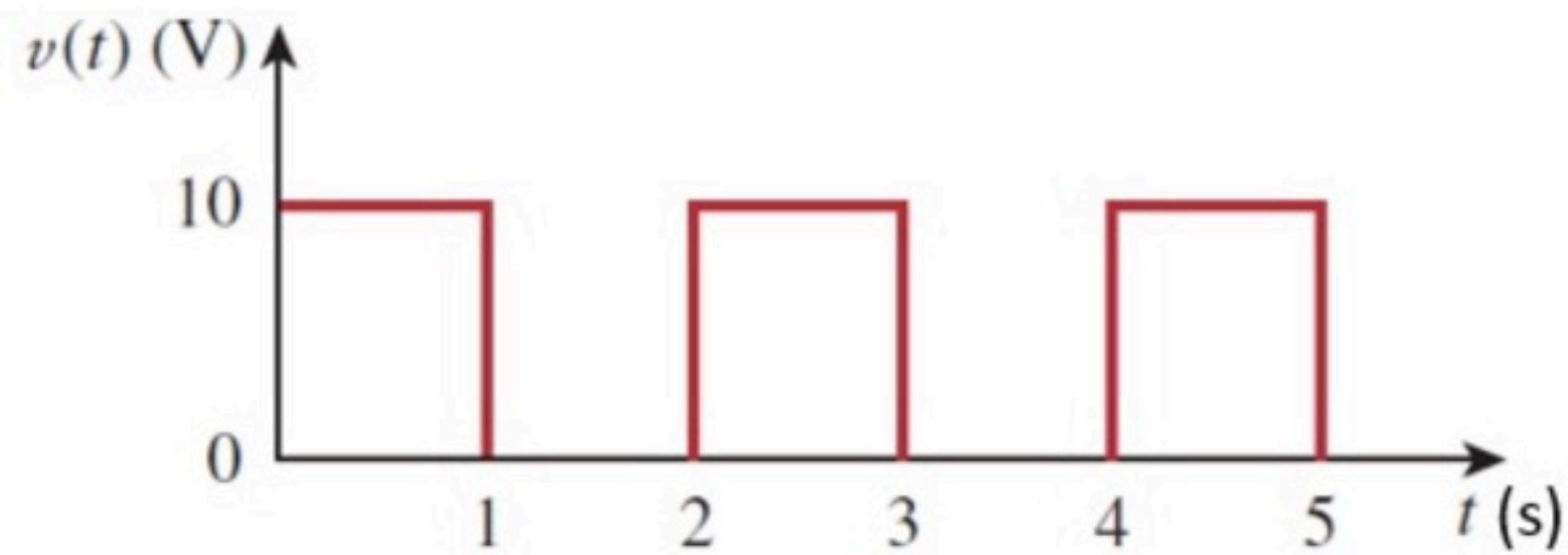What is the current i_2 through the inductor at time $t = 4.5$ s?



Given Variables:

...

Calculate the following:

i_1 (A) :

1.5



i_2 (A) :

2.75



Hint: Check initial condition.