
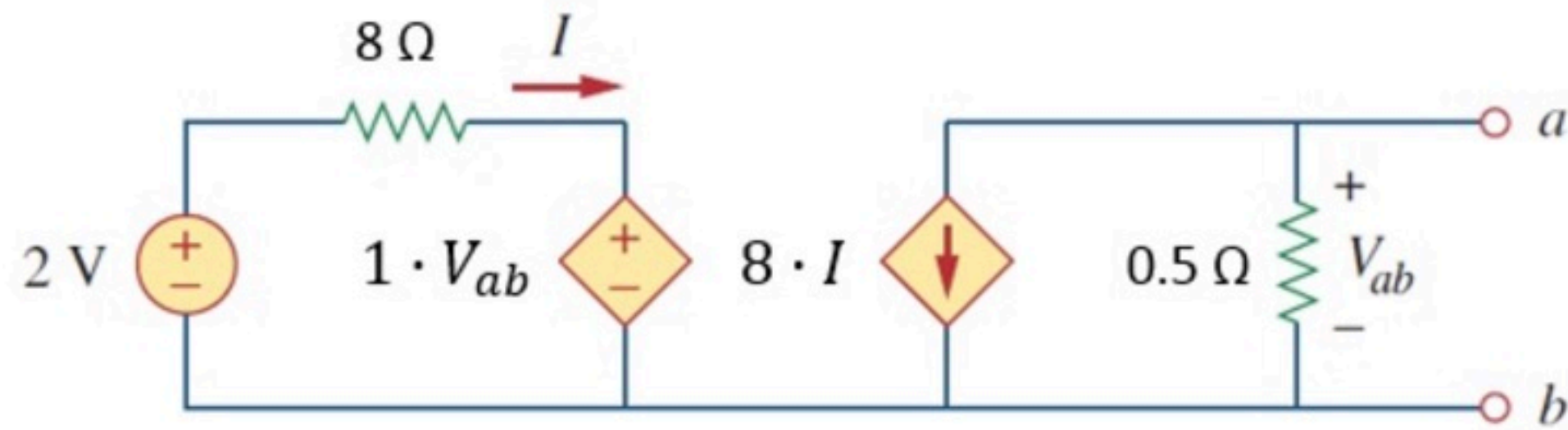


PP Circuit theorems 018

Unlimited Attempts.

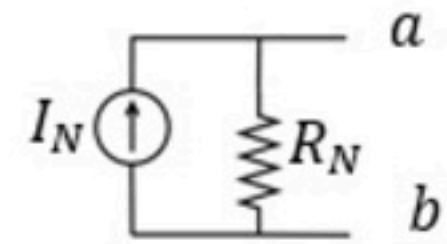Find the Norton equivalent model of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

I_N (A) :

-2



R_N (ohm) :

1



Hint: Find I_{sc} and V_{oc}