

ECE 35, Winter 2019

Quiz 3

/ 12

Last name

First + middle  
name(s)

PID


**Instructions:**

- Read each problem completely and thoroughly before beginning
- All calculations need to be done on these sheets
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit

(1) For  $t < 2$  s, the switch is closed, and you may assume the system has reached steady state.  
The switch opens at time  $t = 2$  s.


(a) Find  $i_a(2^-)$ . (1 point)

$i_a(2^-)$

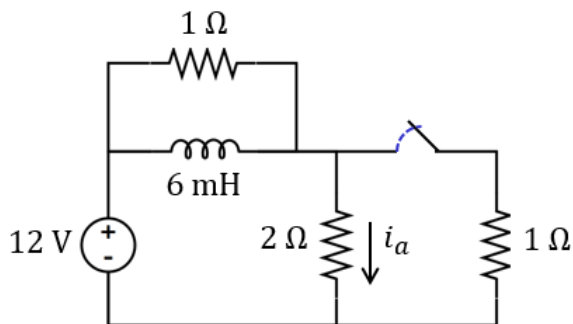

- (b) Find  $i_a(t)$  for  $t > 2$  s.  
Write the equation.  
(6 points)

$i_a(t)$

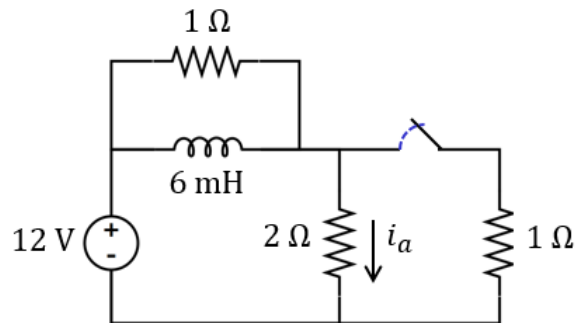

- (2) For  $t < 3$  s, the switch is open. The switch closes at time  $t = 3$  s. The switch opens again at time  $t = 5$  s.

At  $t = 0$ , the capacitor is charged to **1 V**.

(a) Find  $v_a(2$  s). (2 points)

$v_a(2$  s)

(b) Find  $v_a(3^+$  s). (1 point)

$v_a(3^+$  s)

(c) Find  $v_a(\infty)$ . (2 points)

$v_a(\infty)$

