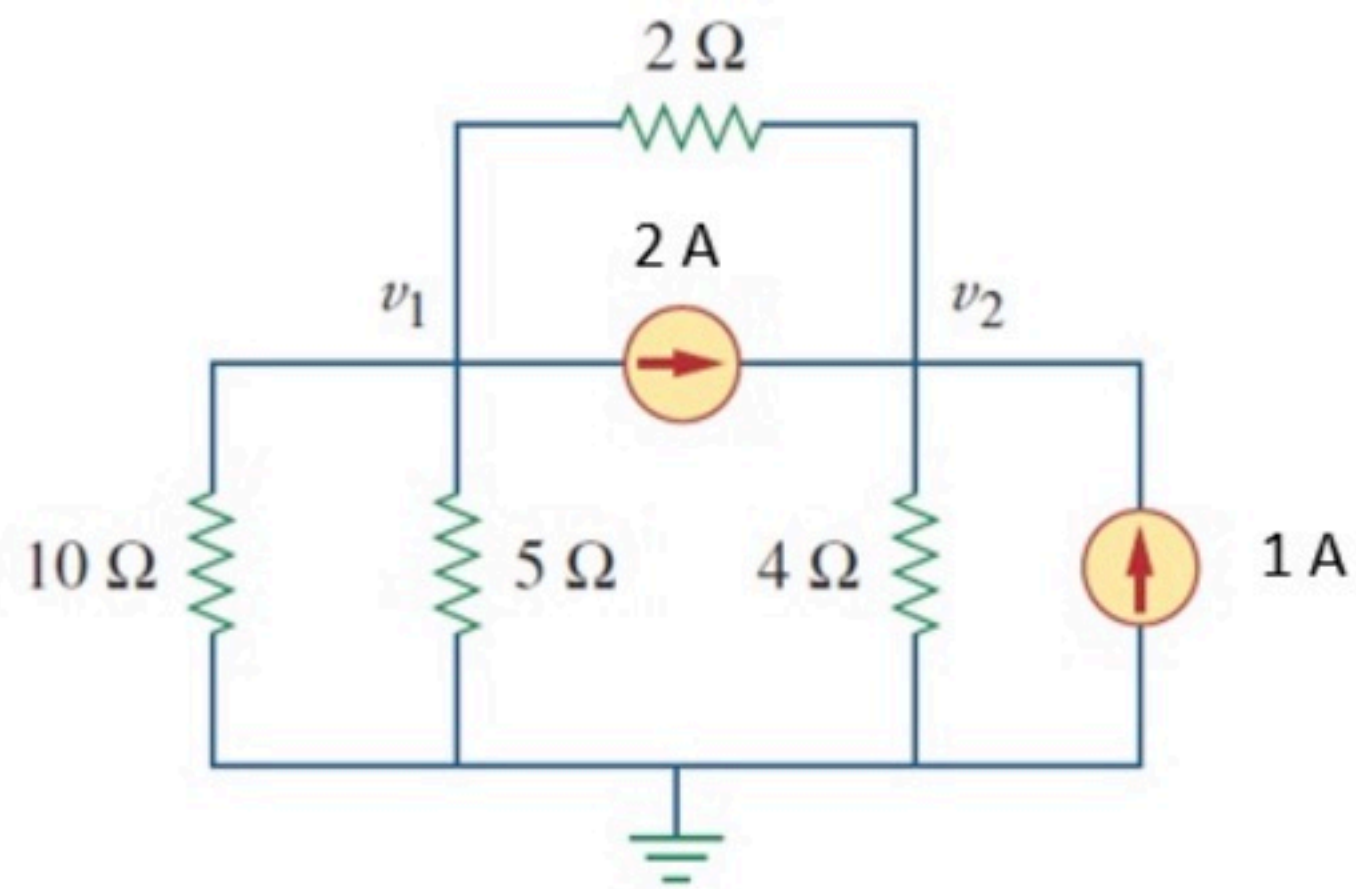


# PP - Nodal Mesh 001

Problem has been graded.

Find  $v_1$  and  $v_2$ . Solve using nodal analysis.

For extra practice: Afterwards solve again using mesh analysis.



Given Variables:

...

Calculate the following:

$v_1$  (V) :

0



$v_2$  (V) :

4



Hint: No supernodes