

ECE 65: Components & Circuits Lab

Lecture 15

CMOS introduction and transfer function


Reference notes: sections 4.4

Sedra & Smith (7th Ed): sections 5.1.8, 14.3


Saharnaz Baghdadchi

Course map

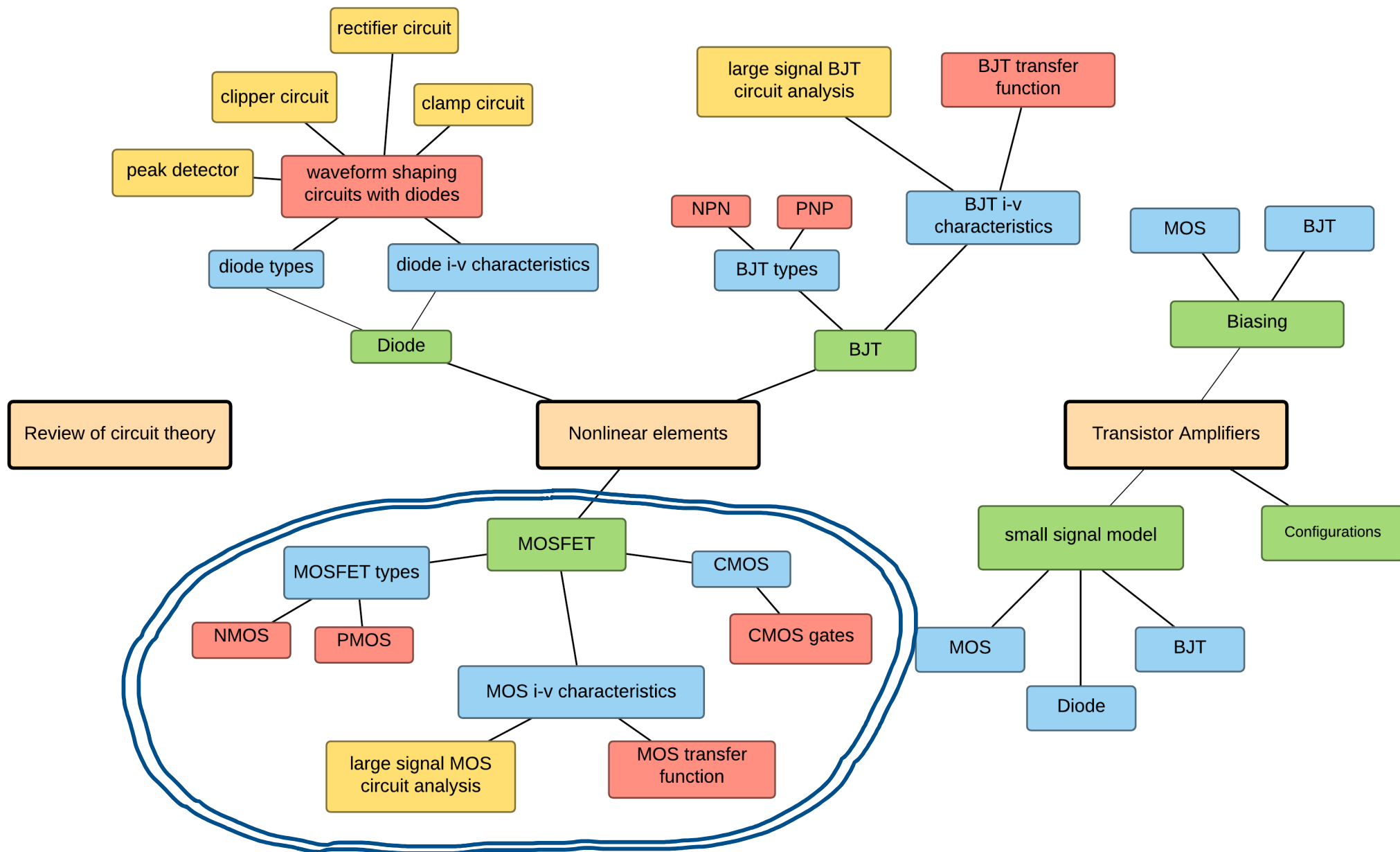4. Metal Oxide Semiconductor Field Effect Transistor (MOSFET)




 Complementary MOS (CMOS) is based on NMOS/PMOS pairs




CMOS Inverter

NMOS Inverter

 

Replace R_D with a PMOS

CMOS Inverter

 

Low State: 0, High State: V_{DD}

- Maximum signal swing

Zero “static” power dissipation ($i_D = 0$ in each state).

The case of $i_D = 0$

When MOS is in cut-off, $i_D = 0$. However, $i_D = 0$, does not mean that MOS is in cut-off.

Assume that a MOS is in triode.

MOS ON: $V_{OV} > 0$ and $v_{DS} \leq V_{OV}$

Condition of $i_D = 0$ gives:

$$i_D = 0.5\mu_n C_{ox} \frac{W}{L} [2V_{OV}v_{DS} - v_{DS}^2] = 0 \quad \rightarrow v_{DS} = 0$$

The case of $i_D = 0$

Assume that a MOS is in saturation.

MOS ON: $V_{OV} > 0$ and $v_{DS} \geq V_{OV}$

Condition of $i_D = 0$ gives:

$$i_D = 0.5\mu_n C_{ox} \frac{W}{L} (V_{OV})^2 = 0 \quad \rightarrow V_{OV} = 0 \quad \text{Not valid}$$

i_D can be zero if a MOS is in the triode mode **and** $v_{DS} = 0$.

Analysis of CMOS Inverter

Circuit equations:


GS1 KVL: $v_{GS1} = v_i$

GS2 KVL: $V_{DD} = v_{SG2} + v_i$

DS1&2 KVL: $V_{DD} = v_{SD2} + v_{DS1}$

KCL: $i_{D1} = i_{D2}$

$$v_o = v_{DS1} = V_{DD} - v_{SD2}$$

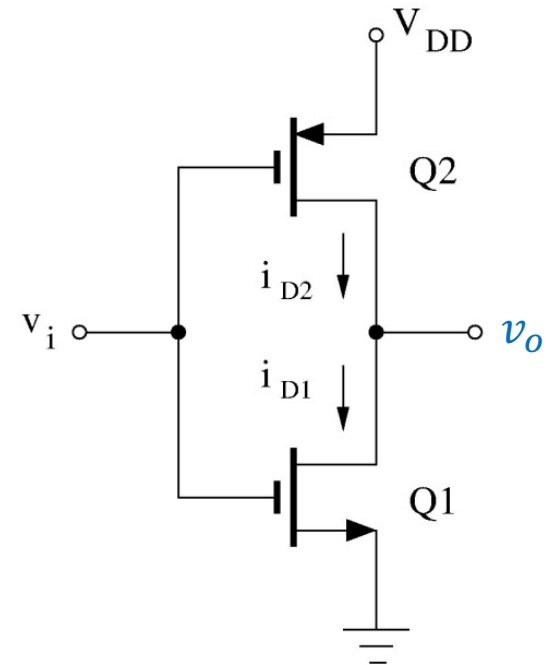

Analysis of CMOS Inverter


Case 1: $v_i = 0$

$$v_{GS1} = v_i < V_{tn} \rightarrow \text{Q1 is OFF} \rightarrow i_{D1} = 0$$

$$i_{D1} = 0 \rightarrow i_{D2} = 0$$

$$V_{DD} = v_{SG2} + v_i \rightarrow v_{SG2} = V_{DD} > |V_{tp}| \rightarrow \text{Q2 is ON}$$

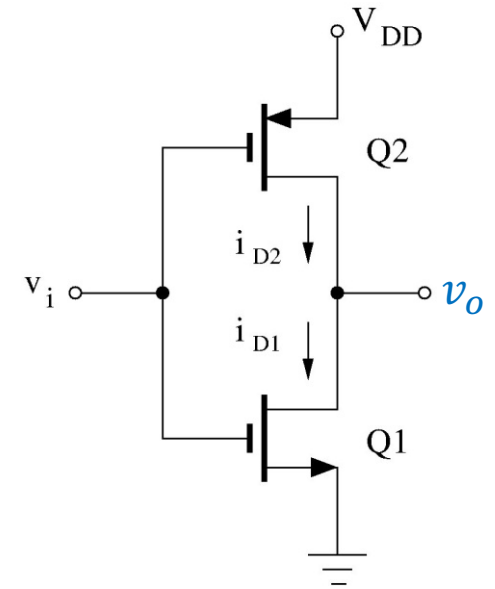Q2 is ON and $i_{D2} = 0 \rightarrow$ Q2 is in Triode and $v_{SD2} = 0$.



For $v_i = 0$, $v_o = V_{DD} - v_{SD2} = V_{DD}$, and $(i_{D1} = 0, i_{D2} = 0)$

Gate remains in this state as long as $v_i < V_{tn}$ (Q1 OFF)

Analysis of CMOS Inverter


Case 2: $v_i = V_{DD}$

$$v_{SG2} = V_{DD} - v_i = 0 < |V_{tp}| \rightarrow \text{Q2 is OFF} \rightarrow i_{D2} = 0$$

$$i_{D2} = 0 \rightarrow i_{D1} = 0$$

$$v_{GS1} = v_i = V_{DD} > V_{tn} \rightarrow \text{Q1 is ON}$$

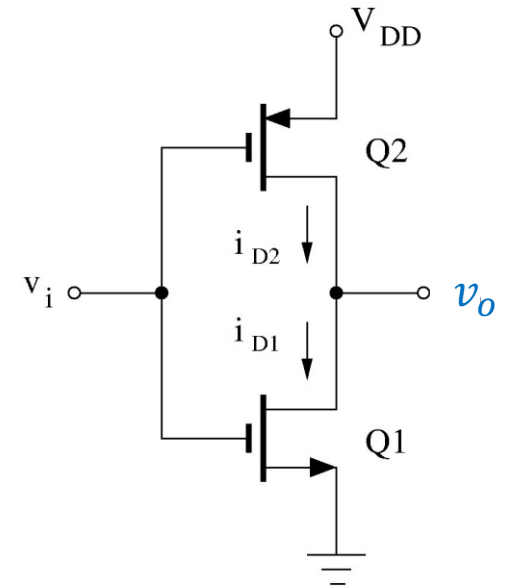Q1 is ON and $i_{D1} = 0 \rightarrow$ Q1 is in Triode and $v_{DS1} = 0$.




For $v_i = V_{DD}$, $v_o = v_{DS1} = 0$ and $(i_{D1} = 0, i_{D2} = 0)$

Gate remains in this state as long as $v_i > V_{DD} - |V_{tp}|$, (Q2 OFF)

CMOS transfer function example

In the below circuit, find v_i and i_D when both NMOS and PMOS are in saturation. What is the range of v_o in this case?

$$V_{tn} = |V_{tp}| = 1\text{ V}, k_n = k_p = 1\text{ mA/V}^2, \lambda = 0.$$

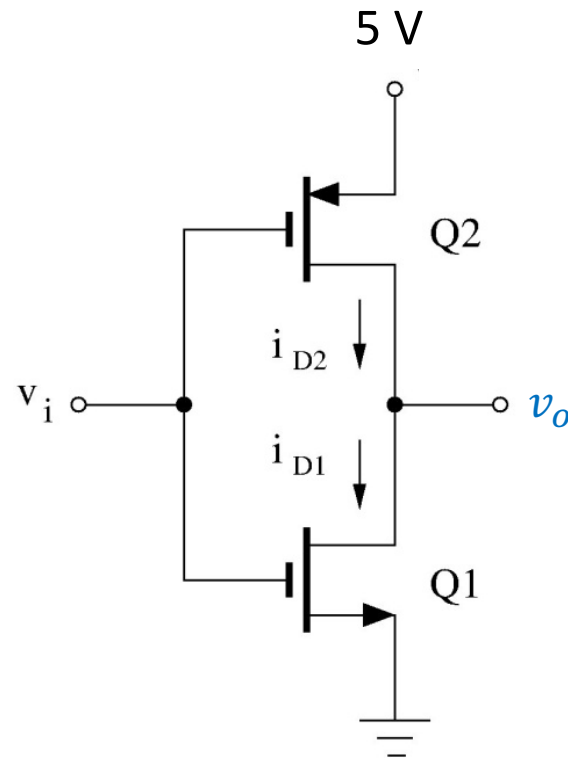

KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$

$$v_{SG2} = 5 - v_i$$

Let's first find the range of v_i for which Q1 or Q2 are off.

Q1 off: $v_{GS1} < V_{tn}$, $i_{D1} = 0$


$$V_{tn} = |V_{tp}| = 1\text{ V} \quad v_{GS1} = v_i \rightarrow v_i < 1\text{ V}$$

$$i_{D1} = i_{D2} = 0$$

$$v_{SG2} = 5 - v_i \rightarrow v_i = 5 - v_{SG2} < 1\text{ V} \rightarrow v_{SG2} > 4\text{ V}$$

$$v_{SG2} > |V_{tp}| \rightarrow \text{Q2 is ON}$$

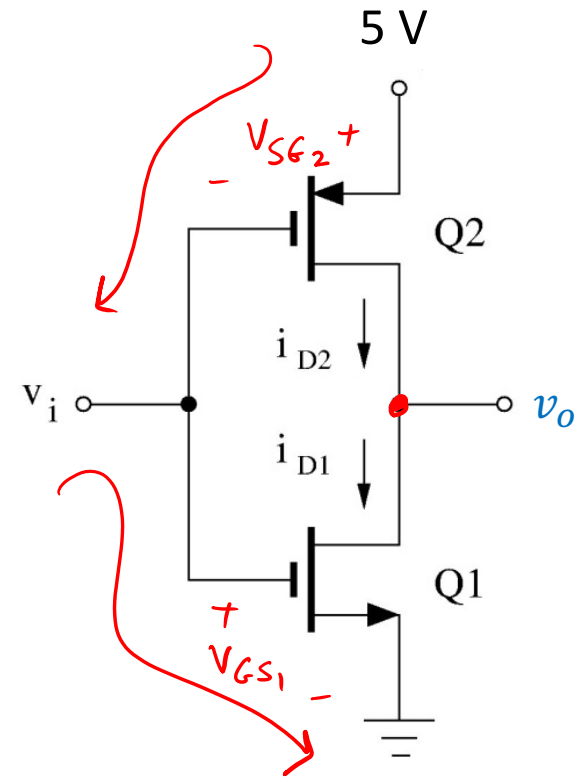Q2 is ON and $i_{D2} = 0 \rightarrow v_{SD2} = 0$ and Q2 is in Triode mode.





KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$

$$v_{SG2} = 5 - v_i$$

For $v_i < 1\text{ V}$, Q1 is off and Q2 is in Triode-mode.

$$v_o = 5 - v_{SD2} = 5\text{ V}$$

  

KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$

$$v_{SG2} = 5 - v_i$$

Q2 off: $v_{SG2} < |V_{tp}|$, $i_{D2} = 0$


$$V_{tn} = |V_{tp}| = 1\text{ V}$$

$$v_{SG2} = 5 - v_i < 1\text{ V} \rightarrow v_i > 4\text{ V}$$

$$i_{D1} = i_{D2} = 0$$

$$v_{GS1} = v_i > 4\text{ V} \rightarrow v_{GS1} > V_{tn} \rightarrow \text{Q1 is ON}$$

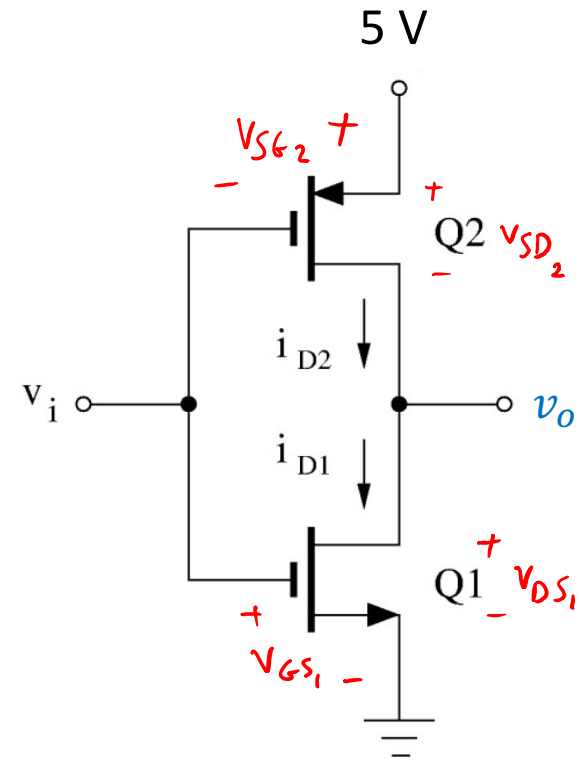Q1 is ON and $i_{D1} = 0 \rightarrow v_{DS1} = 0$ and Q1 is in Triode mode.





KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$

$$v_{SG2} = 5 - v_i$$

For $v_i > 4\text{ V}$, Q2 is off and Q1 is in Triode-mode.

$$v_o = 0$$

 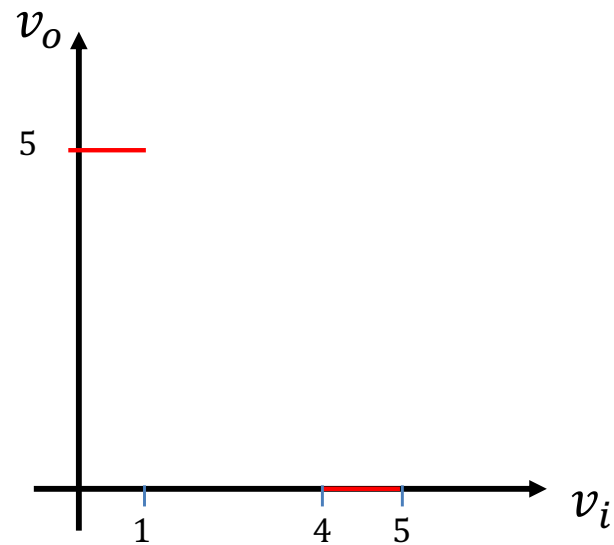

KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$

$$v_{SG2} = 5 - v_i$$


When both Q1 and Q2 are in saturation:

$$i_{D1} = \frac{1}{2} k_n (V_{OVn})^2$$

$$i_{D2} = \frac{1}{2} k_p (V_{OVp})^2$$

$$v_{DS1} > V_{OVn}$$

$$v_{SD2} > V_{OVp}$$

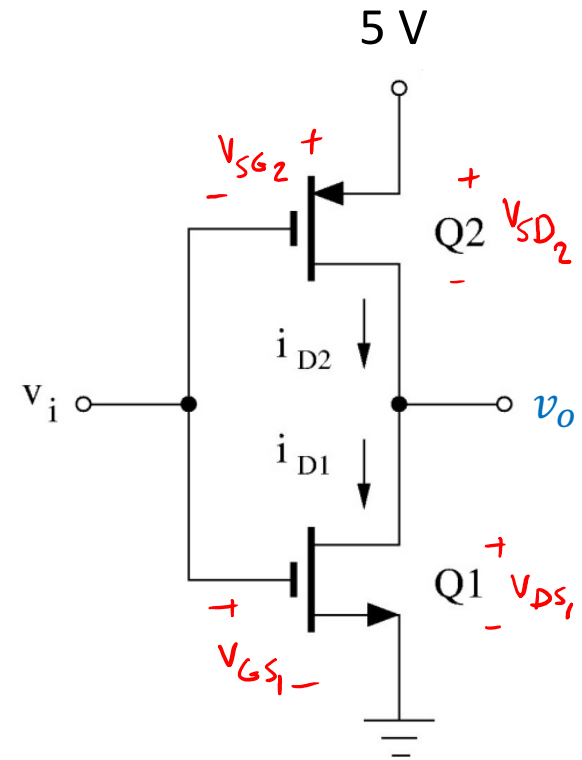

KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$

$$v_{SG2} = 5 - v_i$$

When both Q1 and Q2 are in saturation:


$$V_{OVn} = v_i - V_{tn} = v_i - 1$$

$$V_{OVp} = 5 - v_i - |V_{tp}| = 4 - v_i$$

$$i_{D1} = i_{D2} \rightarrow \frac{1}{2} \times 1 \times (v_i - 1)^2 = \rightarrow \frac{1}{2} \times 1 \times (4 - v_i)^2$$

$$v_i = 2.5 \text{ V}$$

$$i_{D1} = i_{D2} = 1.125 \text{ mA}$$

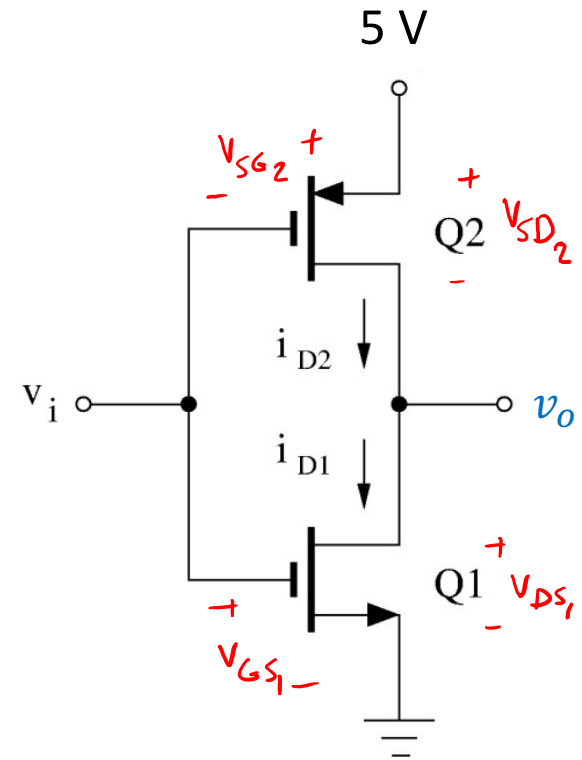

KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$

$$v_{SG2} = 5 - v_i$$

When both Q1 and Q2 are in saturation:


$$v_{DS1} > V_{OVn}$$

$$V_{OVn} = v_{GS1} - V_{tn}$$

$$v_{GS1} = v_i = 2.5 \text{ V} \rightarrow V_{OVn} = 1.5 \text{ V}$$

$$v_{DS1} > 1.5 \text{ V}$$
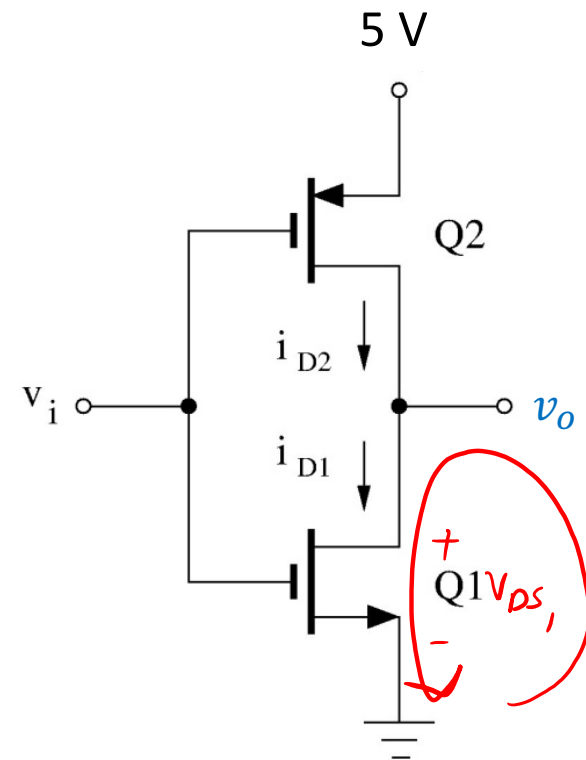
$$v_o = v_{DS1} \rightarrow v_o > 1.5 \text{ V}$$



KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$

$$v_{SG2} = 5 - v_i$$

When both Q1 and Q2 are in saturation:


$$v_{SD2} > V_{OVp}$$

$$V_{OVp} = v_{SG2} - |V_{tp}| \quad \text{and} \quad v_i = 2.5 \text{ V}$$

$$v_{SG2} = 5 - v_i = 2.5 \text{ V} \rightarrow V_{OVp} = 1.5 \text{ V}$$

$$v_{SD2} > 1.5 \text{ V}$$
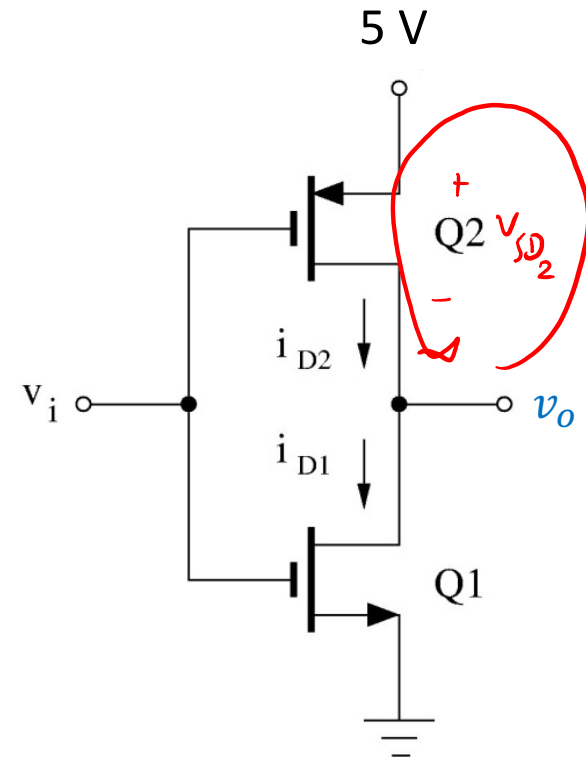
$$v_o = 5 - v_{SD2} \rightarrow v_o < 3.5 \text{ V}$$





KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$

$$v_{SG2} = 5 - v_i$$

For $v_i = 2.5\text{ V}$, Q1 and Q2 are in saturation.

$$1.5 < v_o < 3.5\text{ V}$$

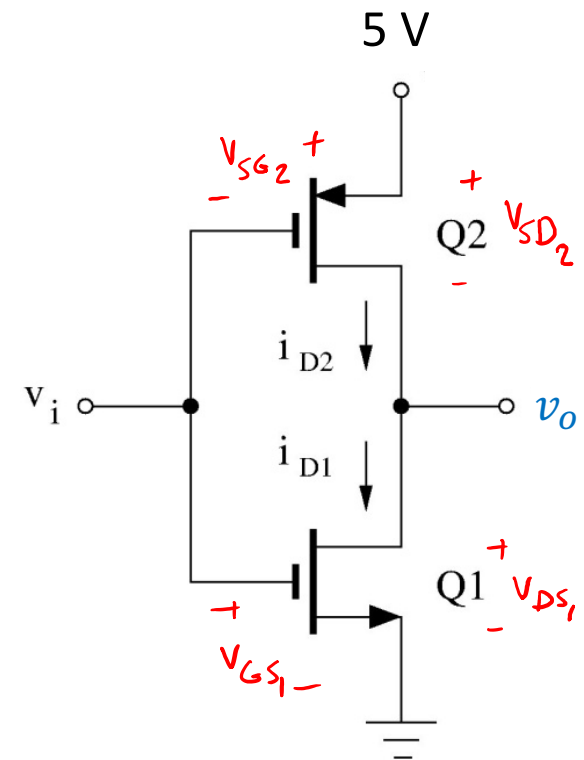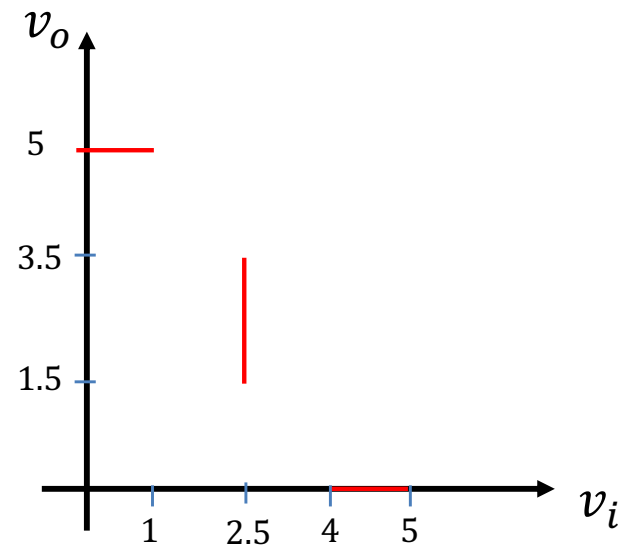

KCL at the output node: $i_{D1} = i_{D2}$

$$v_{GS1} = v_i$$



$$v_{SG2} = 5 - v_i$$

For $1\text{ V} < v_i < 2.5\text{ V}$, Q1 is in saturation and Q2 is in triode.




$$3.5 < v_o < 5\text{ V}$$

For $2.5\text{ V} < v_i < 4\text{ V}$, Q2 is in saturation and Q1 is in triode.

$$0 < v_o < 1.5\text{ V}$$

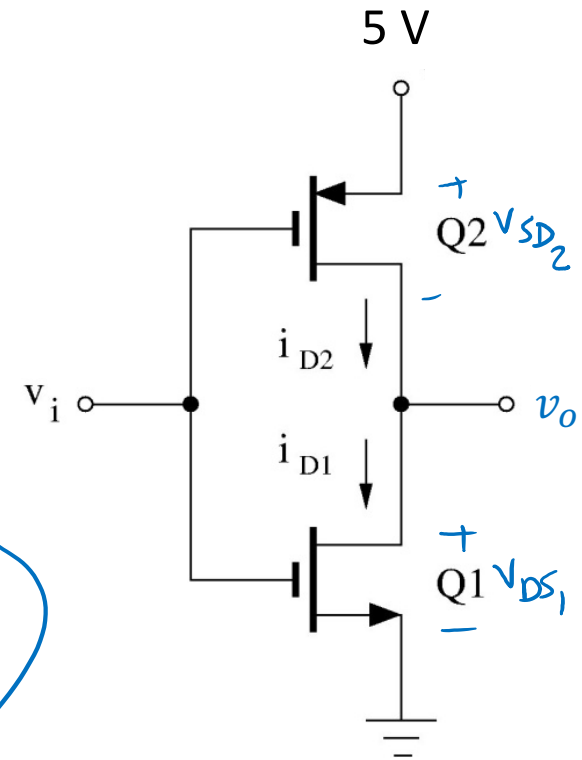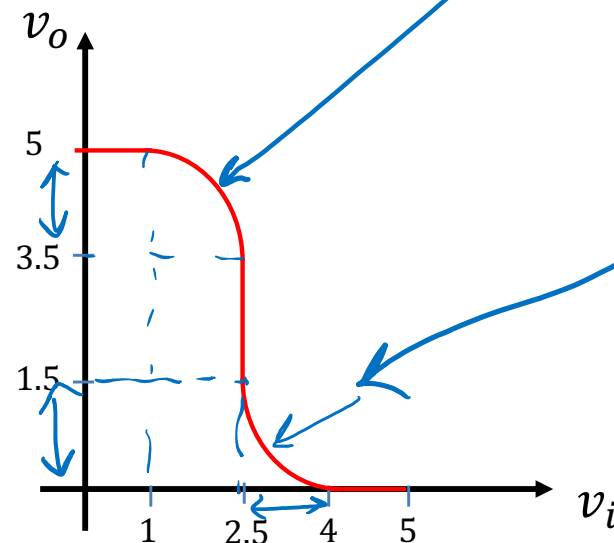

Transfer function of a CMOS inverter

 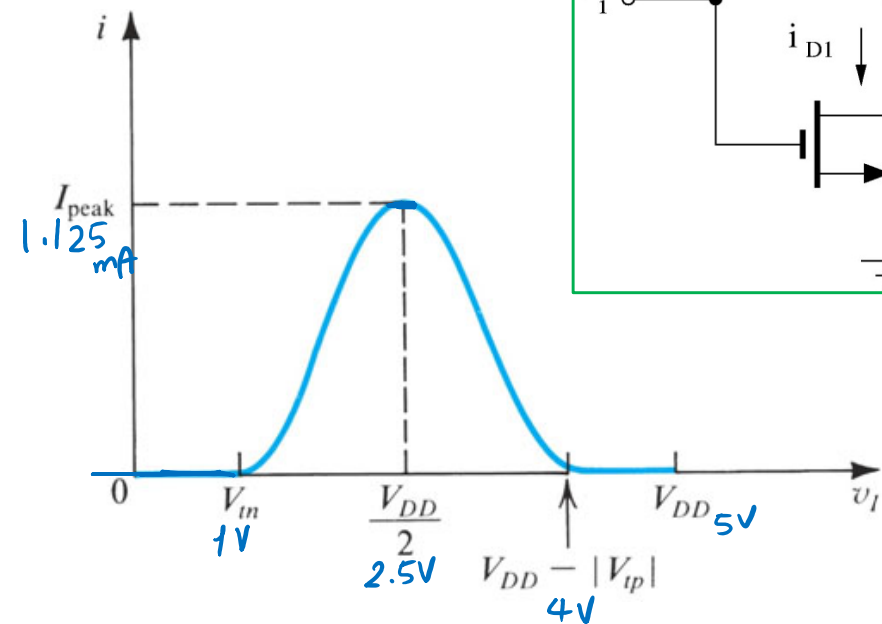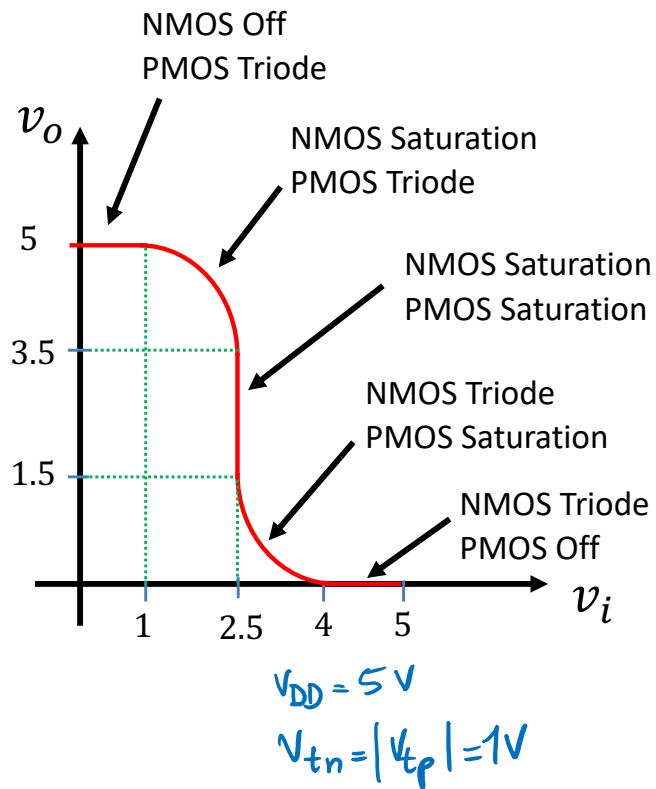

Transfer function is “symmetric” for matched transistors:


$$V_{tn} = |V_{tp}| \quad \& \quad \mu_n(W/L)_n = \mu_p(W/L)_p$$

During transition from one state to another, $i_D > 0$

Lecture 15 reading quiz

In the circuit below, find V_i and i_D when both NMOS and PMOS are in saturation. What is the range of V_o in this case?

 $V_{tn} = 1\text{ V}$, $V_{tp} = -1\text{ V}$ and $k_n = \mu_n C_{ox} (W/L)_n = 1\text{ mA/V}^2$,
 $k_p = \mu_p C_{ox} (W/L)_p = 0.4\text{ mA/V}^2$. $\lambda = 0$.




Discussion question 1. (Pseudo-NMOS inverter)

In the circuit below, find v_o for $v_I = 0$ and $v_I = 1.8\text{ V}$.

The transistor parameters are matched $V_{tn} = |V_{tp}| = 0.4\text{ V}$, and

 $k_n = 0.3\text{ mA/V}^2$, $k_p = 0.2 k_n$, $\lambda = 0$.



Discussion question 1. (Pseudo-NMOS inverter)

In the circuit below, find v_o for $v_I = 0$ and $v_I = 1.8\text{ V}$.

The transistor parameters are matched $V_{tn} = |V_{tp}| = 0.4\text{ V}$, and

$$k_n = 0.3\text{ mA/V}^2, k_p = 0.2 k_n, \lambda = 0.$$

- Label V_{GS} , V_{SG} , V_{DS} , and V_{SD} for PMOS and NMOS.
- Find V_{OV} for each MOSFET and determine if they are ON or in Cut-off.
- If MOSFETs both are ON, there are four possibilities for their modes of operation. You can make an educated guess.

Because this is an inverter, we expect a low output when input is high, and since the output is equal to v_{DS1} , we expect to get a low value for v_{DS1} when $v_I = 1.8\text{ V}$. We also know that when NMOS operates in triode, $v_{DS1} < v_{OVn} = 1.4\text{ V}$, so most probably the low output (small v_{DS1}) will be less than 1.4V, so we assume triode region for Q_N .

Also, $v_{SD2} = 1.8 - v_{DS1}$. With small v_{DS1} , v_{SD2} will probably be a large value close to 1.8 V. v_{SD2} is likely greater than $v_{OVp} = 1.4\text{ V}$, so PMOS probably operates in saturation.

