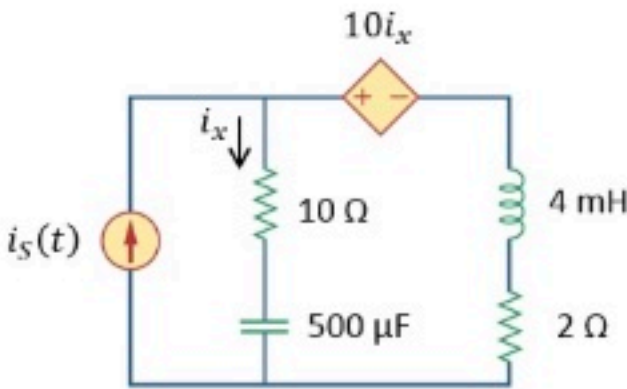


# PP AC power 007

Unlimited Attempts.

$$i_S(t) = 2 \cdot \cos\left(10^3 t + \frac{\pi}{4}\right) \text{ A}$$

- Find the complex power  $\mathbf{S}_1 = a_1 + b_1 j$  supplied by the source  $i_S$ .  
Find the complex power  $\mathbf{S}_2 = a_2 + b_2 j$  received by the  $10\ \Omega$  resistor.  
Find the complex power  $\mathbf{S}_3 = a_3 + b_3 j$  received by the  $2\ \Omega$  resistor.  
Find the complex power  $\mathbf{S}_4 = a_4 + b_4 j$  received by the CCVS.  
Find the complex power  $\mathbf{S}_5 = a_5 + b_5 j$  received by the inductor.  
Find the complex power  $\mathbf{S}_6 = a_6 + b_6 j$  received by the capacitor.



Given Variables:

. . .

Calculate the following:

a1 (W) :

32



b1 (VAR) :

4



a2 (W) :

50



b2 (VAR) :

0



a3 (W) :

2



b3 (VAR) :

0



a4 (W) :

-20



b4 (VAR) :

10



a5 (W) :

0



b5 (VAR) :

4



a6 (W) :

0



b6 (VAR) :

-10



Hint: Keep  $i_S$  algebraic.