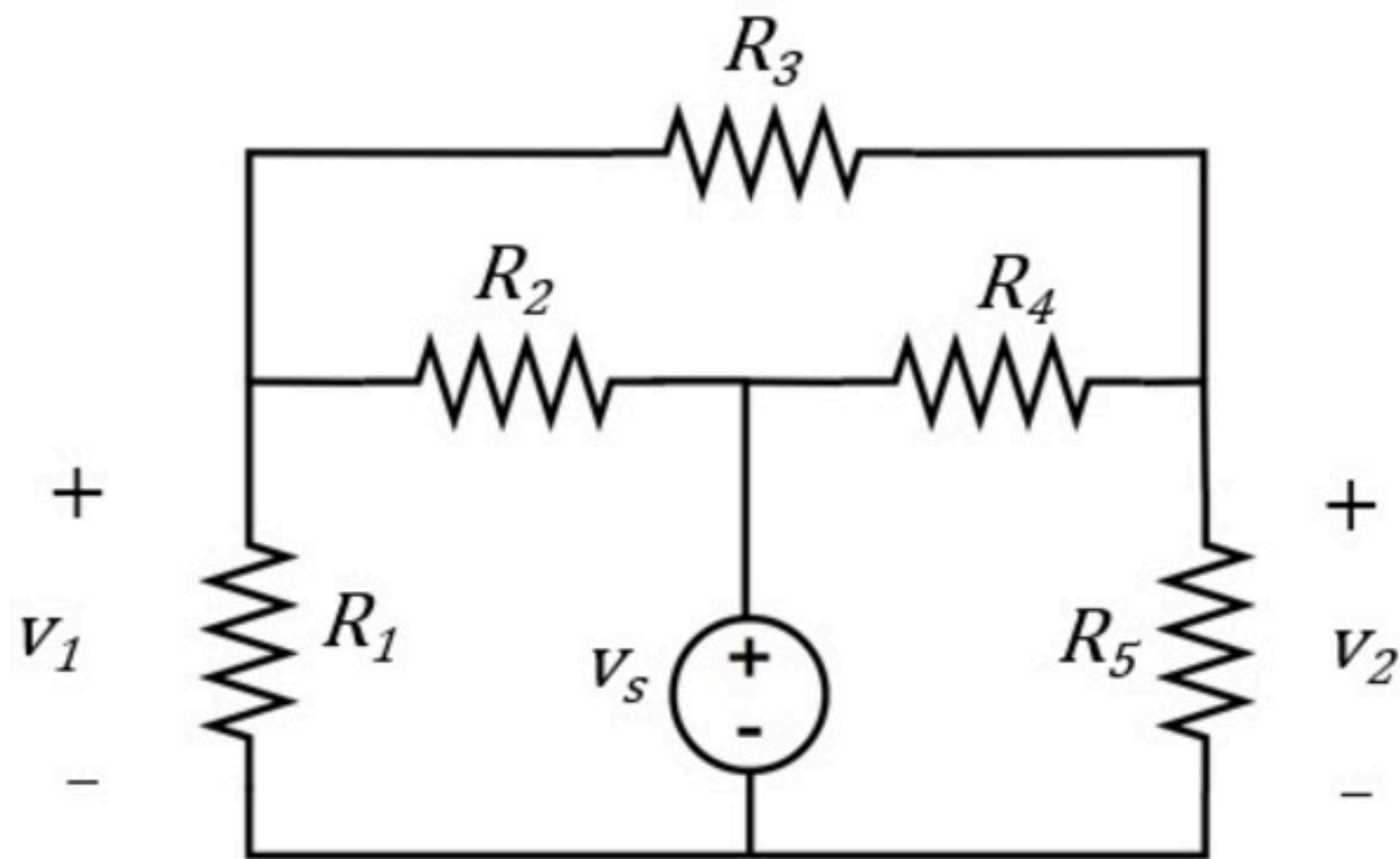


Basic Analysis 001b

Problem has been graded.

We measure v_1 and v_2 .

Determine the values of resistances R_2 and R_3 .



Given Variables:

R_1 : 12 ohm

R_4 : 12 ohm

R_5 : 2 ohm

v_s : 30 V

v_1 : 12 V

v_2 : 6 V

Calculate the following:

R_2 (ohm) :

R_3 (ohm) :

Hint: Find the currents and use Ohm's Law.