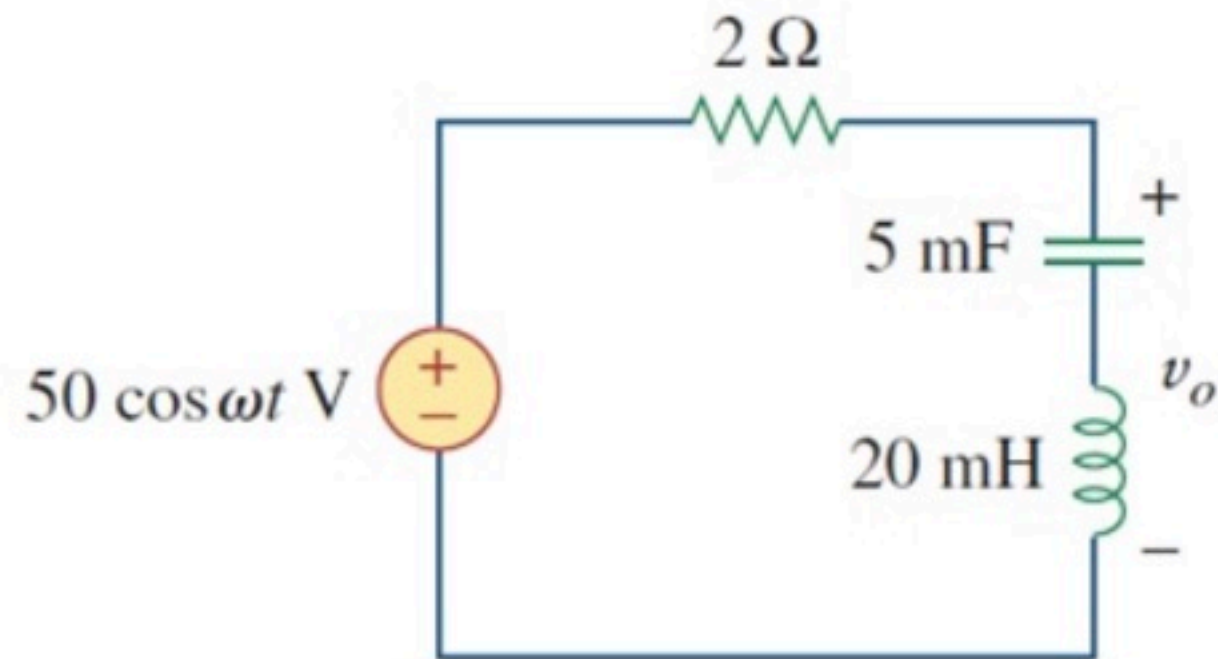


# PP Phasors 015

Unlimited Attempts.

Find the value of  $\omega$  that results in  $v_o = 0$  V.

( $v_o$  is the voltage across the inductor and capacitor together)



Note: This is an example of 'resonance'. For each  $\omega$ , the system behaves differently (i.e.,  $v_o$  is a function of  $\omega$ ). For this one particular value of  $\omega$ , however, the inductor and capacitor perfectly 'compensate' for each other.

Given Variables:

...

Calculate the following:

$\omega$  (rad/s) :

100



Hint: What should be the impedance of C and L in series for  $v_o = 0$ ?