
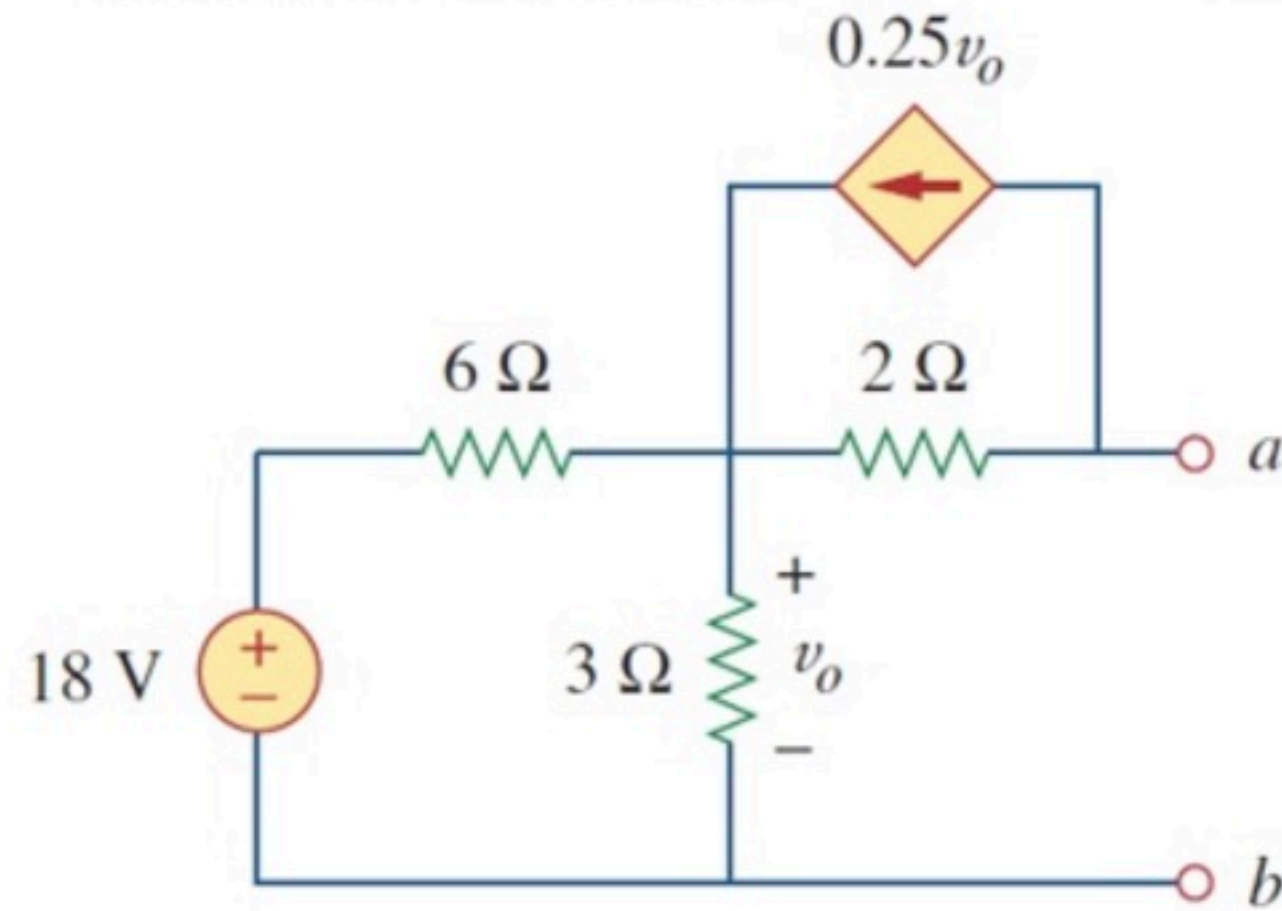


PP Circuit theorems 013

Unlimited Attempts.

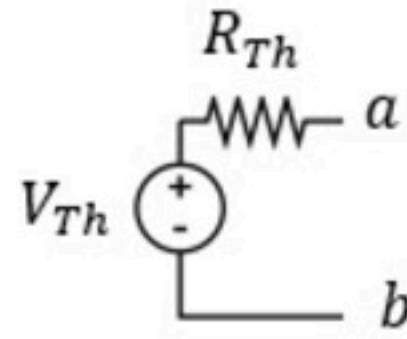Find the Thevenin equivalent resistance of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

R_{th} (ohm) :

3



Hint: Try using a test source. Would you use a voltage or current test source?