

# **ECE 65: Components & Circuits Lab**

## **Practice 4**

### **Amplifier practice problems**


Reference notes: sections 6.1, 6.2

Sedra & Smith (7<sup>th</sup> Ed): section 7.3

Saharnaz Baghdadchi

# Course map
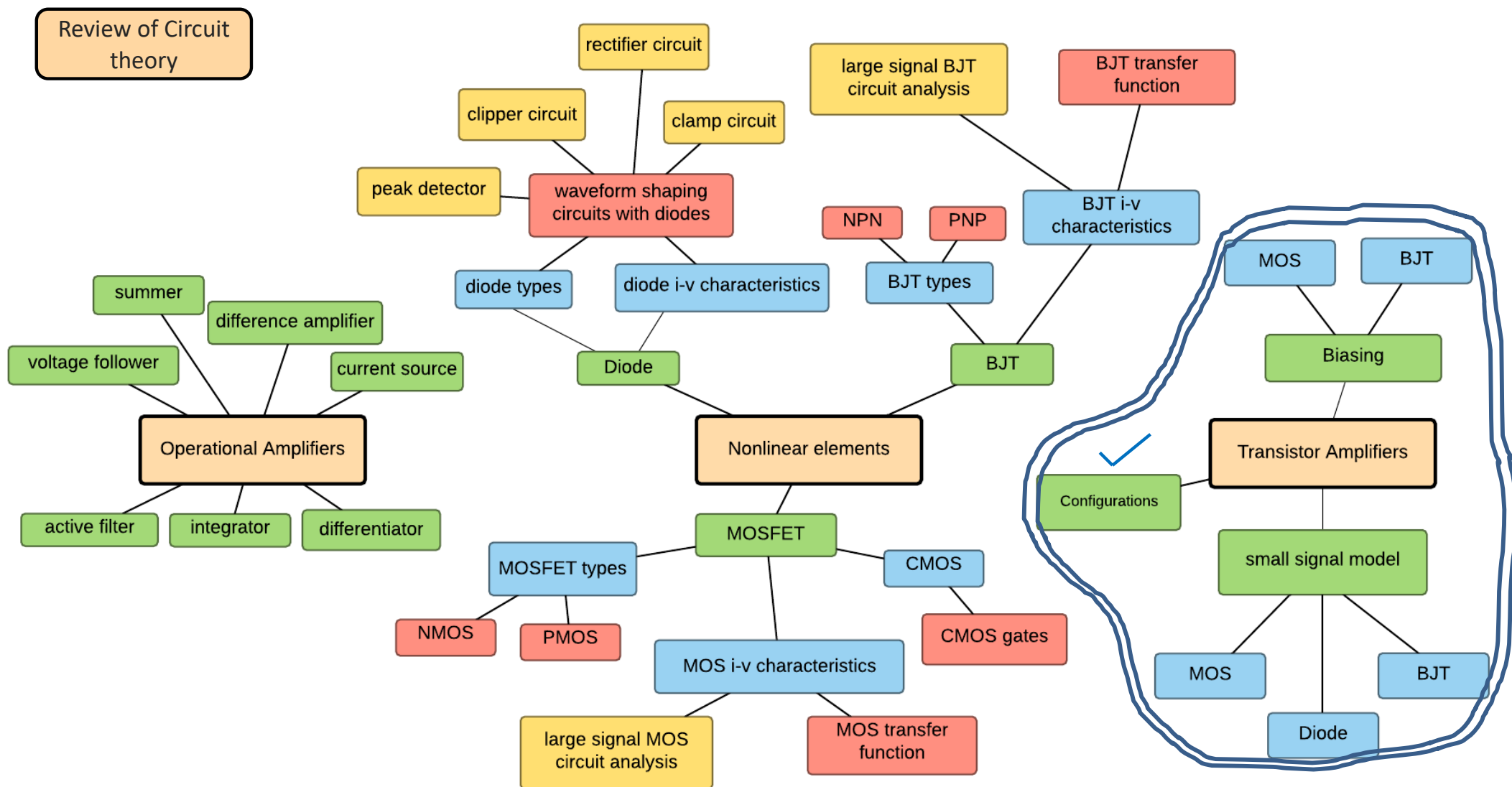
## 7. Transistor Amplifier Configurations




## Practice problem 1.

**Design** the following amplifier circuit, to achieve a voltage gain of  $v_o/v_{sig} = -40 \text{ V/V}$ .

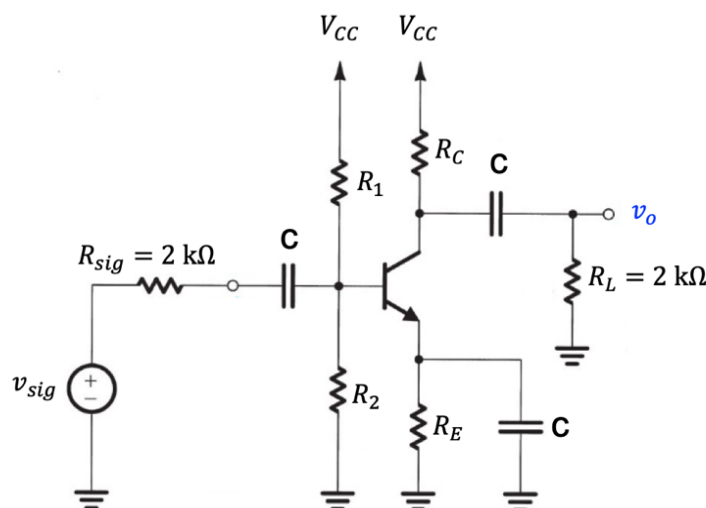- a) You have a 15 V power supply available.
- b) An emitter current of 2 mA is desired.
- c) The current through  $R_2$  is to be one-tenth of  $I_E$ .
- d) The DC voltage at the base should be equal to one-third of the power supply.

The available transistor has  $\beta = 100$  and  $V_{D0} = 0.7 \text{ V}$ . Ignore the early effect in bias and signal circuits. Assume Capacitors are short in the signal circuit. Use  $V_T = 25 \text{ mV}$ .


**Draw** the signal circuit and calculate the signal parameters.



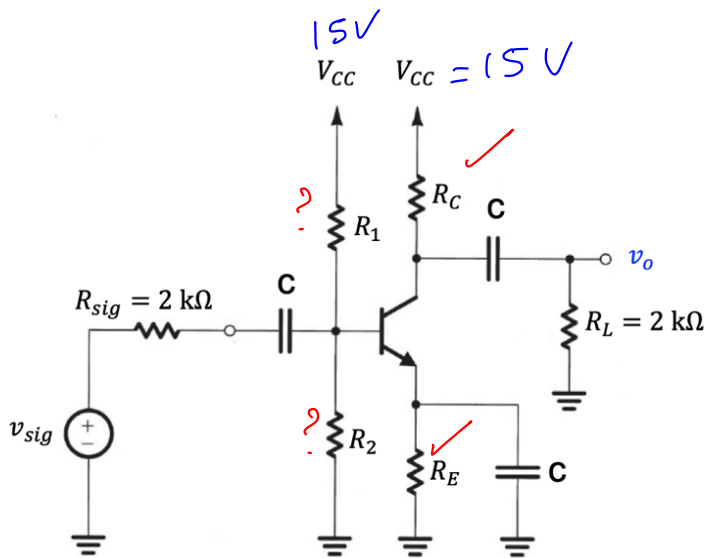
# Practice problem 1.

$$v_o/v_{sig} = -40\text{V/V}$$

- You have a 15 V power supply available.
- An emitter current of 2 mA is desired.
- The current through  $R_2$  is to be one-tenth of  $I_E$ .
- The DC voltage at the base should be equal to one-third of the power supply.



Bias circuit:

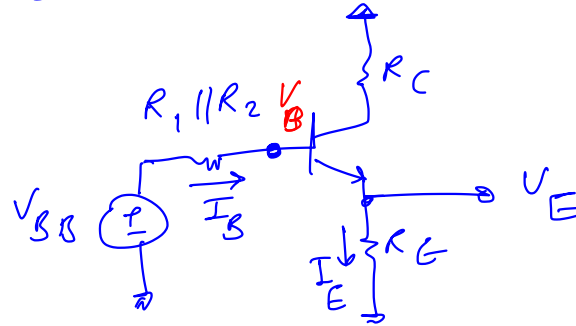

$$V_{BB} = 15\text{V} \times \frac{R_2}{R_1 + R_2}$$

$$V_B = \frac{1}{3} \times V_{CC} = 5\text{V}$$


$$V_B = V_{BE} + V_E$$

$$V_B = V_{BE} + R_E I_E \longrightarrow 5\text{V} = 0.7 + R_E \times 2\text{mA} \longrightarrow R_E = 2.15\text{ k}\Omega$$
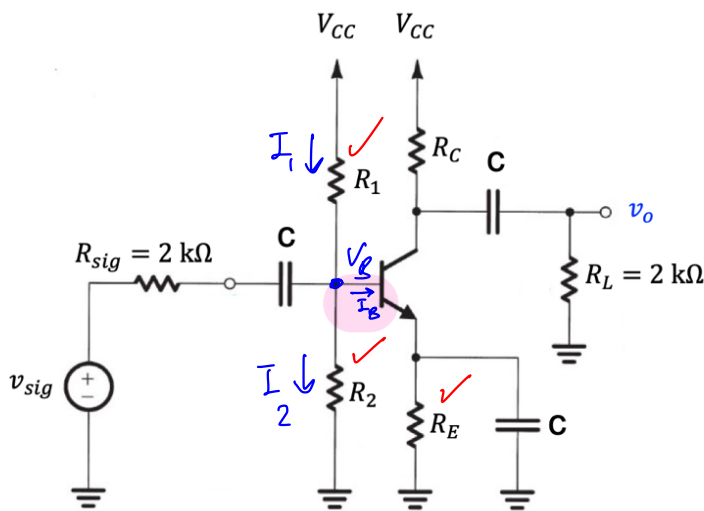
## Practice problem 1.

$$v_o/v_{sig} = -40\text{ V/V}$$

- You have a 15 V power supply available.
- An emitter current of 2 mA is desired.
- The current through  $R_2$  is to be one-tenth of  $I_E$ .
- The DC voltage at the base should be equal to one-third of the power supply.



$$I_2 = \frac{1}{10} \times I_E = 0.2\text{ mA}$$

$$V_B = 5\text{ V}$$

$$V_B = R_2 I_2 \rightarrow R_2 = \frac{5\text{ V}}{0.2\text{ mA}} = 25\text{ k}\Omega$$

$$I_E = I_C + I_B, \quad I_C = \beta I_B = 100 I_B \rightarrow I_E = (1 + \beta) I_B \rightarrow I_B = \frac{I_E}{101}$$


$$I_B = \frac{2}{101}\text{ mA} = 0.0198\text{ mA}$$

KCL at Base:  $I_1 = I_B + I_2 = 0.2198\text{ mA} \rightarrow R_1 = \frac{V_{CC} - V_B}{I_1} = 45.49\text{ k}\Omega$
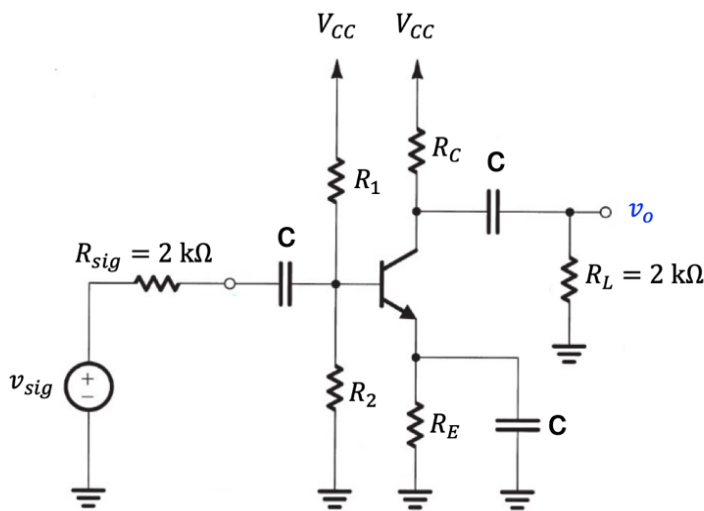
# Practice problem 1.

$$v_o/v_{sig} = -40 \text{ V/V}$$

- You have a 15 V power supply available.
- An emitter current of 2 mA is desired.
- The current through  $R_2$  is to be one-tenth of  $I_E$ .
- The DC voltage at the base should be equal to one-third of the power supply.




$$R_B = R_1 || R_2 = 16.13 \text{ k}\Omega$$

$$r_{\pi} = \frac{V_T}{I_B} = \frac{25 \text{ mV}}{I_{E/101}} = 1.26 \text{ k}\Omega$$

$$g_m = \frac{I_C}{V_T} = 79.36 \text{ mA/V}$$

$$R_i = R_B || r_{\pi} \approx 1.17 \text{ k}\Omega$$

a different method of finding  $R_C$ :

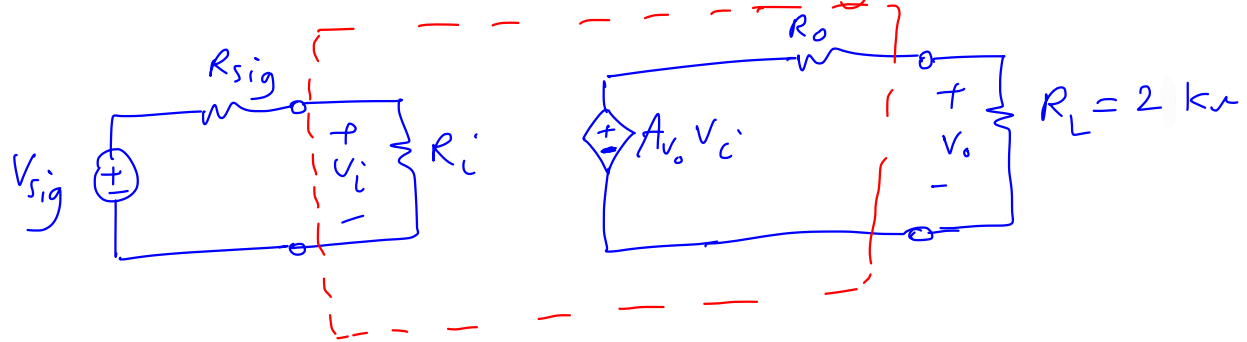


$$R_o = R_C || r_o = R_C || \infty = R_C$$

$$A_{v_o} = -g_m R_C = -79.36 R_C$$
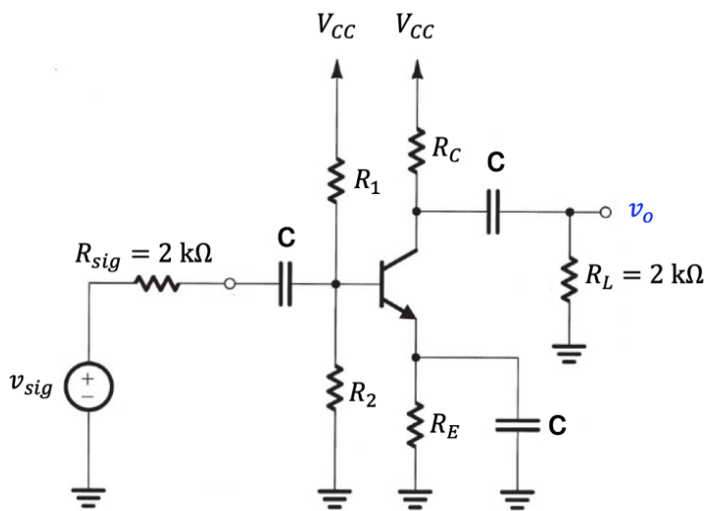
# Practice problem 1.

$$v_o/v_{sig} = -40 \text{ V/V}$$


- You have a 15 V power supply available.
- An emitter current of 2 mA is desired.
- The current through  $R_2$  is to be one-tenth of  $I_E$ .
- The DC voltage at the base should be equal to one-third of the power supply.



$$R_o = R_C \parallel r_o = R_C \parallel \infty = R_C$$

$$A_{v_o} = -g_m R_C = -74.36 R_C$$

a different method of finding  $R_C$ :

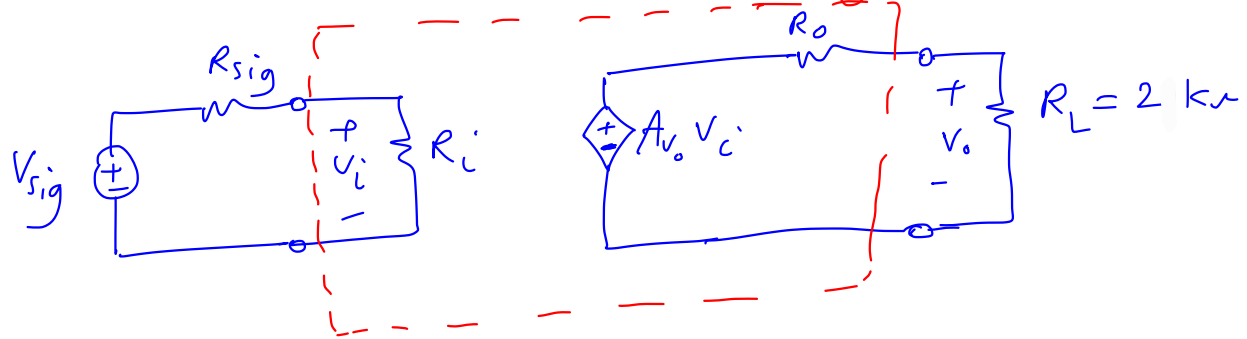

$$\frac{v_o}{v_{sig}} = \frac{R_L}{R_o + R_L} \cdot A_{v_o} \cdot \frac{R_i}{R_i + R_{sig}}$$


$$-40 \text{ V/V} = \frac{2 \text{ k}\Omega}{R_C + 2 \text{ k}\Omega} \cdot (-74.36 R_C) \cdot \frac{1.17 \text{ k}\Omega}{3.17 \text{ k}\Omega}$$

$$R_C = 4.3 \text{ k}\Omega$$
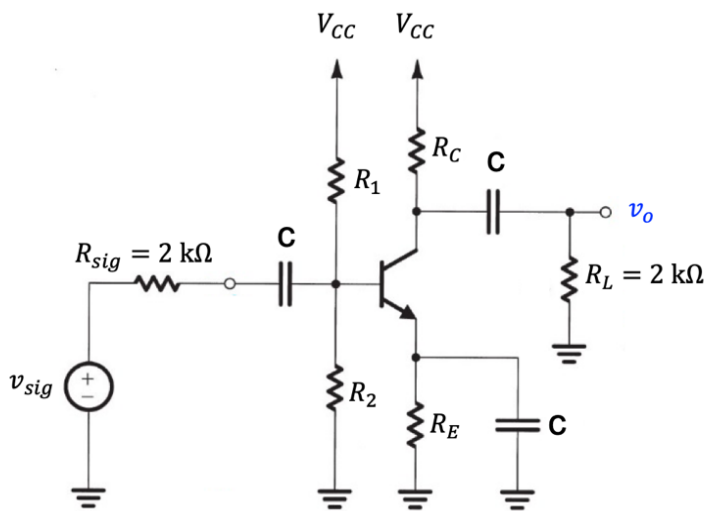
# Practice problem 1.

$$v_o/v_{sig} = -40 \text{ V/V}$$


- You have a 15 V power supply available.
- An emitter current of 2 mA is desired.
- The current through  $R_2$  is to be one-tenth of  $I_E$ .
- The DC voltage at the base should be equal to one-third of the power supply.



$$R_o = R_C \parallel r_o = R_C \parallel \infty = R_C$$

$$A_{v_o} = -g_m R_C = -74.36 R_C$$

a different method of finding  $R_C$ :

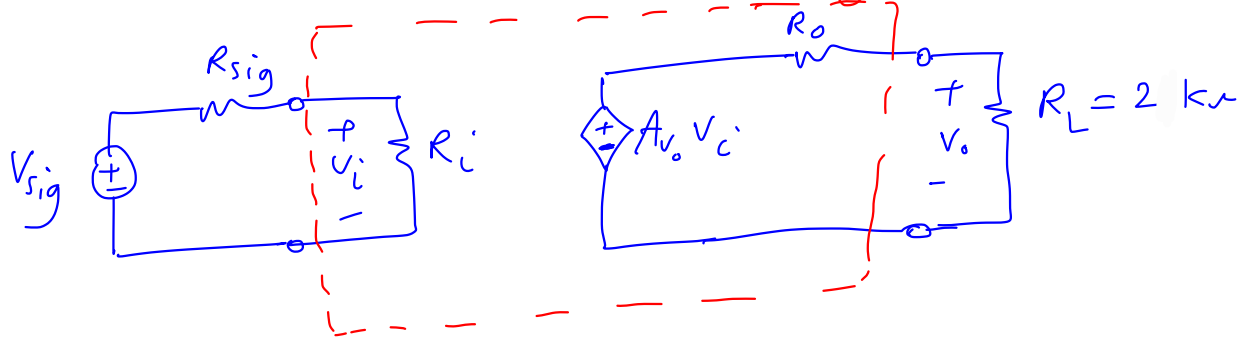

$$\frac{v_o}{v_{sig}} = \frac{R_L}{R_o + R_L} \cdot A_{v_o} \cdot \frac{R_i}{R_i + R_{sig}}$$

$$-40 \text{ V/V} = \frac{2 \text{ k}\Omega}{R_C + 2 \text{ k}\Omega} \cdot (-74.36 R_C) \cdot \frac{1.17 \text{ k}\Omega}{3.17 \text{ k}\Omega}$$

$$R_C = 4.3 \text{ k}\Omega$$




# Practice problem 1.


$$r_o = \infty$$

$$v_o/v_{sig} = -40 \text{ V/V}$$

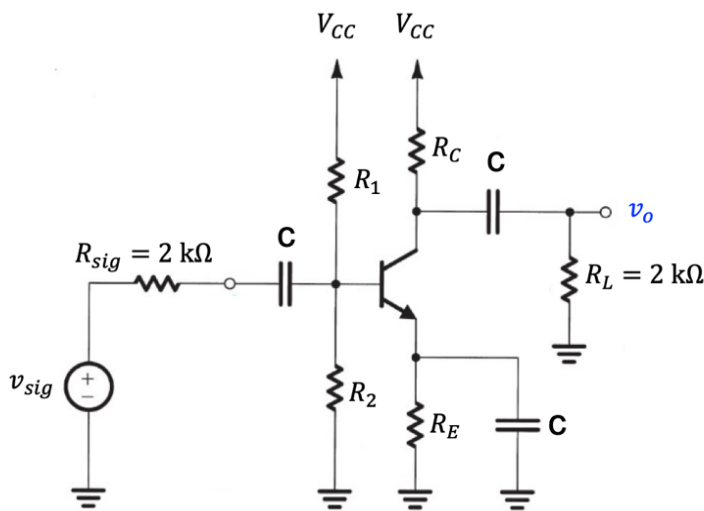- You have a 15 V power supply available.
- An emitter current of 2 mA is desired.
- The current through  $R_2$  is to be one-tenth of  $I_E$ .
- The DC voltage at the base should be equal to one-third of the power supply.



draw the signal circuit to find  $R_c$ .

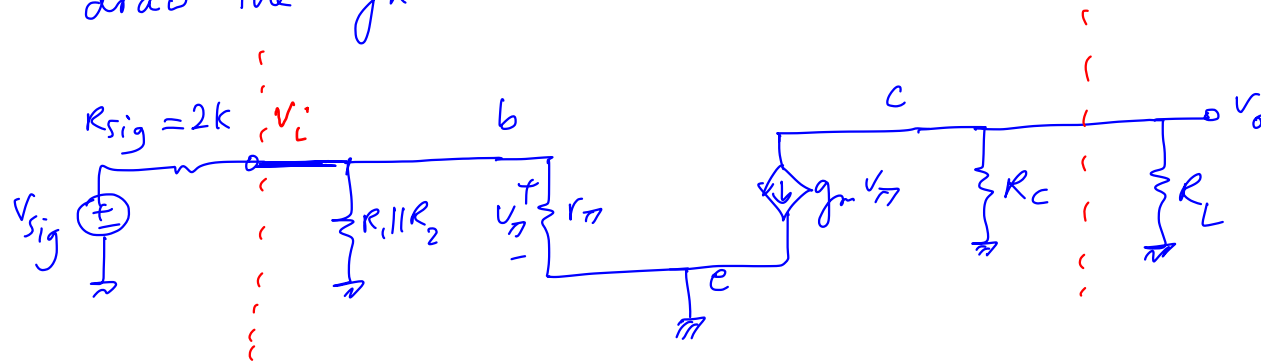

Common-emitter, in the signal circuit:

$$R_B = R_1 \parallel R_2, \quad R_E = 0, \quad R_C = ?$$

$$\frac{V_o}{V_{sig}} = -40 \text{ V/V}$$


$$\begin{cases} V_o = -g_m v_{\pi} (R_C \parallel R_L) \\ v_{\pi} = \frac{(r_{\pi} \parallel R_1 \parallel R_2)}{(r_{\pi} \parallel R_1 \parallel R_2) + R_{sig}} V_{sig} \end{cases}$$

# Practice problem 1.


$$r_o = \infty$$

$$v_o/v_{sig} = -40 \text{ V/V}$$

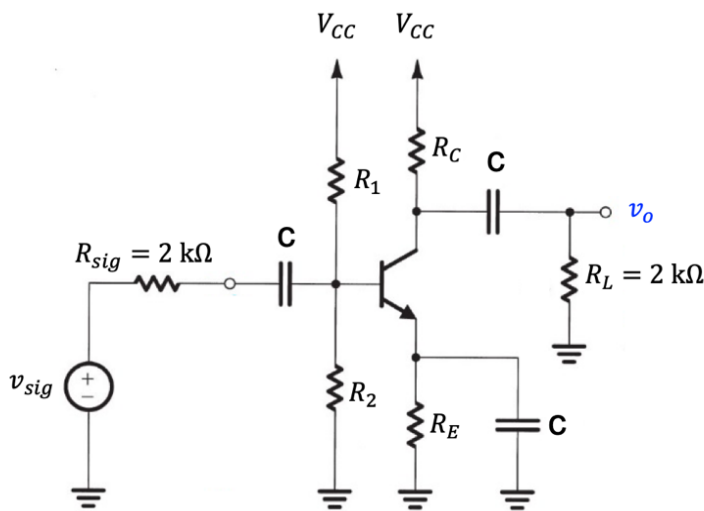- You have a 15 V power supply available.
- An emitter current of 2 mA is desired.
- The current through  $R_2$  is to be one-tenth of  $I_E$ .
- The DC voltage at the base should be equal to one-third of the power supply.



draw the signal circuit to find  $R_C$ .

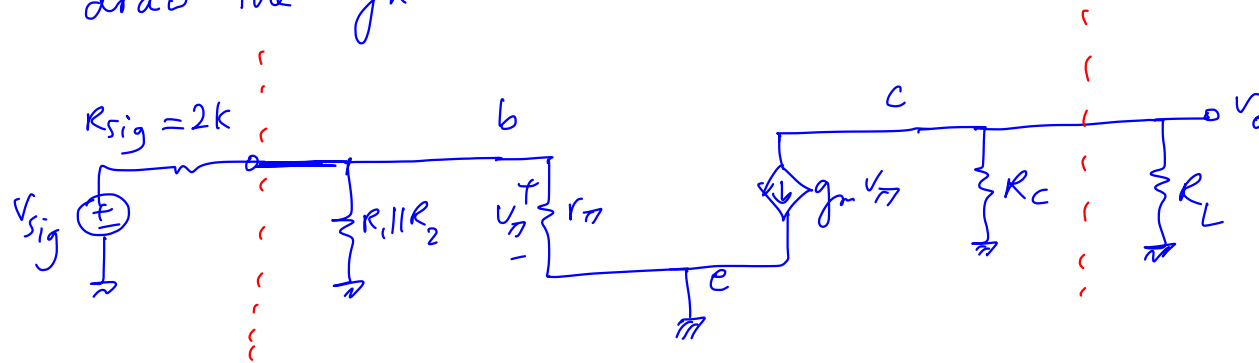

Common-emitter, in the signal circuit:

$$R_B = R_1 \parallel R_2, \quad R_E = 0, \quad R_C = ?$$

$$\frac{V_o}{V_{sig}} = -40 \text{ V/V}$$

$$\begin{cases} V_o = -g_m v_{\pi} (R_C \parallel R_L) \\ v_{\pi} = \frac{(r_{\pi} \parallel R_1 \parallel R_2)}{(r_{\pi} \parallel R_1 \parallel R_2) + R_{sig}} V_{sig} \end{cases}$$


# Practice problem 1.

$$r_o = \infty$$


$$R_1 \parallel R_2 = R_B$$

$$v_o/v_{sig} = -40 \text{ V/V}$$

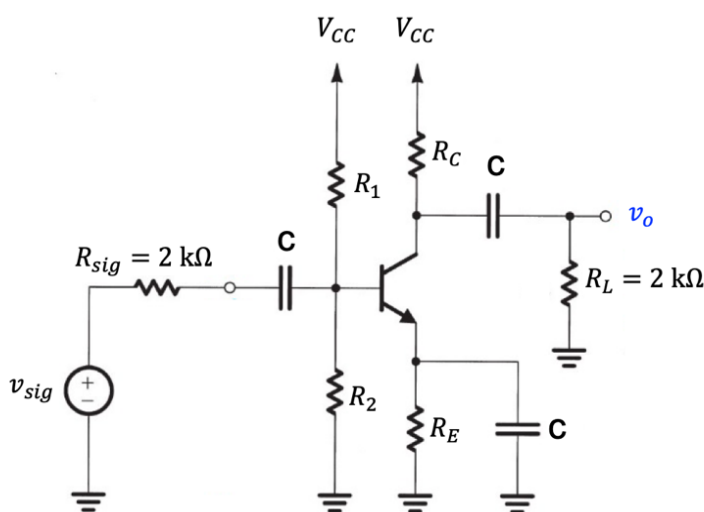- You have a 15 V power supply available.
- An emitter current of 2 mA is desired.
- The current through  $R_2$  is to be one-tenth of  $I_E$ .
- The DC voltage at the base should be equal to one-third of the power supply.



draw the signal circuit to find  $R_C$ .

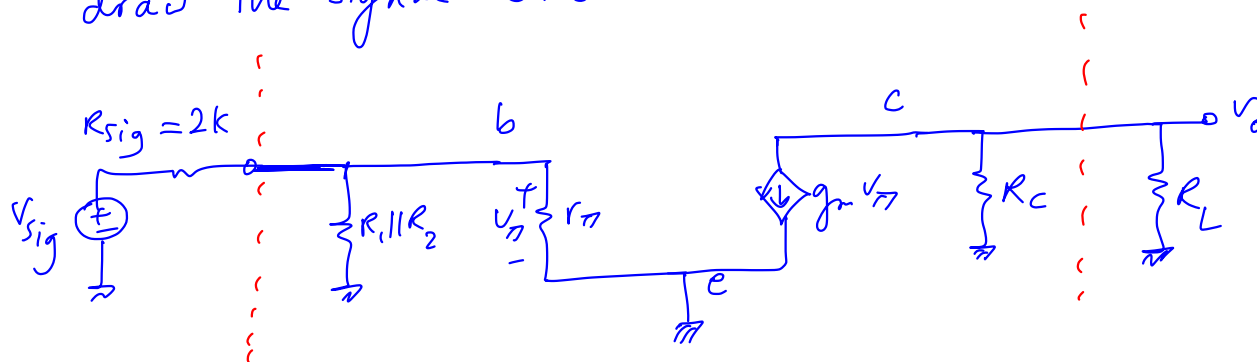

$$\left\{ \begin{aligned} v_o &= -g_m v_{\pi} (R_C \parallel R_L) \\ v_{\pi} &= \frac{(r_{\pi} \parallel R_B) V_{sig}}{(r_{\pi} \parallel R_B) + R_{sig}} \end{aligned} \right.$$


$$\Rightarrow \frac{v_o}{v_{sig}} = \frac{(r_{\pi} \parallel R_B)}{(r_{\pi} \parallel R_B) + R_{sig}} \cdot (-g_m) \left( \frac{R_C R_L}{R_C + R_L} \right)$$

$$\Rightarrow R_C = 4.3 \text{ k}\Omega$$

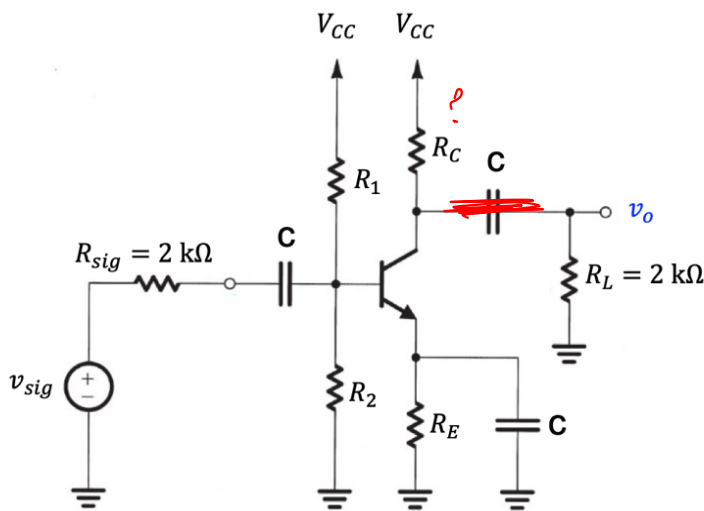
# Practice problem 1.

$$v_o/v_{sig} = -40 \text{ V/V}$$

- You have a 15 V power supply available.
- An emitter current of 2 mA is desired.
- The current through  $R_2$  is to be one-tenth of  $I_E$ .
- The DC voltage at the base should be equal to one-third of the power supply.



draw the signal circuit to find  $R_C$ .

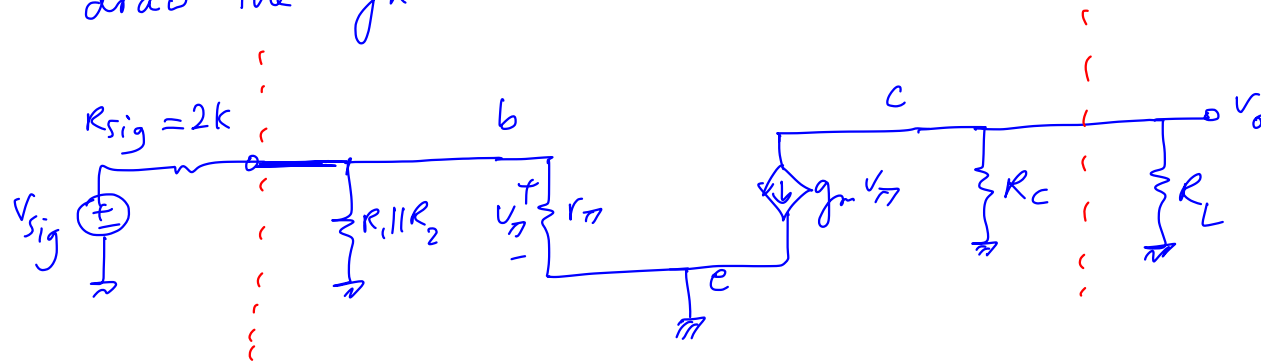

We can rewrite the same equation:

$$\begin{cases} v_o = -g_m v_{\pi} (R_C \parallel R_L) \\ v_{\pi} = \frac{(r_{\pi} \parallel R_1 \parallel R_2)}{(r_{\pi} \parallel R_1 \parallel R_2) + R_{sig}} v_{sig} \end{cases}$$

$$\Rightarrow \frac{v_o}{v_{sig}} = \frac{\overbrace{(r_{\pi} \parallel R_B)}^{R_i}}{\underbrace{(r_{\pi} \parallel R_B) + R_{sig}}_{R_i}} \cdot (-g_m) \left( \frac{R_C R_L}{R_C + R_L} \right)$$

$$\frac{v_o}{v_{sig}} = \frac{R_i}{R_i + R_{sig}} (-g_m R_C) \frac{R_L}{R_C + R_L}$$

## Practice problem 2.

In the below amplifier circuit,


- Find the DC emitter currents and the DC Base node voltages of Q1 and Q2.
- Find the small signal parameters.
- If a load resistance  $R_L = 10\text{ k}\Omega$  is connected to the output terminal, and a signal source with  $R_{sig} = 0$  is connected to the input terminal, find  $A = \frac{v_o}{v_{sig}}$ .

$$\beta_1 = 60, \beta_2 = 100, V_T = 25\text{ mV}, V_{D0} = 0.7\text{ V}.$$

Neglect the early effect in the bias and signal circuits. The capacitors are short for the signal circuit.

The input resistance of the second stage will act as the load resistor for the first stage.

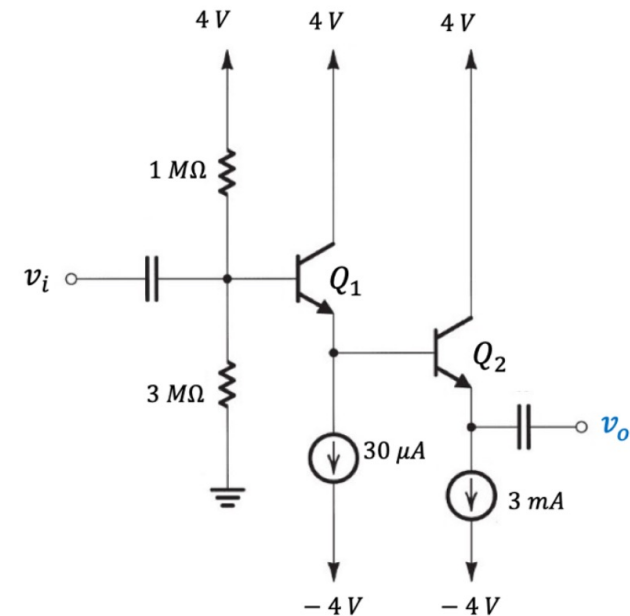For a common-collector amplifier use  $A_{vo} = \frac{(1/g_m) \parallel r_\pi \parallel R_E \parallel r_o}{(1/g_m) \parallel r_\pi}$



## Practice problem 2.

$$a) I_{E_2} = 3 \text{ mA}$$


$$\text{KCL at Emitter of } Q_1: I_{E_1} = I_{B_2} + 30 \mu\text{A}$$

This is an amplifier circuit so the BJTs will be in active mode.

$$I_{B_2} = \frac{I_{E_2}}{1 + \beta_2} = \frac{3 \text{ mA}}{101} = 29.7 \mu\text{A}$$



$$I_{E_1} = 29.7 \mu\text{A} + 30 \mu\text{A} = 59.7 \mu\text{A}$$

$$I_{E_1} = 59.7 \mu\text{A}$$

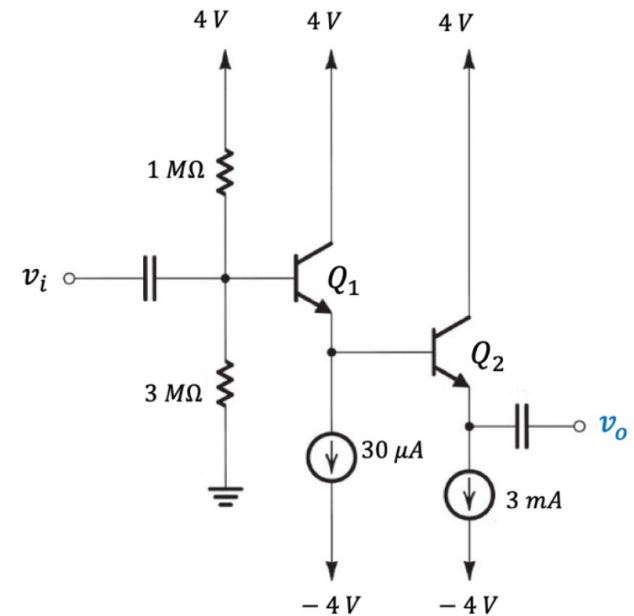

## Practice problem 2.

The Thevenin equivalent

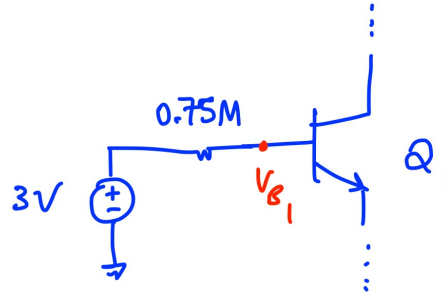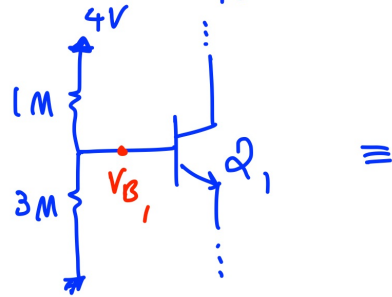


$$V_{B_1} = 3V - 0.75M\Omega \times I_{B_1}$$

$$I_{B_1} = \frac{I_{E_1}}{1 + \beta_1} = \frac{59.7\mu A}{61} \approx 0.98\mu A$$

$$V_{B_1} = 3V - 0.75 \times 0.98 = 2.265 V$$

$$V_{B_1} = 2.265 V$$

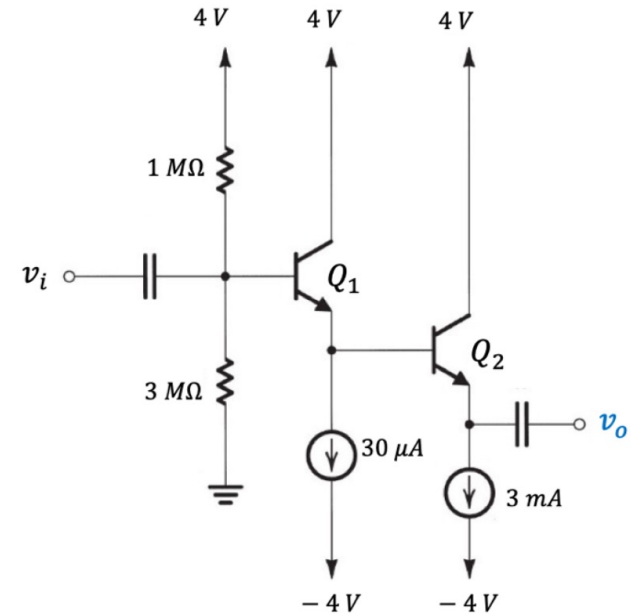

$$V_{B_2} = V_{E_1} = V_{B_1} - V_{BE_1} = 1.565 V$$

$$V_{B_2} = 1.565 V$$

## Practice problem 2.


b)

$$g_{m_2} = \frac{I_{C_2}}{V_T} = \frac{3 \text{ mA} \times \frac{100}{101}}{25 \text{ mV}} \approx 118.8 \text{ mA/V}$$

$$r_{\pi_2} = \frac{\beta_2}{g_{m_2}} = 842 \Omega$$

$$g_{m_1} = \frac{I_{C_1}}{V_T} = \frac{59.7 \mu\text{A} \times \frac{60}{61}}{25 \text{ mV}} = 2.35 \text{ mA/V}$$


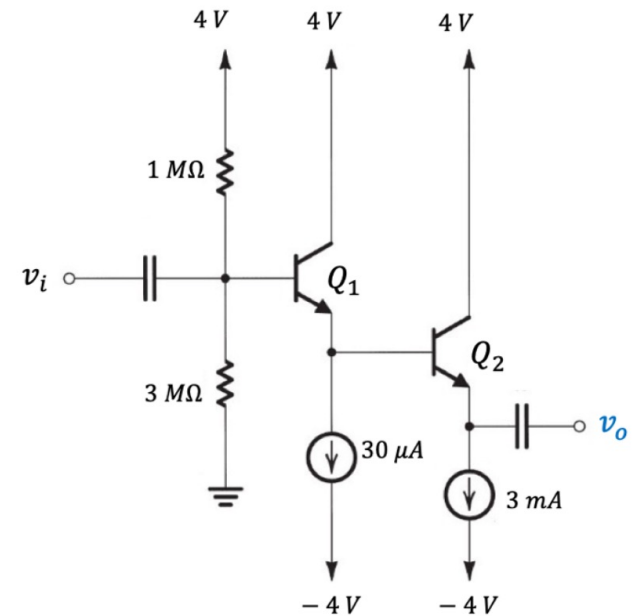
$$r_{\pi_1} = \frac{\beta_1}{g_{m_1}} = 25.53 \text{ k}\Omega$$







## Practice problem 2.

Small signal circuit:

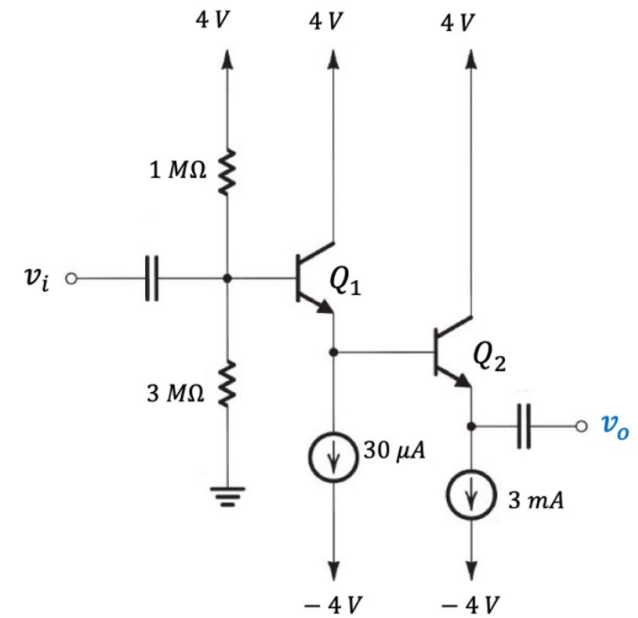
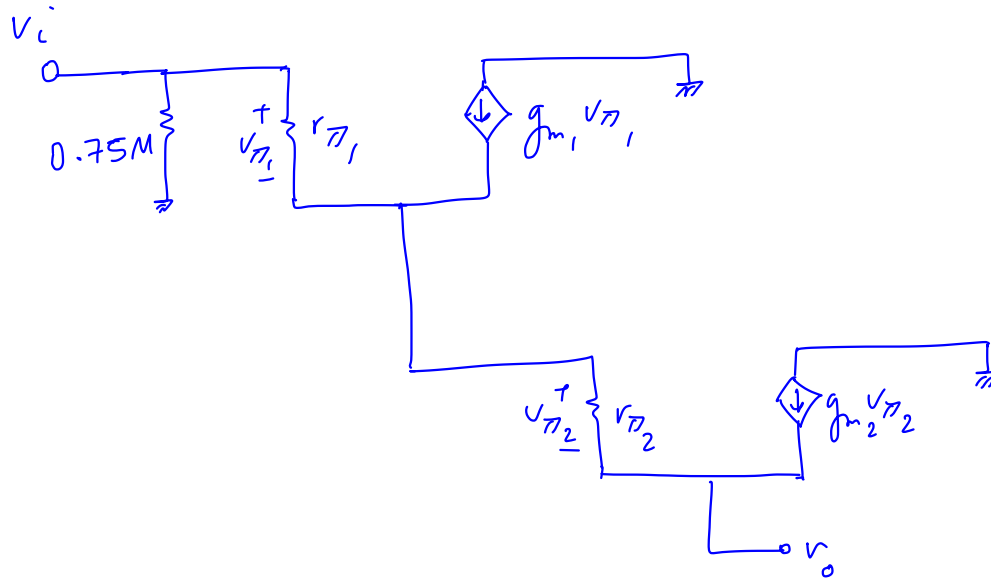

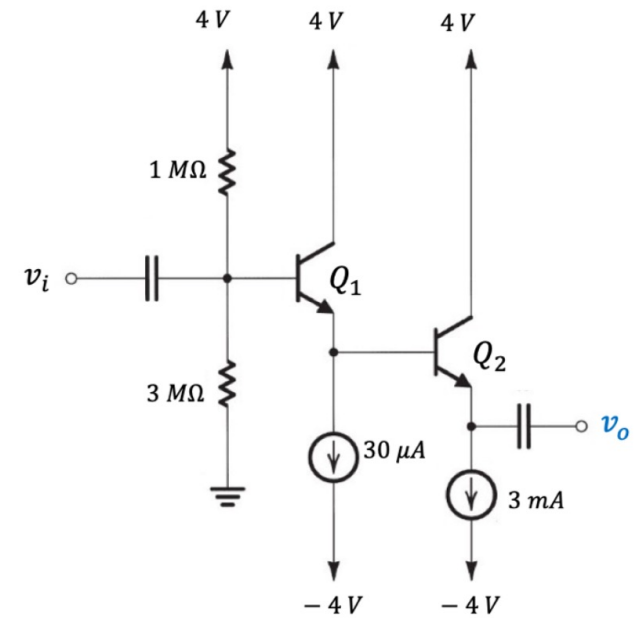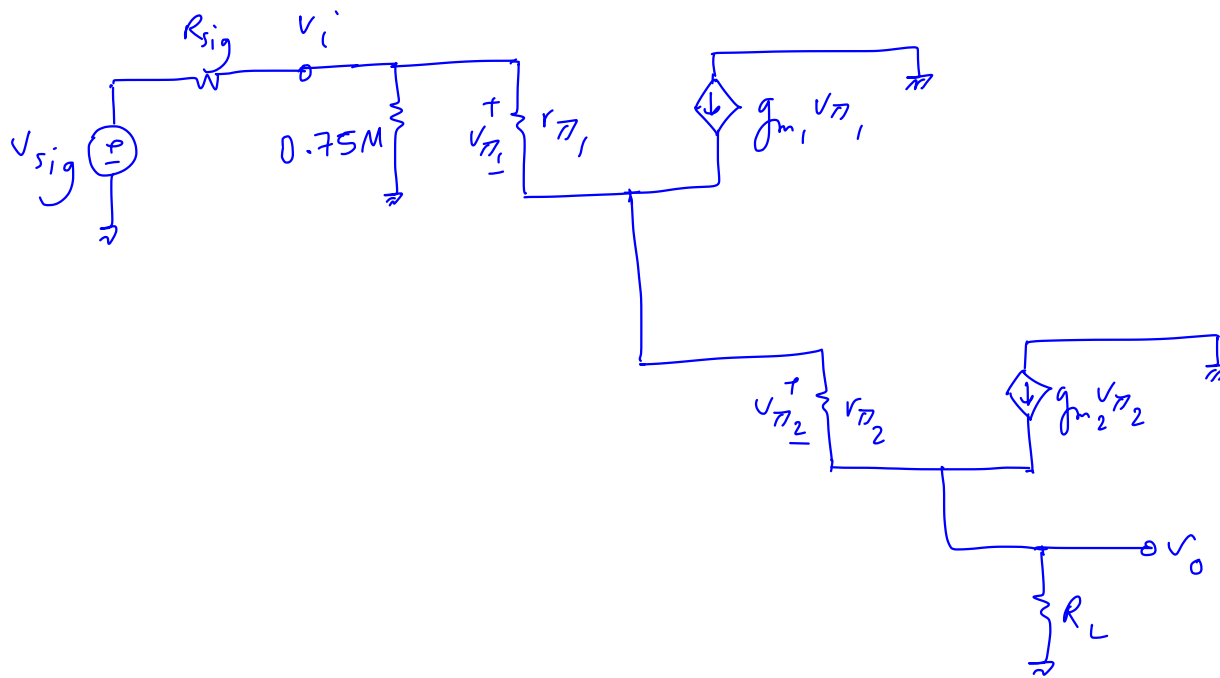
## Practice problem 2.

Small signal circuit After adding the load  
and the signal source:



## Practice problem 2.

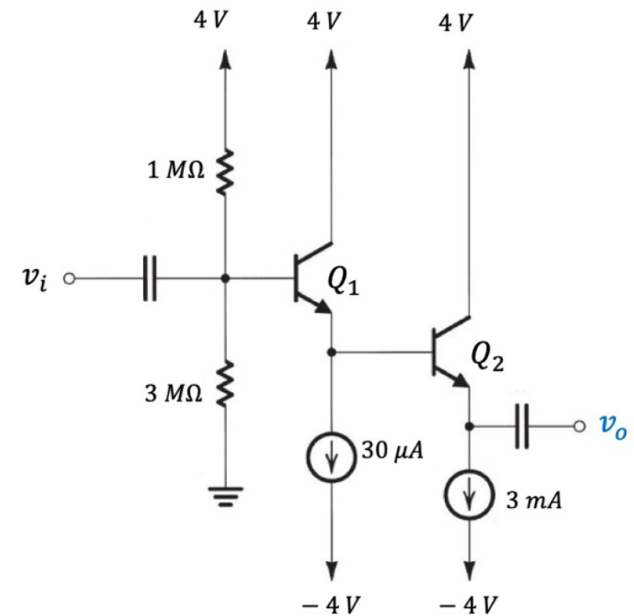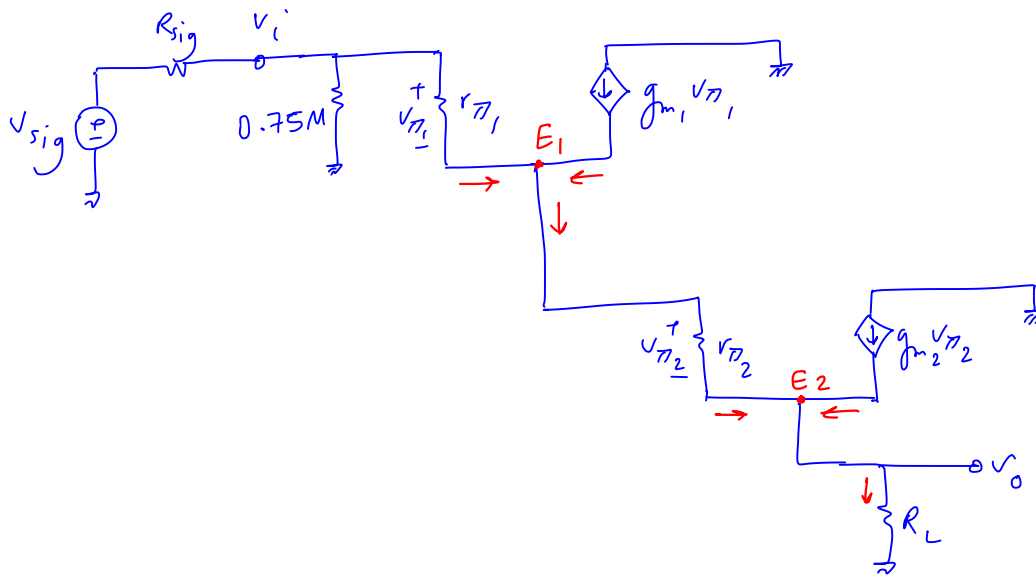


KCL at  $E_2$ :

$$g_{m2} v_{\pi 2} + \frac{v_{\pi 2}}{r_{\pi 2}} = \frac{V_o}{R_L} \rightarrow v_{\pi 2} = \frac{1}{R_L} \left( \frac{1}{g_{m2} + \frac{1}{r_{\pi 2}}} \right) V_o$$

KCL at  $E_1$ :

$$g_{m1} v_{\pi 1} + \frac{v_{\pi 1}}{r_{\pi 1}} = \frac{v_{\pi 2}}{r_{\pi 2}} \rightarrow v_{\pi 1} = \frac{1}{r_{\pi 2}} \left( \frac{1}{g_{m1} + \frac{1}{r_{\pi 1}}} \right) v_{\pi 2}$$


## Practice problem 2.

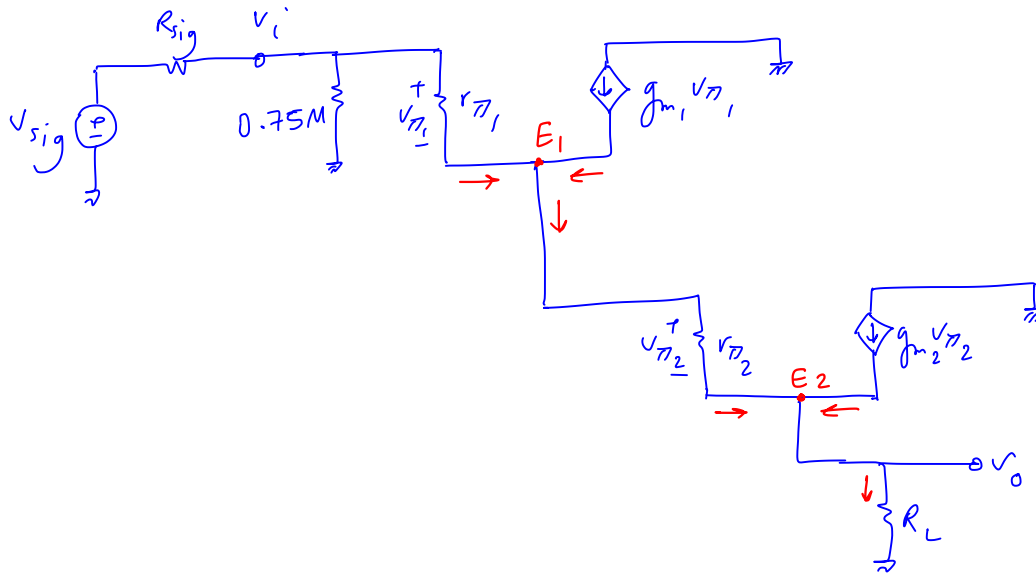


$$v_{\pi_2} = \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) v_o$$

$$v_{\pi_1} = \frac{1}{r_{\pi_2}} \left( \frac{1}{g_{m_1} + \frac{1}{r_{\pi_1}}} \right) v_{\pi_2}$$
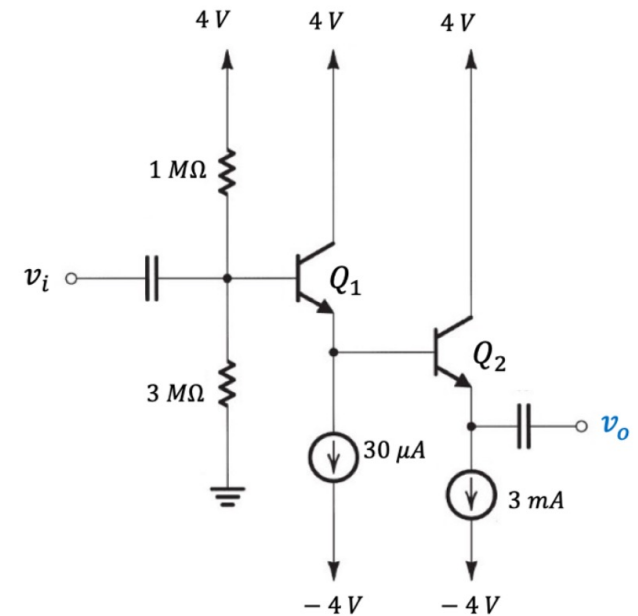
$$v_{\pi_1} = \frac{1}{r_{\pi_2}} \left( \frac{1}{g_{m_1} + \frac{1}{r_{\pi_1}}} \right) \left( \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) \right) v_o$$




## Practice problem 2.

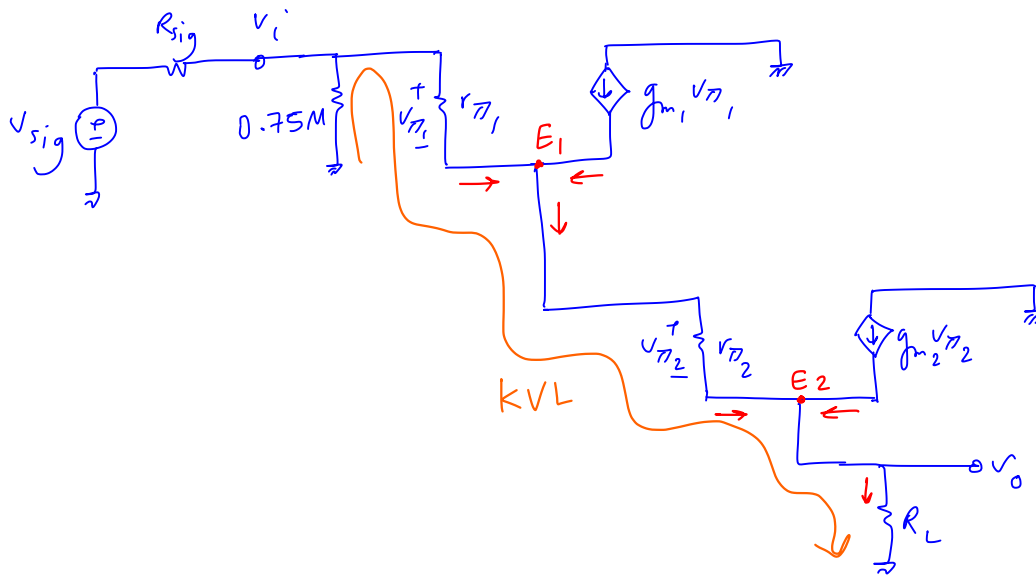


B<sub>1</sub>E<sub>2</sub> KVL :

$$V_i = v_{\pi_1} + v_{\pi_2} + v_o = V_o \left( \boxed{\frac{v_{\pi_1}}{V_o}} + \boxed{\frac{v_{\pi_2}}{V_o}} + \boxed{1} \right)$$
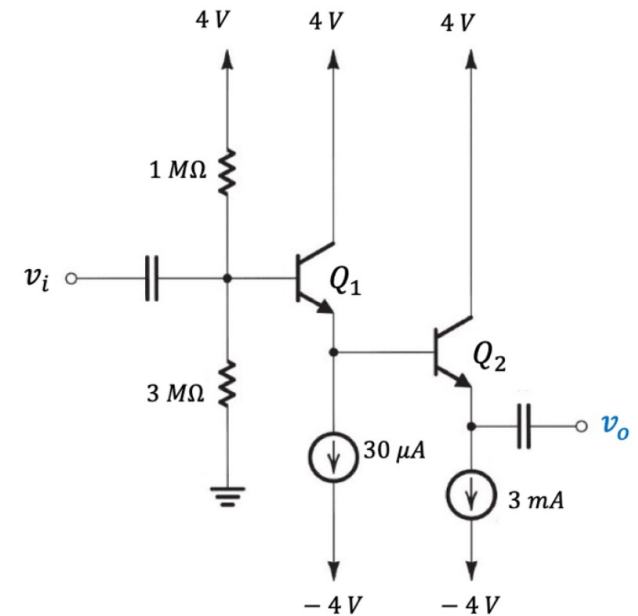
$$V_i = V_o \left( \boxed{\frac{1}{r_{\pi_2}} \left( \frac{1}{g_{m_1} + \frac{1}{r_{\pi_1}}} \right) \left( \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) \right)} + \boxed{\frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right)} + \boxed{1} \right)$$




## Practice problem 2.

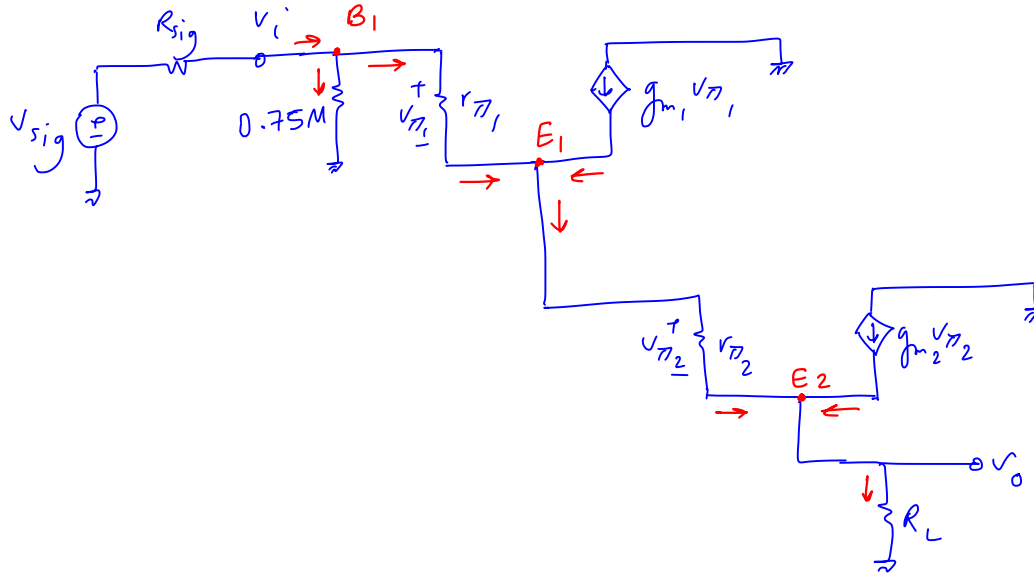

KCL at  $B_1$

$$\frac{v_{sig} - v_i}{R_{sig}} = \frac{v_i}{0.75 M\Omega} + \frac{v_{\pi 1}}{r_{\pi 1}}$$
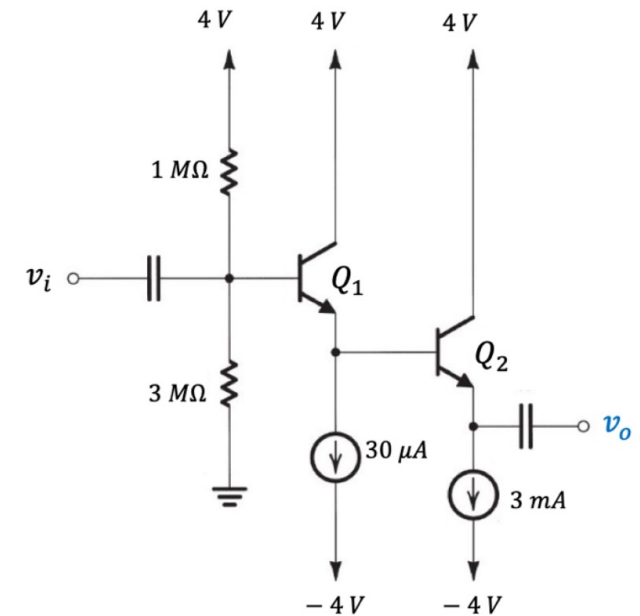
$$v_{sig} = \left(1 + \frac{R_{sig}}{0.75 M\Omega}\right) v_i + \frac{R_{sig}}{r_{\pi 1}} v_{\pi 1}$$




## Practice problem 2.

$$V_{sig} = \left(1 + \frac{R_{sig}}{0.75 \text{ M}\Omega}\right) \boxed{V_i} + \boxed{\frac{R_{sig}}{r_{\pi_1}} V_{\pi_1}}$$

$$\boxed{\frac{R_{sig}}{r_{\pi_1}} V_{\pi_1}} = \frac{R_{sig}}{r_{\pi_1}} \left( \frac{1}{r_{\pi_2}} \left( \frac{1}{g_{m_1} + \frac{1}{r_{\pi_1}}} \right) \left( \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) \right) \right) V_o$$
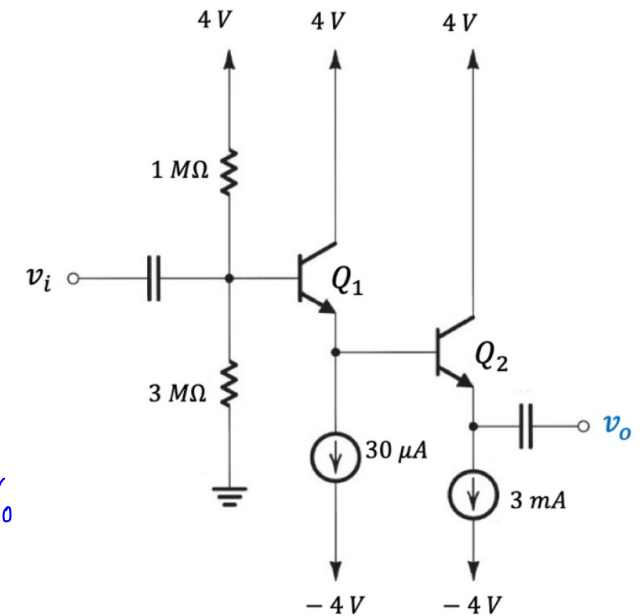
$$\boxed{V_i} = V_o \left( \frac{1}{r_{\pi_2}} \left( \frac{1}{g_{m_1} + \frac{1}{r_{\pi_1}}} \right) \left( \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) \right) + \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) + 1 \right)$$



# Practice problem 2.

$$V_{sig} = \left(1 + \frac{R_{sig}}{0.75 \text{ M}\Omega}\right) \boxed{V_i} + \boxed{\frac{R_{sig}}{r_{\pi_1}} V_{\pi_1}}$$

$$\boxed{\frac{R_{sig}}{r_{\pi_1}} V_{\pi_1}} = \frac{R_{sig}}{r_{\pi_1}} \left( \frac{1}{r_{\pi_2}} \left( \frac{1}{g_{m_1} + \frac{1}{r_{\pi_1}}} \right) \left( \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) \right) \right) V_o$$

$$\boxed{V_i} = V_o \left( \frac{1}{r_{\pi_2}} \left( \frac{1}{g_{m_1} + \frac{1}{r_{\pi_1}}} \right) \left( \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) \right) + \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) + 1 \right)$$

$$\frac{V_{sig}}{V_o} = \left(1 + \frac{R_{sig}}{0.75 \text{ M}\Omega}\right) \left( \frac{1}{r_{\pi_2}} \left( \frac{1}{g_{m_1} + \frac{1}{r_{\pi_1}}} \right) \left( \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) \right) + \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) + 1 \right) +$$

$$\frac{R_{sig}}{r_{\pi_1}} \left( \frac{1}{r_{\pi_2}} \left( \frac{1}{g_{m_1} + \frac{1}{r_{\pi_1}}} \right) \left( \frac{1}{R_L} \left( \frac{1}{g_{m_2} + \frac{1}{r_{\pi_2}}} \right) \right) \right)$$

$$\boxed{\frac{V_o}{V_{sig}} \approx 0.997 \text{ V/V}}$$

