

ECE 35, Fall 2021

Your sequence number

Quiz 4

/ 12

Last name

First + middle  
name(s)

PID


**Instructions:**

- Read each problem completely and thoroughly before beginning
- All calculations need to be done on these sheets
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit

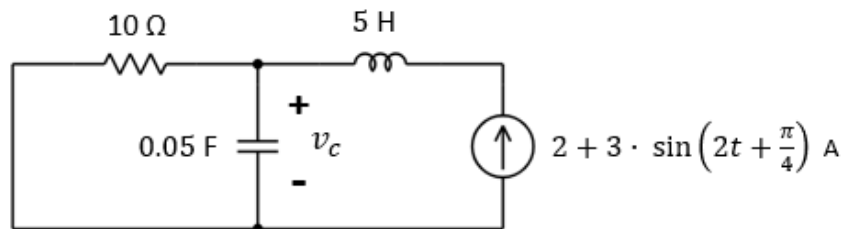(1) The system is in steady state.

Find  $v_c\left(-\frac{\pi}{4} \text{ s}\right)$ , i.e.,  $v_c$  at time  $t = -\frac{\pi}{4} \text{ s}$ . (6 points)

$v_c\left(-\frac{\pi}{4} \text{ s}\right)$



(2) The AC circuit below is in steady-state, and you are not told what the  $\omega$  of the source is.

The phasor diagram shows the phasors of  $\mathbf{i}_S$  and  $\mathbf{i}_a$ .

The rectangular boxes represent two circuit elements. You are told that one of them is an inductor of **1 mH** (but you don't know if this one corresponds to  $i_a$  and  $i_b$ ). The other one can be a resistor of  $2\ \Omega$ , a capacitor of  $2\ \text{mF}$  or an inductor of  $2\ \text{mH}$ .

Finally, you are also told that the maximum value of the  $i_S(t)$  waveform is **4 A** and the maximum value of the  $i_a(t)$  waveform is **3 A**. (6 points)

(a) What is the maximum value of the  $i_b(t)$  waveform?



$i_b^{max}$


(b) With  $i_a(t)$  expressed as  $A \cdot \cos(\omega t + \theta)$ , and  $A > 0$ , what is the value of  $\theta$ ?

$\theta$

(c) What is the value of  $\omega$ ? (Note: if you eliminate an option for what the mystery element could be, make sure it is clear why)

$\omega$

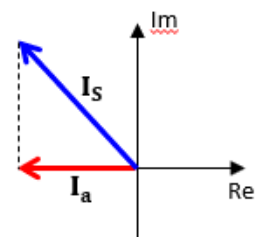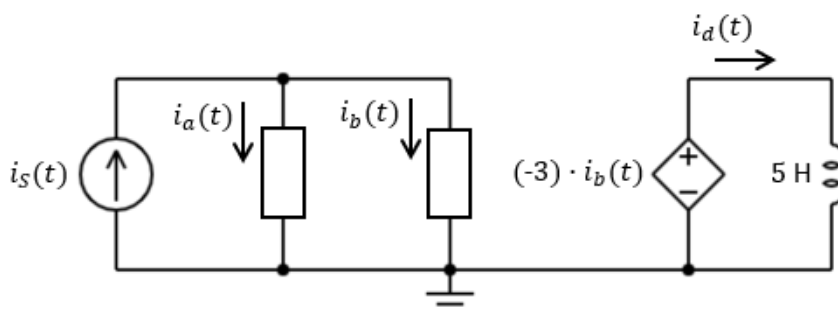

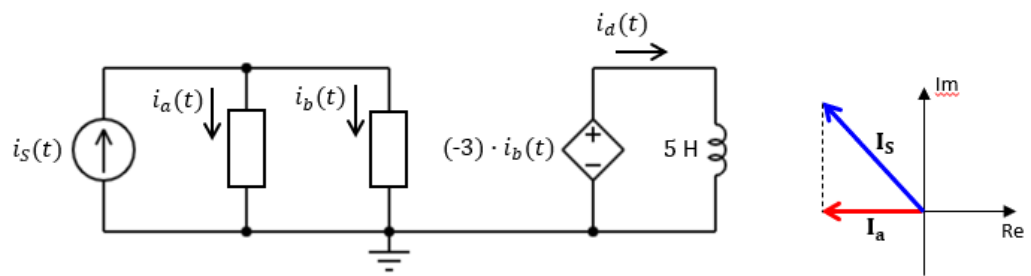

## ECE35 Equation Sheet

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

**Trigonometry:**

$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$	$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$						
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$	$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$	$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	$\infty$
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$						