
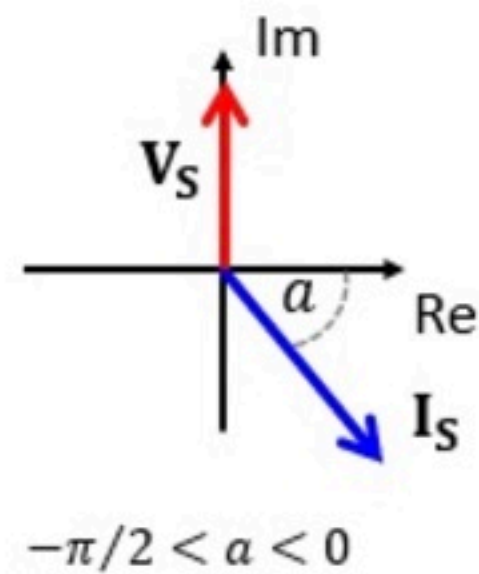


# Phasors 019

0 of 5 attempts made

The AC circuit below has  $\omega = W_1$  and is in steady state. The phasor diagram shows the phasors of  $v_S$  and  $i_S$ . You are given the angle  $a$ , and vector lengths  $|\mathbf{I}_S| = A_1$  and  $|\mathbf{V}_S| = A_2\sqrt{b}$ . The diagram is not necessarily drawn to scale (but  $\mathbf{V}_S$  is along the imaginary axis). The element in the center (rectangular box) is either an inductor or a capacitor but you are not told which.

- At what time does  $v_R$  reach its maximum value? Enter  $k = t_0 \cdot \frac{12}{\pi}$ , where  $t_0$  is the first time that the maximum is reached, for  $t_0 \geq 0$ . (Hint: convert  $a$  to radians first)
- We select the mystery element such that  $|\mathbf{I}_a|$  is minimized (note that this is the current through the voltage source). What is the mystery element type (enter 1 for capacitor, 2 for inductor)? What is its value  $X$  (i.e., either the capacitance or the inductance value, in F or H respectively)?

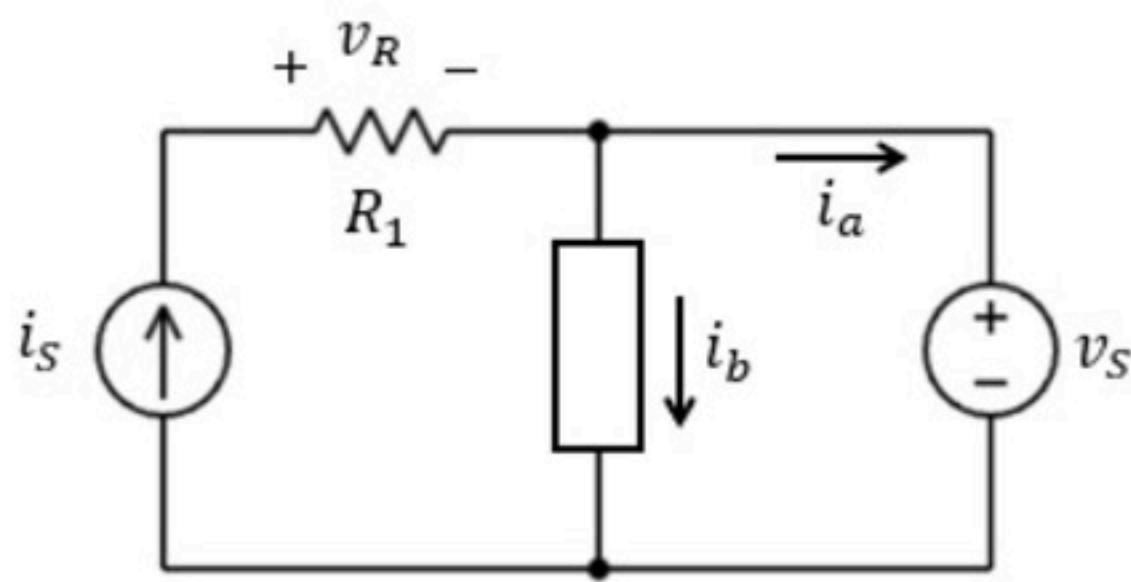

Given Variables:

W1 : 4 rad/s

a : -30 degrees

A1 : 1 A

A2 : 10 V

b : 3

R1 : 1 ohm

Calculate the following:

k (s) :

0.5



Type :

2



X :

5

