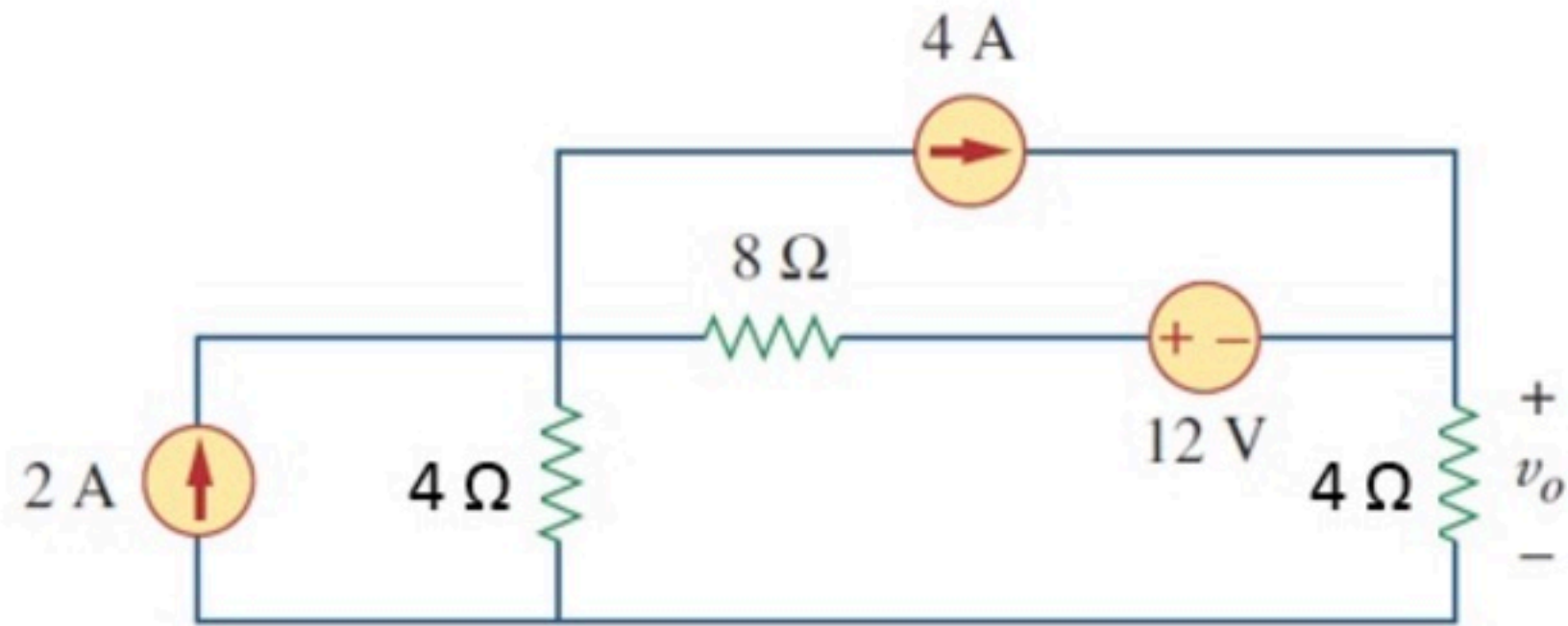


PP Circuit theorems 004

Unlimited Attempts.

Use superposition to find v_o .



Given Variables:

...

Calculate the following:

v_o (V) :

7



Hint: Mind the signs.