


PP First order circuits 004

Unlimited Attempts.

The switch has been in position A for a long time. At time $t = 0$, the switch moves to position B.

Find $v_1(t) = D1$ for $t = 0^-$
 $= A1 \cdot e^{-t/\tau_{au1}} + B1$ for $t > 0$

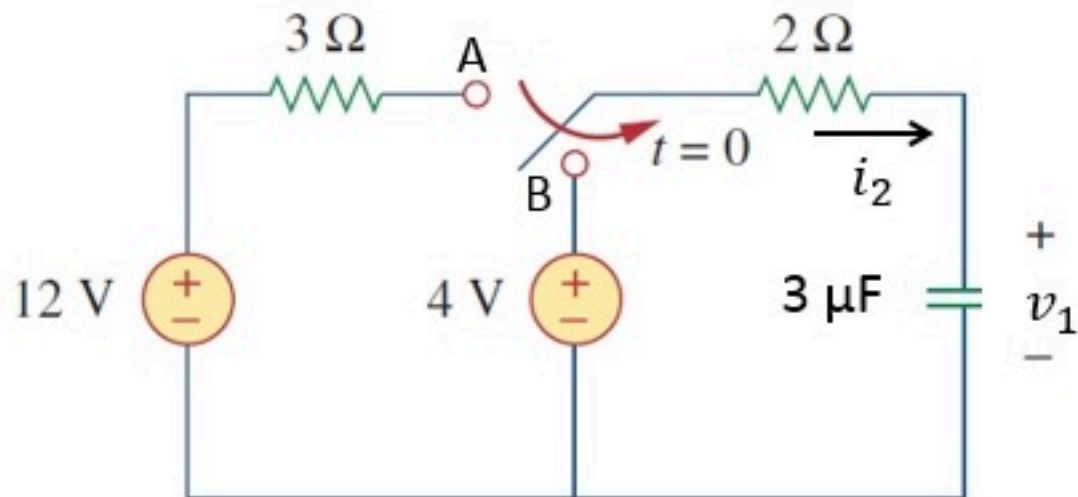Find $i_2(t) = D2$ for $t = 0^-$
 $= A2 \cdot e^{-t/\tau_{au2}} + B2$ for $t > 0$



Given Variables:

...

Calculate the following:

D1 (V) :

12

✓

A1 (V) :

8

✓

B1 (V) :

4

✓

τ_{au1} (us) :

6

✓

D2 (A) :

0

✓

A2 (A) :

-4

✓

B2 (A) :

0

✓

τ_{au2} (us) :

6

✓

Hint: Find the capacitor voltage before and after the switch