

# PP - Basic concepts 001

Problem has been graded.

---

What is the current  $i$  flowing through the element at time  $t = 0.25$  seconds, when the charge flow is  $q(t)$ ?

$$q(t) = \frac{6}{\pi} \cdot \cos(10\pi t) \quad \mu\text{C}$$

Given Variables:

. : . .

Calculate the following:

$i$  (mA) :

-0.06



---

 Hint: Pay attention to the units

# PP - Basic concepts 002

Problem has been graded.

---

A current of 5 mA is flowing through a conductor. What is the amount of charge  $q$  that has passed through any cross-section of this conductor in 10 seconds?

Given Variables:

...

Calculate the following:

$q$  (C) :

0.05




 Hint: Pay attention to the units

# PP - Basic concepts 003

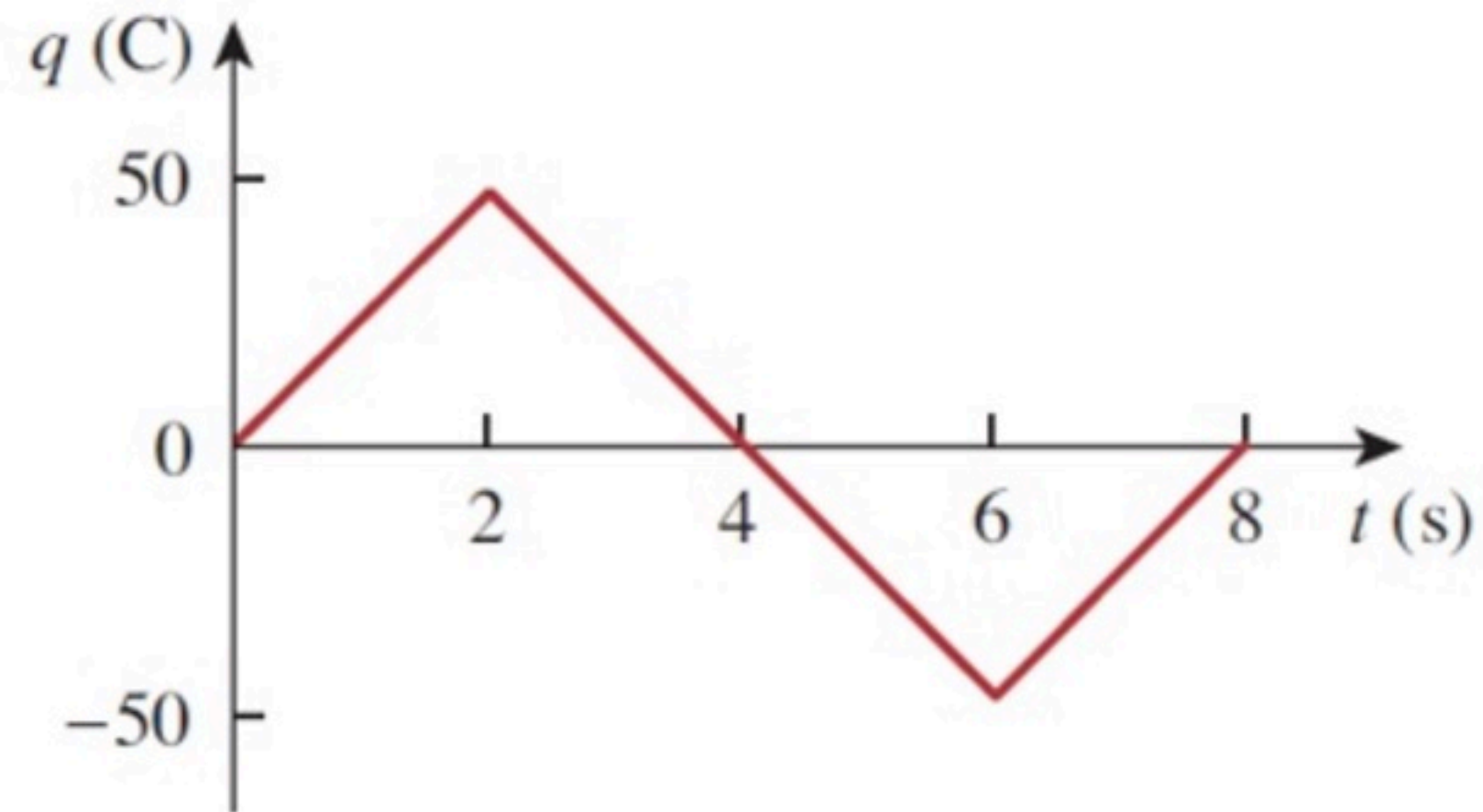Problem has been graded.

What is the current  $i$  flowing through the element at time  $t = 7$  seconds, when the charge flow is as shown in the figure?



Given Variables:

...

Calculate the following:

$i$  (A) :

25



Hint: Current is the derivative of charge at a certain time




# PP - Basic concepts 004

Problem has been graded.

The current flowing through an element is shown in the figure. At time  $t = 0$ , the charge that has passed through the element already is 2 C.

What is the total amount of charge  $q_1$  that has passed through the element at time  $t_1 = 3$  seconds?

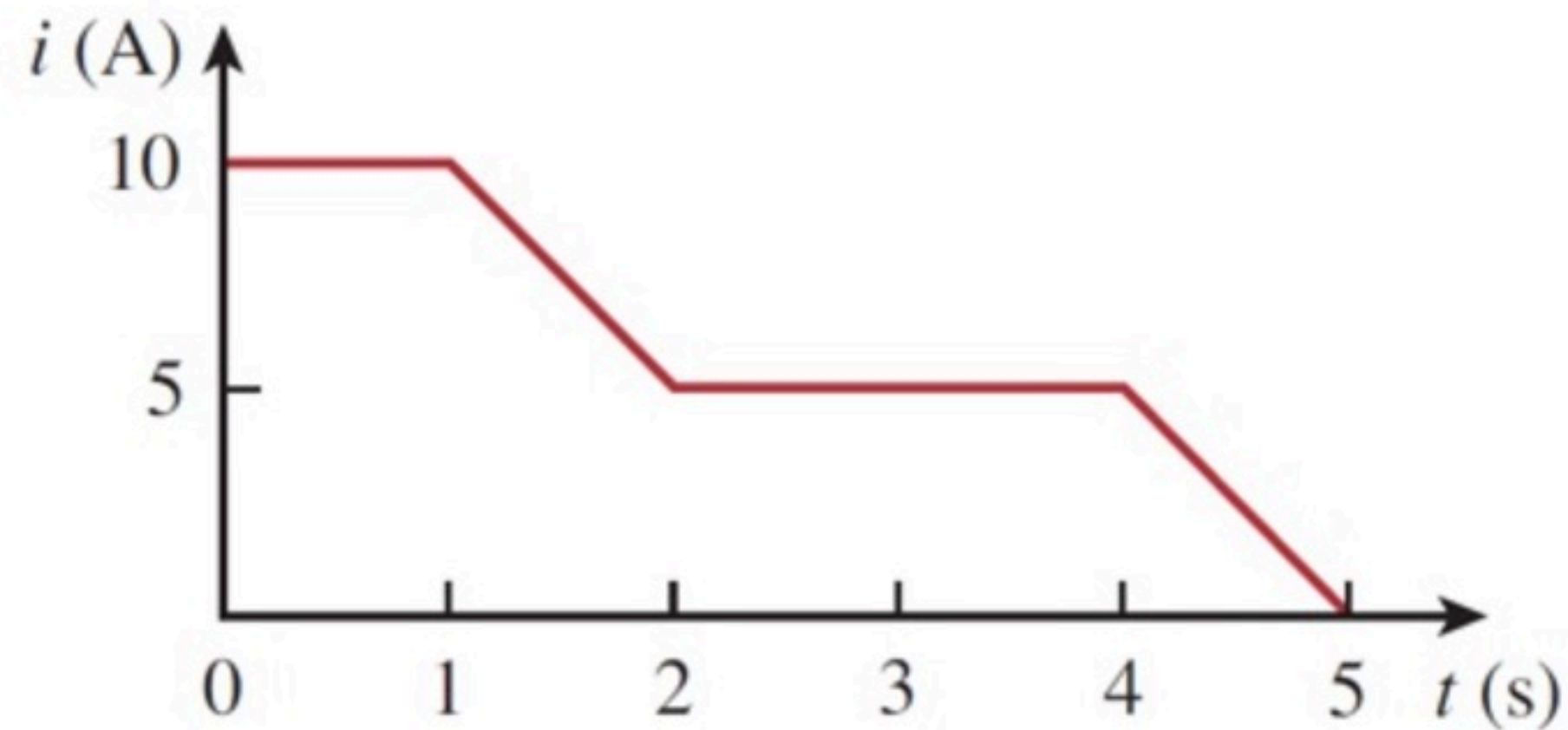What is the total amount of charge  $q_2$  that has passed through the element at time  $t_2 = 5$  seconds?



Given Variables:

...

Calculate the following:

$q_1$  (C) :

24.5

✓

$q_2$  (C) :

32


✓

Hint: Don't forget the initial charge


# PP - Basic concepts 005

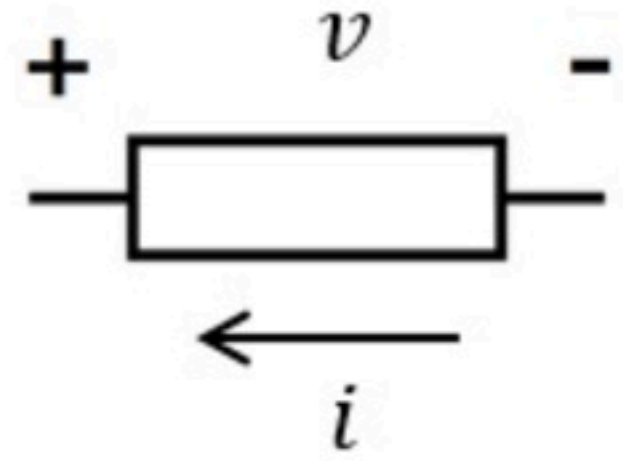Problem has been graded.


Find the power  $P_1$  received by this element:



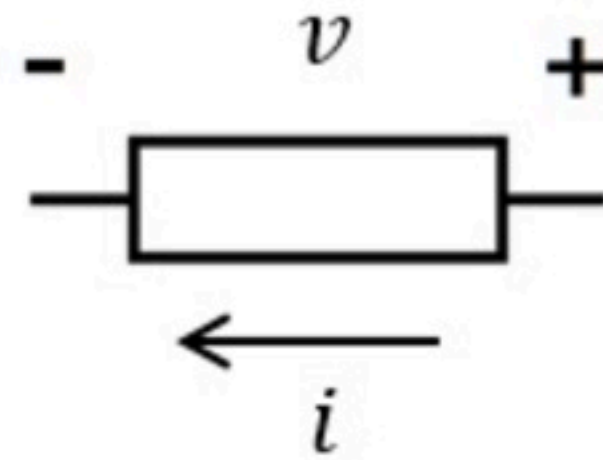Find the power  $P_2$  received by this element:



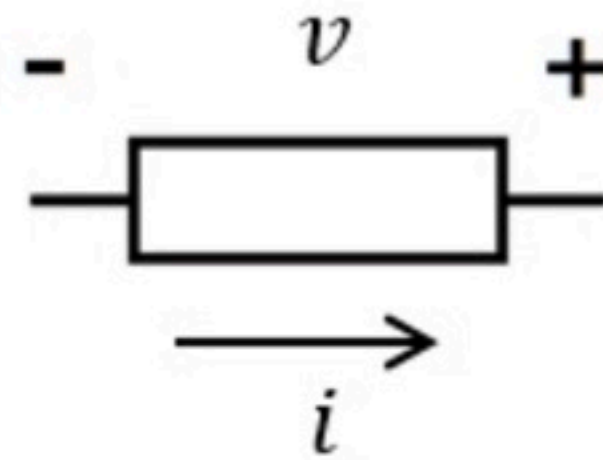Find the power  $P_3$  supplied by this element:



Given Variables:

$v : 2 \text{ V}$

$i : -3 \text{ A}$

Calculate the following:

$P_1 \text{ (W) :}$

6



$P_2 \text{ (W) :}$

-6



$P_3 \text{ (W) :}$

-6



Hint: Convert first to passive sign convention




# PP - Basic concepts 007

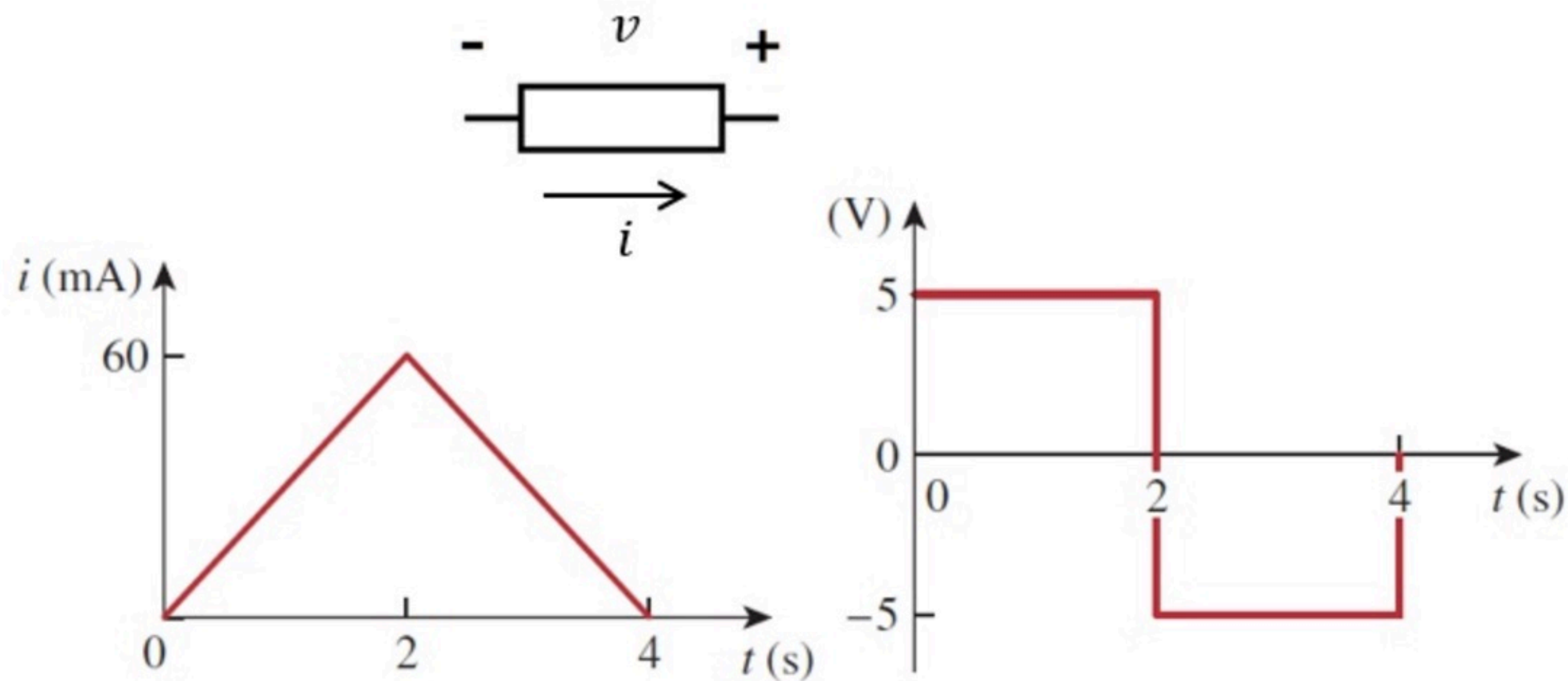Problem has been graded.

The current flowing through an element and the voltage across this element are shown in the figures.

Find the total energy  $E$  received by the element for the period time  $0 < t < 3$  s.



Given Variables:

...

Calculate the following:

$E$  (J) :


-0.075



# PP - Basic concepts 008

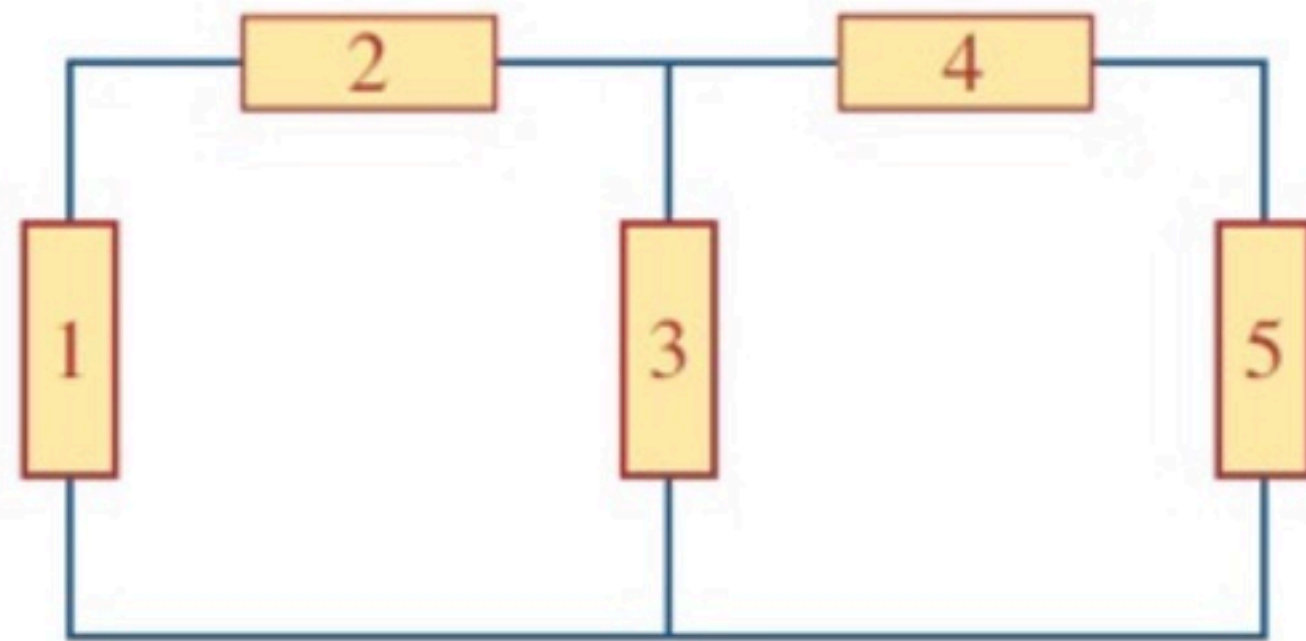Problem has been graded.

The figure shows a circuit with 5 circuit elements.



Element 1 supplies 3 W  
Element 2 supplies -5 W  
Element 3 receives 8 W  
Element 4 receives -1 W

How much power  $P$  does element 5 supply?

Given Variables:

$\therefore \dots$

Calculate the following:

$P$  (W) :

9

