
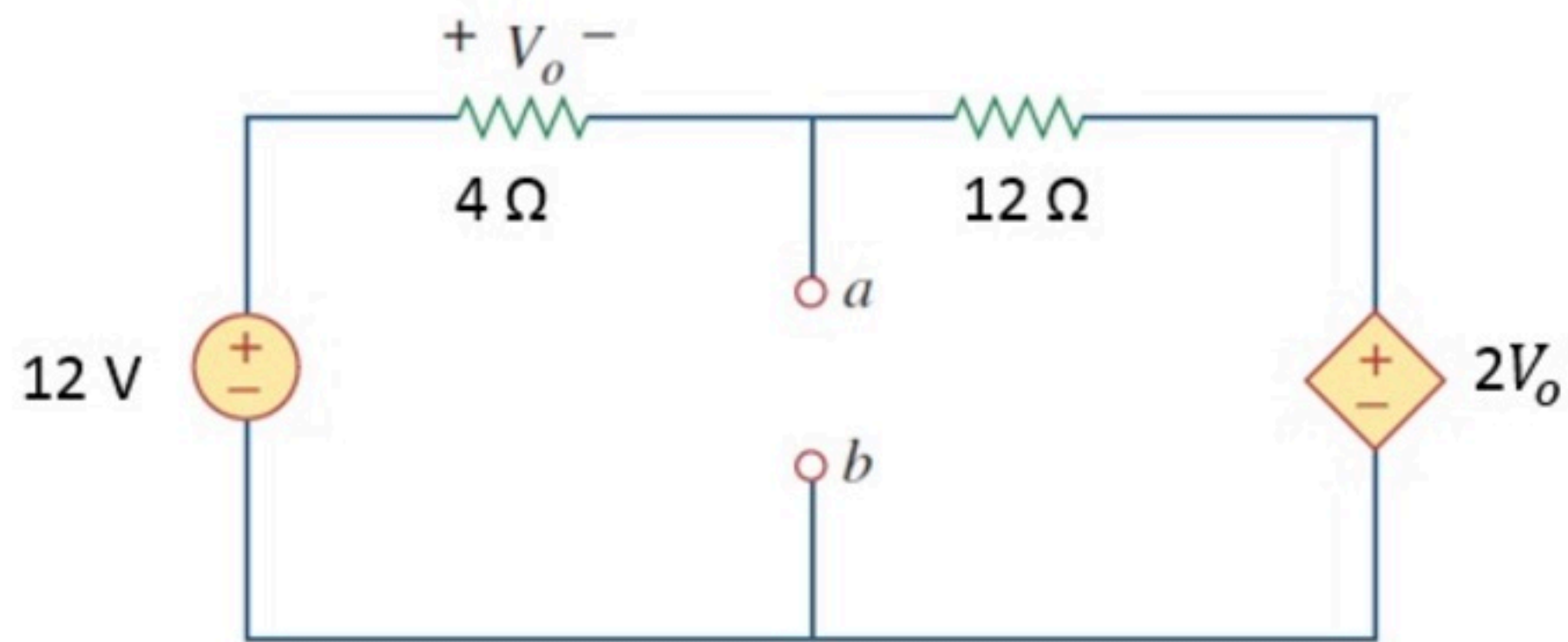


PP Circuit theorems 011

Unlimited Attempts.

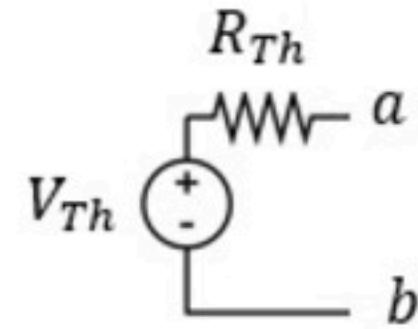Find the Thevenin equivalent model of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

V_{th} (V) :

10



R_{th} (ohm) :

2



Hint: Find V_{oc} ; and then I_{sc} or use a test source to find R_{th} .