

The resistance R_1 is a variable resistor that can take on values in the range $0 \leq R_1 \leq 24\Omega$.

1. Find the value of $R_1 = R_{1a}$ that maximizes current i_1 and the resulting current $i_1 = i_{1a}$.
2. Find the value of $R_1 = R_{1b}$ that maximizes voltage v_1 and the resulting current $v_1 = v_{1b}$.
3. Find the value of $R_1 = R_{1c}$ that maximizes the power received by R_1 and the resulting power P_{1c} .



$$V_s = 12 \text{ V}$$

$$I_s = 3 \text{ A}$$


$$R_2 = 12 \text{ ohm}$$

$$R_3 = 18 \text{ ohm}$$


$$R_4 = 24 \text{ ohm}$$

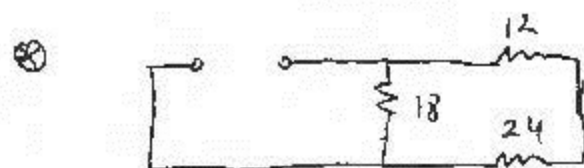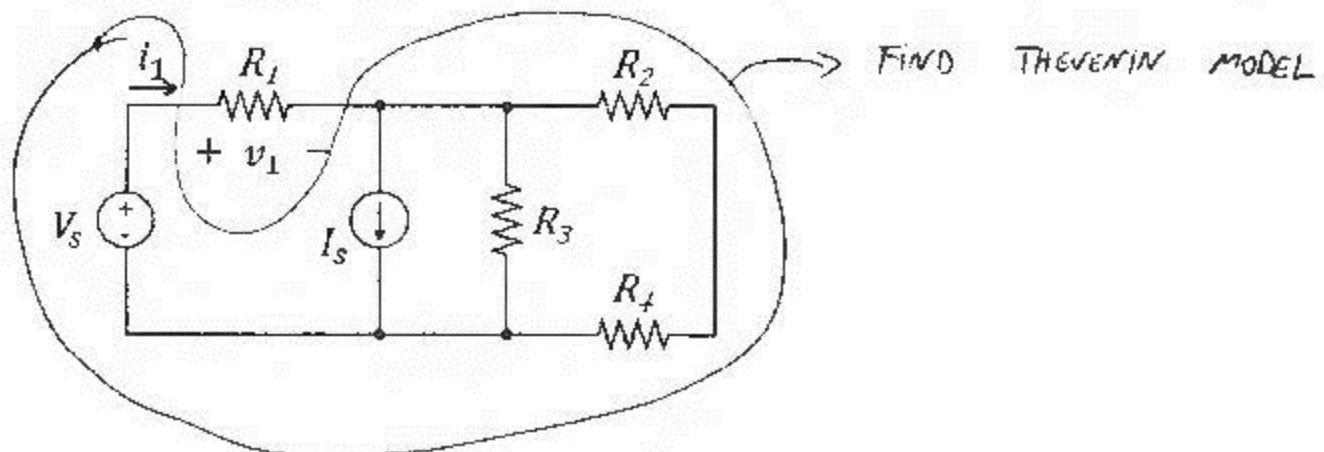

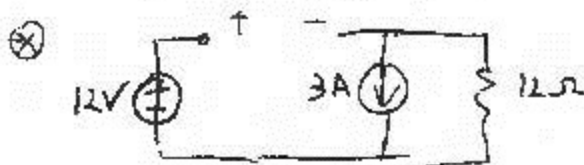
$$\Rightarrow R_{TH} = 18 \parallel (12 + 24) = \left(\frac{1}{18} + \frac{1}{36} \right)^{-1} = \left(\frac{3}{36} \right)^{-1} = 12 \Omega$$



SOURCE TRANSFORM

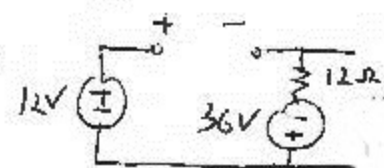

$$V_{oc} = 48 \text{ V}$$

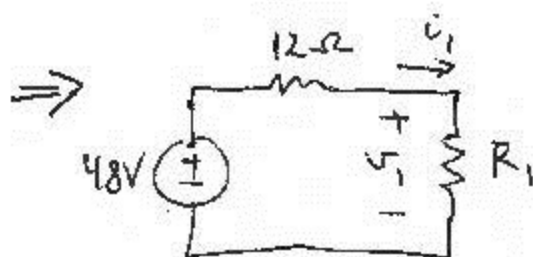

$$\textcircled{1} \quad R_1 = 0 \quad I_1 = \frac{48}{12} = 4 \Rightarrow \boxed{I_1 = 4 \text{ A}}$$

$$\textcircled{2} \quad R_1 = 24 \Omega \quad V_1 = 48 \cdot \frac{24}{24 + 12} = 48 \cdot \frac{2}{3} = 32 \Rightarrow \boxed{V_1 = 32 \text{ V}}$$

$$\textcircled{3} \quad R_1 = R_{TH} \Rightarrow \boxed{R_1 = 12 \Omega}$$

$$I = \frac{48}{24} = 2 \text{ A} \Rightarrow P = I^2 R = 4 \cdot 12$$

$$\boxed{P = 48 \text{ W}}$$