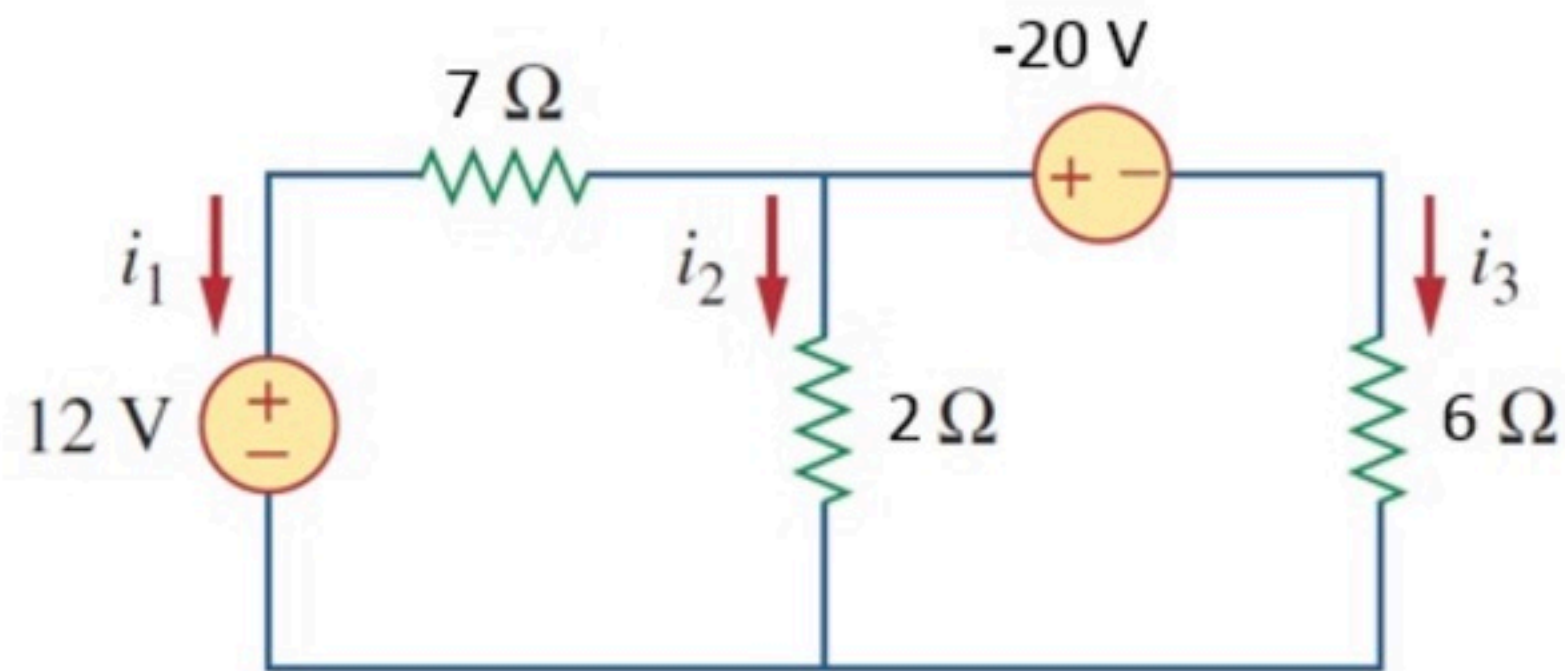


PP Nodal Mesh 011

Problem has been graded.

Find the currents i_1 , i_2 , and i_3 . Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

i_1 (A) :

-2



i_2 (A) :

-1



i_3 (A) :

3




Hint: Define 2 mesh currents

PP Nodal Mesh 012

Unlimited Attempts.

Find the value of v_o . Solve using mesh analysis.

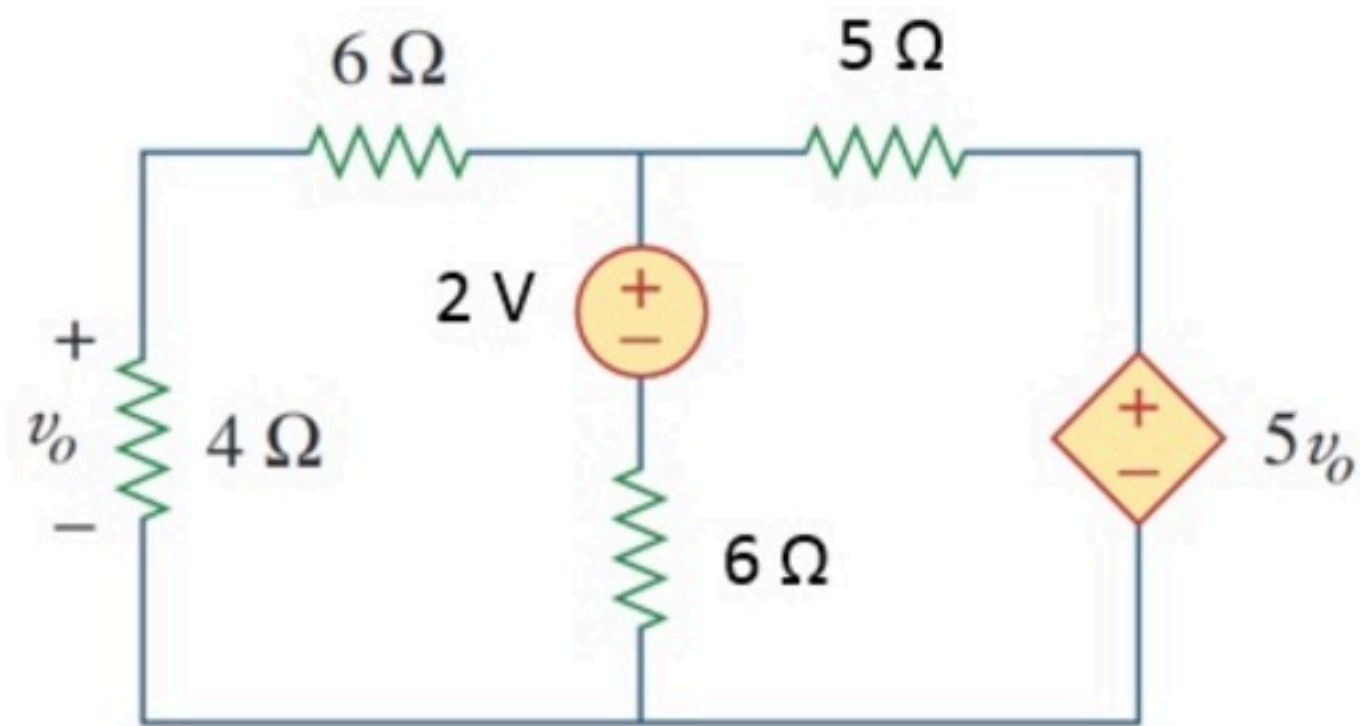For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

v_o (V) :

2




Hint: Ignore v_o at the start. Just find the two mesh currents.

PP Nodal Mesh 013

Unlimited Attempts.

Find the current I_o . Solve using mesh analysis.

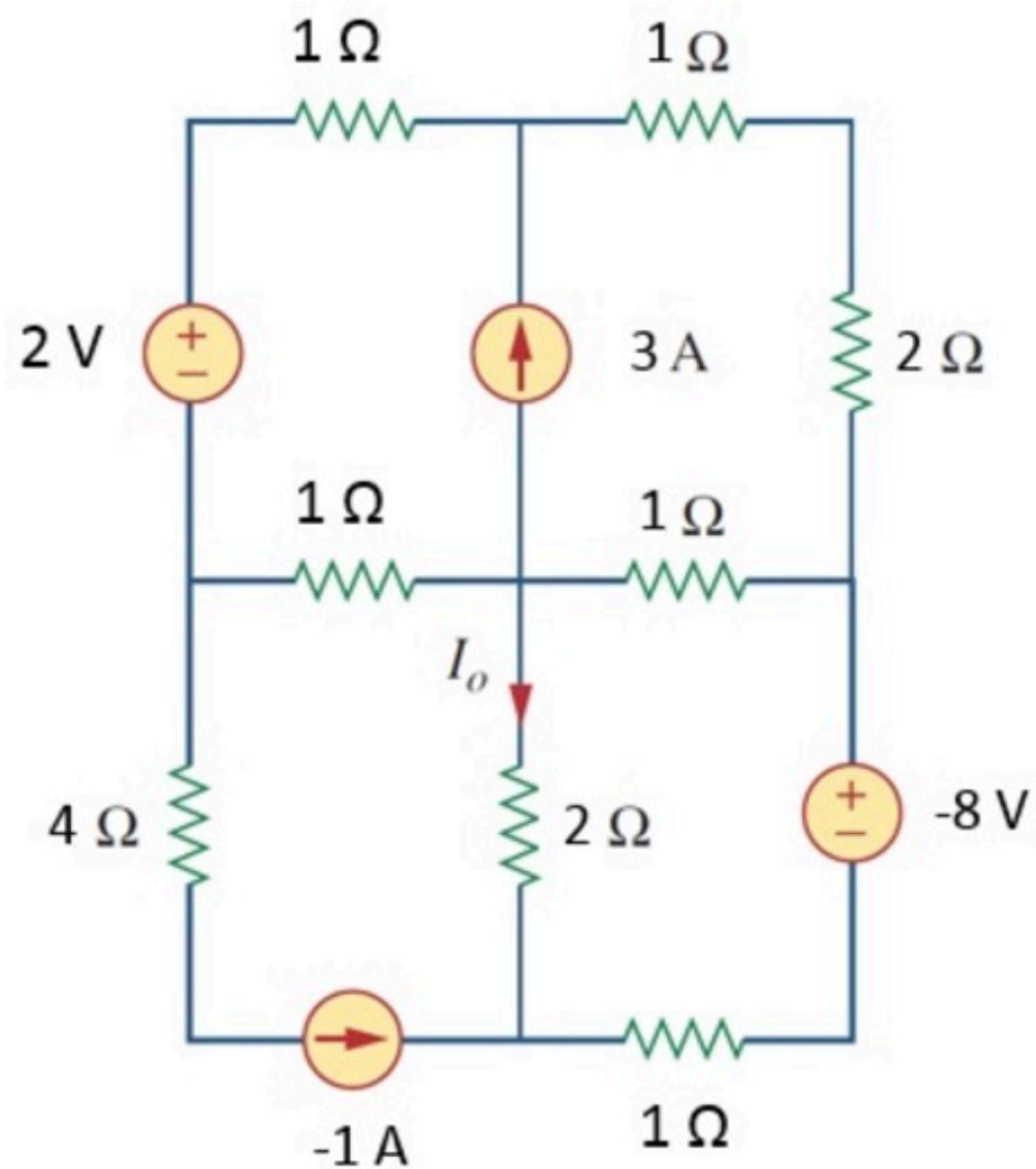For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

I_o (A) :

-2

Hint: Use a supermesh




PP Nodal Mesh 014

Unlimited Attempts.

Find the current i_o . Solve using mesh analysis.

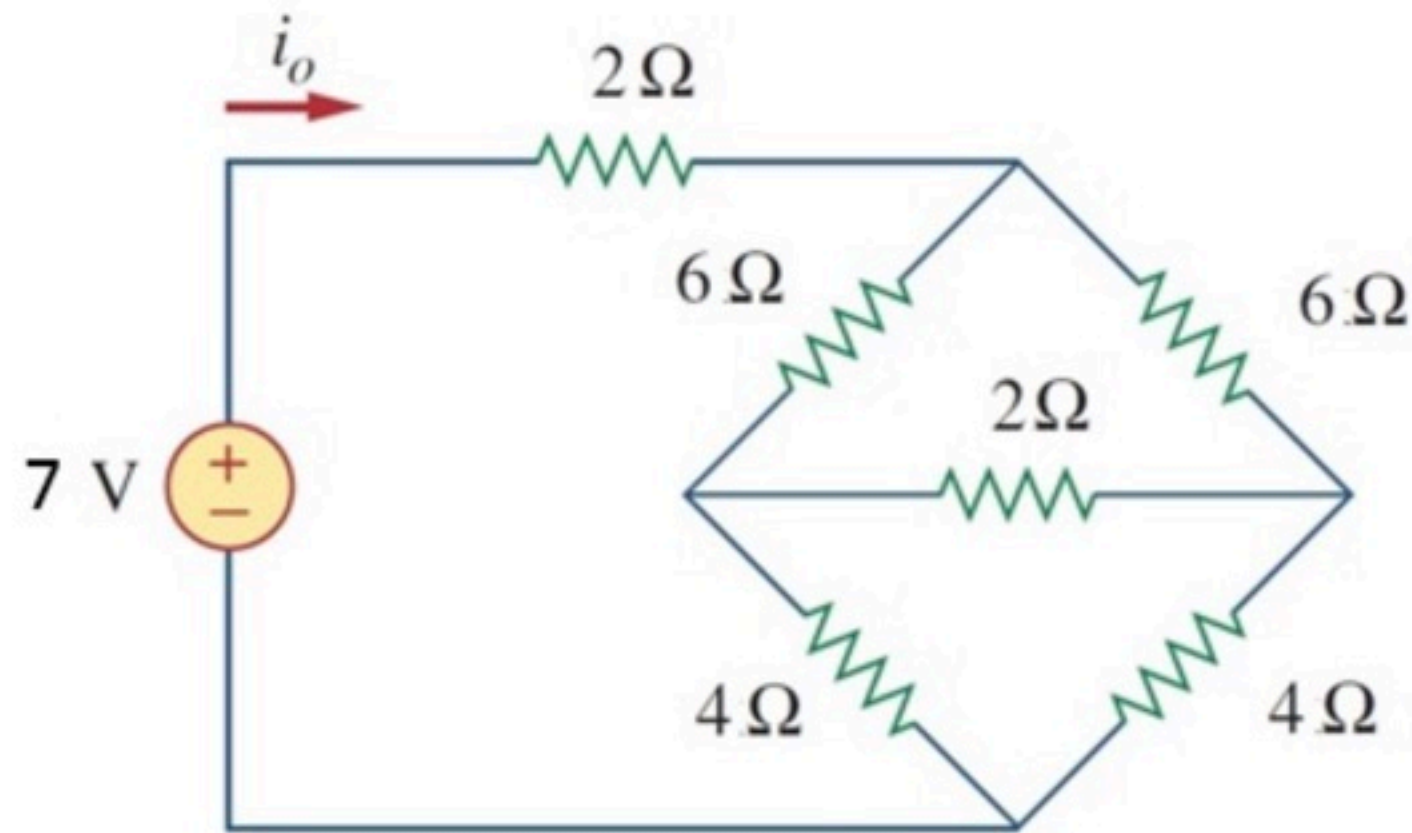For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

i_o (A) :

1




Hint: Symmetry will result in easier equations

PP Nodal Mesh 015

Unlimited Attempts.

Find the current i . Solve using mesh analysis.

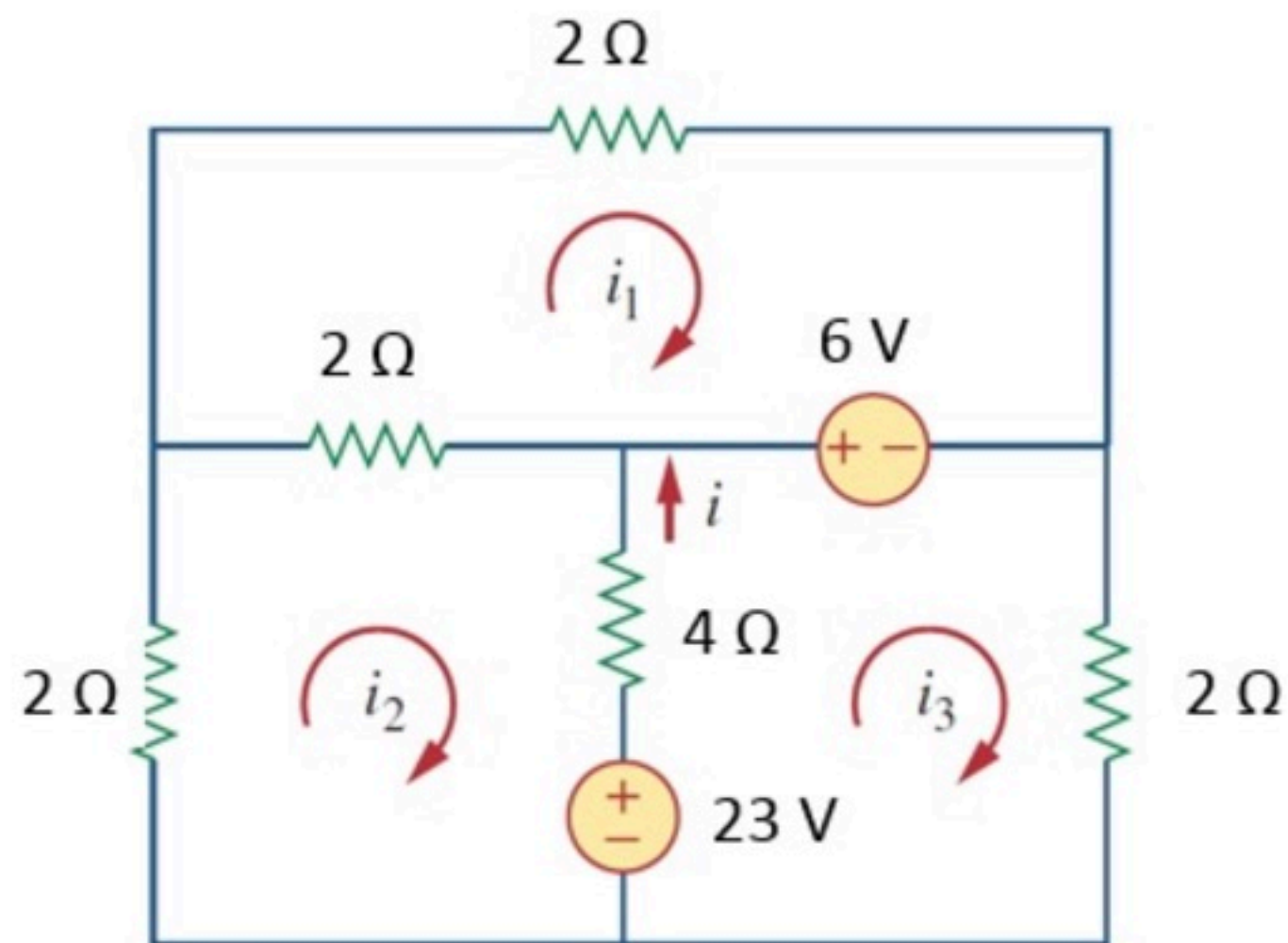For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

i (A) :

3.5




Hint: Mind the direction of the sources

PP Nodal Mesh 016

Unlimited Attempts.

Find the current i_o and the voltage v_{ab} . Solve using mesh analysis.

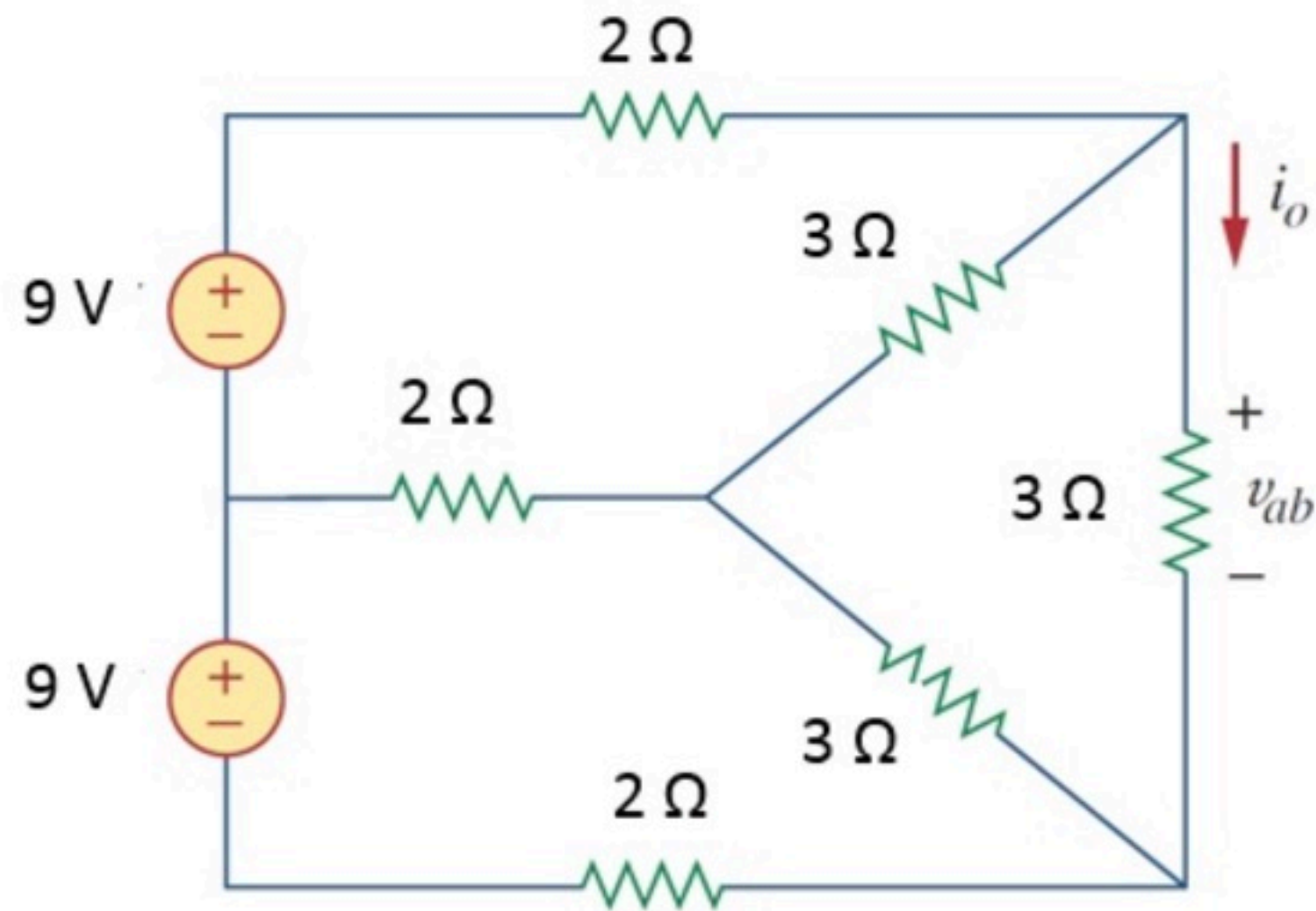For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

. . .

Calculate the following:

i_o (A) :

2



v_{ab} (V) :

6




Hint: Afterward, check the symmetry

PP Nodal Mesh 017

Unlimited Attempts.

Find the current i . Solve using mesh analysis.

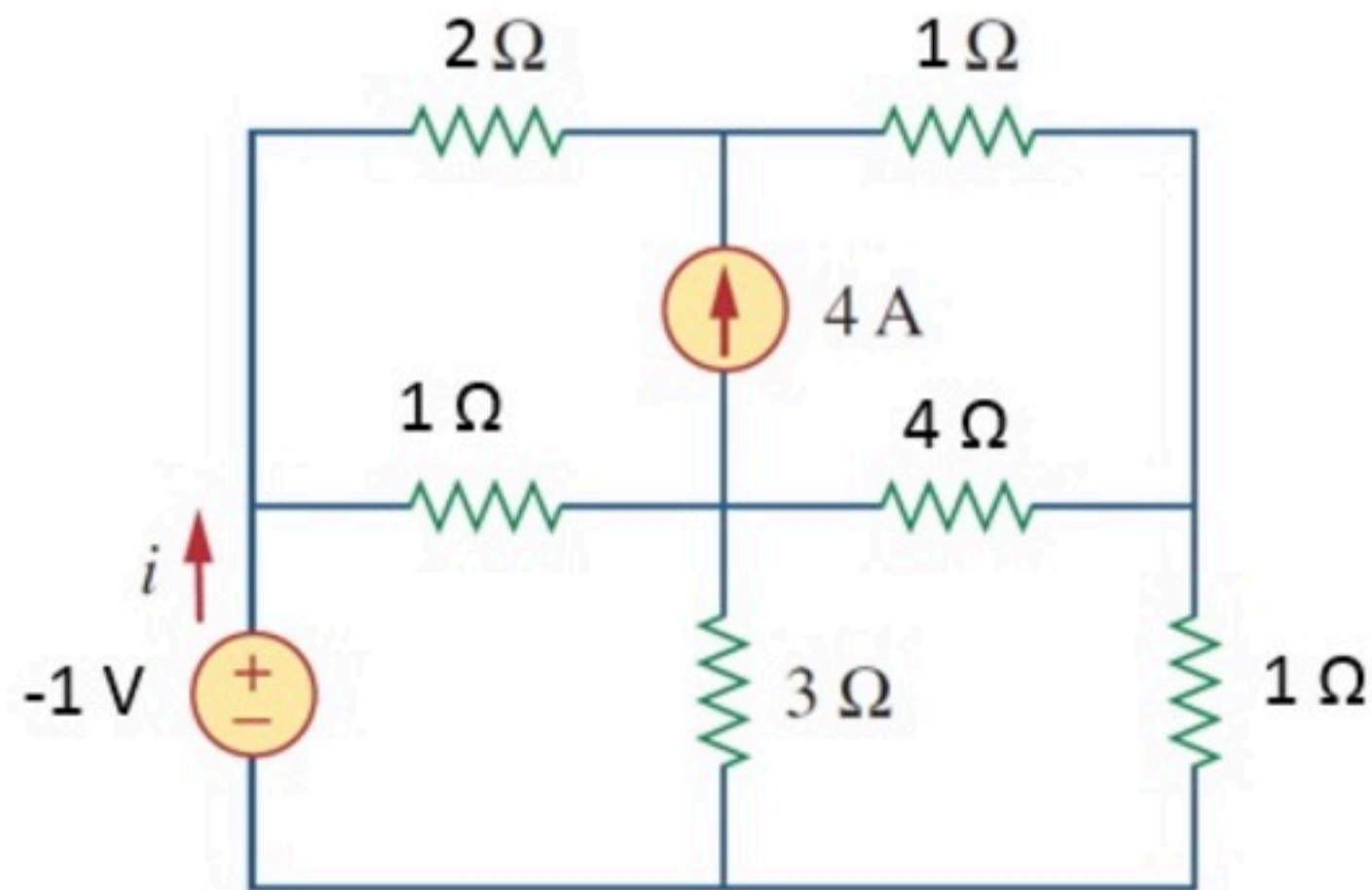For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

i (A) :

0




Hint: Use a supermesh

PP Nodal Mesh 018

Unlimited Attempts.

Find the current i_o and the voltage v_o . Solve using mesh analysis.

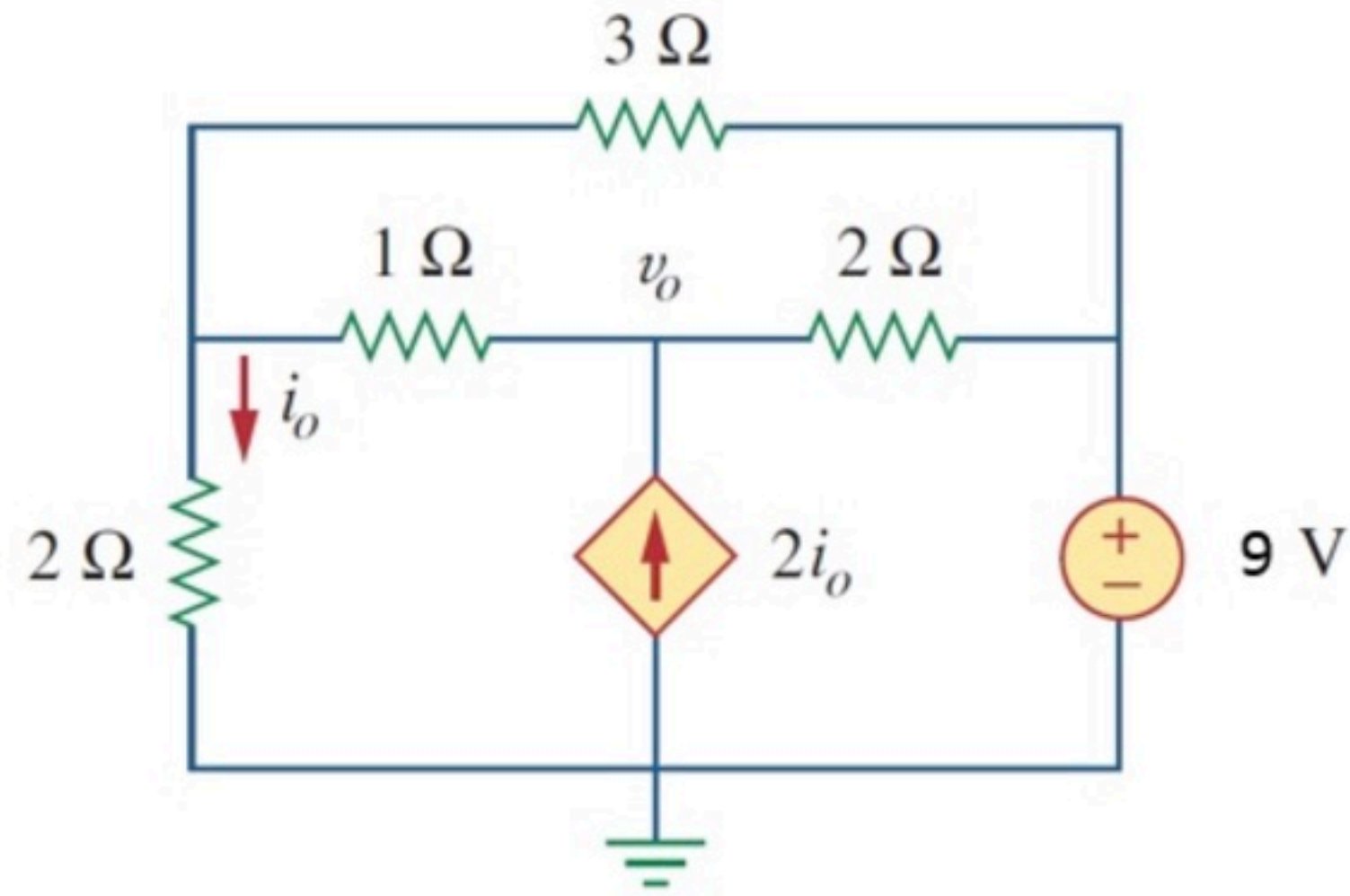For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

i_o (A) :

6



v_o (V) :

19




Hint: Use a supermesh

PP Nodal Mesh 019

Unlimited Attempts.

Find the current i_o . Solve using mesh analysis.

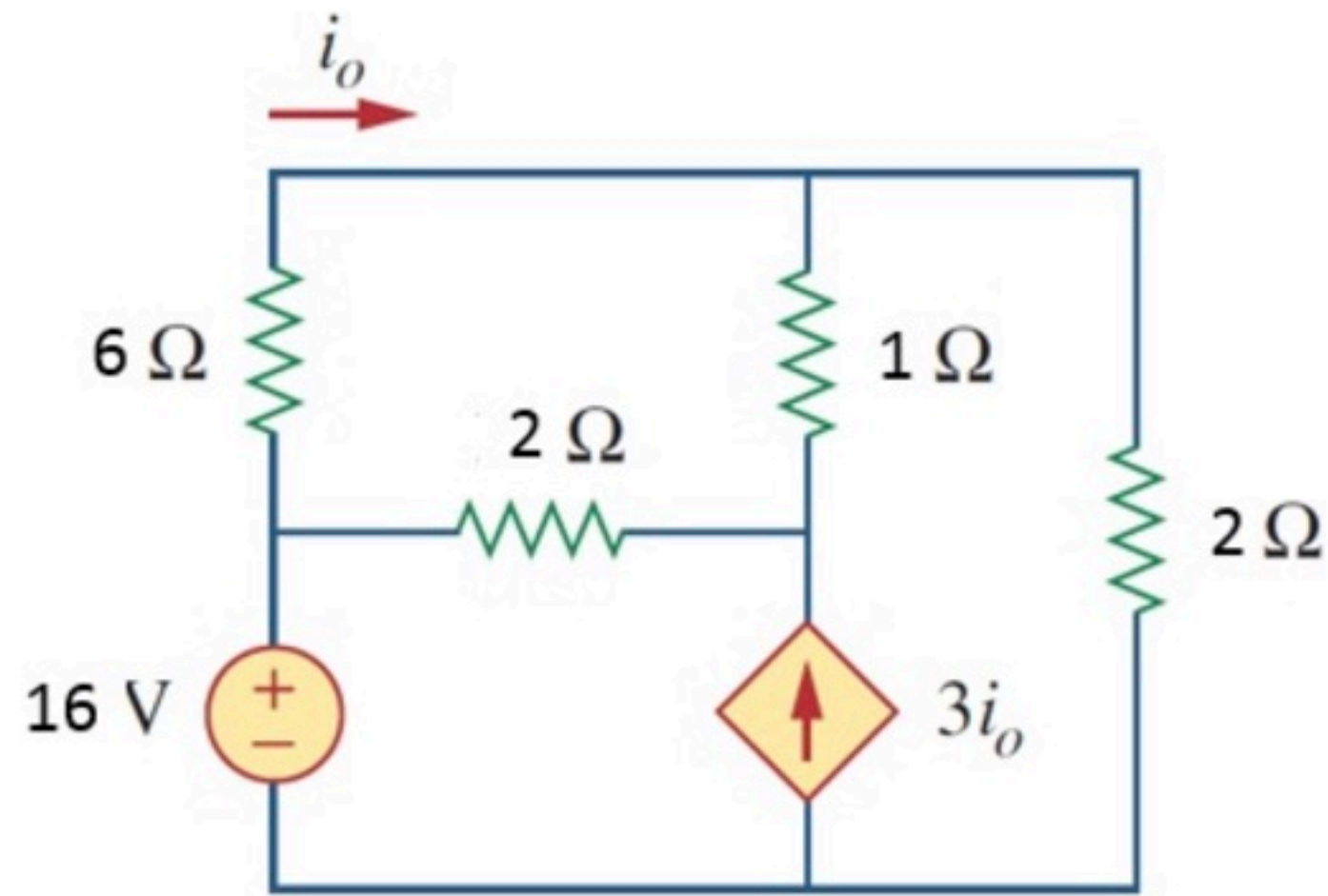For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

i_o (A) :

1




Hint: Use a supermesh

PP Nodal Mesh 020

Unlimited Attempts.

Find the voltage v_o . Solve using mesh analysis.

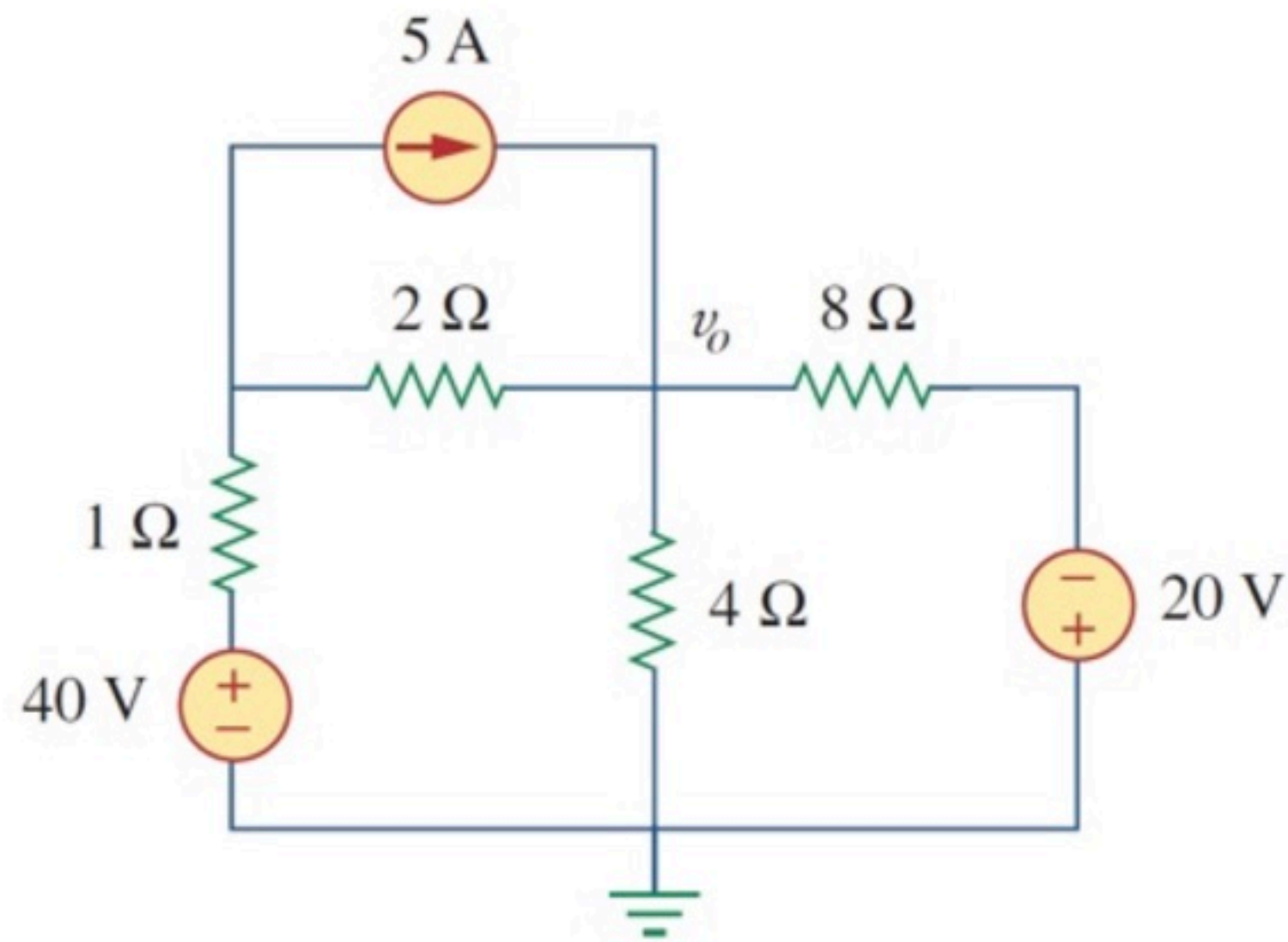For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

v_o (V) :

20



Hint: Can we find a mesh current directly?