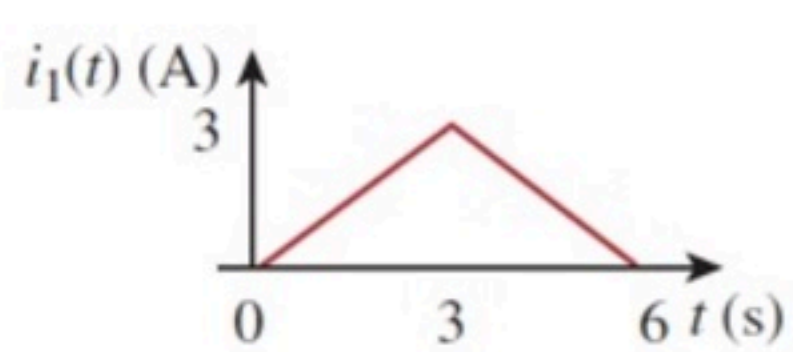
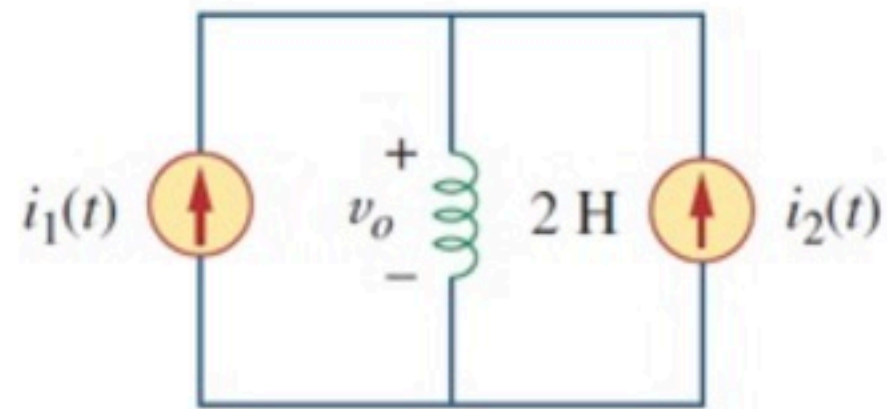


# PP Capacitors Inductors 006

Unlimited Attempts.

What is the voltage  $v_o$  at time  $t = 5$  s?



Given Variables:

...

Calculate the following:

$v_o$  (V) :

-6



Hint: Use superposition