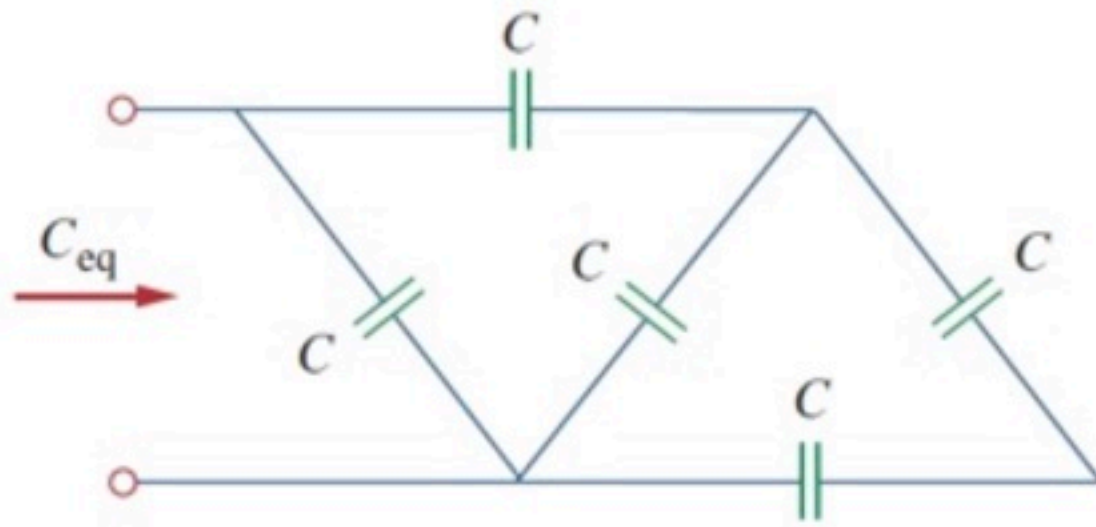


# PP Capacitors Inductors 008

Unlimited Attempts.

Find  $X = \frac{C_{eq}}{C}$ .



Given Variables:

...

Calculate the following:

X (F/F) :

1.6



Hint: Series/parallel equations are 'opposite' of those for resistors.