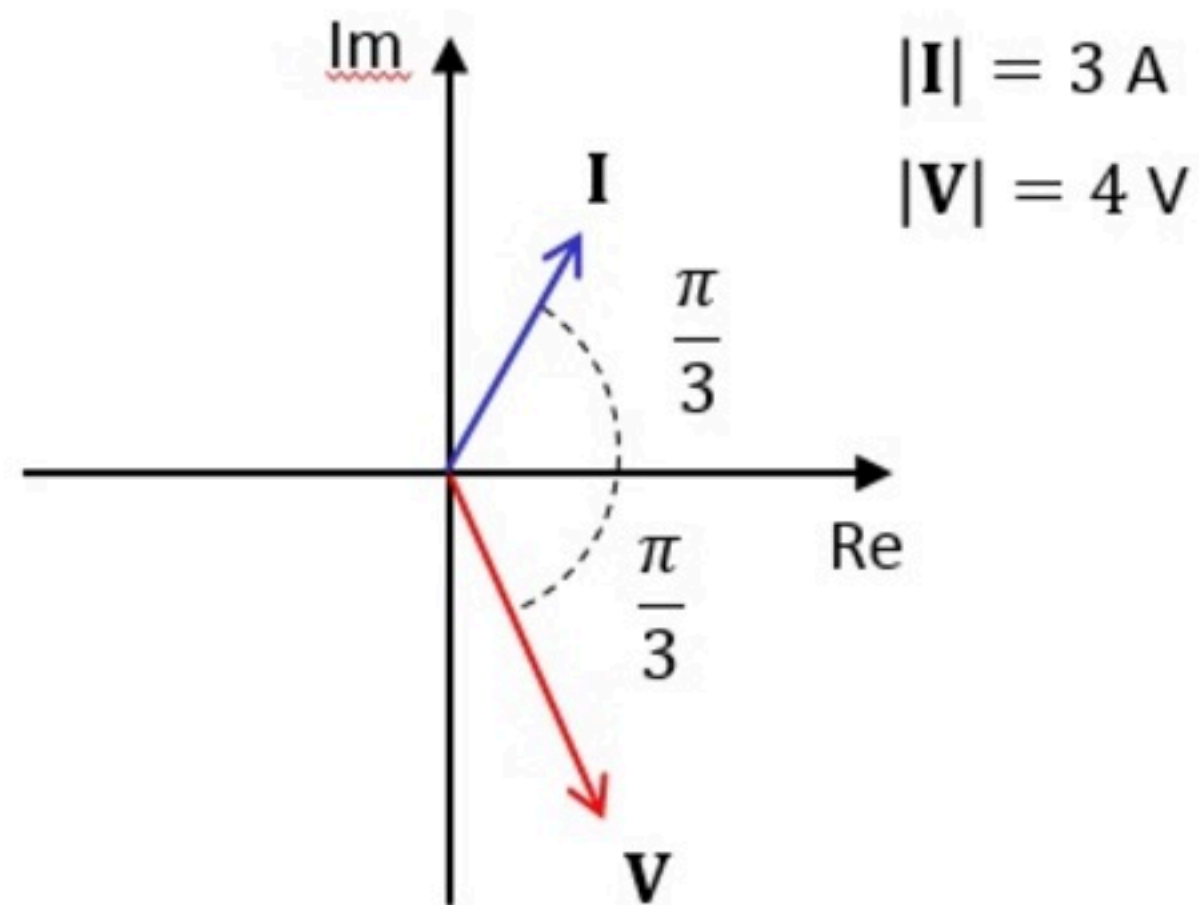


# PP AC power 001

Unlimited Attempts.

In the diagram are the phasors of the voltage across an element and the current through that element (according to the passive sign convention).

What is the average power  $P$  received by the element?



Given Variables:

...

Calculate the following:

$P$  (W) :

-3



Hint: Write average power as a function of the angle between the voltage and current.

$$I = 3 e^{j\frac{\pi}{3}}$$

$$V = 4 e^{-j\frac{\pi}{3}}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \cdot 4 \cdot 3 \cdot \cos\left(-\frac{\pi}{3} - \frac{\pi}{3}\right)$$

$$= \frac{1}{2} \cdot 4 \cdot 3 \cdot \cos\left(-\frac{2\pi}{3}\right)$$

$$= \frac{1}{2} \cdot 4 \cdot 3 \cdot \left(-\frac{1}{2}\right)$$

$$= -3$$

$$\boxed{P = -3W}$$


$\rightarrow$  So THIS ELEMENT  
 SUPPLIES POWER

# PP AC power 002

Unlimited Attempts.

In the diagram are the phasors of the voltage across an element and the current through that element (according to the passive sign convention).

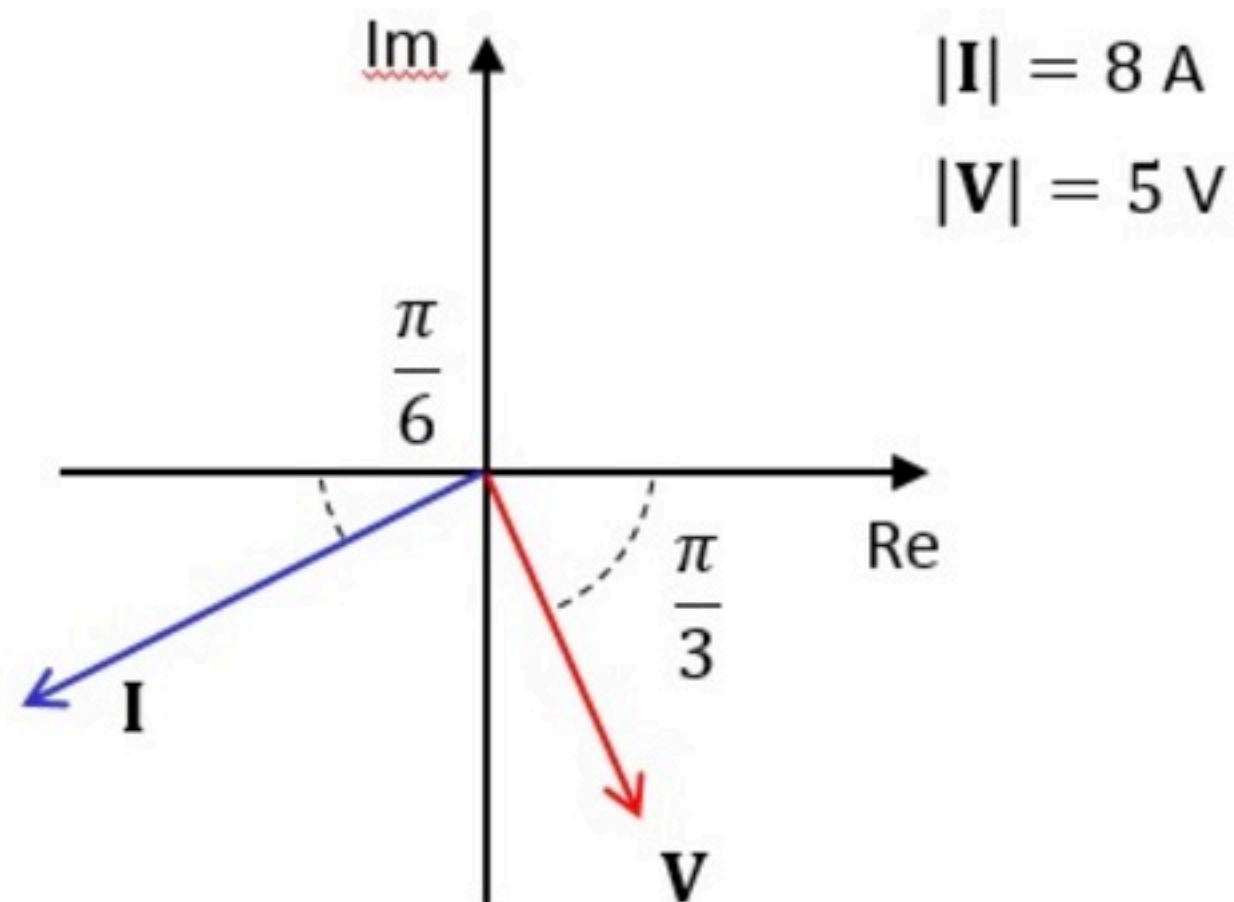What is the average power  $P$  received by the element?



Given Variables:

...

Calculate the following:

$P$  (W) :

0



Hint: Write average power as a function of the angle between the voltage and current.

$$I = 8 e^{-j \frac{5\pi}{6}}$$

$$V = 5 e^{-j \frac{\pi}{3}}$$

$$P = \frac{1}{2} \cdot I_m \cdot V_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \cdot 8 \cdot 5 \cdot \cos\left(-\frac{\pi}{3} + \frac{5\pi}{6}\right)$$

$$= \frac{1}{2} \cdot 8 \cdot 5 \cdot \cos\left(\frac{\pi}{2}\right)$$

$$= \frac{1}{2} \cdot 8 \cdot 5 \cdot 0$$

$$\boxed{P = 0 \text{ W}}$$

$\leadsto$  AS EXPECTED SINCE

$V$  &  $I$  ARE ORTHOGONAL

IN THIS CASE, "I LAGS V"


BY  $90^\circ \Rightarrow$  THE ELEMENT  
IS AN INDUCTOR

$$I = \frac{V}{j\omega L} = \frac{V}{\omega L} e^{-j \frac{\pi}{2}}$$

# PP AC power 003

Unlimited Attempts.

Find  $I_{rms}$  for this waveform.

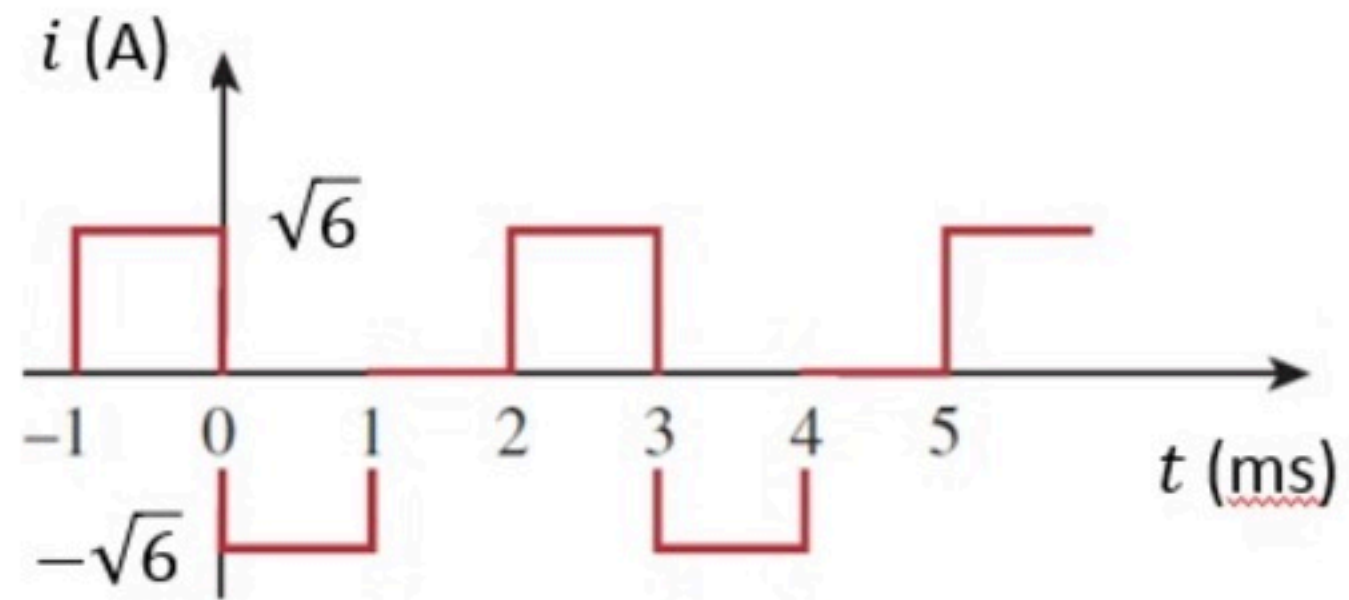

Given Variables:

...

Calculate the following:

$I_{rms}$  (A) :

2



Hint: Square the waveform first.

$$A = \frac{1}{T} \int_0^T i^2 dt$$

$$= \frac{1}{3 \cdot 10^{-3}} \cdot \left[ (-\sqrt{6})^2 \cdot 10^{-3} + 0 + (\sqrt{6})^2 \cdot 10^{-3} \right]$$

$$= \frac{1}{3} [6 + 6]$$


$$= 4$$

$$I_{rms} = \sqrt{A} \quad \Rightarrow \quad \boxed{I_{rms} = 2}$$

# PP AC power 004

Unlimited Attempts.

Find  $V_{rms}$  for this waveform.

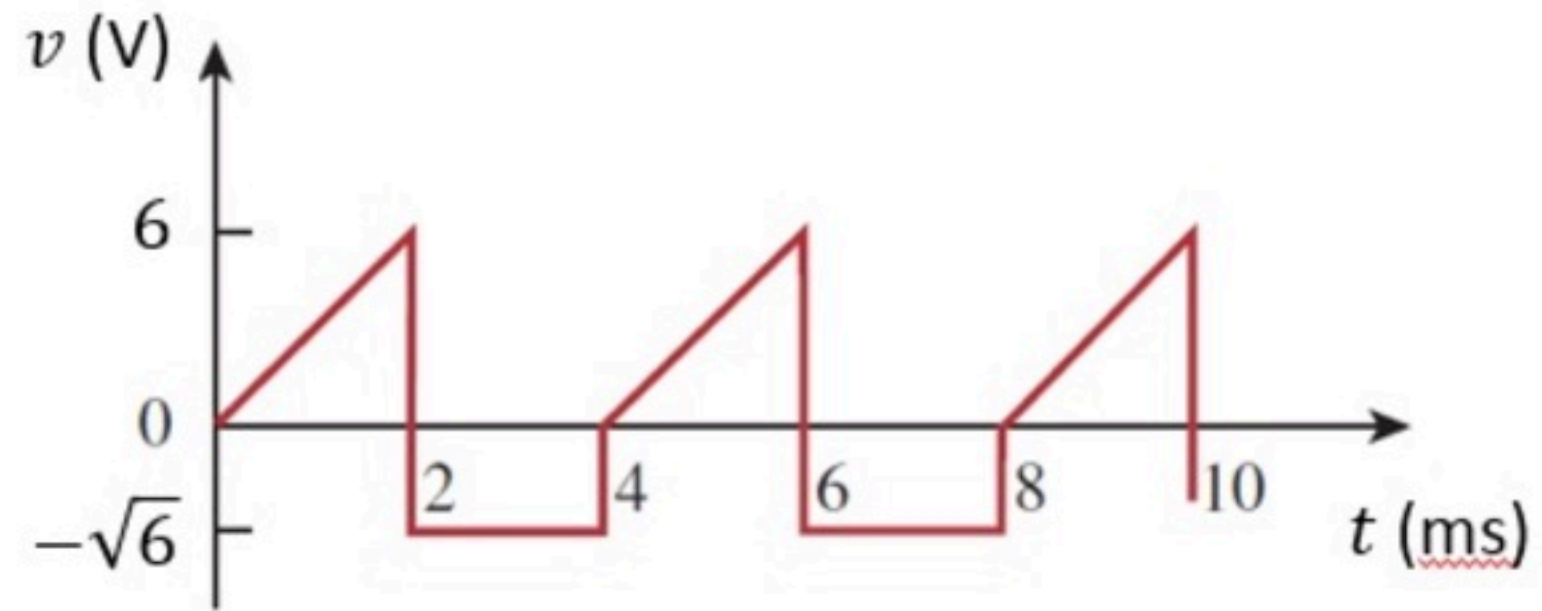

Given Variables:

...

Calculate the following:

$V_{rms}$  (V) :

3



Hint: Write the equation of the waveform in parts.

**OPTION 1**  $t$  EXPRESSED IN SECONDS

$$f(t) = 3 \cdot 10^3 \cdot t, \quad 0 \leq t < 2 \cdot 10^{-3}$$
$$= -\sqrt{6}, \quad 2 \cdot 10^{-3} \leq t < 4 \cdot 10^{-3}$$

$$\begin{aligned} \frac{1}{T} \int_0^T f^2(t) dt &= \frac{1}{4 \cdot 10^{-3}} \left[ \int_0^{2 \cdot 10^{-3}} (3 \cdot 10^3 t)^2 dt + \int_{2 \cdot 10^{-3}}^{4 \cdot 10^{-3}} (-\sqrt{6})^2 dt \right] \\ &= \frac{1}{4 \cdot 10^{-3}} \left[ 9 \cdot 10^6 \cdot \frac{t^3}{3} \Big|_0^{2 \cdot 10^{-3}} + 6 \cdot 2 \cdot 10^{-3} \right] \\ &= \frac{1}{4 \cdot 10^{-3}} \left[ \frac{9 \cdot 8 \cdot 10^{-3}}{3} + 12 \cdot 10^{-3} \right] \\ &= \frac{24 + 12}{4} = \frac{36}{4} = 9 \end{aligned}$$

$$\sqrt{\frac{1}{T} \int_0^T f^2(t) dt} = \boxed{V_{rms} = 3V}$$

**OPTION 2**  $t$  EXPRESSED IN ms

$$f(t) = 3 \cdot t, \quad 0 \leq t < 2$$
$$= -\sqrt{6}, \quad 2 \leq t < 4$$

$$\begin{aligned} \frac{1}{T} \int_0^T f^2(t) dt &= \frac{1}{4} \left[ \int_0^2 (3t)^2 dt + \int_2^4 (\sqrt{6})^2 dt \right] = \frac{1}{4} \left[ 9 \frac{t^3}{3} \Big|_0^2 + 6 \cdot 2 \right] \\ &= \frac{1}{4} \left[ \frac{9 \cdot 8}{3} + 12 \right] = \frac{36}{4} = 9 \end{aligned}$$


$$\boxed{V_{rms} = 3V}$$


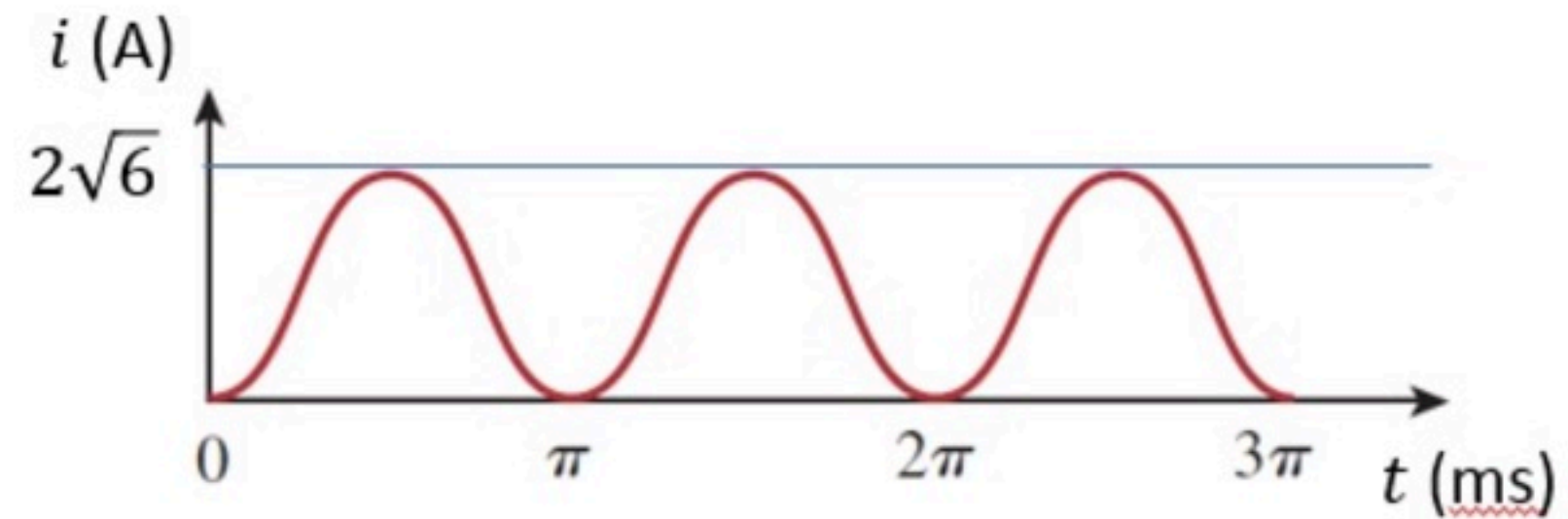
# PP AC power 005

Unlimited Attempts.

Find  $I_{rms}$  for this waveform (it is a sine wave that has an offset, i.e., it is shifted up).



Given Variables:

...

Calculate the following:

$I_{rms}$  (A) :

3



Hint: Utilize the fact that you know the  $I_{rms}$  for a sine wave.

$$i = \sqrt{6} - \sqrt{6} \cos(\omega t) = \sqrt{6} (1 - \cos(\omega t))$$

$$i^2 = 6 (1 - \cos(\omega t))^2$$

$$A = \frac{1}{T} \int_0^T i^2 dt = \frac{6}{T} \int_0^T [1 - 2\cos(\omega t) + \cos^2(\omega t)] dt$$

$$= \frac{6}{T} \int_0^T dt - \frac{12}{T} \int_0^T \cos(\omega t) dt + \frac{6}{T} \int_0^T \cos^2(\omega t) dt$$

$$= \frac{6}{T} \cdot T - \frac{12}{T} \cdot 0 + 6 \cdot \frac{1}{2}$$

↳ WE KNOW FOR A COS

$$I_{RMS} = \frac{I_M}{\sqrt{2}} \Rightarrow I_{RMS}^2 = \frac{I_M^2}{2}$$

$$I_{RMS}^2 = \frac{I_M^2}{T} \int_0^T \cos^2(\omega t) dt$$

$$\Rightarrow \frac{1}{T} \int_0^T \cos^2(\omega t) dt = \frac{1}{2}$$

$$A = 6 + \frac{6}{2} = 9$$

$$I_{RMS} = \sqrt{A} \Rightarrow \boxed{I_{RMS} = 3A}$$

# PP AC power 006

Unlimited Attempts.

$$v_S(t) = 10\sqrt{2} \cdot \cos\left(10^6 t + \frac{\pi}{6}\right) \text{ V}$$


Find the average power  $P_1$  supplied by the source  $v_S$ .

Find the average power  $P_2$  received by the  $5\ \Omega$  resistor.

Find the average power  $P_3$  received by the  $4\ \Omega$  resistor.

Find the average power  $P_4$  received by the capacitor.

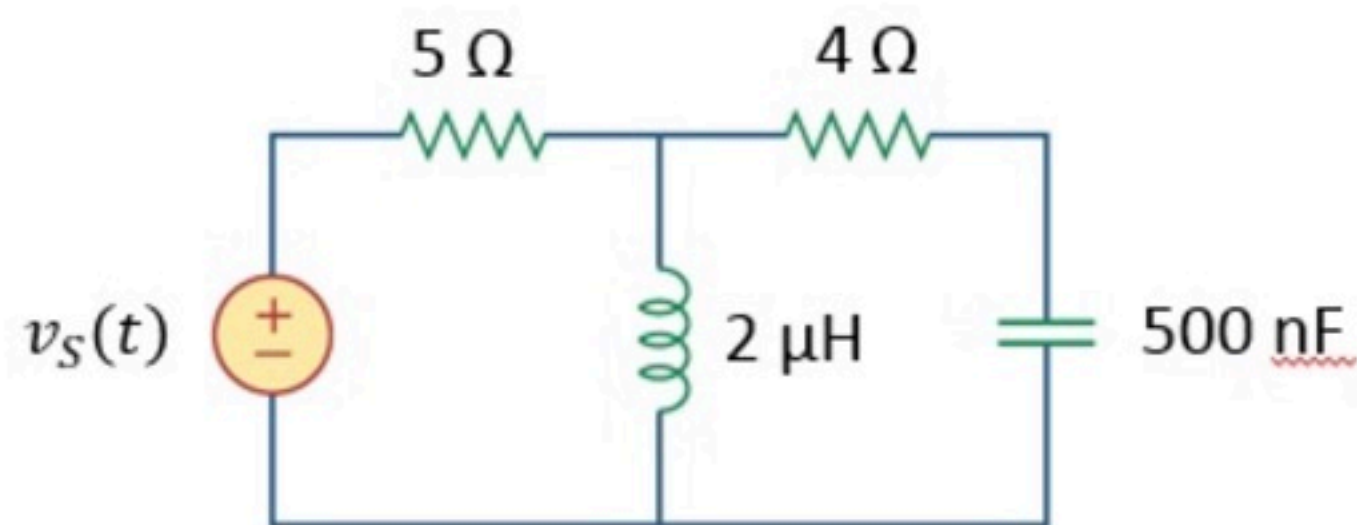Find the average power  $P_5$  received by the inductor.



Given Variables:

. . .

Calculate the following:

P1 (W) :

15

✓

P2 (W) :

12.5

✓

P3 (W) :

2.5

✓

P4 (W) :

0


✓

P5 (W) :

0

✓

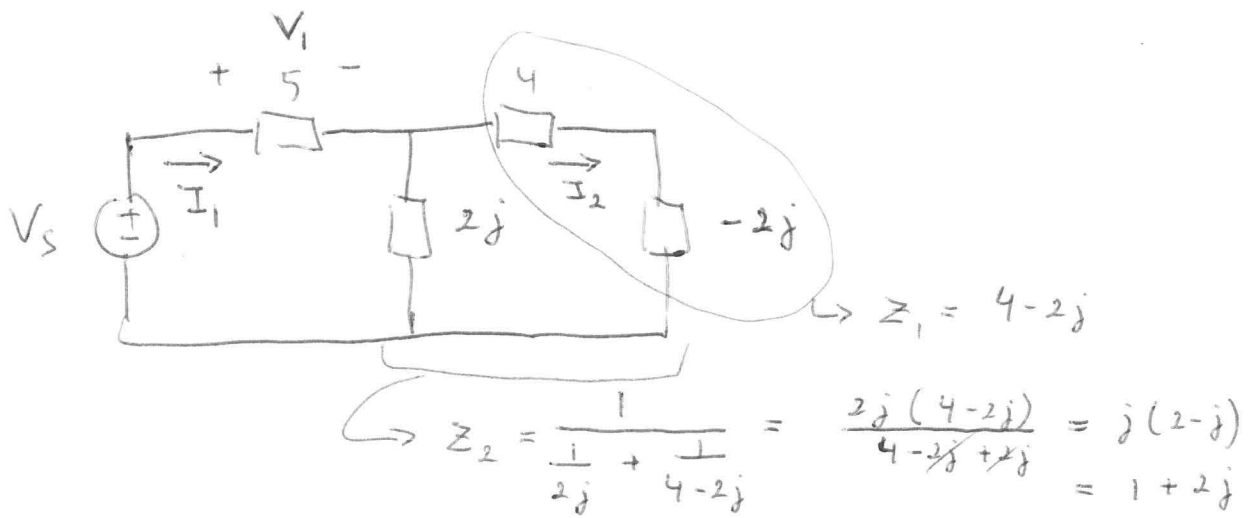Hint: Find S first for each element. Keep  $V_s$  algebraic. Can you predict P for the cap and inductor? Check.



$$I_1 = \frac{V_s}{5 + Z_2} = \frac{V_s}{6 + 2j}$$

①  $S_1 = \frac{1}{2} V_s \cdot I_1^*$  (SUPPLIED!)  $V_s \uparrow I_1$

$$= \frac{1}{2} V_s \frac{V_s^*}{6-2j} = \frac{|V_s|^2}{2} \cdot \frac{6+2j}{40} = \frac{100 \cdot 2}{2} \cdot \frac{(6+2j)}{40} \quad P_1 = \text{Re}[S_1]$$

$$\boxed{P_1 = 15 \text{ W}}$$

②  $S_2 = \frac{1}{2} V_1 I_1^* = \frac{1}{2} \cdot Z_{5\Omega} \cdot I_1 \cdot I_1^* = \frac{1}{2} Z_{5\Omega} |I_1|^2$

$$S_2 = \frac{1}{2} \cdot 5 \cdot \frac{|V_s|^2}{|6+2j|^2} = \frac{5}{2} \cdot \frac{100 \cdot 2}{40} = 12.5$$

$$\boxed{P_2 = 12.5 \text{ W}}$$

③  $I_2 = I_1 \cdot \frac{2j}{2j + Z_1} = I_1 \cdot \frac{2j}{2j + 4 - 2j} = I_1 \cdot \frac{2j}{4} = I_1 \cdot \frac{j}{2}$

$$S_3 = \frac{1}{2} Z_{4\Omega} |I_2|^2 = \frac{1}{2} \cdot 4 \cdot |I_1|^2 \cdot \frac{|j|^2}{4} = \frac{|I_1|^2}{2} = \frac{1}{2} \cdot \frac{|V_s|^2}{|6+2j|^2}$$

$$= \frac{1}{2} \cdot \frac{100 \cdot 2}{40} = 2.5$$

$$\boxed{P_3 = 2.5 \text{ W}}$$

WE KNOW A CAPACITOR AND INDUCTOR ONLY  
HAVE REACTIVE POWER  $\Rightarrow \boxed{P_4 = P_5 = 0}$


CHECK:  $P_{\text{REC.}} = P_{\text{SUPPLIED}} \Rightarrow 12.5 + 2.5 = 15 \quad \underline{\text{OK}}$

# PP AC power 007

Unlimited Attempts.

$$i_S(t) = 2 \cdot \cos\left(10^3 t + \frac{\pi}{4}\right) \text{ A}$$

- Find the complex power  $\mathbf{S}_1 = a_1 + b_1 j$  supplied by the source  $i_S$ .  
Find the complex power  $\mathbf{S}_2 = a_2 + b_2 j$  received by the  $10\ \Omega$  resistor.  
Find the complex power  $\mathbf{S}_3 = a_3 + b_3 j$  received by the  $2\ \Omega$  resistor.  
Find the complex power  $\mathbf{S}_4 = a_4 + b_4 j$  received by the CCVS.  
Find the complex power  $\mathbf{S}_5 = a_5 + b_5 j$  received by the inductor.  
Find the complex power  $\mathbf{S}_6 = a_6 + b_6 j$  received by the capacitor.

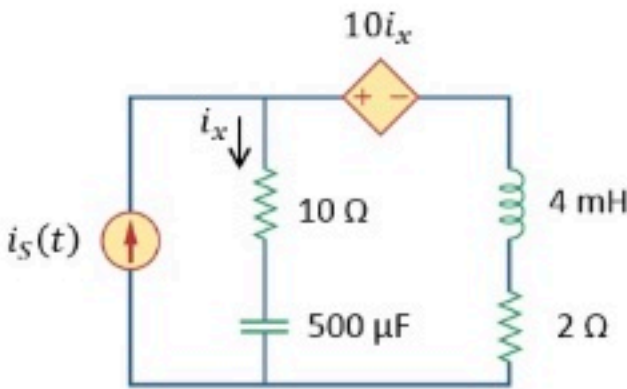

Given Variables:

. . .

Calculate the following:

a1 (W) :

32



b1 (VAR) :

4



a2 (W) :

50



b2 (VAR) :

0



a3 (W) :

2



b3 (VAR) :

0



a4 (W) :

-20



b4 (VAR) :

10



a5 (W) :

0



b5 (VAR) :

4



a6 (W) :

0




b6 (VAR) :

-10



Hint: Keep  $i_S$  algebraic.

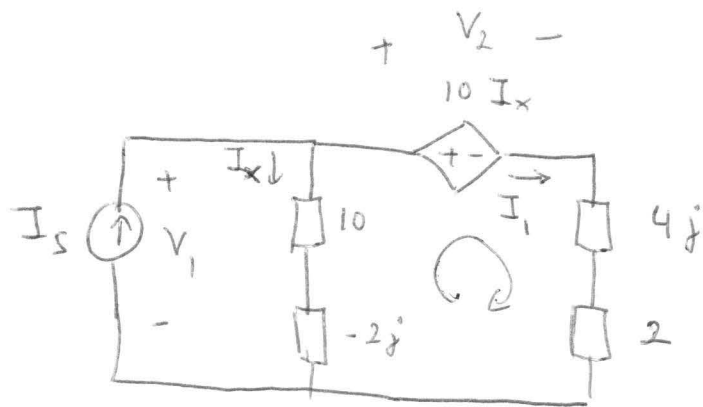

$$I_1 = I_s - I_x$$

$$|I_s|^2 = 4$$

$$\text{KVL: } I_x (10 - 2j) = 10 I_x + (2 + 4j) I_1$$

$$= 10 I_x + (2 + 4j)(I_s - I_x)$$

$$I_x (\cancel{10} - 2j - \cancel{10} + 2 + 4j) = (2 + 4j) I_s$$

$$I_x (2 + 2j) = I_s (2 + 4j) \Rightarrow I_x = I_s \frac{(1 + 2j)}{(1 + j)} = I_s \frac{(3 + j)}{2}$$

$$\textcircled{1} V_1 = I_x (10 - 2j) = I_s \frac{(3 + j)(10 - 2j)}{2} = I_s (16 + 2j)$$

NOTE  
DIRECTION  
OPPOSITE

PASSIVE  
SIGN  
CONVENTION

$$\textcircled{1} S_1 = \frac{1}{2} V_1 \cdot I_s^* = \frac{1}{2} I_s (16 + 2j) I_s^* = |I_s|^2 (8 + j) \Rightarrow \boxed{S_1 = 32 + 4j}$$

$$\textcircled{2} S_2 = \frac{1}{2} \cdot Z_{10\Omega} \cdot |I_x|^2 = \frac{1}{2} \cdot 10 \cdot |I_s|^2 \cdot \frac{10}{4} \Rightarrow \boxed{S_2 = 50 + 0j}$$

AS  
EXPECTED

$$\textcircled{3} I_1 = I_s - I_x = I_s \left(1 - \frac{3 + j}{2}\right) = I_s \frac{(-1 - j)}{2}$$

$$S_3 = \frac{1}{2} Z_{2\Omega} |I_1|^2 = \frac{1}{2} \cdot 2 \cdot |I_s|^2 \cdot \frac{|-1 - j|^2}{4} = \frac{|I_s|^2}{4} \cdot 2 \Rightarrow \boxed{S_3 = 2 + 0j}$$

$$\textcircled{4} S_4 = \frac{1}{2} V_2 I_1^* = \frac{1}{2} \cdot 10 I_x \cdot I_1^* = 5 \cdot I_s \frac{(3 + j)}{2} \cdot I_s^* \frac{(-1 - j)}{2} = |I_s|^2 \cdot \frac{5}{4} (-4 + 2j)$$

$$\Rightarrow \boxed{S_4 = -20 + 10j}$$

RECEIVED SINCE WE  
USED PASSIVE SIGN CONVENTION

$$\textcircled{5} S_5 = \frac{1}{2} Z_L \cdot |I_1|^2 = \frac{1}{2} \cdot 4j \cdot |I_s|^2 \cdot \frac{|-1 - j|^2}{4} = 2j \cdot 4 \cdot \frac{2}{4} \Rightarrow \boxed{S_5 = 0 + 4j}$$

AS EXPECTED

$$\textcircled{6} S_6 = \frac{1}{2} Z_C |I_x|^2 = \frac{1}{2} (-2j) |I_s|^2 \frac{|3 + j|^2}{4} = -j \cdot 4 \cdot \frac{10}{4} \Rightarrow \boxed{S_6 = 0 - 10j}$$

$$\text{CHECK: } \sum P_{\text{REC}} = \sum P_{\text{SUPPL}} \Rightarrow 50 + 2 - 20 = 32 \quad \text{OK}$$

$$\sum Q_{\text{REC}} = \sum Q_{\text{SUPPL}} \Rightarrow 10 + 4 - 10 = 4 \quad \text{OK}$$




# PP AC power 008

Unlimited Attempts.

Find the value of  $\mathbf{Z_L} = a + jb$  that will receive the maximum amount of power

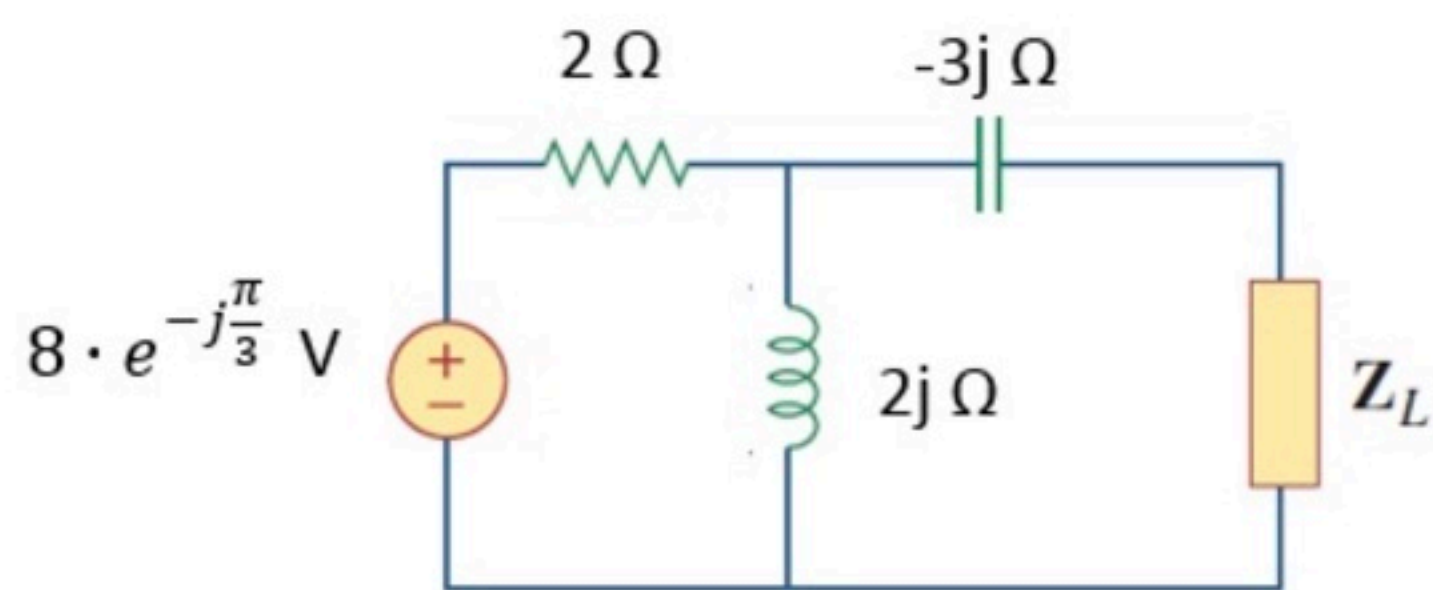Find the resulting complex power  $\mathbf{S} = c + jd$  received by the load.



Given Variables:

. . .

Calculate the following:

a (ohm) :

1



b (ohm) :

2



c (W) :

4




d (VAR) :

8



Hint: Set the independent source to zero. Find  $\mathbf{Z_{th}}$ .

①

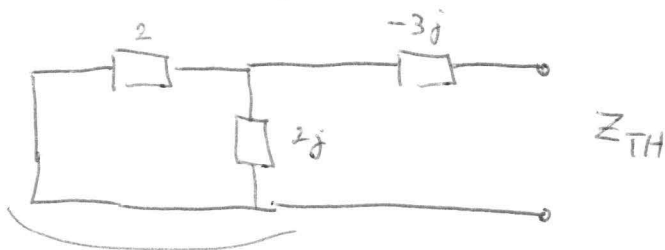


$$\hookrightarrow Z_1 = \frac{1}{\frac{1}{2} + \frac{1}{2j}} = \frac{4j}{2+2j} = \frac{2j}{1+j} = \frac{2j(1-j)}{2} = 1+j$$

$$\Rightarrow Z_{TH} = Z_1 - 3j = 1 - 2j$$

MAX POWER:  $Z_L = Z_{TH}^* = 1 + 2j$

②

OPTION 1:

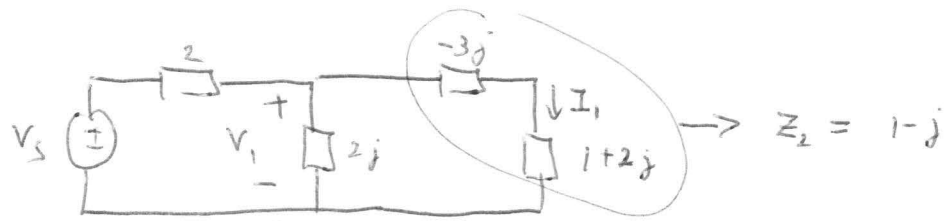

$$\hookrightarrow Z_3 = \frac{1}{\frac{1}{2j} + \frac{1}{1-j}} = \frac{2j(1-j)}{1-j+2j} = \frac{2j+2}{1+j} = 2$$


$$V_1 = V_S \frac{Z_3}{Z_3 + 2} = \frac{V_S}{2}$$

$$I_1 = \frac{V_1}{Z_2} \Rightarrow S_L = \frac{1}{2} Z_L |I_1|^2 = \frac{1}{2} (1+2j) \frac{|V_S|^2}{4} \cdot \frac{1}{|Z_2|^2}$$

$$= \frac{1}{2} \cdot \frac{64}{4} \cdot \frac{1}{2} (1+2j)$$

$$S_L = 4 + 8j$$

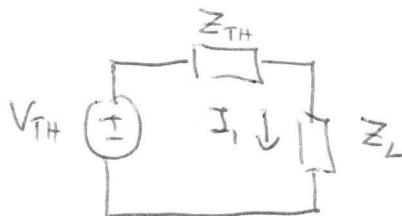OPTION 2: FIND  $V_{TH} \Rightarrow V_{OC} = V_S \cdot \frac{2j}{2+j} = V_S \cdot \frac{j}{1+j} = V_{TH}$



$$I_1 = \frac{V_{TH}}{Z_{TH} + Z_L} = \frac{V_{TH}}{(1-2j) + (1+2j)} = \frac{V_{TH}}{2}$$

AS EXPECTED

$$S_L = \frac{1}{2} Z_L |I_1|^2 = \frac{1}{2} (1+2j) \frac{|V_{TH}|^2}{4} = \frac{(1+2j)}{8} |V_S|^2 \frac{|j|^2}{|1+j|^2}$$


$$S_L = (1+2j) \cdot \frac{64}{8} \cdot \frac{1}{2} \Rightarrow S_L = 4 + 8j$$


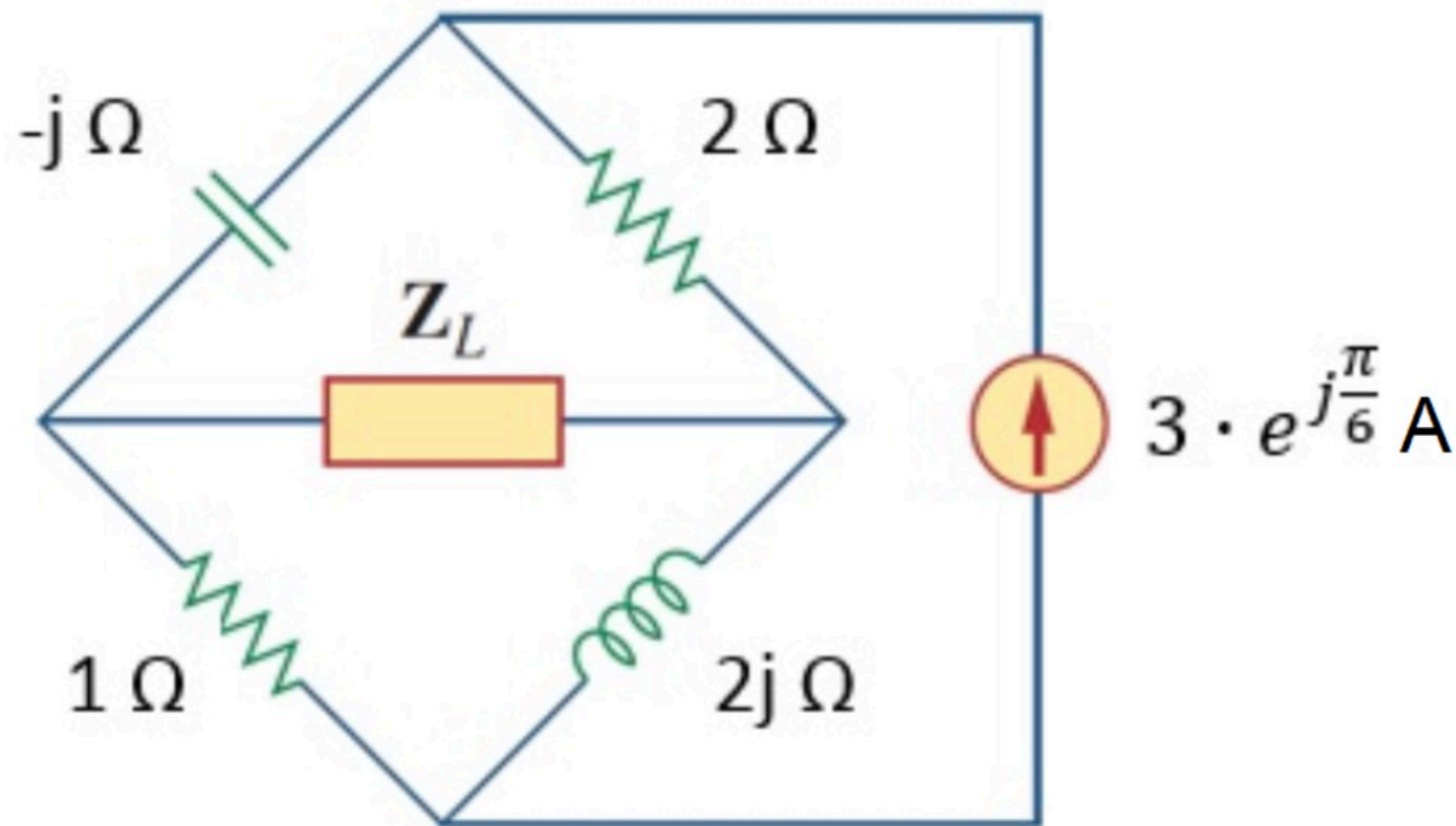
# PP AC power 009

Unlimited Attempts.

Find the value of  $\mathbf{Z_L} = a + jb$  that will receive the maximum amount of power



Given Variables:

...

Calculate the following:

a (ohm) :

1.5


✓

b (ohm) :

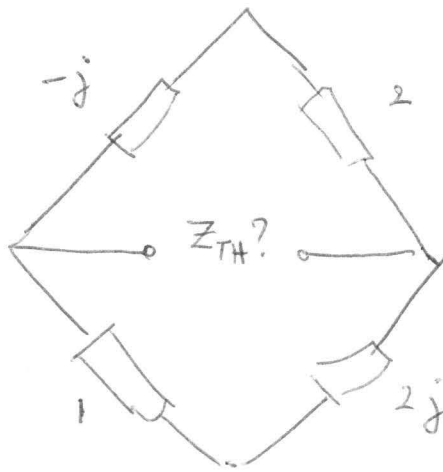-0.5

✓

Hint: Find ZTh by setting independent sources to zero.



$$\begin{aligned}
 Z_{TH} &= (2-j) \parallel (1+2j) = \frac{1}{\frac{1}{2-j} + \frac{1}{1+2j}} \\
 &= \frac{(2-j)(1+2j)}{2-j+1+2j} = \frac{2-j+4j+2}{3+j} \cdot \frac{3-j}{3-j} \\
 &= \frac{1}{10} \cdot (4+3j)(3-j) \\
 &= \frac{1}{10} (12+9j-4j+3) \\
 &= 1.5 + 0.5j
 \end{aligned}$$


$$Z_L^* = Z_{TH} \quad \text{FOR MAX POWER}$$

$$Z_L = 1.5 - 0.5j$$
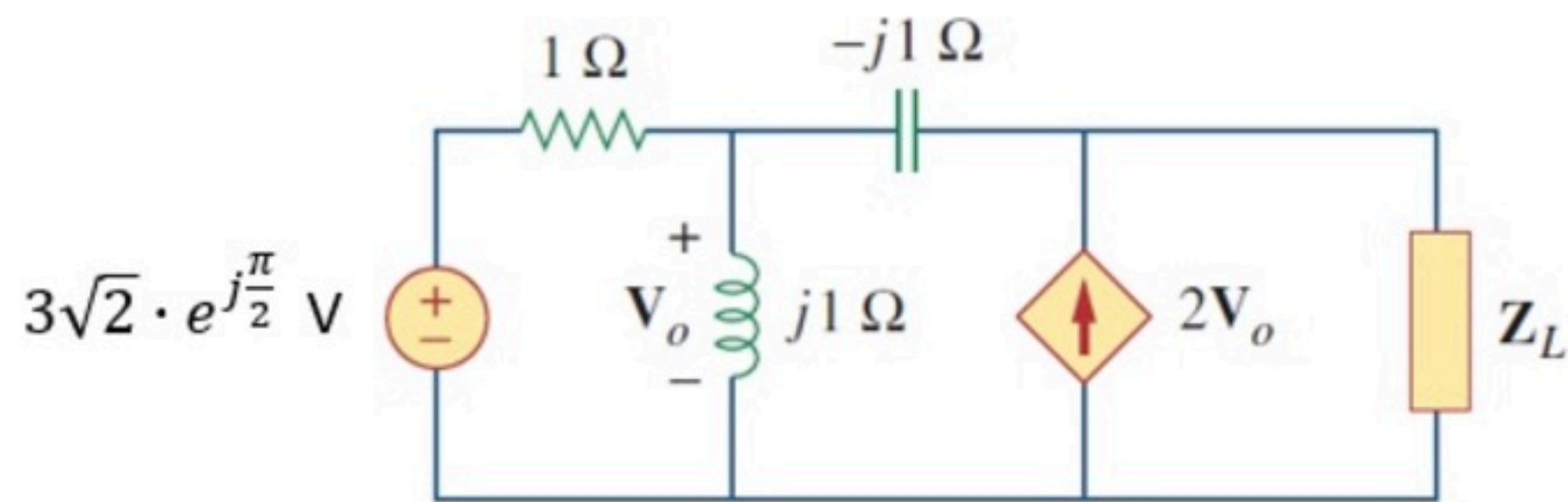
# PP AC power 010

Unlimited Attempts.

Find the value of  $\mathbf{Z_L} = a + jb$  that will receive the maximum amount of power



Given Variables:

...

Calculate the following:

a (ohm) :

0.5




b (ohm) :

-0.5



Hint: Use a test source to find the ZTh.

FIND  $Z_{TH}$ :

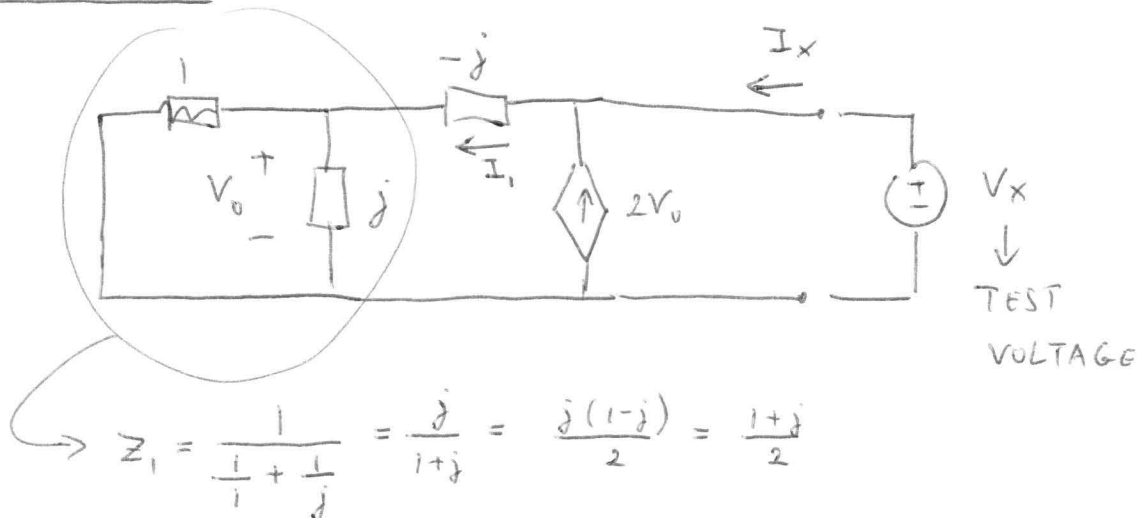

$$I_1 = \frac{V_x}{Z_1 - j} = \frac{V_x}{\frac{1-j}{2}}$$

$$V_0 = V_x \cdot \frac{Z_1}{Z_1 - j} = V_x \frac{(1+j)}{(1-j)}$$

$$I_x = I_1 - 2V_0 = \frac{2V_x}{1-j} - 2V_x \frac{(1+j)}{1-j} = V_x \frac{(-2j)}{1-j}$$

$$\cancel{Z_{TH}} Z_{TH} = \frac{V_x}{I_x} = \frac{V_x (1-j)}{V_x (-2j)} = \frac{1-j}{-2j} = \frac{(1-j) \cdot j}{2} = \frac{1+j}{2}$$

MAX POWER:  $Z_L = Z_{TH}^*$

$$Z_L = 0.5 - 0.5j$$