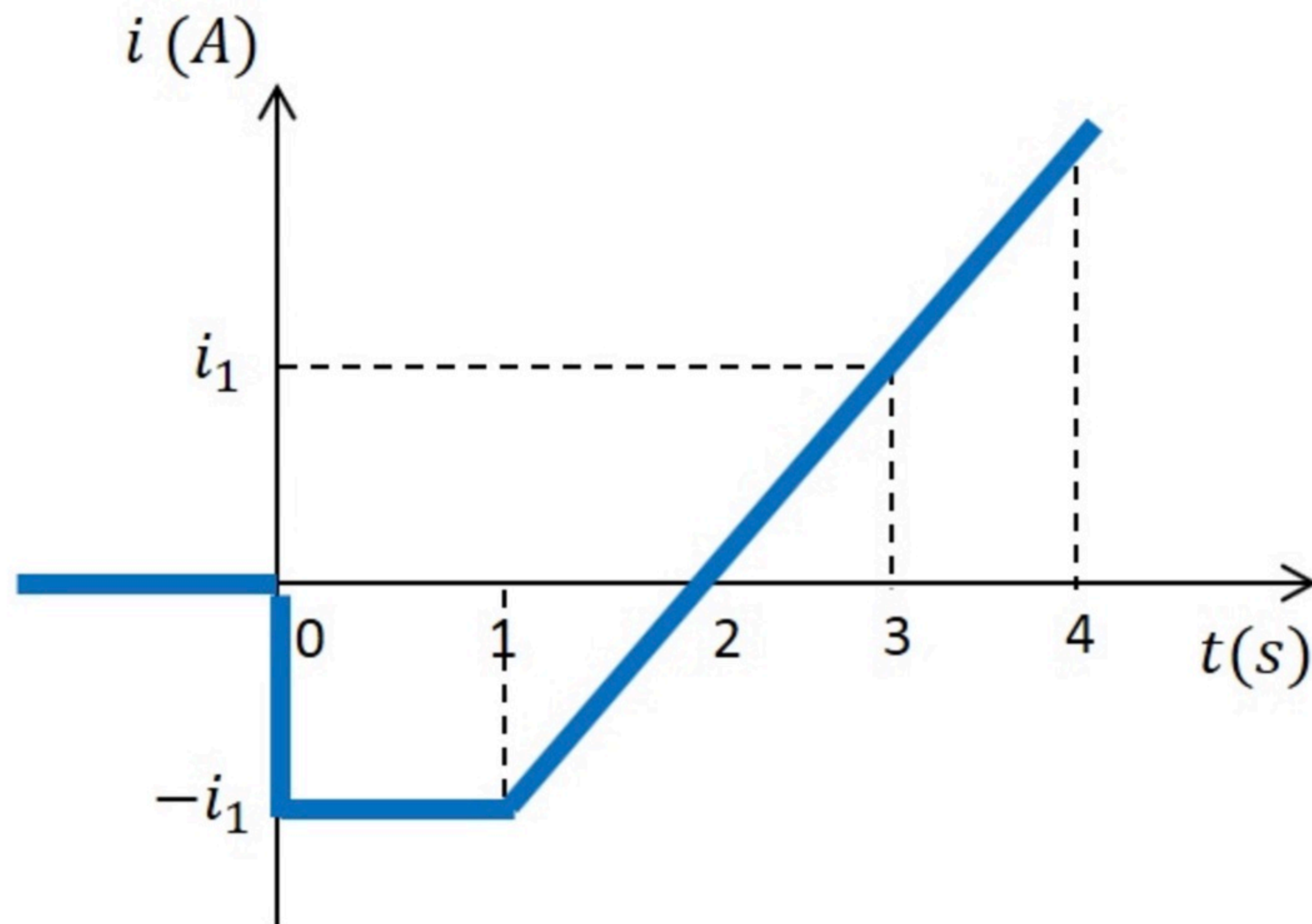


Basic concepts 001

Problem has been graded.

The curve shows the current flowing through a circuit element. Find the net charge q that has entered the element from $t = 0$ s to $t = 4$ s.



Given Variables:


$i_1 : 8$ mA

Calculate the following:

q (C) :

Hint: Check the units.

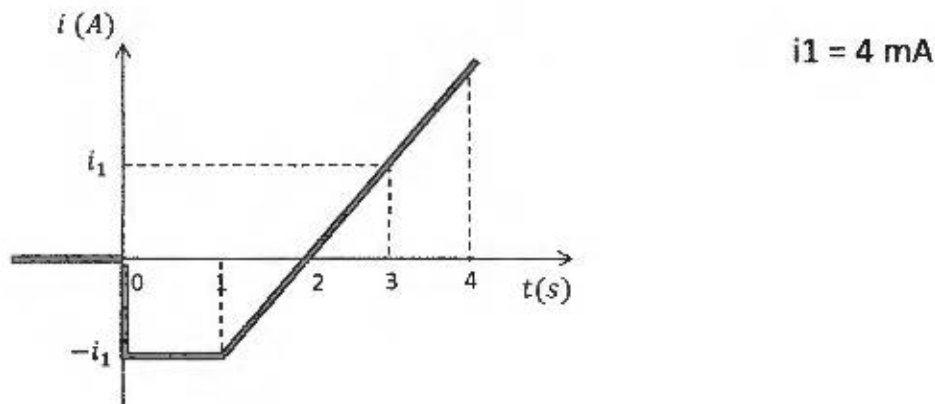The curve shows the current flowing through a circuit element. Find the net charge q that has entered the element from $t = 0$ s to $t = 4$ s.



$$\begin{aligned}
 q &= \int_0^4 i(t) dt = \left(-i_1 \cdot 1 \right) + \left(-\frac{i_1 \cdot 1}{2} \right) \\
 &\quad + \left(\frac{i_1 \cdot 1}{2} \right) + \left(i_1 \cdot 1 + \frac{i_1 \cdot 1}{2} \right) \\
 &= \frac{-i_1}{2} \\
 &= \frac{4 \cdot 10^{-3}}{2}
 \end{aligned}$$

$$q = 0.002 \text{ C}$$

Basic concepts 002

Problem has been graded.

Determine the values of B1, B2 and B3.

The current through a circuit element is

$$\begin{aligned} i(t) &= A1 \cdot e^{\frac{t}{A2}} && \text{for } t \geq 0 \\ &= 0 && \text{for } t < 0 \end{aligned}$$

The total charge that has entered the circuit element can be represented as

$$\begin{aligned} q(t) &= B1 + B2 \cdot e^{\frac{t}{B3}} && \text{for } t \geq 0 \\ &= 0 && \text{for } t < 0 \end{aligned}$$

Given Variables:

A1 : 4 A

A2 : -3 s

Calculate the following:

B1 (C) :

B2 (C) :

B3 (s) :

The current through a circuit element is

$$i(t) = A_1 \cdot e^{\frac{t}{A_2}} \\ = 0$$

$$\text{for } t \geq 0 \\ \text{for } t < 0$$


$$A_1 = 3 \text{ A}$$

$$A_2 = -2 \text{ s}$$

The total charge that has entered the circuit element can be represented as

$$q(t) = B_1 + B_2 \cdot e^{\frac{t}{B_3}} \\ = 0$$
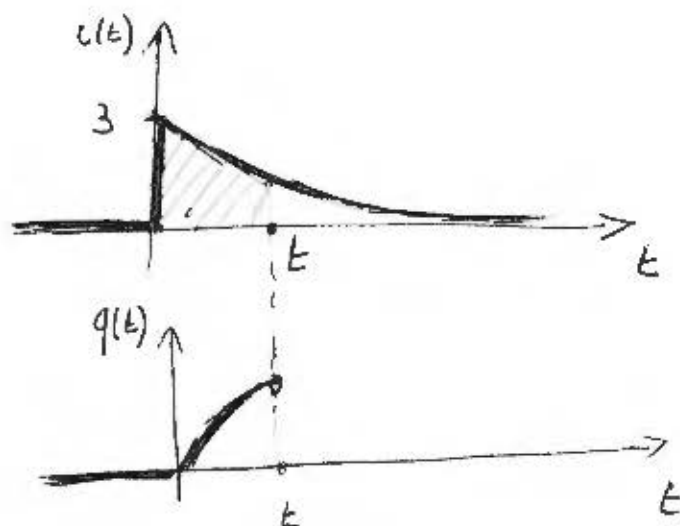
$$\text{for } t \geq 0 \\ \text{for } t < 0$$



at any time t : $q(t)$ is the integral of $i(t)$
up until time t

$$q(t) = \int_{-\infty}^t i(u) du = \int_0^t 3 e^{-\frac{u}{2}} du \\ = 3(-2) \int_0^t e^{-\frac{u}{2}} d\left(-\frac{u}{2}\right) = -6 e^{-\frac{u}{2}} \Big|_0^t = -6 \left(e^{-\frac{t}{2}} - 1 \right)$$

$$q(t) = 6 - 6 e^{-\frac{t}{2}}$$

$$B_1 = 6 \text{ C} \\ B_2 = -6 \text{ C} \\ B_3 = -2 \text{ s}$$

Basic concepts 003


Problem has been graded.

Find the energy received by this element between time $t = 0$ and $t = T1$.

For this element

$$v(t) = 2\pi \cdot \cos(A1 \cdot \pi \cdot t) \quad \text{V}$$
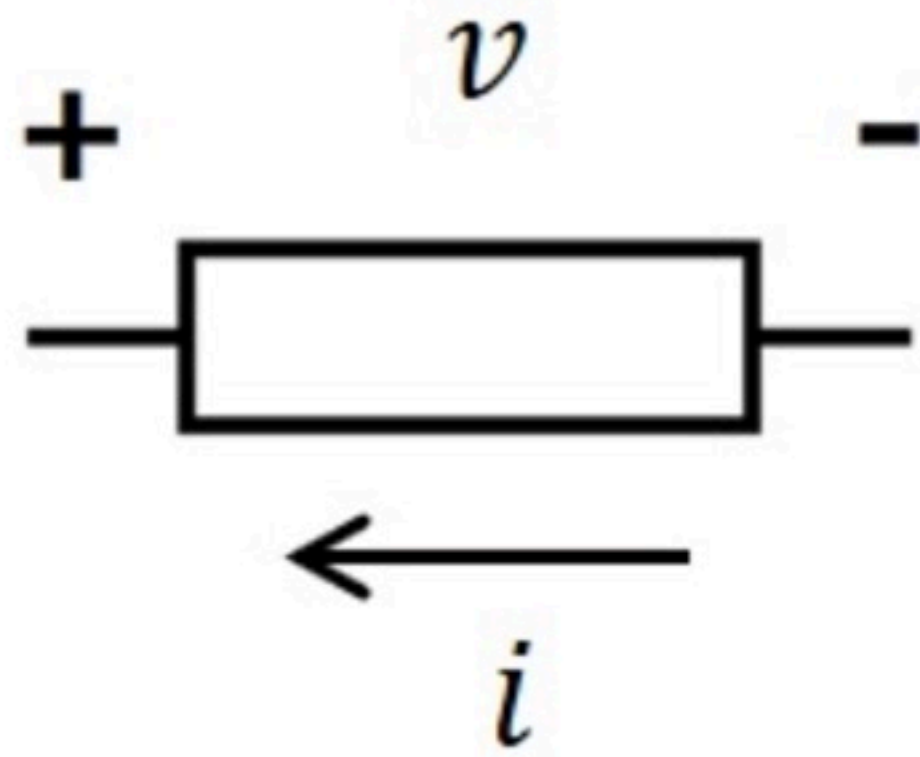
$$i(t) = A2 \cdot \sin(A1 \cdot \pi \cdot t)$$



(Note: Hz is the unit used for frequency. It is equal to s^{-1})

Given Variables:

$A1 : 5 \text{ Hz}$

$A2 : 3 \text{ A}$

$T1 : 2.5 \text{ s}$

Calculate the following:

$E \text{ (J)} :$

Hint: Are we using passive sign convention?

Find the energy received by this element between time $t = 0$ and $t = T_1$.

For this element


$$v(t) = 2\pi \cdot \cos(A_1 \cdot \pi \cdot t) \quad \text{V}$$

$$i(t) = A_2 \cdot \sin(A_1 \cdot \pi \cdot t)$$


$$A_1 = 1 \text{ Hz}$$

$$A_2 = 5 \text{ A}$$

$$T_1 = 1.5 \text{ s}$$

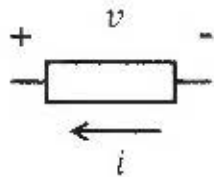

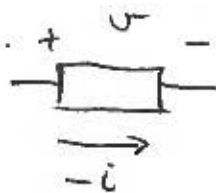(Note: Hz is the unit used for frequency. It is equal to s^{-1})



for passive sign convention \leadsto gives power received

$$p(t) = v(t) \cdot (-i(t)) = -2\pi \cos(\pi t) \cdot 5 \sin(\pi t)$$

$$= -10\pi \sin(\pi t) \cos(\pi t) = -5\pi \sin(2\pi t)$$

$$E = \int_0^{1.5} p(t) dt = -5\pi \int_0^{1.5} \sin(2\pi t) dt = -\frac{5\pi}{2\pi} \int_0^{1.5} \sin(2\pi t) d(2\pi t)$$

$$= -\frac{5}{2} \left(-\cos(2\pi t) \right) \Big|_0^{1.5}$$

$$= -2.5 \left(-\cos(3\pi) + 1 \right)$$

$$= -2.5 \left(-(-1) + 1 \right)$$


$$= -5$$

$$\boxed{E = -5 \text{ J}} \quad \text{received}$$

Basic concepts 004

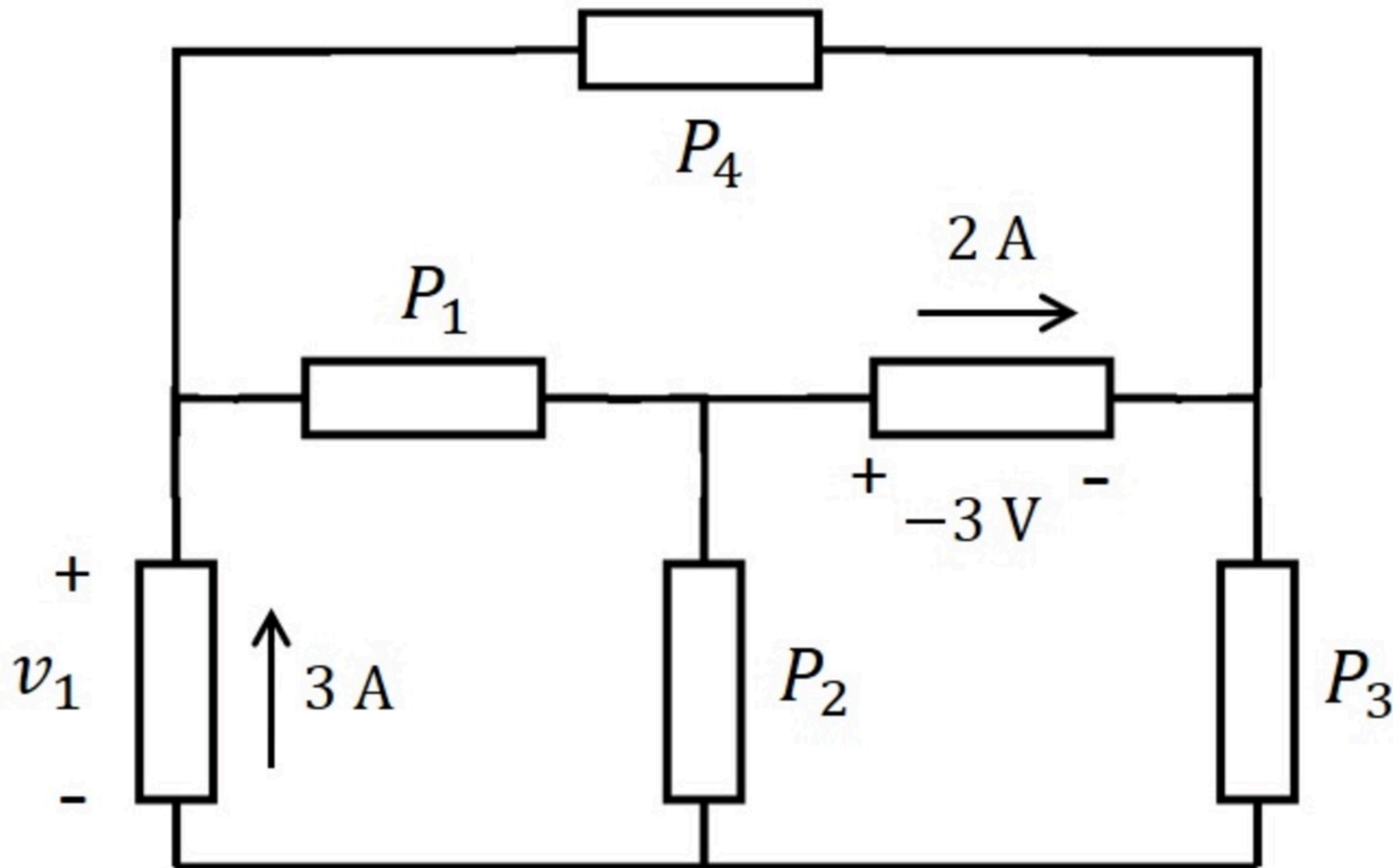Problem has been graded.

We are given the power received P_1 , P_2 , P_3 and the voltage v_1 . Find the power received P_4 .



Given Variables:

$v_1 : 2 \text{ V}$

$P_1 : 16 \text{ W}$

$P_2 : -4 \text{ W}$


$P_3 : 1 \text{ W}$

Calculate the following:

$P_4 \text{ (W)} :$

Hint: Sum of power received is equal to sum of power supplied.

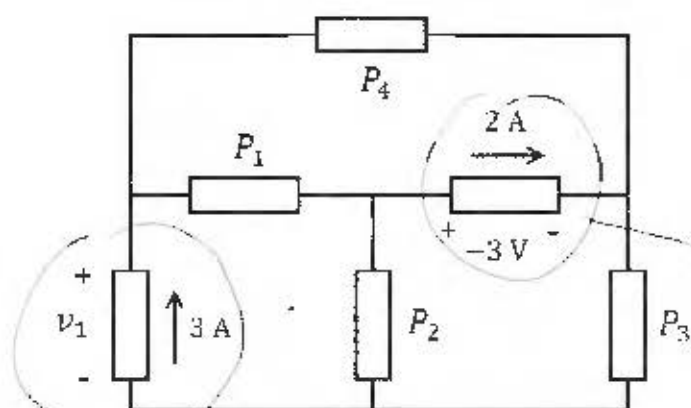We are given the power received P_1 , P_2 , P_3 and the voltage v_1 . Find the power received P_4 .




$$v_1 = 1 \text{ V}$$

$$P_1 = 14 \text{ W}$$

$$P_2 = -5 \text{ W}$$

$$P_3 = -4 \text{ W}$$

→ passive sign convention

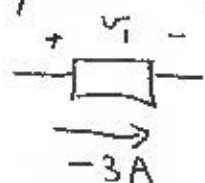

$$P = 1 \cdot (-3) = -3 \text{ W received}$$

→ $P = (-3) \cdot 2 = -6 \text{ W received}$

$$\sum P_{\text{received}} = \sum P_{\text{supplied}} \Rightarrow -3 - 6 + P_1 + P_2 + P_3 + P_4 = 0$$


$$-3 - 6 + 14 - 5 - 4 + P_4 = 0$$

$$\boxed{P_4 = 4 \text{ W}} \text{ received}$$

Basic concepts 005

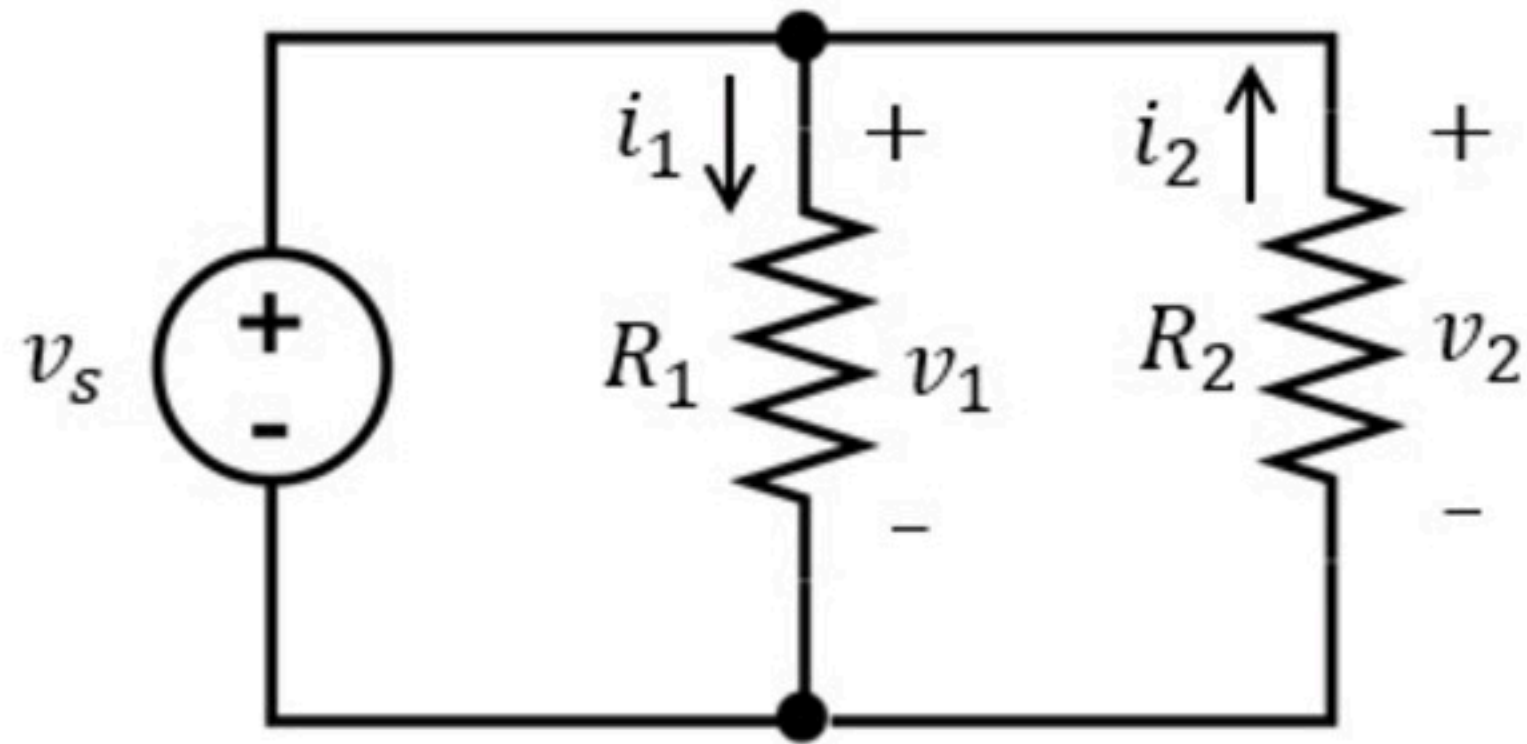Problem has been graded.

For each of the resistors, calculate the current through them and power received by them.



Given Variables:

v_s : 10 V

R_1 : 10 ohm

R_2 : 4 ohm

Calculate the following:

i_1 (A) :


i_2 (A) :

P_1 (W) :

P_2 (W) :

Hint: Find the voltage across the resistors first

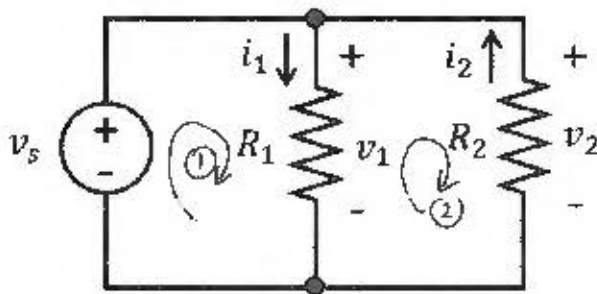For each of the resistors, calculate the current through them and power received by them.



$$v_s = 20 \text{ V}$$

$$R_1 = 20 \Omega$$

$$R_2 = 10 \Omega$$

$$\text{KVL } \textcircled{1} : v_s = v_1 \Rightarrow v_1 = 20 \text{ V}$$

$$\text{KVL } \textcircled{2} : v_1 = v_2 \Rightarrow v_2 = 20 \text{ V}$$

$$i_1 = \frac{v_1}{R_1} = \frac{20}{20} \Rightarrow \boxed{i_1 = 1 \text{ A}}$$

$$i_2 = \frac{-v_2}{R_2} = \frac{-20}{10} \Rightarrow \boxed{i_2 = -2 \text{ A}}$$

$$P_1 = \frac{v_1^2}{R_1} = \frac{400}{20} \Rightarrow \boxed{P_1 = 20 \text{ W}}$$

received

$$P_2 = \frac{v_2^2}{R_2} = \frac{400}{10} \Rightarrow \boxed{P_2 = 40 \text{ W}}$$

received

or could have used


$$P = R \cdot i^2 \text{ or } P = i \cdot v$$

~~or~~


Basic Concepts 011

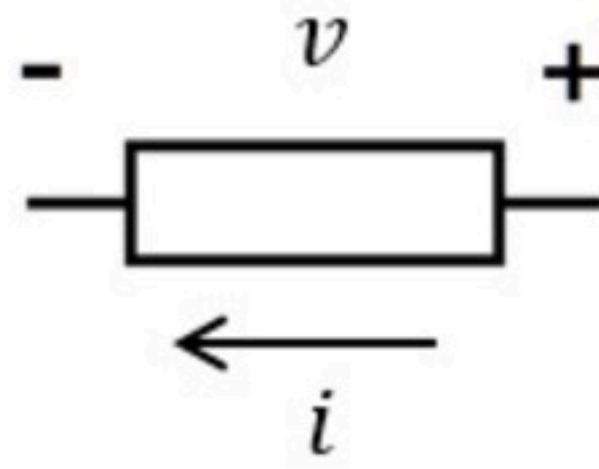Problem has been graded.


Find the power P_1 supplied by this element:



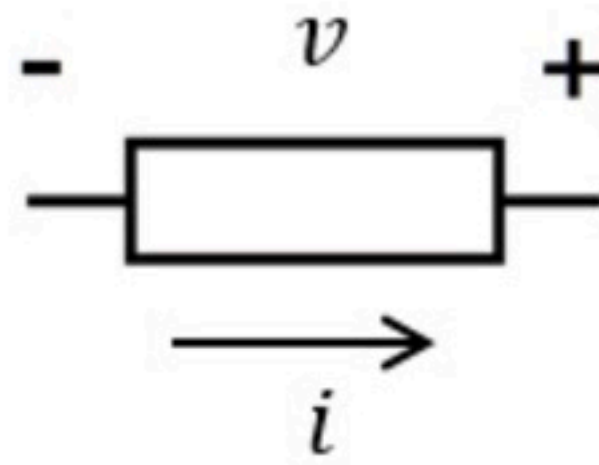Find the power P_2 supplied by this element:



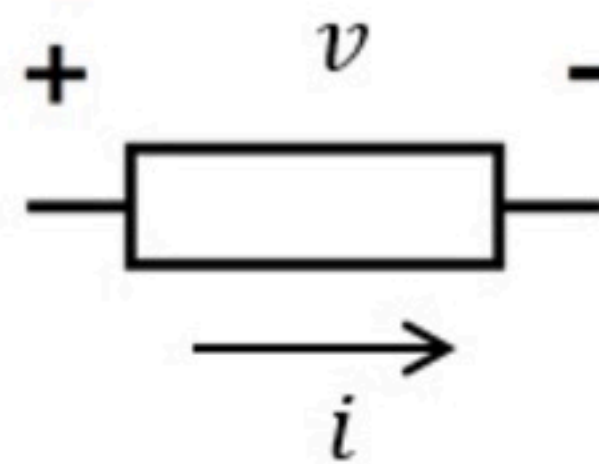Find the power P_3 received by this element:



Given Variables:

v : -5 V

i : 4 A

Calculate the following:


P_1 (W) :

P_2 (W) :

P_3 (W) :

Hint: Convert first to passive sign convention

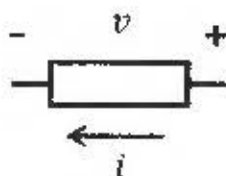
- (a) Find the power P_1 supplied by this element:





$$v = -2 \text{ V}$$

$$i = 3 \text{ A}$$

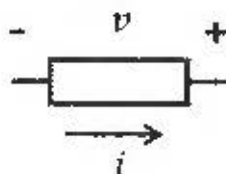- (b) Find the power P_2 supplied by this element:



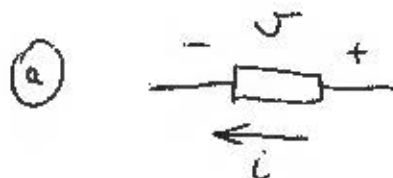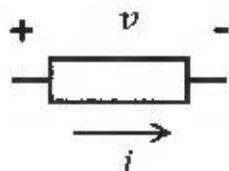
- (c) Find the power P_3 received by this element:



PASSIVE SIGN CONVENTION

$$P = v \cdot i = -6 \rightarrow \text{RECEIVED}$$

$$P_1 = 6 \text{ W SUPPLIED}$$

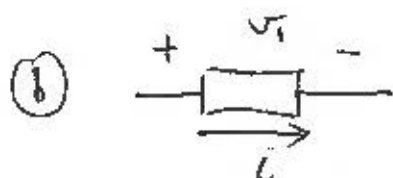


SWITCH TO PASSIVE SIGN CONVENTION

$$v_1 = -v = 2 \text{ V}$$

$$P = v_1 \cdot i = 6 \rightarrow \text{RECEIVED}$$

$$P_2 = -6 \text{ W SUPPLIED}$$

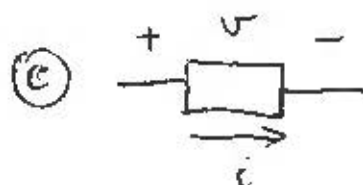

PASSIVE SIGN CONVENTION

$$P = v \cdot i = -6 \rightarrow \text{RECEIVED}$$

$$P_3 = -6 \text{ W RECEIVED}$$