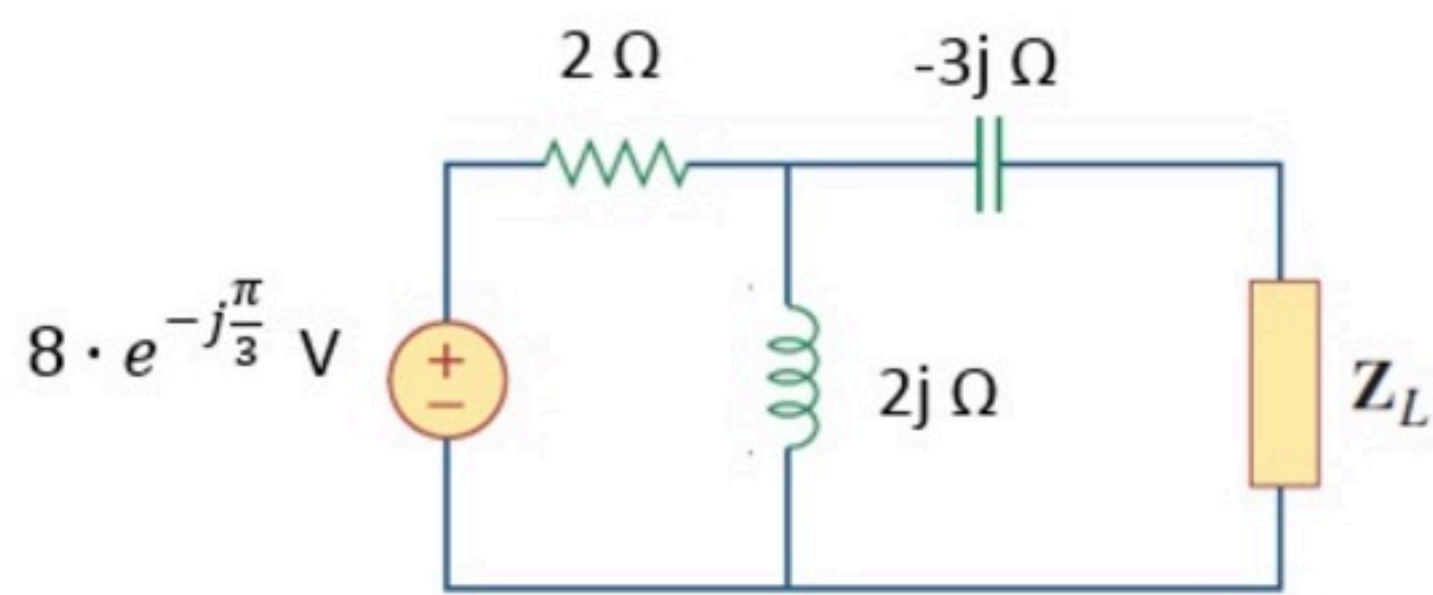


# PP AC power 008

Unlimited Attempts.

Find the value of  $\mathbf{Z_L} = a + jb$  that will receive the maximum amount of power

Find the resulting complex power  $\mathbf{S} = c + jd$  received by the load.



Given Variables:

. . .

Calculate the following:

a (ohm) :

1



b (ohm) :

2



c (W) :

4



d (VAR) :

8



Hint: Set the independent source to zero. Find  $Z_{th}$ .