

Phasors 016


2 of 5 attempts made

The AC circuit below is in steady-state, and you are not told the ω of the source. The phasor diagram shows the phasors of i_s and i_a .

The rectangular boxes represent two circuit elements. One of them is an inductor L_1 (but you don't know if it corresponds to i_a or i_b). The other can be a resistor R_2 , a capacitor C_2 or an inductor L_2 .

You are also told that the maximum value of $i_a(t)$ is A_1 and the maximum value of $i_s(t)$ is A_2 .

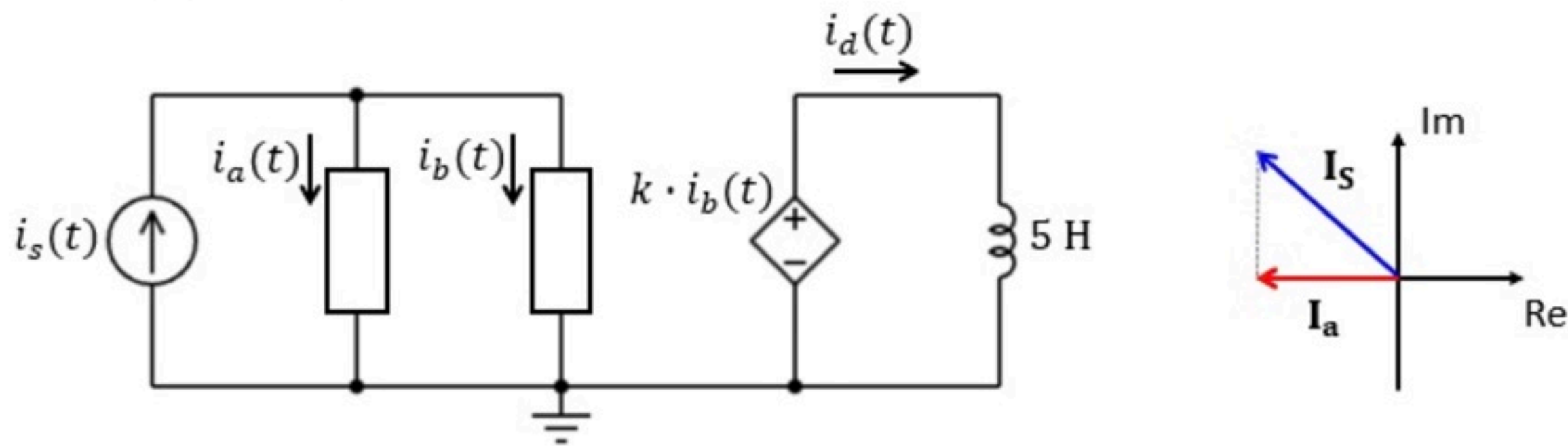- What is the maximum value of the $i_b(t)$ waveform, i_{bmax} ?
- With $i_d(t)$ expressed as $A \cdot \cos(\omega t + B_1)$, what is B_1 ? Constraints: $A > 0$ and $-180^\circ < B_1 \leq 180^\circ$.
- What is the value of ω ?



Given Variables:

A1 : 4 A

A2 : 5 A

L1 : 2 mH

R2 : 3 ohm

C2 : 10 mF

L2 : 3 mH

k : -5 V/A

Calculate the following:

ibmax (A) :

3

✓

B1 (degrees) :

180

✓

omega (rad/s) :

2000

✓