

Circuit theorems 001

Problem has been graded.

A linear system has two inputs, v_a and v_b , and one output, v_{out} .

When $v_a = v_1$ and $v_b = v_2$, then $v_{out} = v_3$.

When $v_a = v_4$ and $v_b = v_5$, then $v_{out} = v_6$.

What is v_{out} , when $v_a = v_7$ and $v_b = v_8$?

Given Variables:

v_1 : 3 V

v_2 : 6 V

v_3 : 12 V

v_4 : 3 V

v_5 : 4 V

v_6 : 48 V

v_7 : 3 V

v_8 : 2 V

Calculate the following:

v_{out} (V) :

Hint: Use the fact that the system is linear