

AC power 002

Unlimited Attempts.


$$v_s(t) = A_1 \cos(1000t + B_1)$$

(a) Find the instantaneous power supplied by the power supply

$$p = A_2\sqrt{3} + A_3 \cos(2000t + B_3) \quad \text{with } -180^\circ < B_3 \leq 180$$

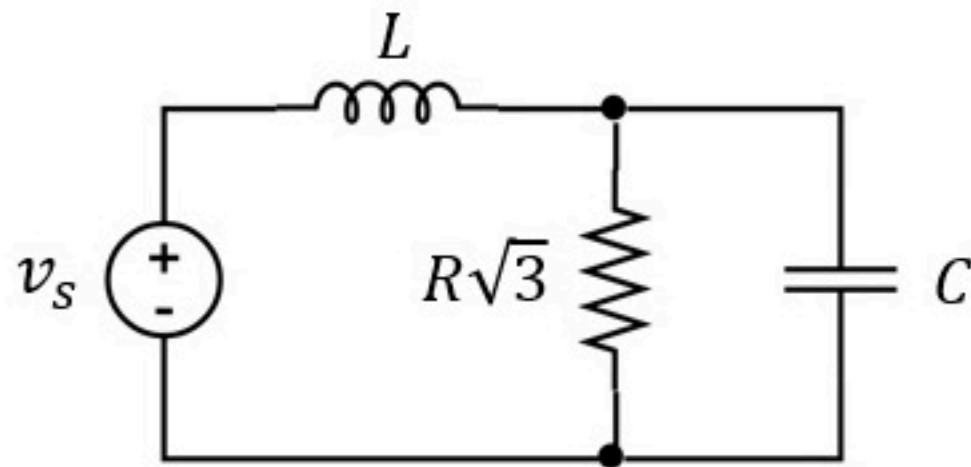(b) Find the instantaneous power received by the inductor

$$p = A_4\sqrt{3} + A_5 \cos(2000t + B_5) \quad \text{with } -180^\circ < B_5 \leq 180$$



Given Variables:

A1 : 6 V

B1 : 45 degrees

R : 2 ohm

C : 500 uF

L : 1 mH

Calculate the following:

A2 (W) :

9

✓

A3 (W) :

18

✓

B3 (degrees) :

120

✓

A4 (W) :

0

✓

A5 (W) :

18

✓

B5 (degrees) :

-120

✓

Hint: Find the $v(t)$ and $i(t)$, or use the equations (video lecture)