


Q1

For the first two sub-questions, the switch is open.

- What is the voltage v_a ?
- What is the power P_1 supplied by the resistor R_1 ?

For the next two sub-questions, the switch is closed.

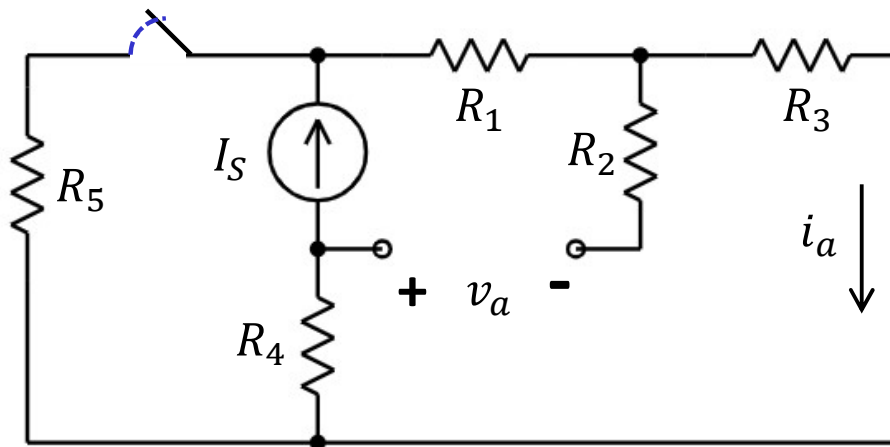- What is the current i_a ?
- What is the power P_2 received by the current source?




R1:	1 Ω
R2:	1 Ω
R3:	5 Ω
R4:	0 Ω
R5:	3 Ω
I _S :	3 A

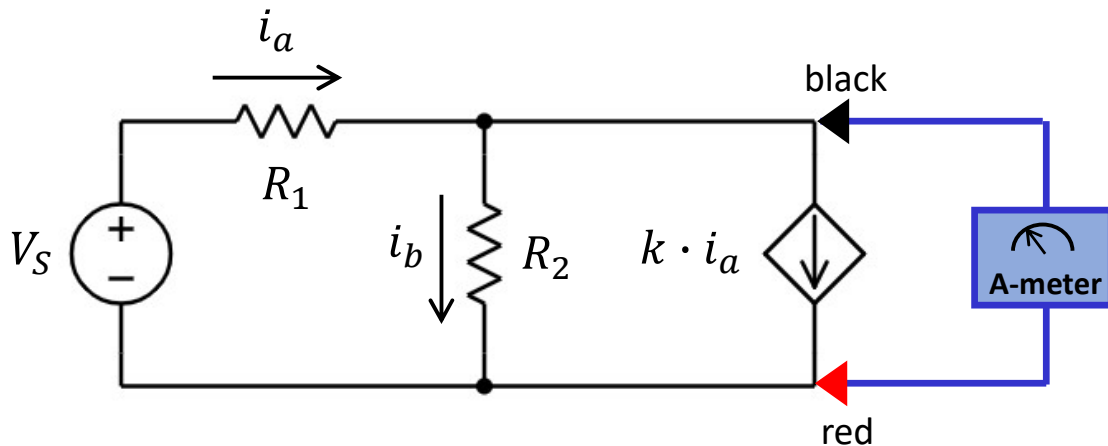Q2

In the problem below, the ammeter is ideal.

- What is the current i_b ?
- What is the reading X of the ammeter?
- We make two changes to the circuit: (1) we replace the ideal ammeter with an ideal voltmeter (without changing the positions the red and black terminals) and (2) we change the value of V_S such that i_a is now 1 A. In this new circuit, what is the reading Y of the newly-placed voltmeter?



R1:	2 Ω
R2:	1 Ω
k:	3
Vs:	2 V