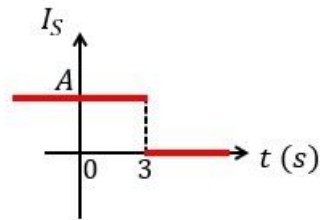



### Q1

The current source  $I_s$  changes from  $A$  to 0 at  $t = 3$  s, as shown on the right. For  $t < 3$  s, you may assume the system has reached steady state. The current  $i_a$  is a mesh current.



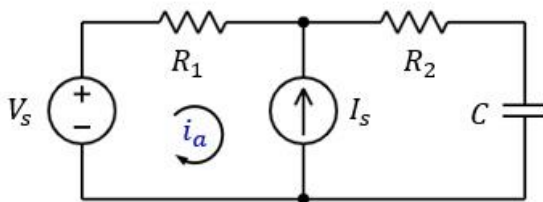- (a) Find  $i_a(3^- \text{ s})$ .  
 (b) Find  $i_a(t)$  for  $t > 3$  s. Write the equation.

R1: 1  $\Omega$   
 R2: 2  $\Omega$   
 Vs: 2 V  
 A: 6 A  
 C: 2 pF



### Q2

For  $t < 0$  s, the switch is open, and you may assume the system has reached steady state. The switch closes at time  $t = 0$  s and opens again at time  $t = 4$  s.

(You can leave your answer written as a function of  $e$ )

- (a) Find  $i_a(2 \text{ s})$ .  
 (b) Find  $i_a(7 \text{ s})$ .

Vs: 4 V  
 R1: 2  $\Omega$   
 L: 4 H

