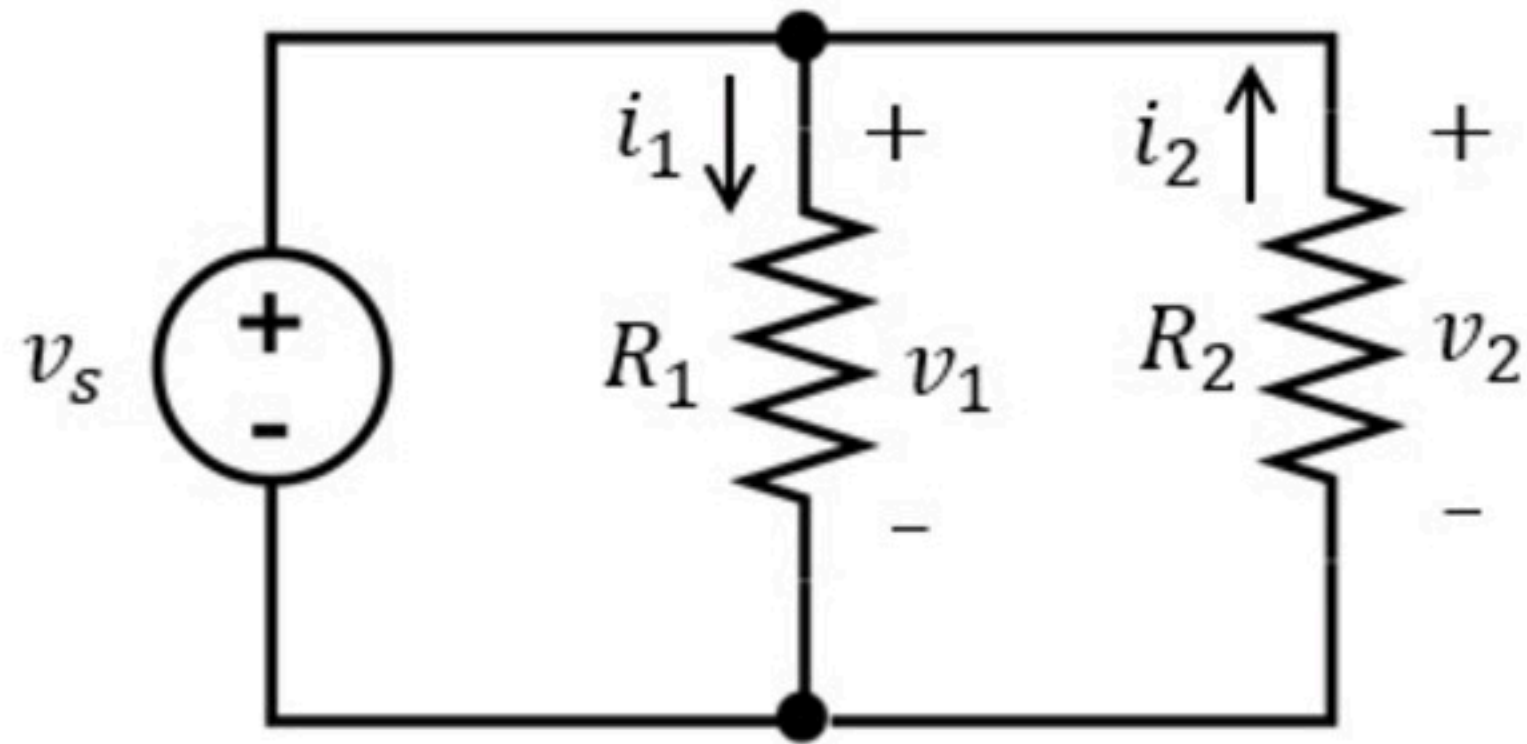


Basic concepts 005

Problem has been graded.

For each of the resistors, calculate the current through them and power received by them.



Given Variables:

v_s : 10 V

R_1 : 10 ohm

R_2 : 4 ohm

Calculate the following:

i_1 (A) :


i_2 (A) :

P_1 (W) :

P_2 (W) :

Hint: Find the voltage across the resistors first

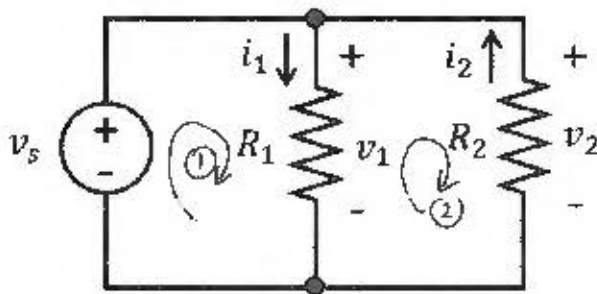For each of the resistors, calculate the current through them and power received by them.



$$v_s = 20 \text{ V}$$

$$R_1 = 20 \Omega$$

$$R_2 = 10 \Omega$$

$$\text{KVL } \textcircled{1} : v_s = v_1 \Rightarrow v_1 = 20 \text{ V}$$

$$\text{KVL } \textcircled{2} : v_1 = v_2 \Rightarrow v_2 = 20 \text{ V}$$

$$i_1 = \frac{v_1}{R_1} = \frac{20}{20} \Rightarrow \boxed{i_1 = 1 \text{ A}}$$

$$i_2 = -\frac{v_2}{R_2} = -\frac{20}{10} \Rightarrow \boxed{i_2 = -2 \text{ A}}$$

$$P_1 = \frac{v_1^2}{R_1} = \frac{400}{20} \Rightarrow \boxed{P_1 = 20 \text{ W}}$$

received

or could have used

$$P = R \cdot i^2 \text{ or } P = i \cdot v$$

$$P_2 = \frac{v_2^2}{R_2} = \frac{400}{10} \Rightarrow \boxed{P_2 = 40 \text{ W}}$$

received