
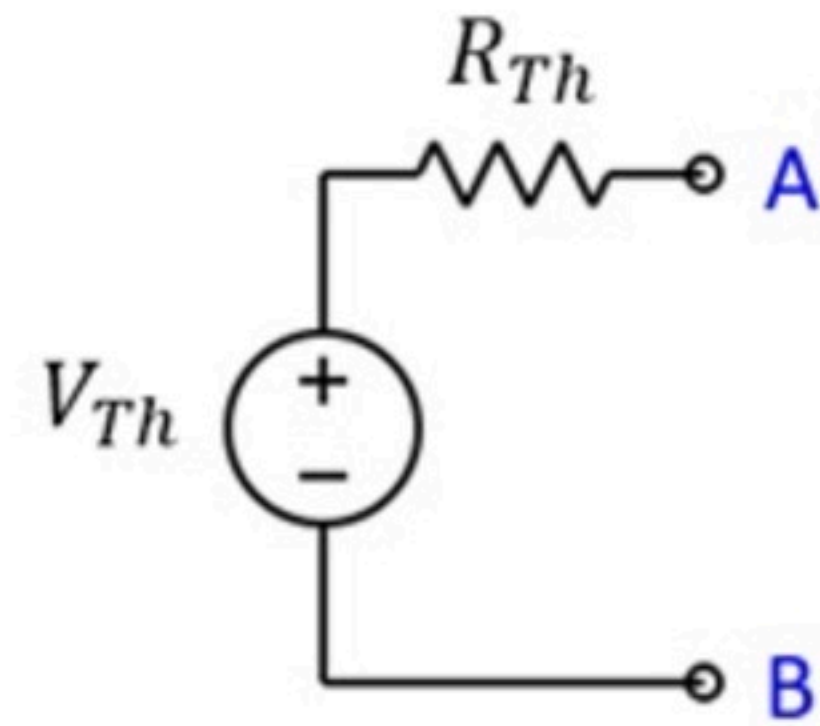


Circuit theorems 014

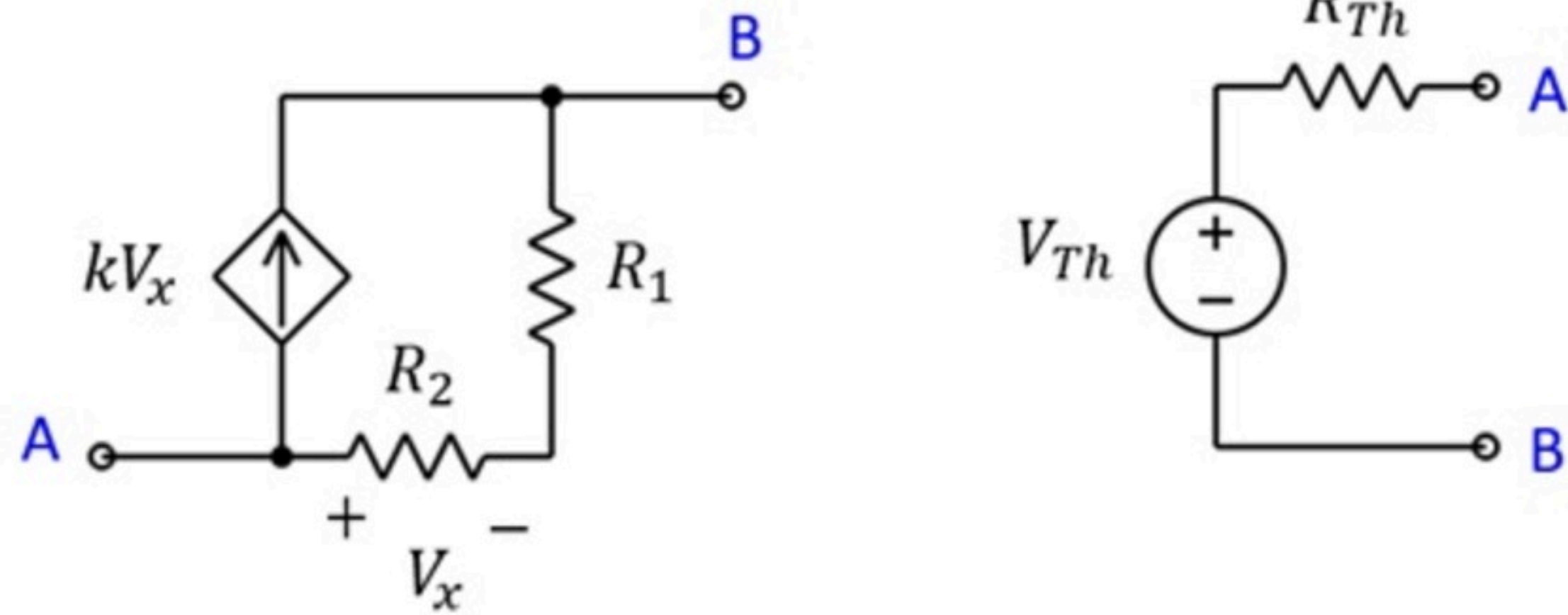Problem has been graded.

The circuit on the right represent the Thevenin model of the circuit on the left. Find the value of V_{Th} and R_{Th} .



Given Variables:

R_1 : 4 ohm

R_2 : 2 ohm

k : -2 A/V

Calculate the following:

V_{th} (V) :

R_{th} (ohm) :