



Name:

PID:

ECE 65 Fall 2018 Final Exam Solutions

Problem 1.

Part a)

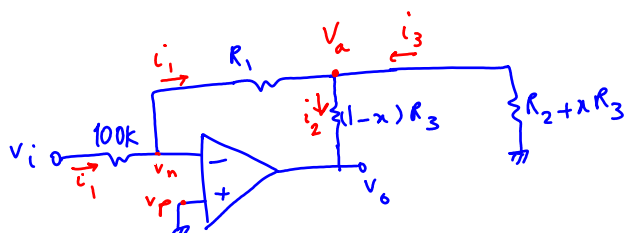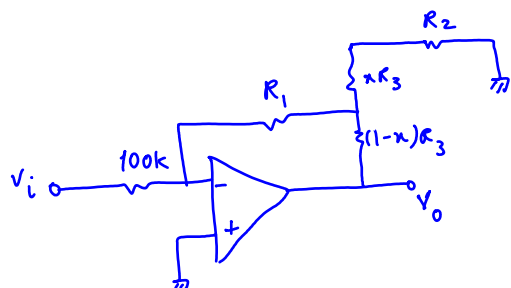

ideal op-amp with negative feedback:

$$i_n = i_p = 0$$

$$V_n = V_p$$

$$i_1 = \frac{V_i}{100k}, \quad V_a = -\frac{R_1}{100k} V_i$$

$$i_3 = \frac{-V_a}{R_2 + xR_3} \quad ; \quad x = 0\% \text{ to } 100\%$$

$$\text{KCL: } i_1 + i_3 = i_2$$

$$i_2 = \frac{V_i}{100k} + \frac{+R_1/(R_2 + xR_3)}{100k} V_i$$

$$V_o = -i_2 \times (1-x)R_3 + V_a$$

$$\Rightarrow V_o = -\frac{(1-x)R_3}{100k} \left(1 + \frac{R_1}{R_2 + xR_3} \right) V_i - \frac{R_1}{100k} V_i$$

$$\text{for } x=1 \rightarrow \frac{V_o}{V_i} = -\frac{R_1}{100k} = -1 \text{ V/V} \rightarrow \boxed{R_1 = 100k\Omega}$$

$$\text{for } x=0 \rightarrow V_o = -\frac{R_3}{100k} \left(1 + \frac{R_1}{R_2} \right) V_i - \frac{R_1}{100k} V_i = -1 \left(1 + \frac{100k}{R_2} \right) V_i - V_i$$

$$\frac{V_o}{V_i} = -2 - \frac{100k}{R_2} = -100 \text{ V/V}$$

$$\frac{100k}{R_2} = 98 \rightarrow \boxed{R_2 = 1.02k\Omega}$$

Part b) $x=0.5$


$$\rightarrow \boxed{\frac{V_o}{V_i} = -2.48 \text{ V/V}}$$

Name:

PID:

Problem 2.

Part a)

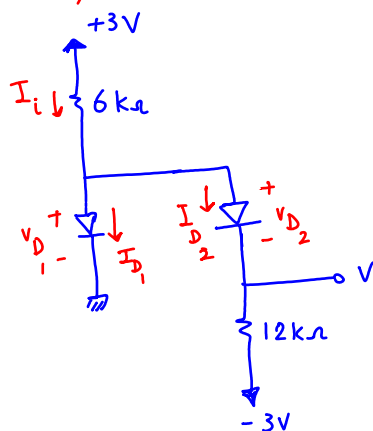

Case 1: Assume D_1 off, D_2 off

$$V_{D1} < V_{D0}, \quad V_{D2} < V_{D0}$$

$$I_{D1} = 0, \quad I_{D2} = 0$$

$$I_i = I_{D1} + I_{D2} = 0$$

$$V_{D1} = 3V - 6k\Omega \times I_i = 3V > V_{D0}$$

\Rightarrow The assumption was wrong

Case 2: Assume D_1 ON, D_2 off

$$V_{D1} = V_{D0}, \quad V_{D2} < V_{D0}$$

$$I_{D1} \geq 0, \quad I_{D2} = 0$$

$$\text{KVL: } V_{D1} = V_{D2} + 12k\Omega \times I_{D2} - 3V$$

$$\rightarrow 0.7V = V_{D2} + 0 - 3V$$

$$\rightarrow V_{D2} = 3.7V > V_{D0}$$

\Rightarrow The assumption was wrong

Case 3: Assume D_1 off, D_2 ON

$$V_{D1} < V_{D0}, \quad V_{D2} = V_{D0}$$

$$I_{D1} = 0, \quad I_{D2} \geq 0$$

$$V_{D2} = 0.7, \quad I_{D2} = I_i$$

$$\text{KVL: } 3V = 6k\Omega \times I_{D2} + V_{D2} + 12k\Omega \times I_{D2} - 3V$$

$$I_{D2} = \frac{6 - 0.7V}{18k} = 0.29mA$$

$$V_{D1} = V_{D2} + 12k\Omega \times I_{D2} - 3V = 1.23V > V_{D0}$$

our assumption was wrong

Name:

PID:

Problem 2.

Case 4: Assume D_1 ON, D_2 ON

$$\begin{aligned} V_{D_1} &= V_{D_0}, & V_{D_2} &= V_{D_0} \\ I_{D_1} &\geq 0, & I_{D_2} &\geq 0 \end{aligned}$$

$$I_i = I_{D_1} + I_{D_2}$$

$$I_i = \frac{3V - V_{D_1}}{6k} = \frac{3 - 0.7}{6k} = 0.38 \text{ mA}$$

$$\text{KVL: } V_{D_1} = V_{D_2} + 12k \times I_{D_2} - 3V \rightarrow I_{D_2} = \frac{3V}{12k} = 0.25 \text{ mA} \geq 0$$

$$I_{D_1} = I_i - I_{D_2} = 0.38 \text{ mA} - 0.25 \text{ mA} = 0.13 \text{ mA} \geq 0$$

$I_{D_1} \geq 0$ and $I_{D_2} \geq 0 \rightarrow$ our assumption was correct.


$$I = I_{D_1} = 0.13 \text{ mA}, \quad V = 12k \times I_{D_2} - 3V = 0V \rightarrow V = 0V$$

Name:

PID:

Problem 2. Part b)

ii) $R = 100\Omega$

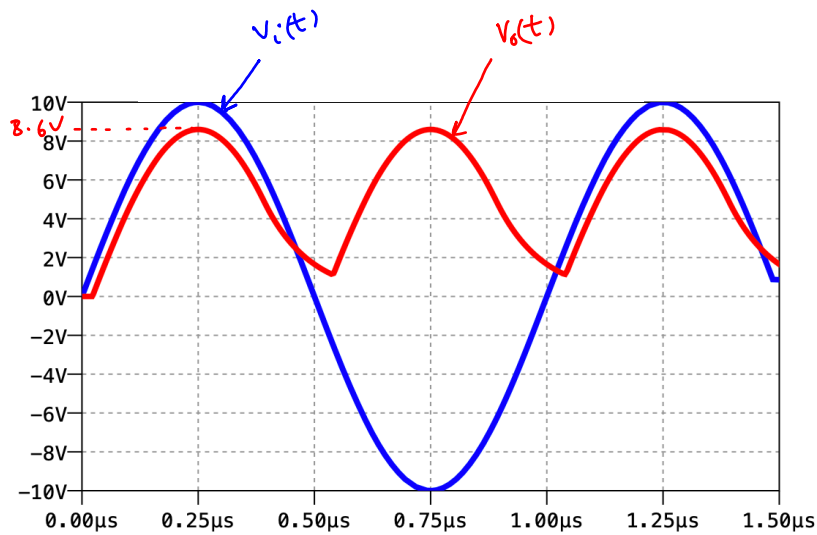


$$RC = 100\Omega \times 1nF = 10^{-7} s$$

$$T = 10^{-6}$$

$$RC = 0.1 T$$

$$V_{o\text{ peak}} = 10 - 2V_{D_o} = 8.6V$$

i) $R = 100k\Omega$

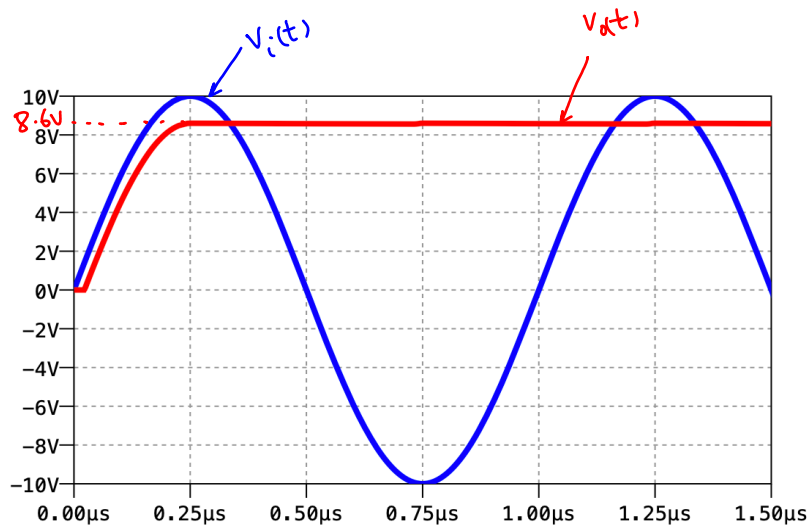

$$RC = 100k\Omega \times 1nF = 10^{-4} s$$

$$RC = 100 T$$


$$V_{o\text{ peak}} = 10 - 2V_{D_o} = 8.6V$$

Name:

PID:

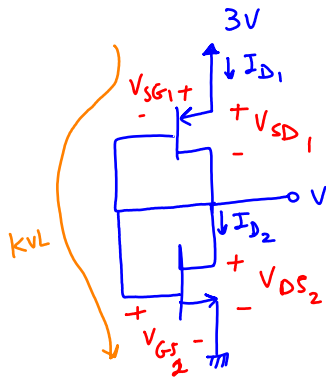Problem 3.

gate and drain are connected to each other in both MOSFETs, so they both will operate in saturation.



$$I_{D1} = I_{D2} = I$$

$$I_{D1} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{SG1} - |V_{tp}|)^2$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{GS2} - V_{tn})^2$$

$$I_{D1} = I_{D2} \rightarrow \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{ovp})^2 = \mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{ovn})^2$$

$$(V_{ovp})^2 = 3 (V_{ovn})^2$$

$$\begin{aligned} \text{KVL: } 3V &= V_{SG1} + V_{GS2} = V_{SG1} - |V_{tp}| + V_{GS2} - V_{tn} + (|V_{tp}| + V_{tn}) \\ &= V_{ovp} + V_{ovn} + 2|V_t| \end{aligned}$$

$$\begin{cases} V_{ovp} + V_{ovn} = 2V \\ V_{ovp} = \sqrt{3} V_{ovn} \end{cases} \rightarrow (\sqrt{3} + 1) V_{ovn} = 2 \rightarrow V_{ovn} = 0.732 V$$


$$V = V_{GS2} = V_{ovn} + V_{tn} = 0.732 + 0.5 \rightarrow \boxed{V = 1.232 V}$$

$$I = I_{D2} = \frac{1}{2} \times 270 \times \frac{3}{1} \times (0.732)^2 = 217 \mu A \rightarrow \boxed{I = 217 \mu A}$$

Name:

PID:

Problem 4.

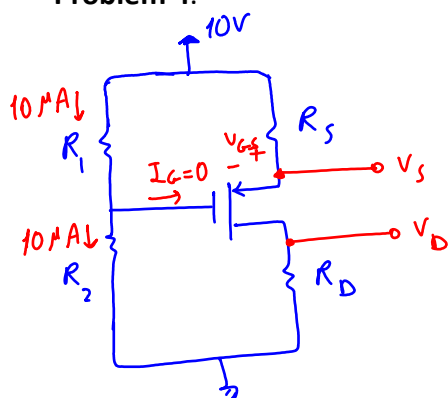PMOS is in saturation: $V_{SD} \geq V_{ov}$ at the edge of saturation: $V_{SD} = V_{ov}$ in this problem: $V_{SD} = V_{ov} + 1$

$$R_D = \frac{V_D}{I_D} = \frac{3V}{1mA} \rightarrow \boxed{R_D = 3k\Omega}$$

$$I_D = \frac{1}{2} k_p V_{ov}^2 \rightarrow 1mA = \frac{1}{2} \times 0.5 mA/V^2 \times V_{ov}^2 \rightarrow V_{ov} = 2V$$

$$V_{SD} = V_{ov} + 1 = 3V$$

$$V_{SD} = V_S - V_D \rightarrow V_S = 3V + V_D \rightarrow \boxed{V_S = 6V}$$

$$R_S = \frac{10V - 6V}{1mA} \rightarrow \boxed{R_S = 4k\Omega}$$

$$V_{ov} = V_{SG} - |V_{tp}| = 2V \rightarrow V_{SG} = 2 + 1 = 3V$$

$$V_{SG} = V_S - V_G = 6V - V_G = 3V \rightarrow \boxed{V_G = 3V}$$

$$V_G = \frac{R_2}{R_1 + R_2} \times 10 = 3 \rightarrow R_2 = \frac{3}{10} (R_1 + R_2) \rightarrow \underline{3R_1 - 7R_2 = 0}$$

$$10V = 10\mu A \times (R_1 + R_2) \rightarrow \underline{R_1 + R_2 = 1M\Omega}$$

Name:

PID:

Problem 4.

$$\begin{cases} 3R_1 - 7R_2 = 0 \\ R_1 + R_2 = 1 \text{ M}\Omega \end{cases}$$



$$R_1 = 0.7 \text{ M}\Omega$$


$$R_2 = 0.3 \text{ M}\Omega$$

Name:

PID:

Problem 5.

part (a)

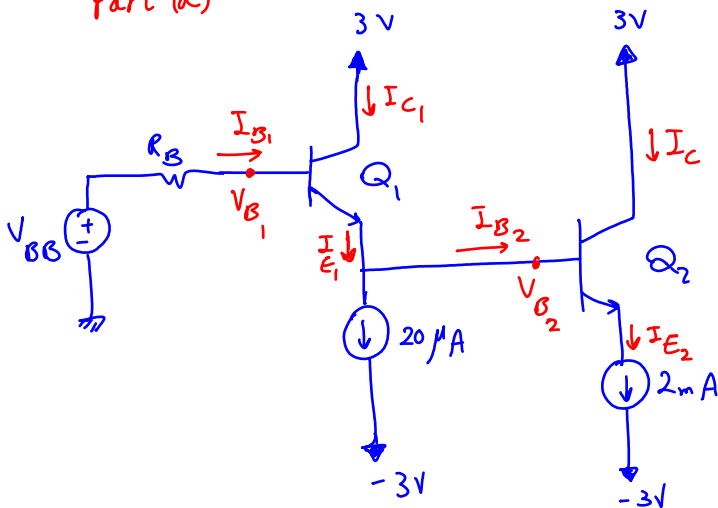

$$I_{E2} = 2 \text{ mA}$$

$$R_B = 3 \text{ M}\Omega \parallel 1 \text{ M}\Omega = 0.75 \text{ M}\Omega$$

$$V_{BB} = \frac{3 \text{ M}\Omega}{3 \text{ M}\Omega + 1 \text{ M}\Omega} \times 3 \text{ V} = 2.25 \text{ V}$$

BJTs will be operating in the active mode \Rightarrow

$$I_{B2} = \frac{I_{E2}}{1 + \beta_2} = \frac{2 \text{ mA}}{201} \approx 9.95 \mu\text{A}$$

$$I_{E1} = 20 \mu\text{A} + I_{B2} = 20 \mu\text{A} + 9.95 \mu\text{A} = 29.95 \mu\text{A}$$

$$I_{E1} = 29.95 \mu\text{A}$$

$$I_{B1} = \frac{I_{E1}}{1 + \beta_1} = \frac{29.95 \mu\text{A}}{51} \approx 0.59 \mu\text{A}$$

$$V_{B1} = V_{BB} - R_B I_{B1} = 2.25 - 0.75 \text{ M}\Omega \times 0.59 \mu\text{A} \approx 1.81 \text{ V}$$

$$V_{B1} \approx 1.81 \text{ V}$$

$$V_{B2} = V_{E1} = V_{B1} - 0.7 \text{ V} = 1.11 \text{ V}$$

$$V_{B2} = 1.11 \text{ V}$$

$$V_{CE1} = V_{C1} - V_{E1} = 3 \text{ V} - 1.11 \text{ V} = 1.89 \text{ V} > V_{D0} \rightarrow Q_1 \text{ is in active mode}$$

$$V_{E2} = V_{B2} - 0.7 \text{ V} = 1.11 \text{ V} - 0.7 \text{ V} = 0.41 \text{ V}$$

$$V_{CE2} = V_{C2} - V_{E2} = 3 \text{ V} - 0.41 \text{ V} = 2.59 \text{ V} > V_{D0} \rightarrow Q_2 \text{ is in active mode}$$

Name:

PID:

Problem 5.

Part b) $g_{m1} = \frac{I_{C1}}{V_T}$, $r_{\pi1} = \frac{\beta_1}{g_{m1}}$

$$I_{C1} = \frac{\beta_1}{\beta_1 + 1} I_{E1} = \frac{50}{51} \times 29.95 \mu A = 29.36 \mu A$$

$$g_{m1} = \frac{29.36 \mu A}{25 mV} = 1.17 (mA/V) \rightarrow g_{m1} = 1.17 (mA/V)$$

$$r_{\pi1} = \frac{50}{1.17} = 42.73 k\Omega \rightarrow r_{\pi1} = 42.73 k\Omega$$


$$g_{m2} = \frac{I_{C2}}{V_T} , \quad r_{\pi2} = \frac{\beta_2}{g_{m2}}$$

$$I_{C2} = \frac{\beta_2}{1 + \beta_2} I_{E2} = \frac{200}{201} \times 2 mA = 1.99 mA$$

$$g_{m2} = \frac{1.99 mA}{25 mV} = 79.6 mA/V \rightarrow g_{m2} = 79.6 mA/V$$

$$r_{\pi2} = \frac{\beta_2}{g_{m2}} = \frac{200}{79.6 mA/V} \approx 2.51 k\Omega \rightarrow r_{\pi2} = 2.51 k\Omega$$

Part c)

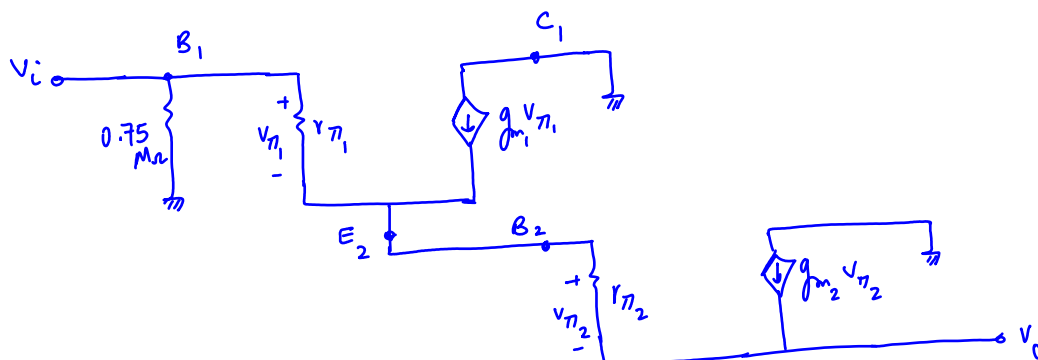


Name:

PID:

Problem 5.

Part d)

The voltage amplifier model:

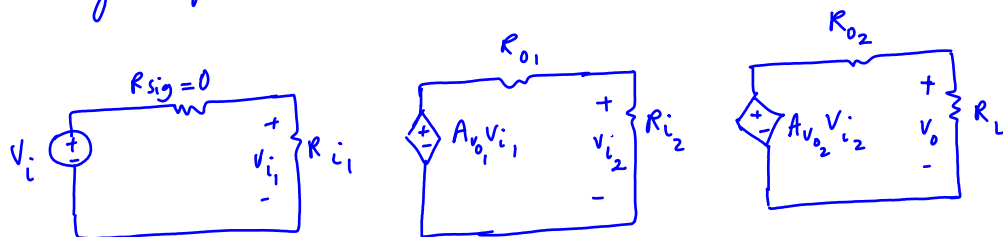

We need to find R_{i1} , R_{i2} , R_{o1} , R_{o2} , $A_{v_{o1}}$, $A_{v_{o2}}$. We can use the given equations for these parameters

Both Q_1 and Q_2 are used in the common-collector configuration.

$$A_{v_{o1}} = \frac{\frac{1}{g_{m1}} \parallel r_{\pi1} \parallel R_{E1} \parallel r_{o1}}{\frac{1}{g_{m1}} \parallel r_{\pi1}} \rightarrow A_{v_{o1}} = \frac{\frac{1}{g_{m1}} \parallel r_{\pi1}}{\frac{1}{g_{m1}} \parallel r_{\pi1}} = 1 \left(\frac{V_o}{V_i} \right) \text{ also } A_{v_{o2}} = 1 \left(\frac{V_o}{V_i} \right)$$

$$R_{o1} = \frac{1}{g_{m1}} \parallel r_{\pi1} \parallel R_{E1} \parallel r_{o1} \rightarrow R_{o1} = \frac{1}{1.17 \text{ mA/V}} \parallel 42.73 \text{ k}\Omega = 838 \Omega$$

$$R_{o2} = \frac{1}{g_{m2}} \parallel r_{\pi2} = \frac{1}{79.6 \text{ mA/V}} \parallel 2.51 \text{ k}\Omega \rightarrow R_{o2} \approx 12.5 \Omega$$

$$R_{i2} = R_{B2} \parallel [r_{\pi2} + (\beta_2 + 1)(R_{E2} \parallel r_{o2} \parallel R_L)] , R_{B2} = \infty, R_{E2} = \infty, r_{o2} = \infty, R_L = 100 \text{ k}\Omega$$

$$R_{i2} = r_{\pi2} + (\beta_2 + 1) R_L = 2.51 \text{ k}\Omega + 201 \times 100 \text{ k}\Omega \approx 20.1 \text{ M}\Omega$$

$$R_{i1} = R_{B1} \parallel [r_{\pi1} + (\beta_1 + 1) R_{i2}] = 0.75 \text{ M}\Omega \parallel [42.73 \text{ k}\Omega + 51 \times 20.1 \text{ M}\Omega]$$

$$R_{i1} \approx 744 \text{ k}\Omega$$

$$\frac{V_o}{V_{sig}} = \left(\frac{R_L}{R_L + R_{o2}} \right) (A_{v_{o2}}) \left(\frac{R_{i1}}{R_{i1} + R_{sig}} \right) A_{v_{o1}} = \frac{100 \text{ k}}{100 \text{ k} + 838 \Omega} \times 1 \times 1 \times 1 \approx 0.99 \frac{V_o}{V_i}$$