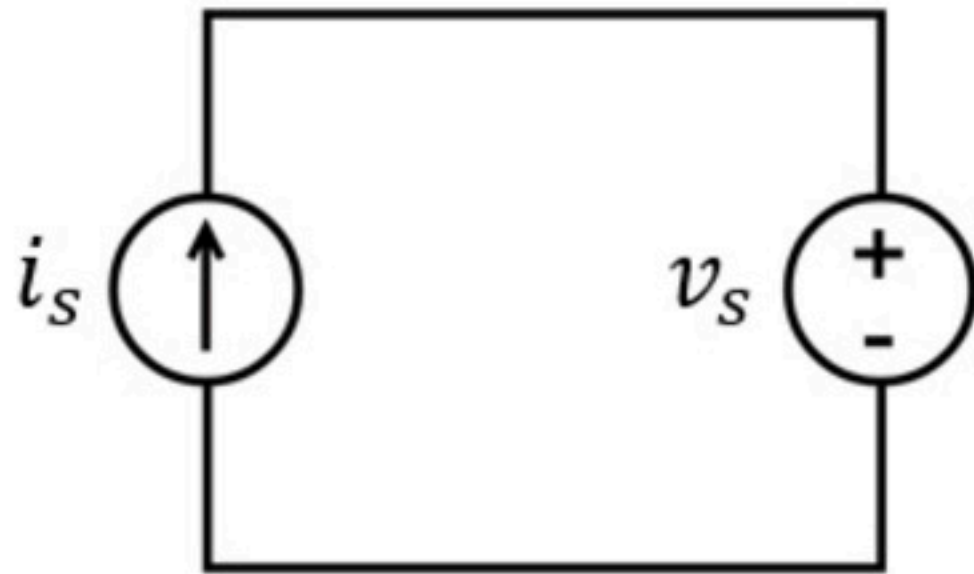


# Basic concepts 007

Problem has been graded.

Find the power  $P_1$  supplied by the current source and the power  $P_2$  supplied by the voltage source.



Given Variables:

$v_s$  : 10 V

$i_s$  : 6 A

Calculate the following:

$P_1$  (W) :


$P_2$  (W) :

Hint: The voltage across a current source can be non-zero

Find the power  $P_1$  supplied by the current source and the power  $P_2$  supplied by the voltage source.

$$V_s = 10 \text{ V}$$

$$I_s = 4 \text{ A}$$

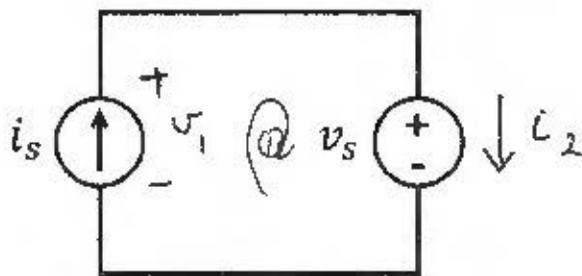

$$\text{KVL } \textcircled{1} : v_1 = v_s = 10 \text{ V}$$

$$\text{KCL} : i_2 = i_s = 4 \text{ A}$$




for passive  
sign convention

$$P_1 = v_1 \cdot i = 10 (-4) = -40 \text{ W} \text{ received}$$

$$i = -i_s = -4 \text{ A}$$

$$P_1 = 40 \text{ W supplied}$$

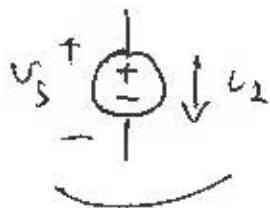

already passive  
sign convention

$$P_2 = v_s \cdot i_2 = 10 \cdot 4 = 40 \text{ W received}$$

$$P_2 = -40 \text{ W supplied}$$

$$\text{Check: } \sum P_{\text{received}} = \sum P_{\text{supplied}} \Rightarrow 0 = 40 - 40$$

OK