
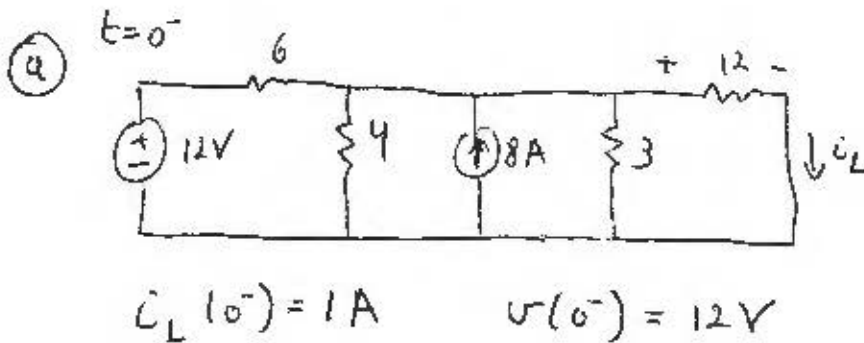


The switch has been closed for a long time before it opens at $t = 0$. After the switch opens, find the resistor voltage $v(t) = A \cdot e^{-t/\tau} + B$.

$$V_s : 12 \text{ V}$$

$$I_s : 8 \text{ A}$$

$$L : 15 \text{ mH}$$

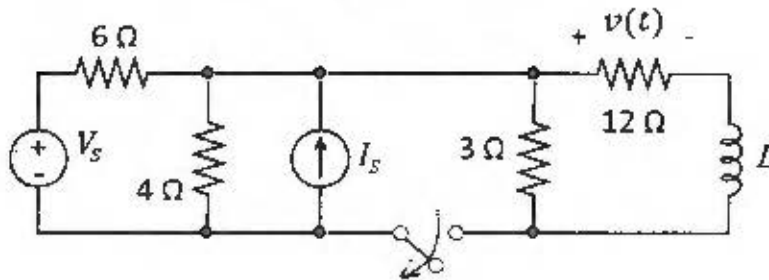


SUPERPOSITION

$$i_{L1} = \frac{12}{6 + 4 \parallel 3 \parallel 12} \cdot \frac{4 \parallel 3}{4 \parallel 3 + 12} = \frac{1}{5} \text{ A}$$


$$i_{L2} = \frac{6 \parallel 4 \parallel 3}{6 \parallel 4 \parallel 3 + 12} \cdot 8 = \frac{4}{5} \text{ A}$$

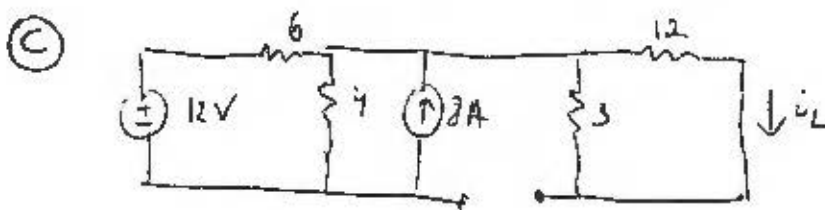b) $t = 0^+ : i_L(0^+) = 1 \text{ A} \Rightarrow v(0^+) = 12 \text{ V}$



$$i_L(\infty) = 0 \text{ A}$$

$$v(\infty) = 0 \text{ V}$$

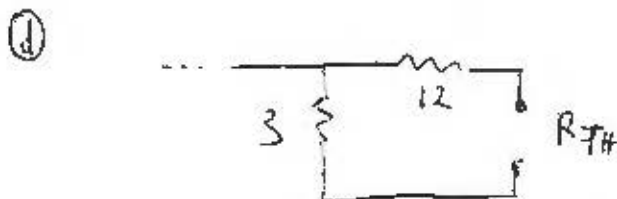

$$R_{TH} = 15 \Omega$$

$$\tau = \frac{L}{R_{TH}} = \frac{15 \cdot 10^{-3}}{15} = 10^{-3} \text{ s}$$

$$\tau = 1 \text{ ms}$$

$$B = v(\infty) \Rightarrow B = 0 \text{ V}$$

$$A + B = v(0^+) \Rightarrow A = 12 \text{ V}$$