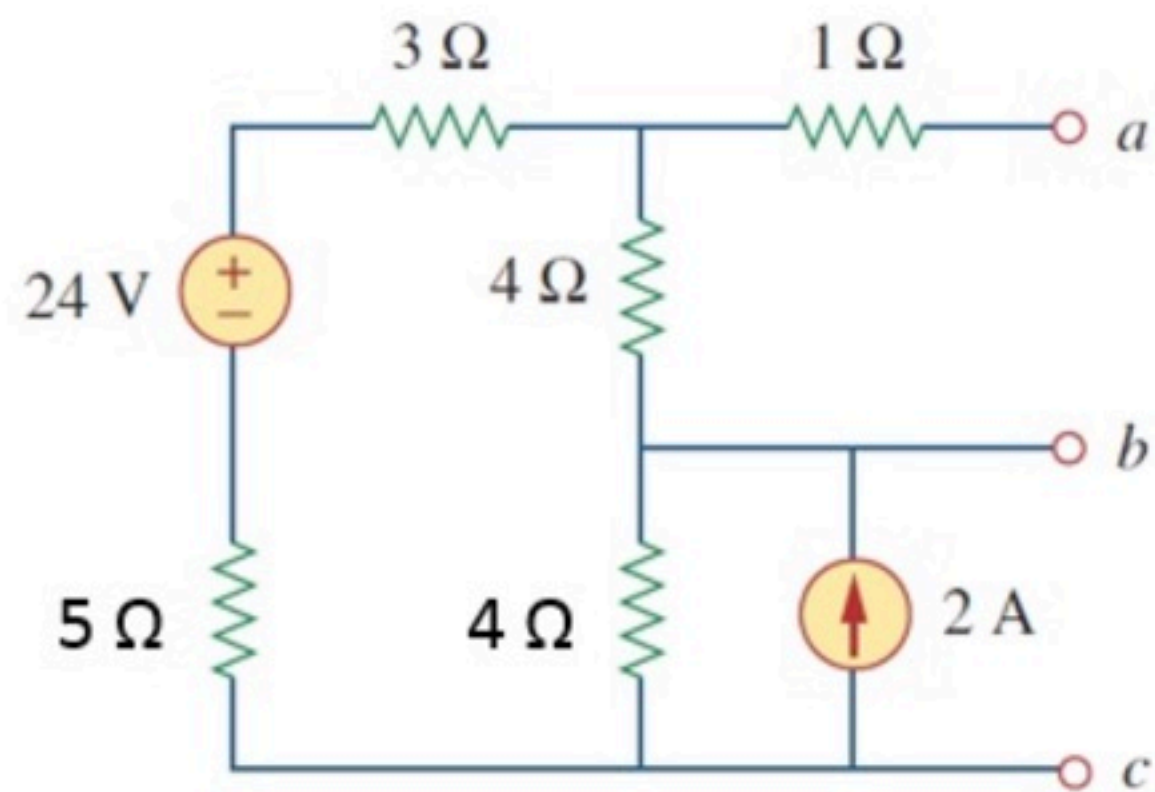
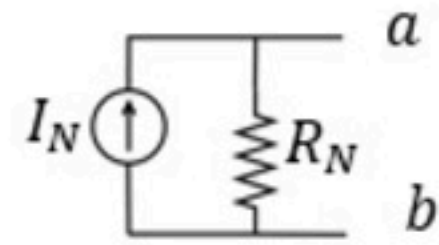


# PP Circuit theorems 020

Unlimited Attempts.

Find the Norton equivalent model of this circuit, as seen between a and b. [Hint: if you have difficult numbers, try to use different tests]



Given Variables:

...

Calculate the following:

$I_N$  (A) :

1



$R_N$  (ohm) :

4



Hint: Can you plug in the 1 ohm resistor afterwards?