

ECE 35, Fall 2021
Final – Section B

Your sequence number

--

Grade

--

 / 45

Last name


First + middle
name(s)**PID**

Instructions:

- Do not look at the questions or start writing until it is announced you can do so.
- Make sure you write your PID on EACH page.
- Read each problem completely and thoroughly before beginning.
- Answers without supporting calculations will receive zero credit. If you are using intuition, write a short explanation.
- All calculations must be done on these pages. It should be clear which question they belong to. Use the front for your actual work and the back as scratch paper.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes. Make sure you list units.
- You must follow the Final Exam Procedures that were posted on Canvas. If you are unsure of anything, ask. As a reminder:
 - Your phone should be turned off and put inside your bag
 - Calculators are not allowed.
 - This is a closed book exam.
 - Follow the Academic Integrity standards.



- (1) (4 points) Consider the circuit below.
What is the reading X of the voltmeter?

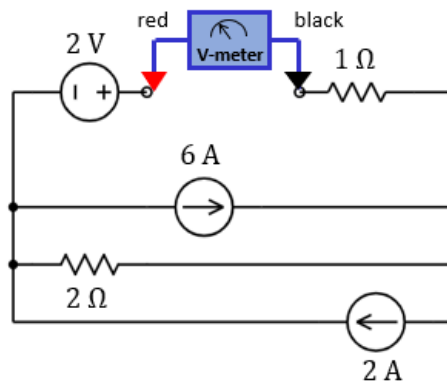 X 

(2) (7 points) Consider the circuit below.


(a) Find the current i_b .

 i_b

(b) Find the power P_1 received by the independent source.


 P_1

(c) Find the power P_2 supplied by the dependent source.

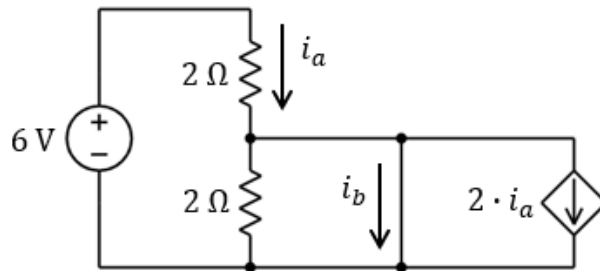
 P_2 

(3) (7 points)

- (a) Consider the circuit below. What is the Thevenin equivalent resistance between A and B?

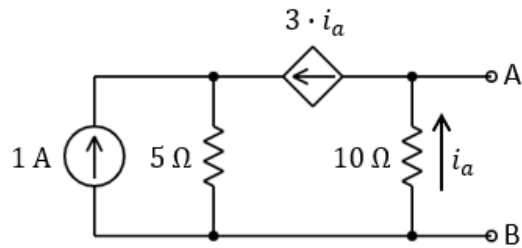 R_{TH} 

- (b) Consider the circuit below (which contains the circuit above). Find the value of resistor R such that the power received by R is maximized.

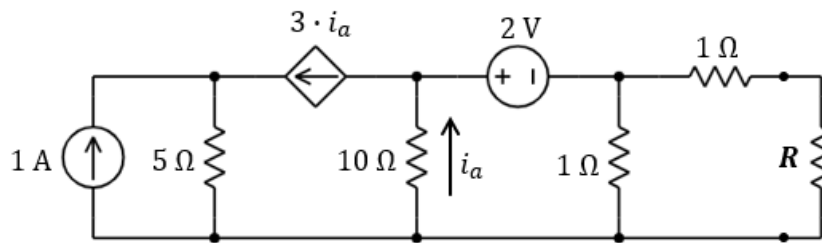 R 

- (4) (10 points) Consider the circuit below. For $t < 2$ s, the switch is closed and you may assume the system has reached steady state. The switch opens at $t = 2$ s and remains open.

Note: make sure you don't mix up v_a and v_b in the questions below.

- (a) Find the node voltage $v_a(2^-)$. (i.e., just before the switch opens).

 $v_a(2^-)$


- (b) Find the node voltage $v_b(2^+)$. (i.e., just after the switch opens).


 $v_b(2^+)$

- (c) Find the node voltage $v_a(10$ s).

 $v_a(10$ s)


- (d) Find the node voltage $v_b(\infty)$.

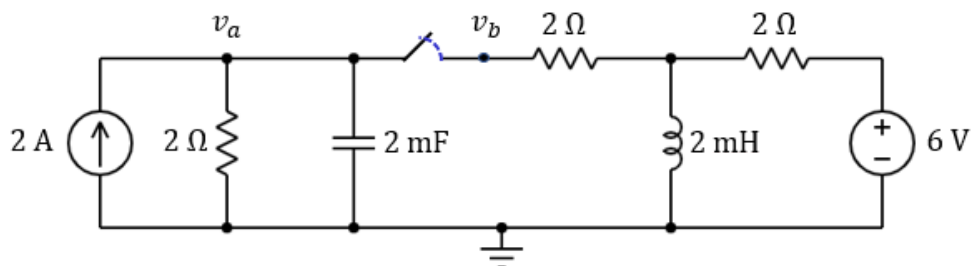 $v_b(\infty)$

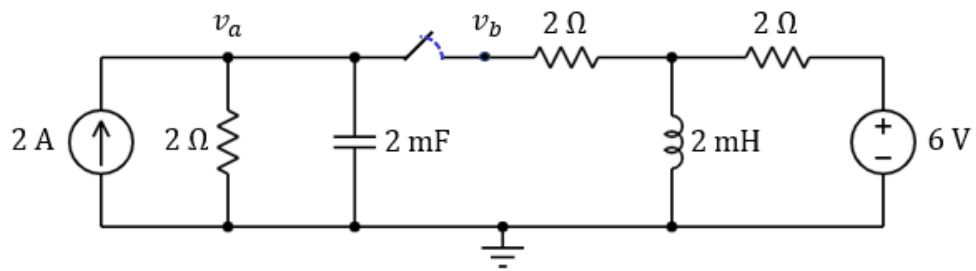


PID

Page 7 of 12

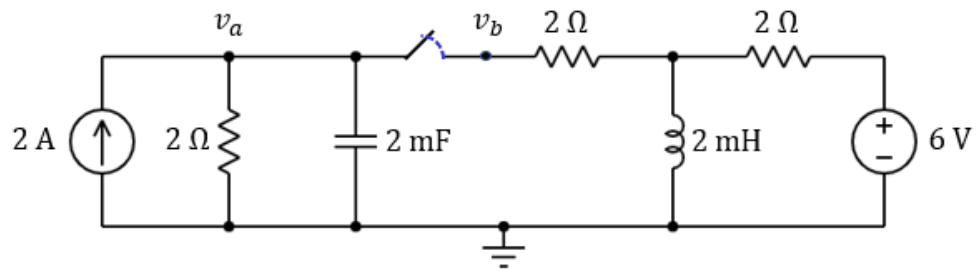



- (5) (9 points) Consider the circuit below. For $t < \frac{\pi}{2}$ s, the switch is in position 1 and you may assume the system has reached steady state. The source i_s is an AC source with $\omega = 2$ rad/s. Its phasor diagram is shown on the left. The switch moves from position 1 to position 2 at $t = \frac{\pi}{2}$ s and remains in position 2.



(a) Find the current $i_a\left(\frac{\pi^-}{2} \text{ s}\right)$. (i.e., just before the switch moves).

$$i_a\left(\frac{\pi^-}{2} \text{ s}\right)$$

(b) Find the current $i_a(2\pi \text{ s})$.

$$i_a(2\pi \text{ s})$$

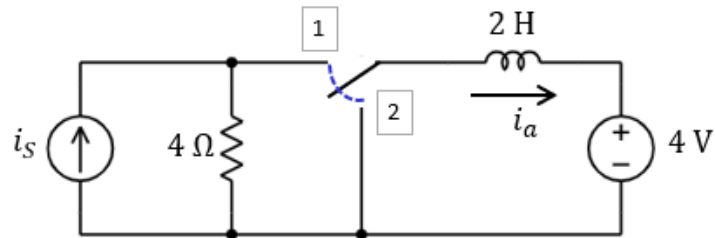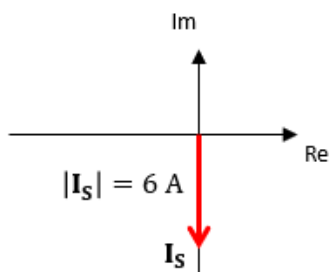

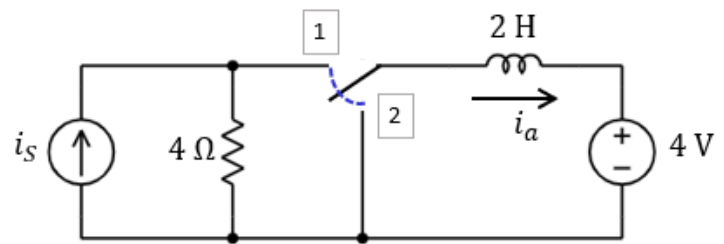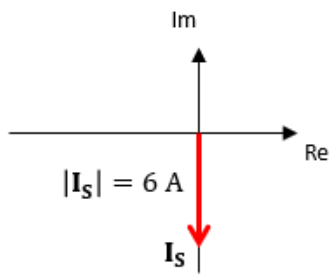

(6) (8 points) The circuit below is in steady state.

- (a) Sketch the phasor of i_a (make sure the magnitude and phase are labeled).



- (b) Find complex power S_L received by the inductor.


 S_L

- (c) If the complex power supplied by the independent source is $0.2 - 0.4j$ VA, what is the total complex power S received by both capacitors ($S_{C1} + S_{C2}$) and the average power P_R received by the resistor?


 $S_{C1} + S_{C2}$

 P_R
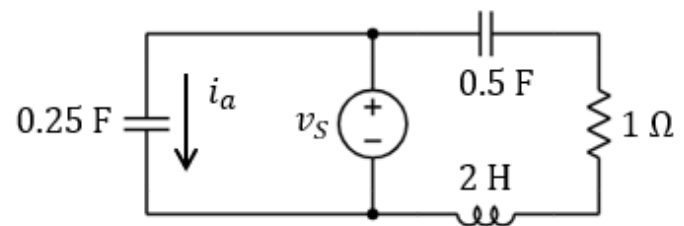
$$v_S = 2 \cdot \sin\left(2t + \frac{\pi}{12}\right) \text{ V}$$


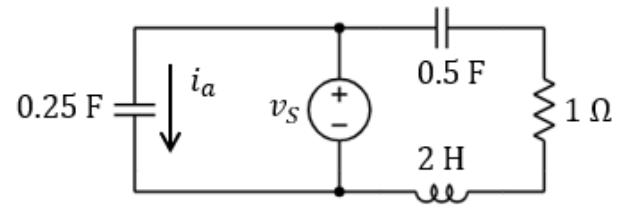
$$v_S = 2 \cdot \sin\left(2t + \frac{\pi}{12}\right) \text{ V}$$



ECE35 Equation Sheet

Basics: $i \triangleq \frac{dq}{dt}$ $v_{ab} \triangleq \frac{dw}{dq}$ $R = \rho \frac{l}{A}$

Capacitors: $C = \epsilon \cdot \frac{A}{d}$ $Q = C \cdot v$ $w_C = \frac{1}{2} C v^2$

Inductors: $L = \mu \cdot \frac{N^2 A}{l}$ $B \sim i$ $w_L = \frac{1}{2} L i^2$

AC power: $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

Trigonometry:

$$\begin{aligned} \sin(-\alpha) &= -\sin(\alpha) & \cos(-\alpha) &= \cos(\alpha) \\ \sin(\pi - \alpha) &= \sin(\alpha) & \cos(\pi - \alpha) &= -\cos(\alpha) \\ \sin\left(\frac{\pi}{2} - \alpha\right) &= \cos(\alpha) & \cos\left(\frac{\pi}{2} - \alpha\right) &= \sin(\alpha) \\ \sin\left(\alpha - \frac{\pi}{2}\right) &= -\cos(\alpha) & \cos\left(\alpha - \frac{\pi}{2}\right) &= \sin(\alpha) \\ \sin(2\alpha) &= 2 \sin(\alpha) \cos(\alpha) & \cos(2\alpha) &= \cos^2(\alpha) - \sin^2(\alpha) \end{aligned}$$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$	$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$						
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$	$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$	$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	∞
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$						