


First order circuits 006

Problem has been graded.

When $t < 0$, $i_s = I_0$

When $t > 0$, $i_s = I_1$

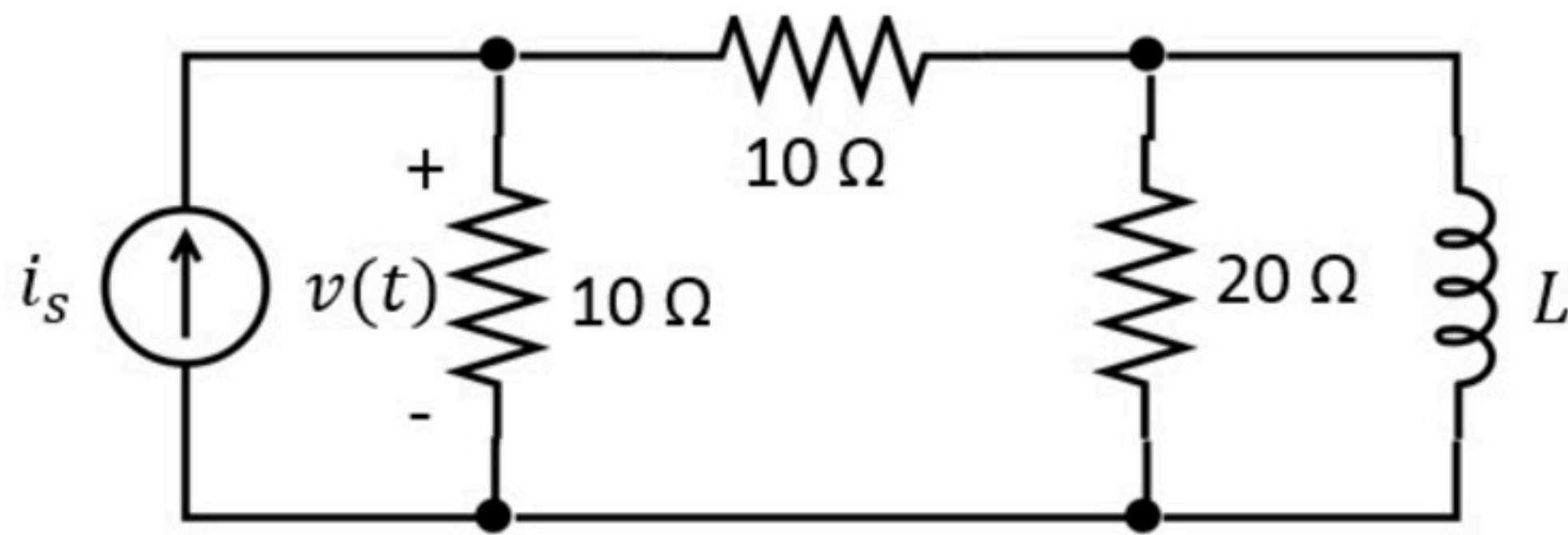Find $v(t) = A \cdot e^{-t/\tau} + B$ for $t > 0$



Given Variables:

$I_0 : 2\text{ A}$

$I_1 : 10\text{ A}$

$L : 0.25\ \mu\text{H}$

Calculate the following:

A (V) :

20

✓

B (V) :

50

✓

τ (ns) :

25

✓

Hint: What is the inductor current for $t < 0$?