

ECE 65: Components & Circuits Lab

Lecture 6

Diode waveform shaping circuits

Rectifier circuits


Reference notes: sections 2.9

Sedra & Smith (7th Ed): sections 4.4-4.6

Saharnaz Baghdadchi

Course map




2. Diodes

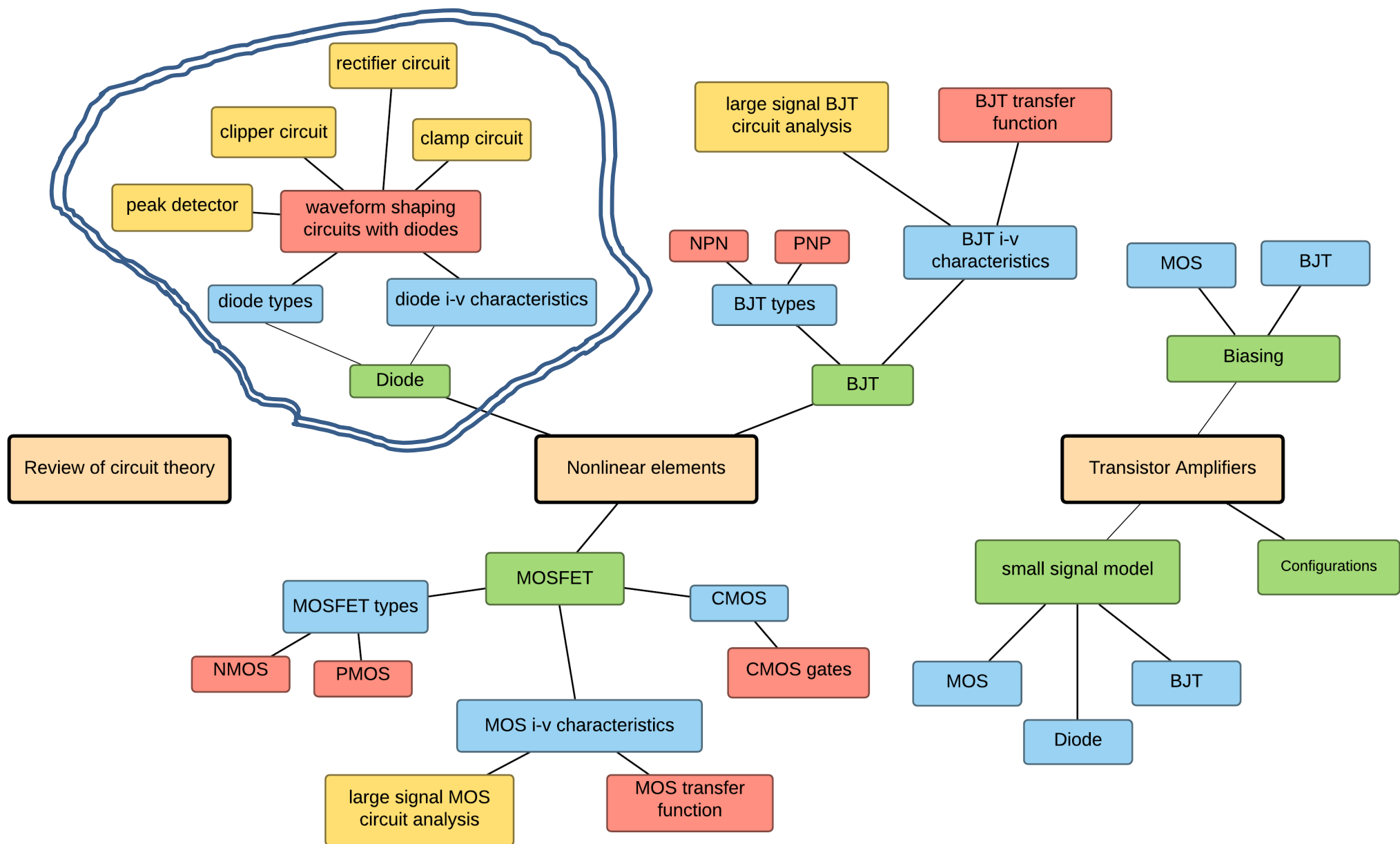

Diodes Waveform shaping Circuits

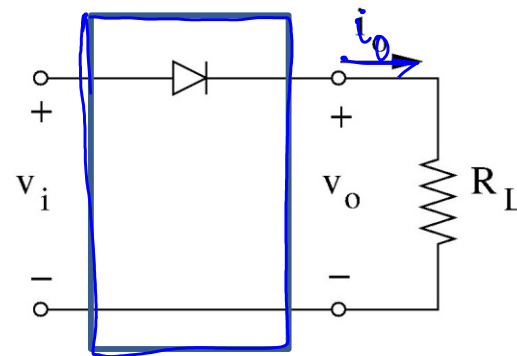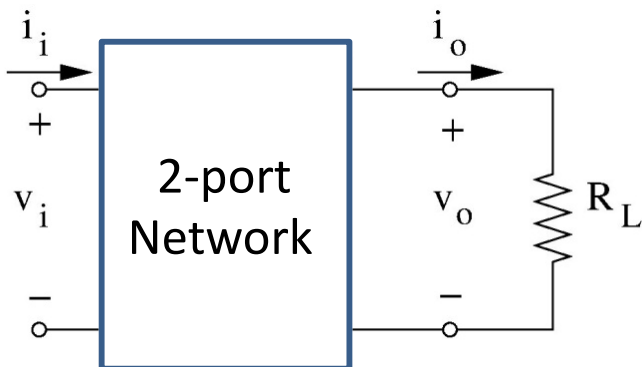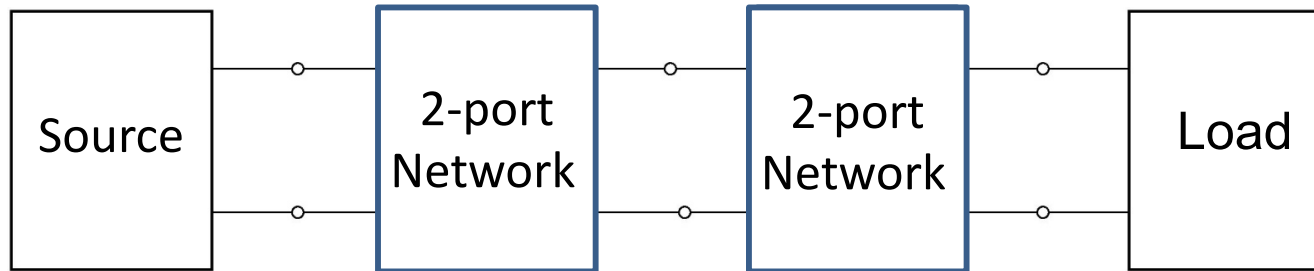- 1. Rectifier Circuit**
- 2. Clipper Circuit**
- 3. Peak Detector**
- 4. Clamp Circuit**

Diode waveform shaping circuits as two-port networks



We would like to find the transfer function, v_o vs v_i


“Open-loop” Transfer function is v_o vs v_i when $R_L \rightarrow \infty$ or $i_o = 0$.

Rectifier Circuit

$$\text{KVL: } \underline{v_i = v_D + v_o} \rightarrow v_o = v_i - v_D$$

$$\text{Ohm's law: } i_D = v_o / R_L$$

$$i_D = i_o$$

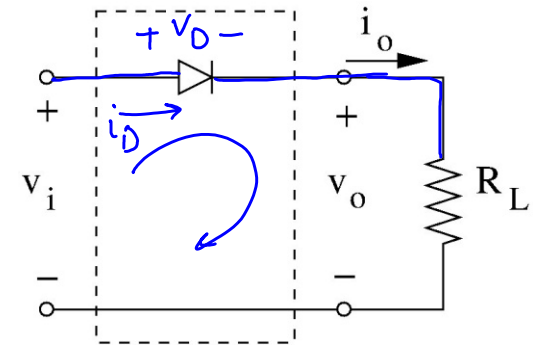

Diode OFF: $i_D = 0$ & $v_D < V_{D0}$

$$v_o = R_L i_D = 0$$

$$v_i = v_D + v_o \Rightarrow v_i = v_D < V_{D0} \rightarrow v_i < V_{D0}$$

Diode ON: $v_D = V_{D0}$ & $\underline{i_D \geq 0}$

$$v_o = v_i - V_{D0}$$



$$i_D = \frac{v_i - V_{D0}}{R} \geq 0 \rightarrow v_i \geq V_{D0}$$

Rectifier Circuit


Transfer Function is non-linear:

For $v_i \geq V_{D0}$, $v_o = v_i - V_{D0}$ (Diode is ON)

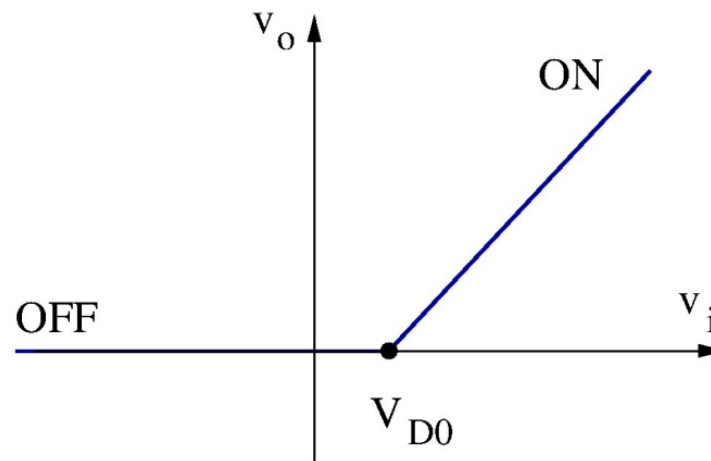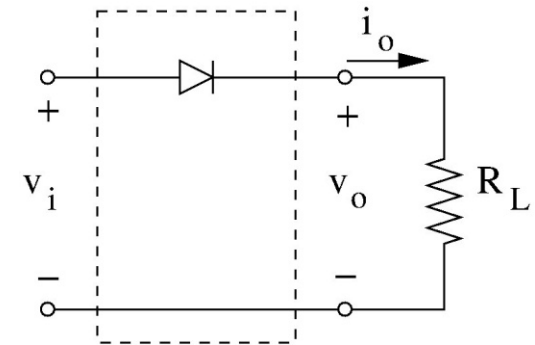For $v_i < V_{D0}$, $v_o = 0$ (Diode is OFF)



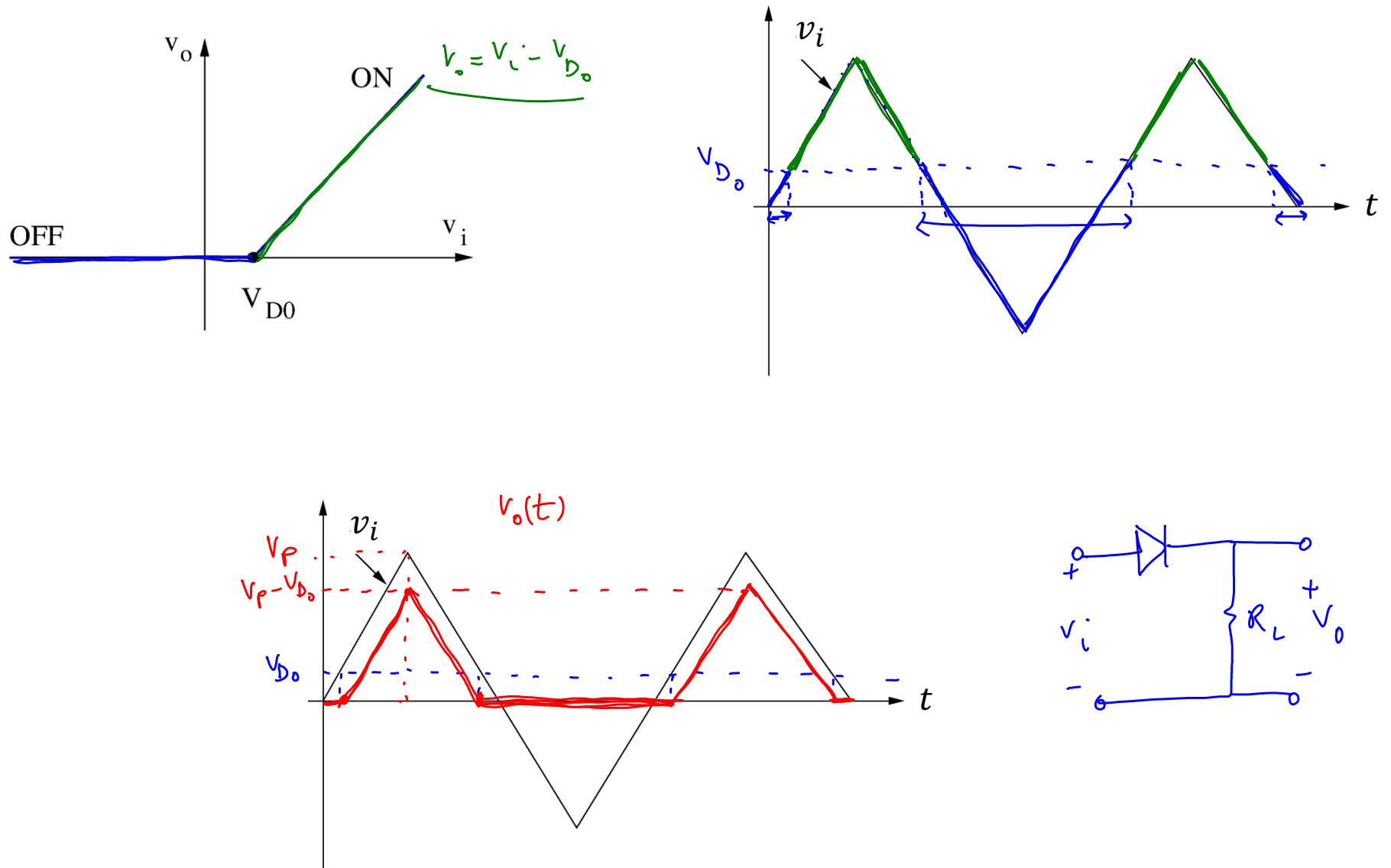Rectifier Circuit: example input - output waveforms




Rectifier Circuit for the negative part of v_i

Transfer Function is non-linear:

For $v_i \leq -V_{D0}$, $v_o = v_i + V_{D0}$ (Diode is ON)

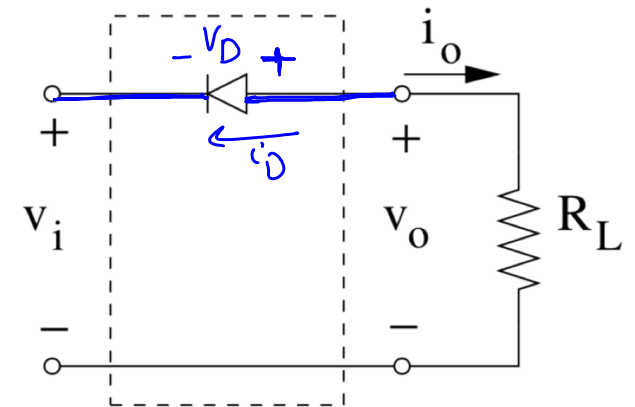For $v_i > -V_{D0}$, $v_o = 0$ (Diode is OFF) $\rightarrow i_D = 0$



Diode ON: $i_D \geq 0$, $V_D = V_{D0}$


KVL:

$$v_i = -V_D - R_L i_D$$

$$\rightarrow i_D = \frac{-V_D - v_i}{R_L}$$



$$i_D = \frac{-V_{D0} - v_i}{R_L} \geq 0$$

$$\rightarrow v_i \leq -V_{D0}$$


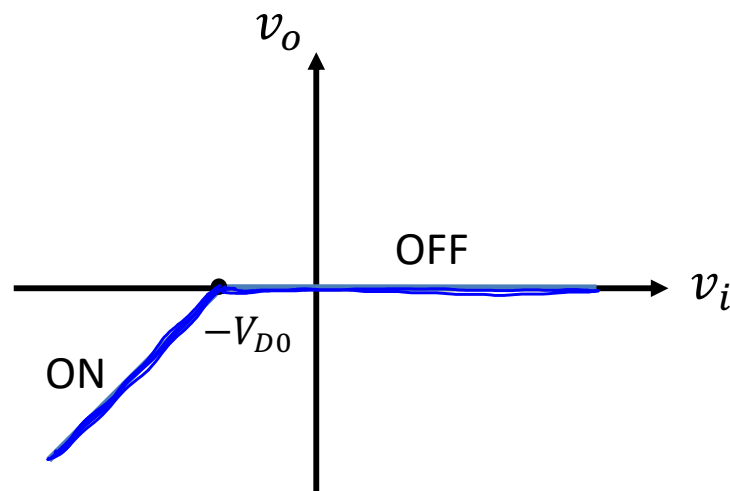


Application of Rectifier Circuit: AC to DC convertor for power supply




Half-wave rectifier

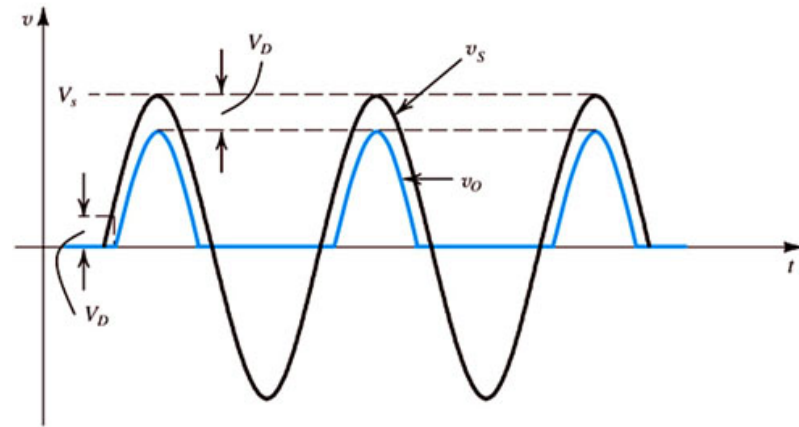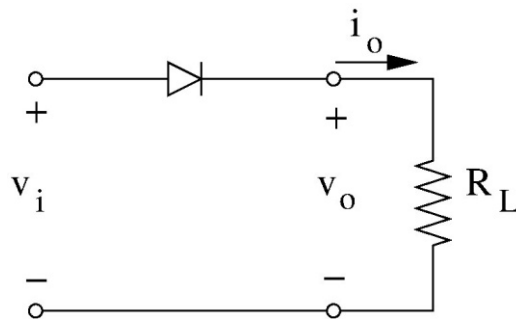

Full-wave rectifier

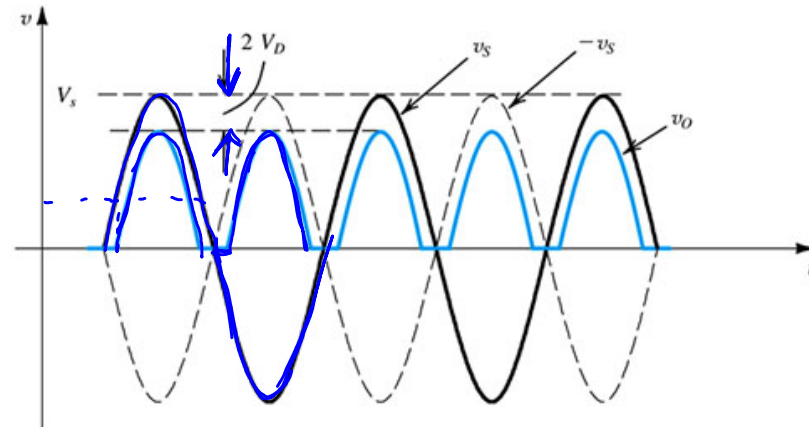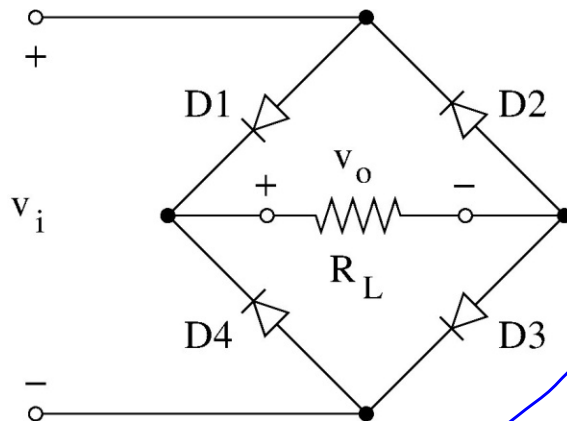

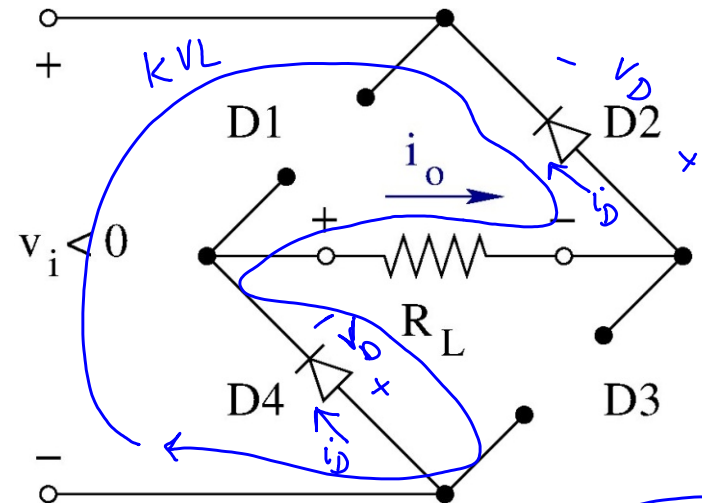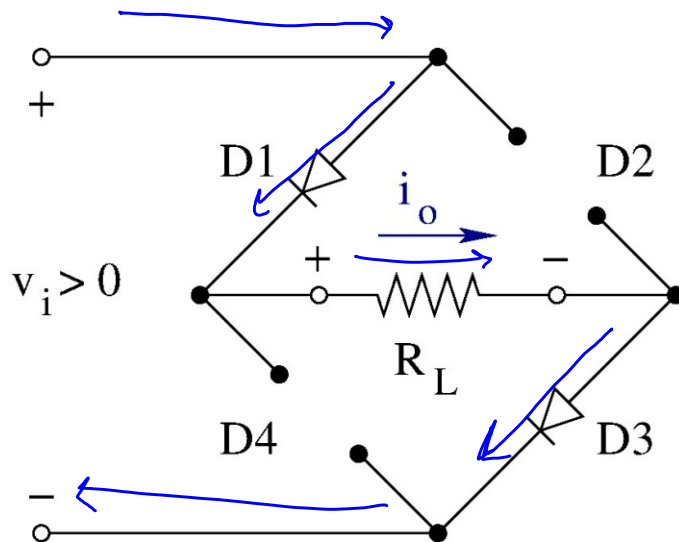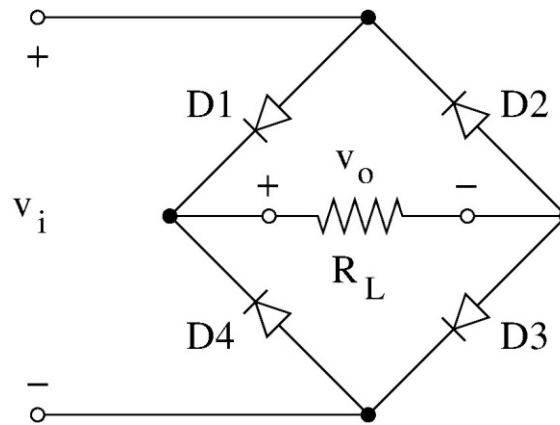Each pair of diodes conduct only for half of the cycle






$$-v_i - v_{D_0} - v_o - v_{D_0} = 0 \rightarrow v_o = -v_i - 2v_{D_0}$$


$$v_i \leq -2v_{D_0}$$

Lecture 6 reading quiz

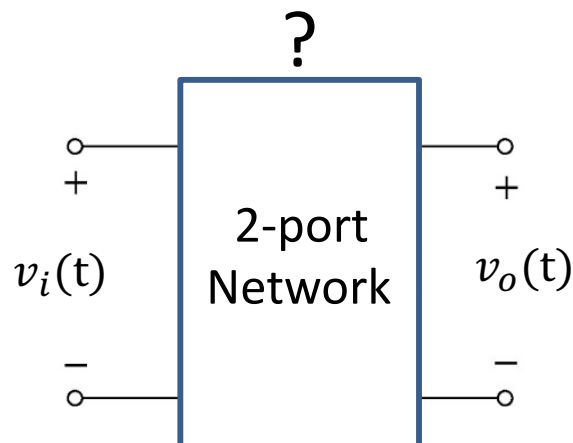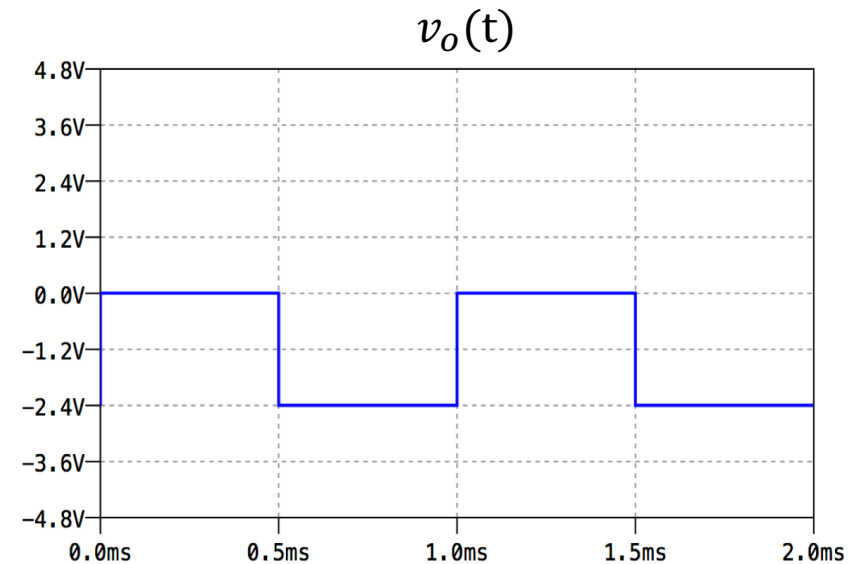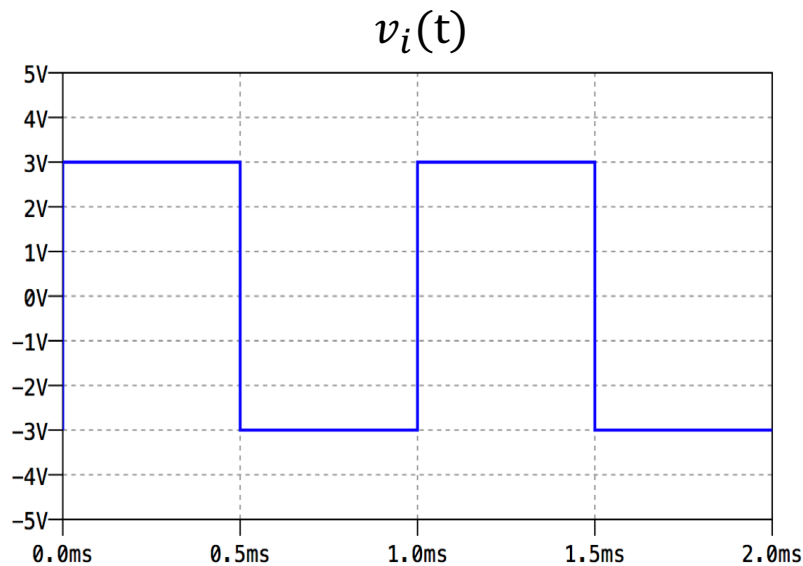Which one of the circuits in the provided options could produce the shown output waveform for the given input signal?




Block Diagram of a DC Power Supply

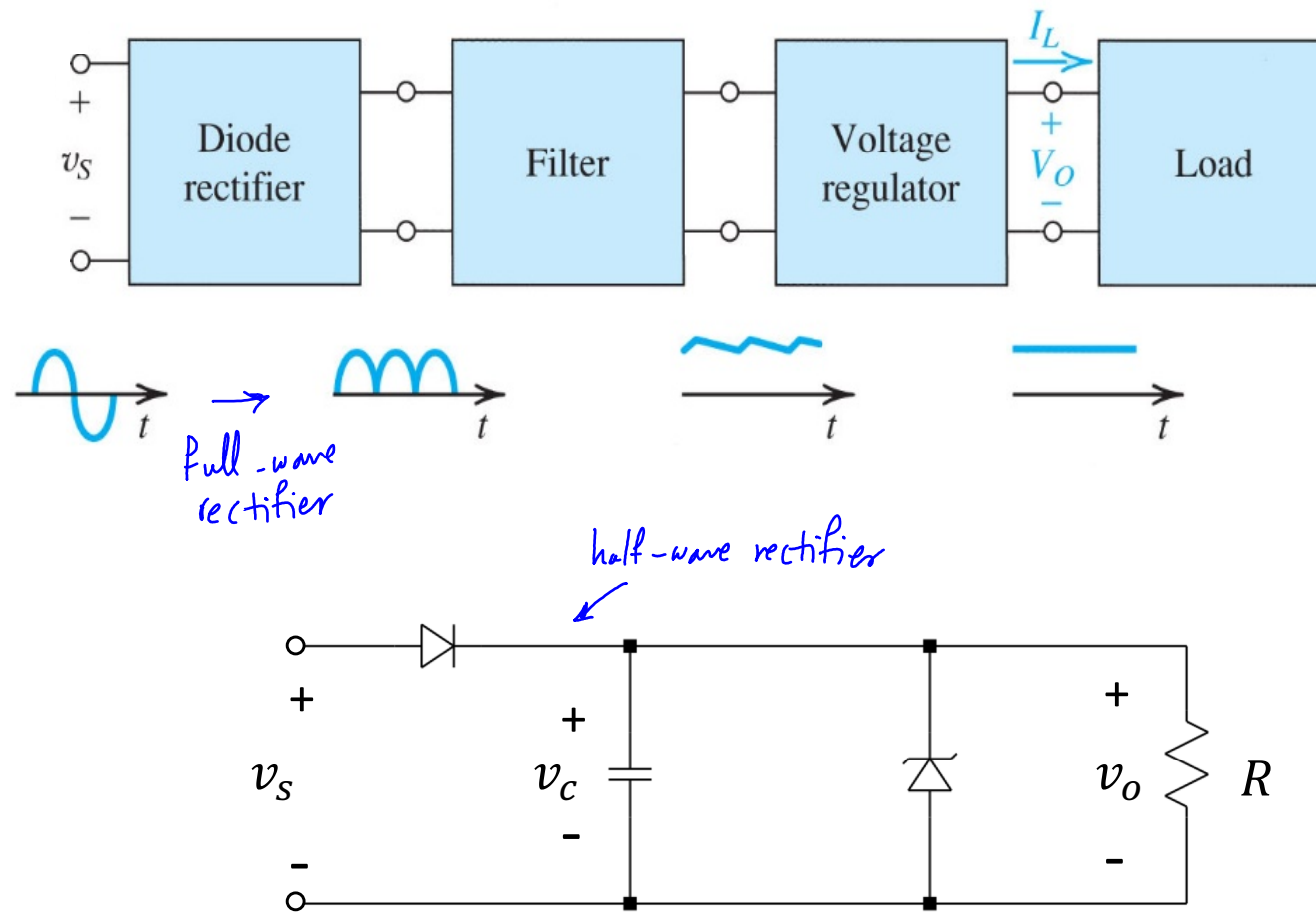

Discussion question 1.

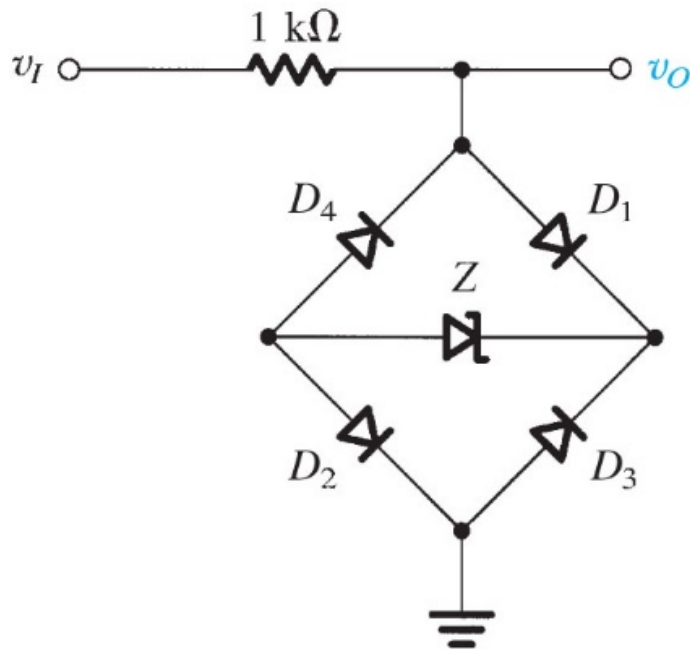Plot the transfer function of the following circuit. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o . Assume $V_{D0} = 0.7\text{ V}$, $V_Z = 4\text{ V}$.




Extra activity:

Draw the output voltage waveform if $v_i = 2 \sin(\omega t)$.

Hints:

Discussion question 1.

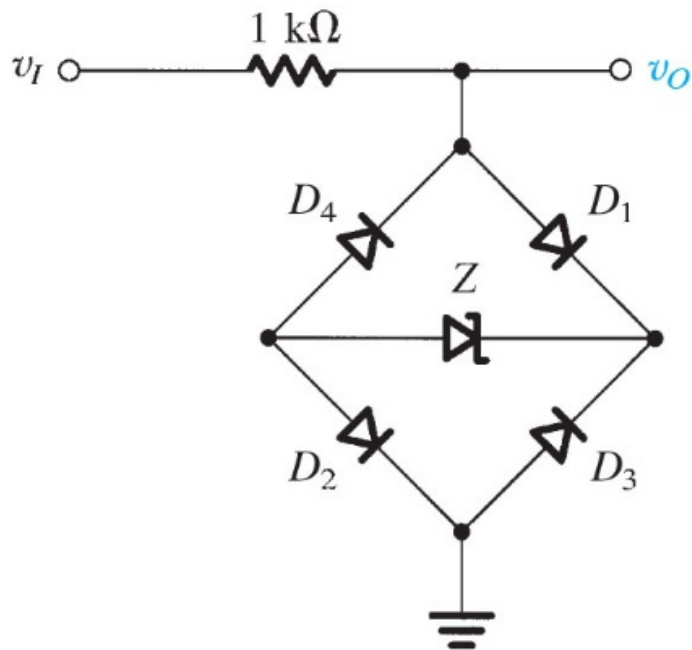Plot the transfer function of the following circuit. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o . Assume $V_{D0} = 0.7\text{ V}$, $V_Z = 4\text{ V}$.



- Label all the diode currents and voltages.
- Think about how current can flow in the circuit. Trace the direction of the current flow, starting from the positive terminal of the v_i and ending at the negative terminal of v_i and the other way around.
- Which diodes will conduct when v_i is positive enough, and which diodes will conduct when v_i is negative enough?
- Use your answer to the above question to create the list of diode cases for this problem.
- For each case, using KVL (and KCL, if needed) and the diode current or voltage inequality, find the range of v_i .
- For each case, using KVL (and KCL, if needed), find v_o as a function of v_i . Note that v_o might be constant and independent of v_i for some ranges of v_i . It will translate to a line with a slope of zero in the graph of v_o vs. v_i (the transfer characteristic graph)


Extra activity:

Draw the output voltage waveform if $v_i = 2 \sin(\omega t)$.

Hints:

Discussion question 1.

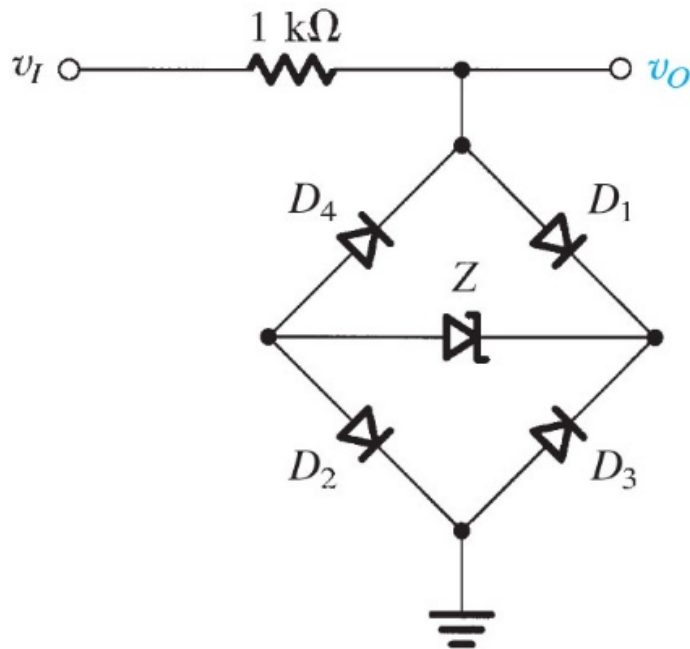Plot the transfer function of the following circuit. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o . Assume $V_{D0} = 0.7\text{ V}$, $V_Z = 4\text{ V}$.



Extra activity:


- What are the maximum and minimum amplitudes of the given v_i ?
- Looking at the transfer characteristic graph, what are the corresponding amplitudes for v_o ?

Extra activity:

Draw the output voltage waveform if $v_i = 2 \sin(\omega t)$.

Discussion question 2.

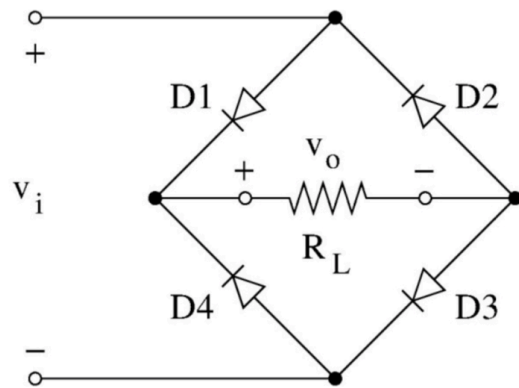Plot the transfer function of the following full-wave rectifier. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o .



Extra activity: Draw the output voltage waveform if $v_i = 2 \sin(\omega t)$.