

# AC power 002

Unlimited Attempts.


$$v_s(t) = A_1 \cos(1000t + B_1)$$

- (a) Find the instantaneous power supplied by the power supply

$$p = A_2\sqrt{3} + A_3 \cos(2000t + B_3) \quad \text{with } -180^\circ < B_3 \leq 180$$

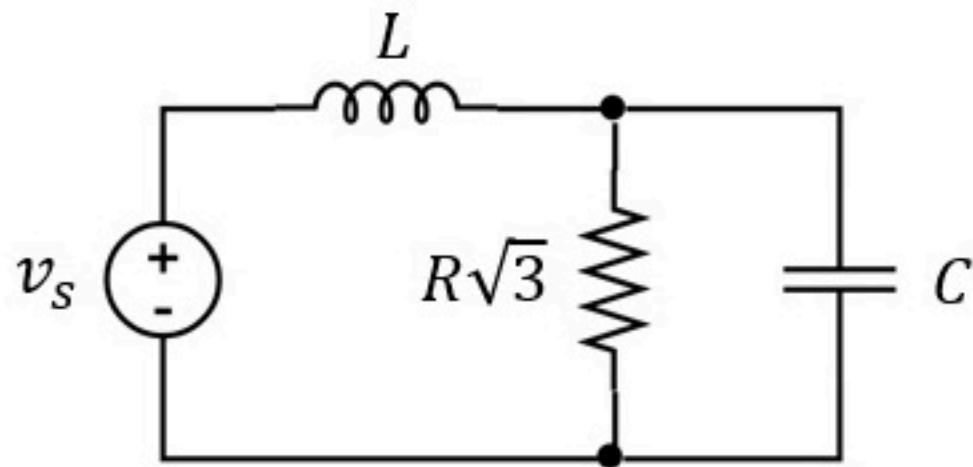- (b) Find the instantaneous power received by the inductor

$$p = A_4\sqrt{3} + A_5 \cos(2000t + B_5) \quad \text{with } -180^\circ < B_5 \leq 180$$



Given Variables:

A1 : 6 V

B1 : 45 degrees

R : 2 ohm

C : 500  $\mu$ F

L : 1 mH

Calculate the following:

A2 (W) :

9



A3 (W) :

18



B3 (degrees) :

120



A4 (W) :

0



A5 (W) :

18



B5 (degrees) :

-120



$$v_s(t) = A_1 \cos(1000t + B_1)$$

A1 : 8 V

(a) Find the instantaneous power supplied by the power supply

$$p = A_2 \sqrt{3} + A_3 \cos(2000t + B_3)$$

B1 : 135 degrees


(b) Find the instantaneous power received by the inductor

$$p = A_4 \sqrt{3} + A_5 \cos(2000t + B_5)$$


R : 2 ohm

C : 500  $\mu$ F

L : 1 mH

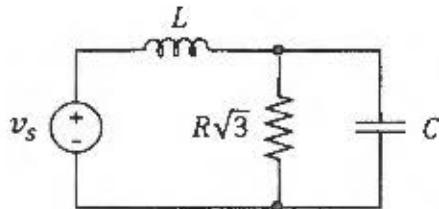

$$V_s = 8 e^{j135^\circ}$$

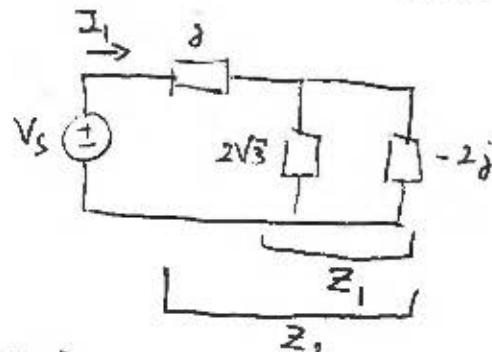

$$Z_1 = \frac{1}{\frac{1}{2\sqrt{3}} + \frac{j}{2}} = \frac{2\sqrt{3}}{1 + \sqrt{3}j} = \frac{\sqrt{3}}{2} (1 - \sqrt{3}j)$$

$$Z_2 = Z_1 + j = \frac{\sqrt{3}}{2} - \frac{j}{2} = 1 \cdot e^{-30^\circ}$$

$$I_1 = \frac{V_s}{Z_2} = 8 e^{j165^\circ}$$

### INSTANTANEOUS POWER

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$\textcircled{a} \quad V = V_s \Rightarrow V_m = 8 \text{ V} \quad \theta_v = 135^\circ$$

$$I = I_1 \Rightarrow I_m = 8 \text{ A} \quad \theta_i = 165^\circ$$

$$A_2 \sqrt{3} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \cdot 8 \cdot 8 \cdot \cos(-30^\circ) = 16\sqrt{3} \Rightarrow \boxed{A_2 = 16 \text{ W}}$$

$$A_3 = \frac{1}{2} V_m I_m = \frac{1}{2} \cdot 8 \cdot 8 \Rightarrow \boxed{A_3 = 32 \text{ W}} \quad \theta_v + \theta_i = 300^\circ \quad \boxed{B_3 = -60^\circ}$$

$$\textcircled{b} \quad I = I_1 \Rightarrow I_m = 8 \text{ A} \quad \theta_i = 165^\circ$$

$$V = j I_1 \Rightarrow V_m = 8 \text{ V} \quad \theta_v = 165^\circ + 90^\circ = 255^\circ$$

$$A_4 \sqrt{3} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \cdot 8 \cdot 8 \cos(90^\circ) = 0 \Rightarrow \boxed{A_4 = 0 \text{ W}}$$


$$A_5 = \frac{1}{2} V_m I_m = \frac{1}{2} \cdot 8 \cdot 8 \Rightarrow \boxed{A_5 = 32 \text{ W}} \quad \theta_v + \theta_i = 420^\circ$$

$$\boxed{B_5 = 60^\circ}$$

# AC power 003

Problem has been graded.

Find  $I_{rms}$  for this waveform.

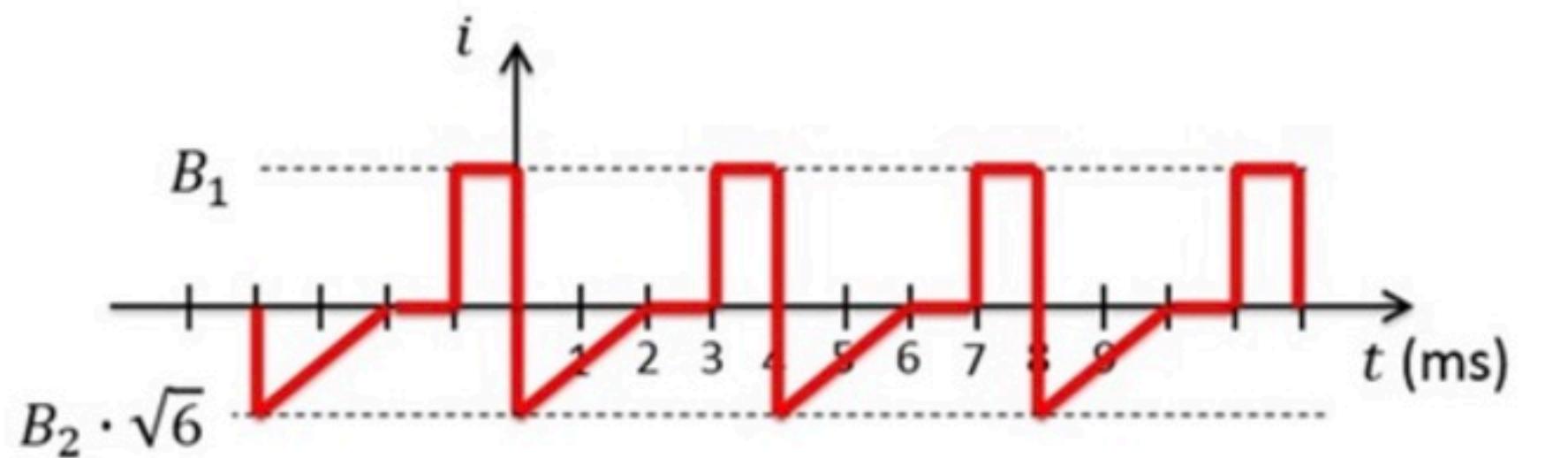

Given Variables:

$B_1 : 6 \text{ A}$

$B_2 : -4 \text{ A}$

Calculate the following:

$I_{rms} (\text{A}) :$

5




Hint: Square the time waveform, integrate, average and take sqrt()

Find  $I_{rms}$  for this waveform.

B1 : 6 A

B2 : -4 A

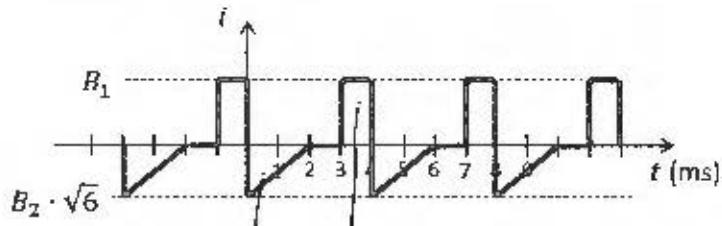

$$i(t) = 6 \Rightarrow i(t)^2 = 36$$

$$i(t) = 2\sqrt{6}(t-2) \Rightarrow i(t)^2 = 24(t-2)^2$$

$$\begin{aligned} \int_0^4 i^2 dt &= \int_0^2 24(t-2)^2 dt + \int_2^4 36 dt \\ &= 24 \left[ \frac{(t-2)^3}{3} \right]_0^2 + 36 \\ &= 8 \cdot (0 - (-2)^3) + 36 \\ &= 64 + 36 \\ &= 100 \end{aligned}$$

$$\sqrt{\frac{1}{4} \int_0^4 i^2 dt} = \sqrt{\frac{1}{4} \cdot 100} = 5 \Rightarrow \boxed{I_{rms} = 5 A}$$



# AC power 004

Problem has been graded.

You are told that the sources in the two circuits below supply the same average power.

(a) Find the average power  $P$  supplied.

(b) Find  $A_1$ .

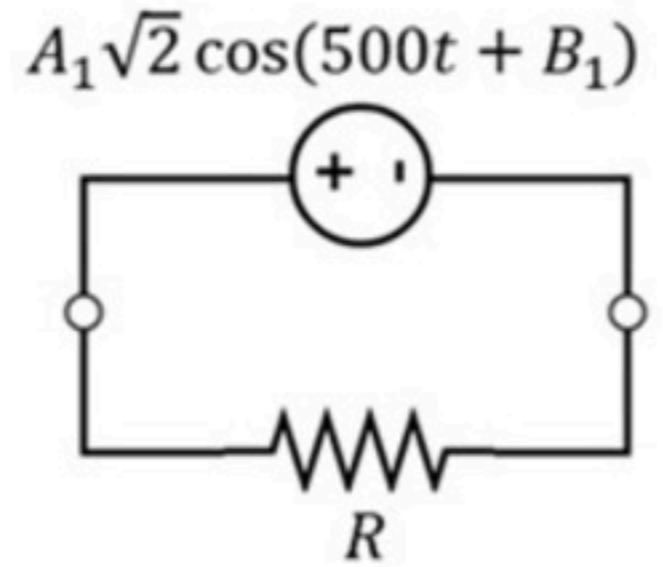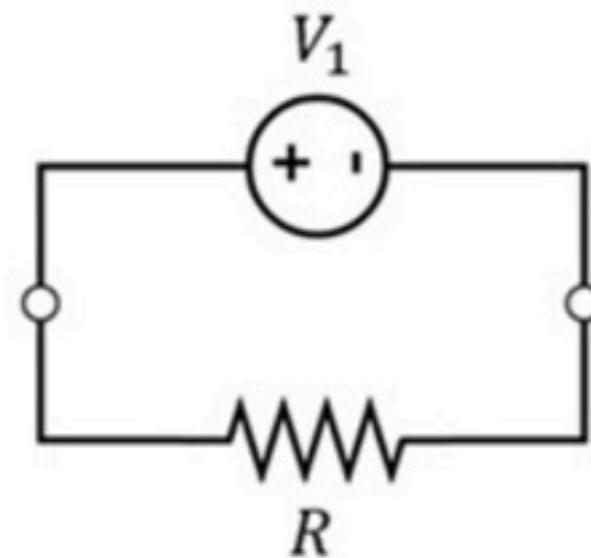

Given Variables:

$V_1 : 10 \text{ V}$

$R : 5 \text{ ohm}$

$B_1 : 135 \text{ degrees}$

Calculate the following:

$P (\text{W}) :$

20



$A_1 (\text{V}) :$

10



Hint: What is the definition of  $V_{\text{rms}}$ ?

You are told that the sources in the two circuits below supply the same average power.


V<sub>1</sub> : 6 V

(a) Find the average power  $P$  supplied.

R : 2 ohm

(b) Find  $A_1$ .

B<sub>1</sub> : 60 degrees

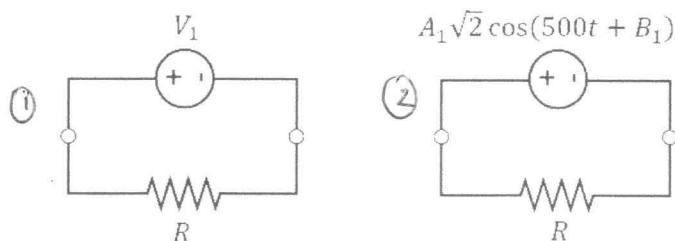

(a) CIRCUIT (1) :  $P = \frac{V_1^2}{R} = \frac{36}{2} \Rightarrow P = 18 \text{ W}$

(b) FOR THE SAME AVERAGE POWER

$$V_{RMS} = V_1 = 6 \text{ V}$$

$$V_{RMS} = \frac{V_m}{\sqrt{2}} = \frac{A_1 \sqrt{2}}{\sqrt{2}}$$

$$\left. \right) \Rightarrow A_1 = 6 \text{ V}$$

# AC power 005

0 of 5 attempts made


$$v_s(t) = A_1 \cos(500t + B_1)$$

Find the complex power  $S_1 = a_1 + b_1j$  received by the source  $v_s$ .

Find the complex power  $S_2 = a_2 + b_2j$  received by the resistor  $R_1$ .

Find the complex power  $S_3 = a_3 + b_3j$  received by the resistor  $R_2$ .

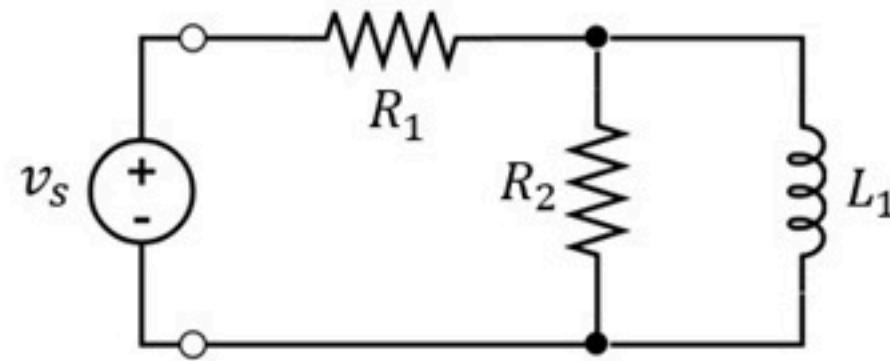Find the complex power  $S_4 = a_4 + b_4j$  received by the inductor  $L_1$ .



Given Variables:

$$A_1 : 6 \text{ V}$$

$$B_1 : 45 \text{ degrees}$$

$$R_1 : 4 \text{ ohm}$$

$$R_2 : 4 \text{ ohm}$$

$$L_1 : 8 \text{ mH}$$

Calculate the following:

a1 (W) :

-2.7



b1 (VAR) :

-0.9



a2 (W) :

1.8



b2 (VAR) :

0



a3 (W) :

0.9



b3 (VAR) :

0



a4 (W) :

0



b4 (VAR) :

0.9



$$v_s(t) = A_1 \cos(500t + B_1)$$

$$A1 : 3 \text{ V}$$

Find the complex power  $S_1 = a_1 + b_1j$  received by the source  $v_s$ .

Find the complex power  $S_2 = a_2 + b_2j$  received by the resistor  $R_1$ .


$$B1 : 30 \text{ degrees}$$

Find the complex power  $S_3 = a_3 + b_3j$  received by the resistor  $R_2$ .

$$R1 : 1 \text{ ohm}$$

Find the complex power  $S_4 = a_4 + b_4j$  received by the inductor  $L_1$ .

$$R2 : 2 \text{ ohm}$$

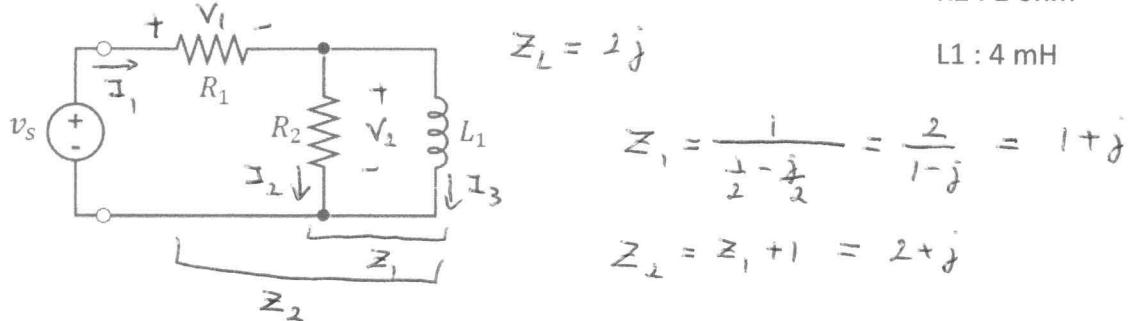

$$V_s = 3 e^{j30^\circ}$$

$$I_1 = \frac{V_s}{Z_2}$$

$$V_1 = i \cdot I_1$$

$$V_2 = Z_1 I_1$$

$$I_2 = \frac{V_1}{2}$$

$$I_3 = \frac{V_1}{2j}$$

$$\textcircled{a} \quad S_1 = \frac{1}{2} V_s (-I_1^*) = -\frac{1}{2} \frac{V_s \cdot V_s^*}{Z_2^*} = -\frac{|V_s|^2}{2} \frac{Z_2}{|Z_2|^2} = -\frac{9}{2} \frac{(2+j)}{5}$$

$$a_1 = -1.8 \text{ W}$$

$$b_1 = -0.9 \text{ VAR}$$

$$\textcircled{b} \quad S_2 = \frac{1}{2} V_1 I_1^* = \frac{I_1 I_1^*}{2} = \frac{|I_1|^2}{2} = \frac{|V_s|^2}{2 |Z_2|^2} = \frac{9}{2 \cdot 5}$$

$$a_2 = 0.9 \text{ W}$$

$$b_2 = 0 \text{ VAR}$$

$$\textcircled{c} \quad S_3 = \frac{1}{2} V_2 I_2^* = \frac{1}{2} V_2 \frac{V_1}{2}^* = \frac{|V_2|^2}{4} = \frac{|Z_1|^2 |I_1|^2}{4} = \frac{|Z_1|^2 |V_s|^2}{4 |Z_2|^2} = \frac{2 \cdot 9}{4 \cdot 5}$$

$$a_3 = 0.9 \text{ W}$$

$$b_3 = 0 \text{ VAR}$$

$$\textcircled{d} \quad S_4 = \frac{1}{2} V_2 I_3^* = \frac{1}{2} V_2 \frac{V_1}{2}^* = j \frac{|V_2|^2}{4} = j \frac{|Z_1|^2}{4} \frac{|V_s|^2}{|Z_2|^2} = j \cdot \frac{2 \cdot 9}{4 \cdot 5}$$

$$a_4 = 0 \text{ W}$$

$$b_4 = 0.9 \text{ VAR}$$

$$\text{CHECK: } S_1 + S_2 + S_3 + S_4 = -1.8 + 0.9 + 0.9 + 0 = 0$$

$$-0.9j + 0j + 0j + 0.9j$$

(  $\sum \text{REC.} = \sum \text{SUPPL.}$  )


# AC power 006

No more attempts left.

For the system below, the source is represented in phasor-notation as:

$$\mathbf{Z}_1 = A_1 + jB_1 \quad \mathbf{V}_S = A_2 \cdot e^{jB_2}$$

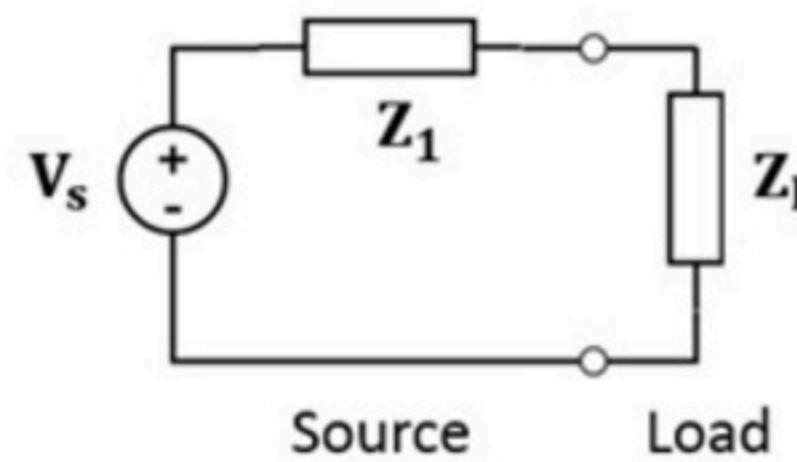- (a) Find the load impedance  $\mathbf{Z}_L = A_3 + jB_3$  that results in the maximum power being received by this load.  
(b) Find the maximum average power  $P$  received by the load.



Given Variables:

A1 : 5 ohm

B1 : 4 ohm

A2 : 2 V

B2 : 75 degrees

Calculate the following:

A3 (ohm) :

5



B3 (ohm) :

-4



P (W) :

0.1



Hint: Keep your calculations algebraic as long as you can.

For the system below, the source is represented in phasor-notation as:

$$Z_1 = A_1 + jB_1 \quad V_S = A_2 \cdot e^{jB_2}$$

A1 : 1 ohm


B1 : -8 ohm

- (a) Find the load impedance  $Z_L = A_3 + jB_3$  that results in the maximum power being received by this load.

A2 : 4 V

B2 : 65 degrees

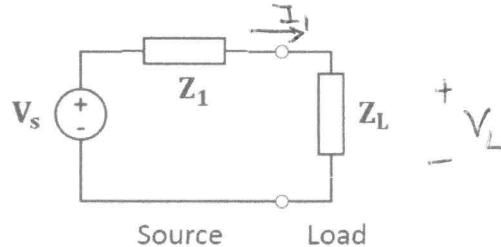- (b) Find the maximum average power  $P$  received by the load.



$$\textcircled{a} \quad Z_L = Z_1^* \Rightarrow Z_L = 1 + j8$$

$A_3 = 1 \Omega$
$B_3 = 8 \Omega$

$$\textcircled{b} \quad I_1 = \frac{V_s}{Z_1 + Z_L} \quad Z_1 + Z_L = 2$$

$$V_s = 4 e^{j65^\circ} \quad V_L = Z_L \cdot I_1$$

$$\begin{aligned} S_L &= \frac{1}{2} V_L \cdot I_1^* = \frac{1}{2} Z_L \cdot I_1 \cdot I_1^* = \frac{Z_L}{2} |I_1|^2 = \frac{Z_L}{2} \frac{|V_s|^2}{|Z_1 + Z_L|^2} \\ &= \frac{(1+j8)}{2} \cdot \frac{4^2}{2^2} = (1+j8) \cdot 2 = \underbrace{2}_{P} + \underbrace{16j}_{Q} \end{aligned}$$

$P = 2 \text{ W}$
-------------------

# AC power 008


Problem has been graded.

Both  $v_S$  and  $i_S$  are AC sources with  $\omega = 400 \text{ rad/s}$ . Someone did two measurements on the circuit and found:

$$v_1(t) = A_1 \cos(400t + B_1) \quad (\text{this is } v_1, \text{ not } v_S !)$$

$$i_S(t) = 2 \cos\left(400t + \frac{\pi}{6}\right)$$

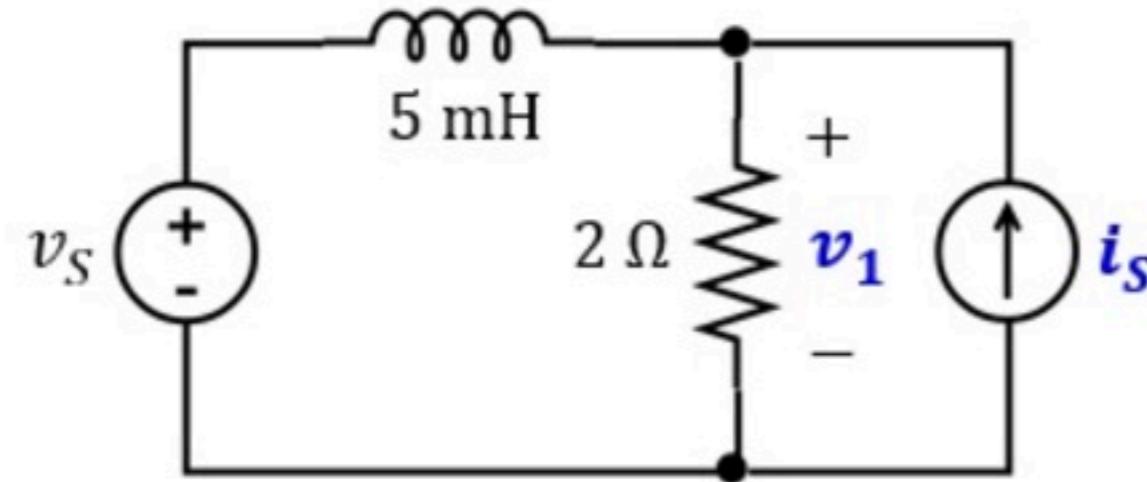- (a) Find the average power  $P_1$  received by the resistor
- (b) Find the average power  $P_2$  supplied by current source  $i_S$
- (c) Find the average power  $P_3$  received by the inductor



Given Variables:

A1 : 8 V

B1 : 90 degrees

Calculate the following:

P1 (W) :

16



P2 (W) :

4




P3 (W) :

0



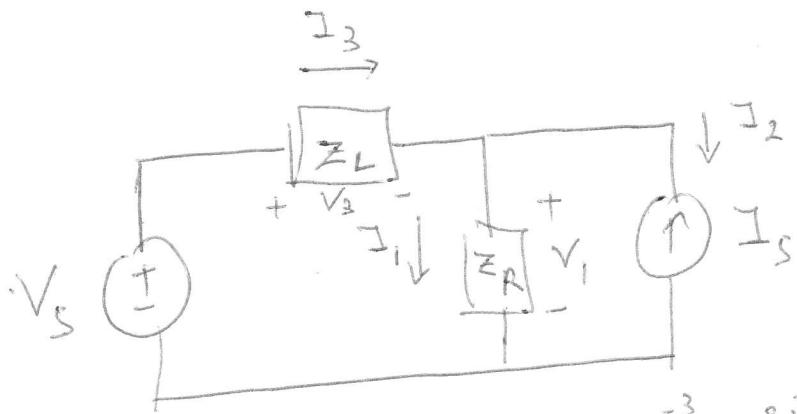Hint: Find S symbolically first. Find phasors and plug in. For c, what do you know about the element?



$A_1: 10V$

$\beta_1: -90^\circ$

$$Z_L = j\omega L = j \cdot 400 \cdot 5 \cdot 10^{-3} = 2j$$

$$Z_R = 2$$

$$\textcircled{a} \quad S_1 = \frac{1}{2} V_1 \cdot I_1^* \quad I_1 = \frac{V_1}{Z_R}$$

$$= \frac{1}{2} V_1 \left( \frac{V_1}{Z_R} \right)^* = \frac{1}{2} \frac{V_1 V_1^*}{Z_R} = \frac{|V_1|^2}{2} \cdot \frac{1}{Z_R} = \frac{A_1^2}{2} \cdot \frac{1}{Z_R} = \frac{100}{2 \cdot 2} = 25$$

$$P_1 = \operatorname{Re}[S_1]$$

$$\boxed{P_1 = 25W} \text{ received}$$

$$\textcircled{b} \quad S_2 = \frac{1}{2} V_1 I_2^* \rightsquigarrow \text{PASSIVE SIGN CONVENTION} \\ (\text{POWER RECEIVED})$$

$$= \frac{1}{2} V_1 (-I_S)^* \quad \begin{cases} V_1 = A_1 e^{j\beta_1} = 10 e^{-j\frac{\pi}{2}} \\ I_S = 2 e^{j\frac{\pi}{6}} \end{cases}$$

$$= -\frac{1}{2} V_1 I_S^* \quad -j\frac{\pi}{6} \quad -j\frac{\pi}{3}$$

$$= -\frac{1}{2} \cdot 10 e^{-j\frac{\pi}{2}} \cdot 2 e^{j\frac{\pi}{6}} = -10 e^{-j\frac{4\pi}{6}} = -10 e^{-j\frac{2\pi}{3}}$$

$$P_2 = \operatorname{Re}[S_2] = -10 \cos(-\frac{2\pi}{3}) = -10 \left(\frac{-1}{2}\right) = +5 \rightsquigarrow \text{received}$$

$$\boxed{P_2 = -5W} \text{ supplied}$$

$$\textcircled{c} \quad \boxed{P_3 = 0W} \text{ inductor always has } P=0$$

$$\text{we can check: } S_3 = \frac{1}{2} V_3 I_3^* \quad V_3 = Z_L \cdot I_3$$

$$= \frac{1}{2} Z_L I_3 \cdot I_3^* = \frac{Z_L}{2} |I_3|^2 = \frac{|I_3|^2 \cdot (2j)}{2}$$


no real part  $\Rightarrow P = \operatorname{Re}[S] = 0$

# PP AC power 001

Unlimited Attempts.

In the diagram are the phasors of the voltage across an element and the current through that element (according to the passive sign convention).

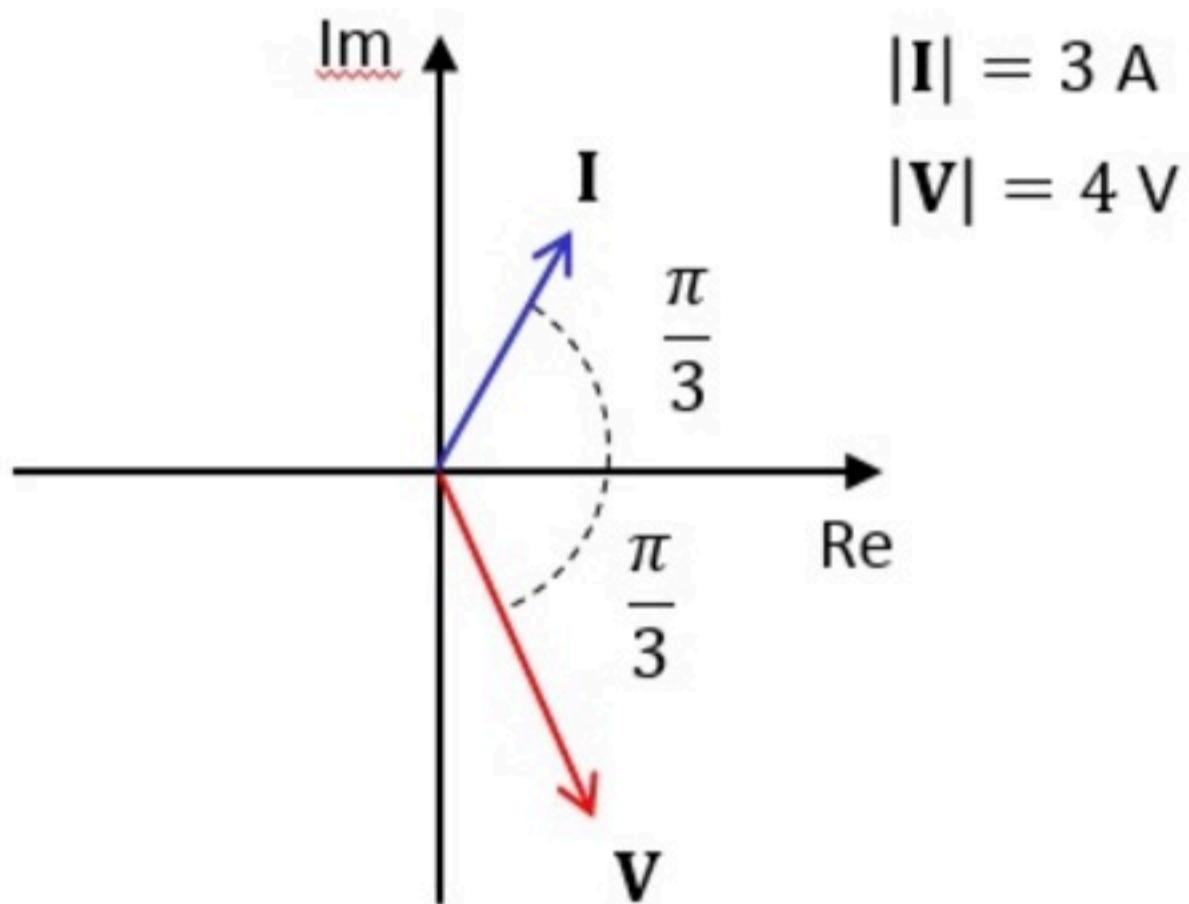What is the average power  $P$  received by the element?



Given Variables:

...

Calculate the following:

$P (\text{W}) :$

-3



Hint: Write average power as a function of the angle between the voltage and current.

$$I = 3 e^{j\frac{\pi}{3}}$$

$$V = 4 e^{-j\frac{\pi}{3}}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \cdot 4 \cdot 3 \cdot \cos\left(-\frac{\pi}{3} - \frac{\pi}{3}\right)$$

$$= \frac{1}{2} \cdot 4 \cdot 3 \cdot \cos\left(-\frac{2\pi}{3}\right)$$

$$= \frac{1}{2} \cdot 4 \cdot 3 \left(-\frac{1}{2}\right)$$

$$= -3$$

$$\boxed{P = -3 \text{ W}}$$


↳ So THIS ELEMENT  
SUPPLIES POWER

# PP AC power 002

Unlimited Attempts.

In the diagram are the phasors of the voltage across an element and the current through that element (according to the passive sign convention).

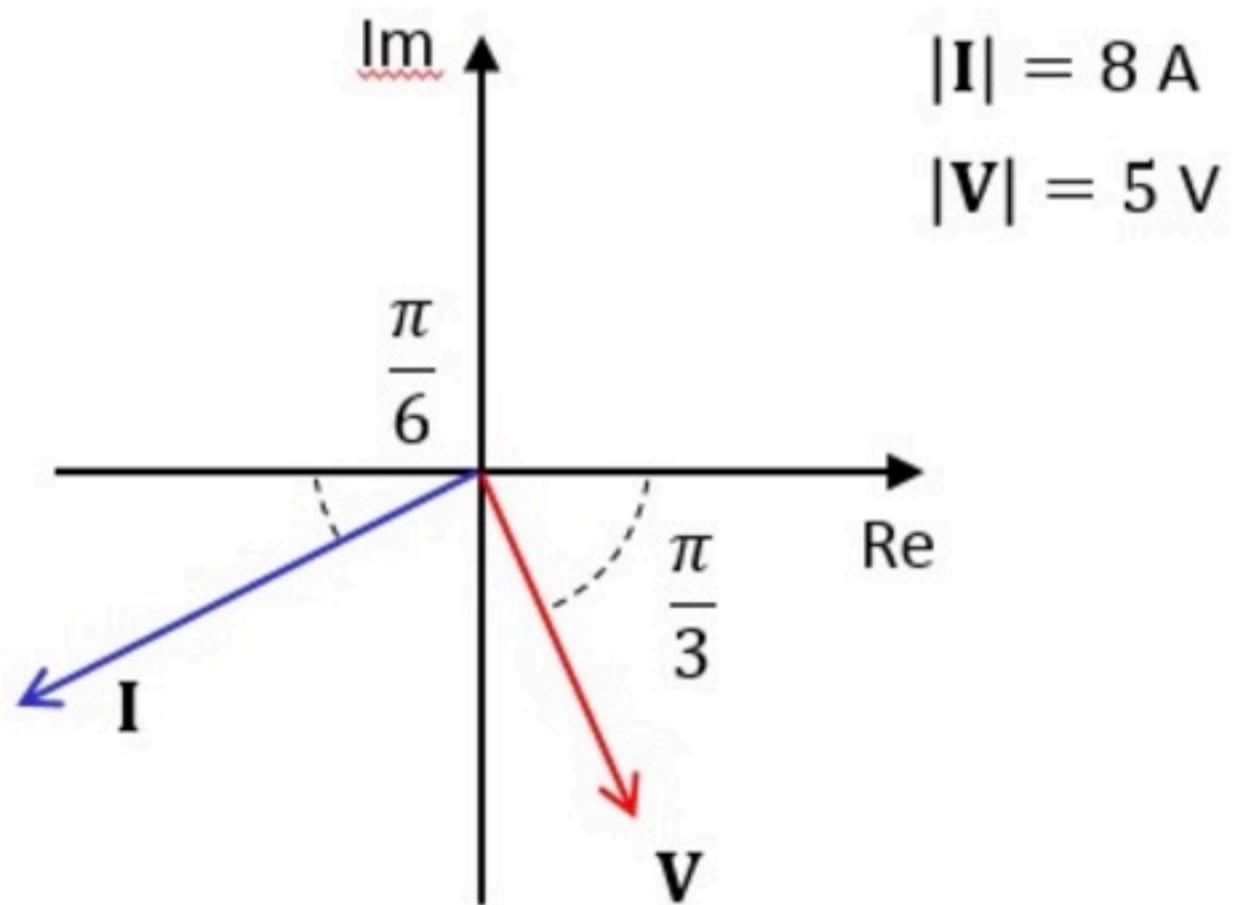What is the average power  $P$  received by the element?



Given Variables:

...

Calculate the following:

$P (\text{W}) :$

0



Hint: Write average power as a function of the angle between the voltage and current.

$$I = 8 e^{-j \frac{5\pi}{6}}$$

$$V = 5 e^{-j \frac{\pi}{3}}$$

$$P = \frac{1}{2} \cdot I_m \cdot V_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \cdot 8 \cdot 5 \cdot \cos\left(-\frac{\pi}{3} + \frac{5\pi}{6}\right)$$

$$= \frac{1}{2} \cdot 8 \cdot 5 \cdot \cos\left(\frac{\pi}{2}\right)$$

$$= \frac{1}{2} \cdot 8 \cdot 5 \cdot 0$$

$P = 0 \text{ W}$

$\Rightarrow$  AS EXPECTED SINCE

$V$  &  $I$  ARE ORTHOGONAL

IN THIS CASE, "I LAGS V"


BY  $90^\circ \Rightarrow$  THE ELEMENT  
IS AN INDUCTOR

$$I = \frac{V}{j\omega L} = \frac{V}{\omega L} e^{-j \frac{\pi}{2}}$$

# PP AC power 003

Unlimited Attempts.

Find  $I_{rms}$  for this waveform.

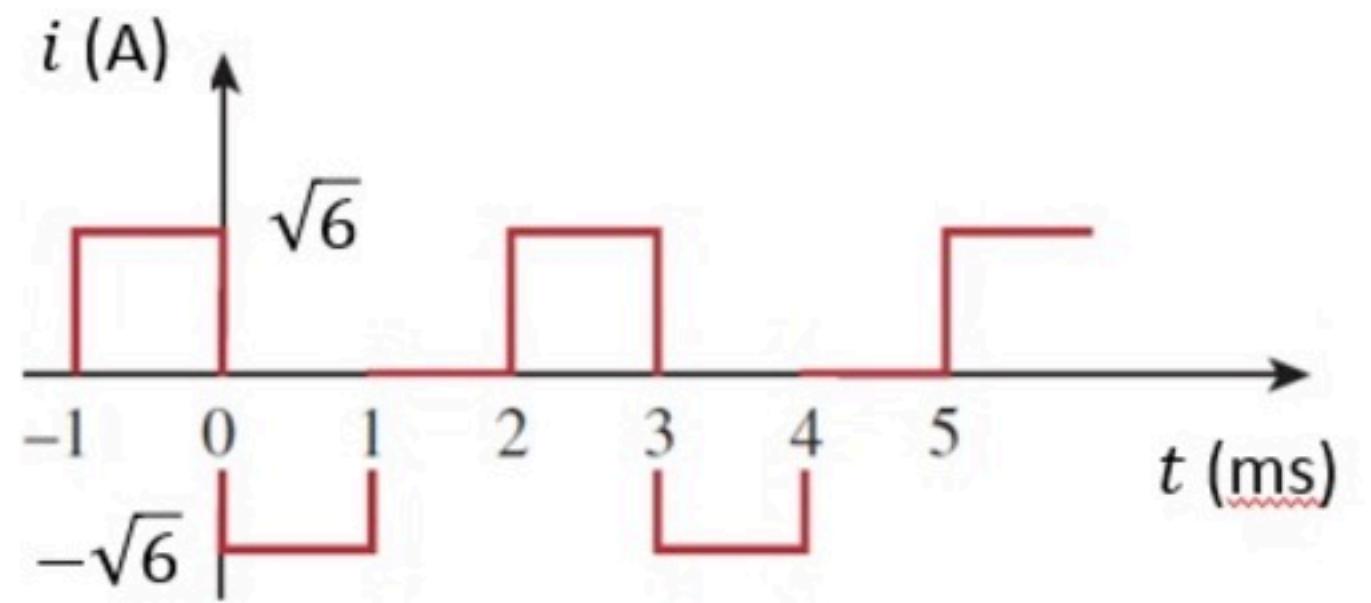

Given Variables:

...

Calculate the following:

$I_{rms}$  (A) :

2



Hint: Square the waveform first.


$$\begin{aligned}
 A &= \frac{1}{T} \int_0^T i^2 dt \\
 &= \frac{1}{3 \cdot 10^{-3}} \cdot \left[ (-\sqrt{6})^2 \cdot 10^{-3} + 0 + (\sqrt{6})^2 \cdot 10^{-3} \right] \\
 &= \frac{1}{3} [6 + 6] \\
 &= 4
 \end{aligned}$$

$$I_{\text{rms}} = \sqrt{A} \quad \Rightarrow \quad I_{\text{rms}} = 2$$

# PP AC power 004

Unlimited Attempts.

Find  $V_{rms}$  for this waveform.

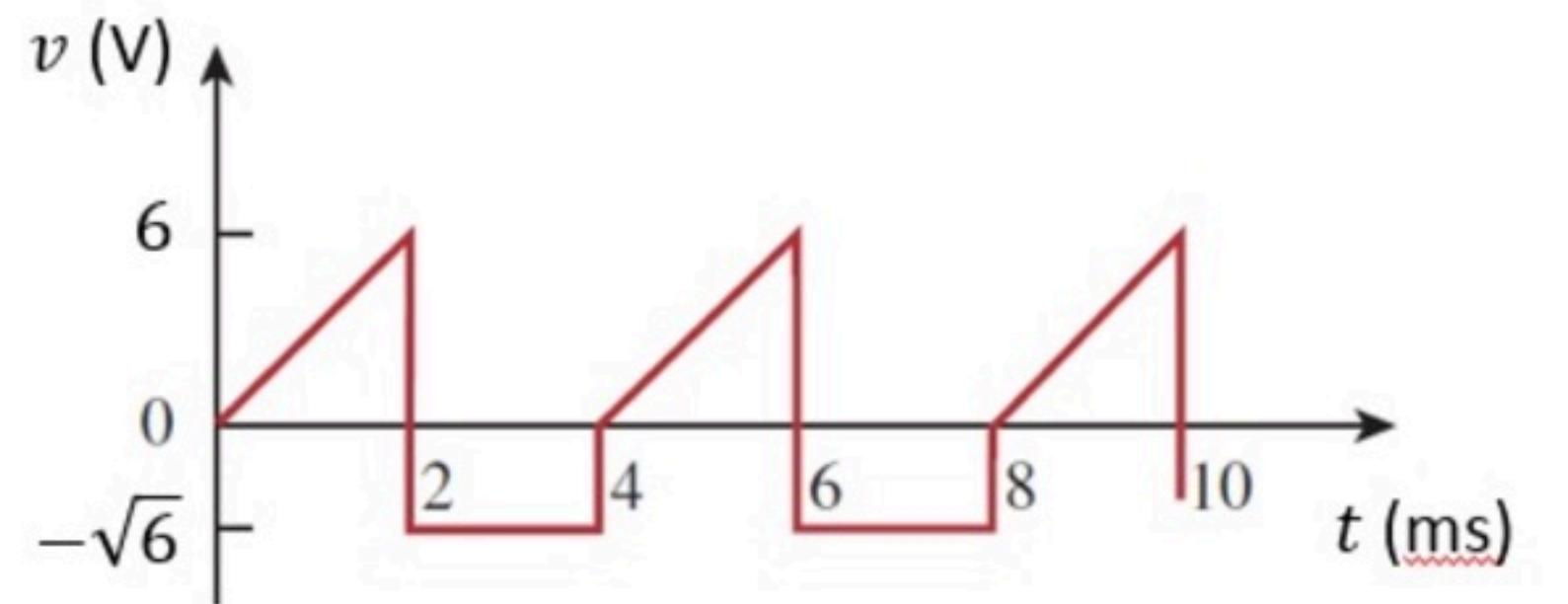

Given Variables:

. . .

Calculate the following:

$V_{rms}$  (V) :

3



Hint: Write the equation of the waveform in parts.

OPTION 1     $t$  EXPRESSED IN SECONDS

$$f(t) = 3 \cdot 10^3 \cdot t, \quad 0 \leq t < 2 \cdot 10^{-3}$$

$$= -\sqrt{6}, \quad 2 \cdot 10^{-3} \leq t < 4 \cdot 10^{-3}$$

$$\frac{1}{T} \int_0^T f^2(t) dt = \frac{1}{4 \cdot 10^{-3}} \left[ \int_0^{2 \cdot 10^{-3}} (3 \cdot 10^3 t)^2 dt + \int_{2 \cdot 10^{-3}}^{4 \cdot 10^{-3}} (-\sqrt{6})^2 dt \right]$$

$$= \frac{1}{4 \cdot 10^{-3}} \left[ 9 \cdot 10^6 \cdot \frac{t^3}{3} \Big|_0^{2 \cdot 10^{-3}} + 6 \cdot 2 \cdot 10^{-3} \right]$$

$$= \frac{1}{4 \cdot 10^{-3}} \left[ \frac{9 \cdot 8}{3} \cdot 10^{-3} + 12 \cdot 10^{-3} \right]$$

$$= \frac{24 + 12}{4} = \frac{36}{4} = 9$$

$$\sqrt{\frac{1}{T} \int_0^T f^2(t) dt} = \boxed{V_{RMS} = 3V}$$

OPTION 2     $t$  EXPRESSED IN mS

$$f(t) = 3 \cdot t, \quad 0 \leq t < 2$$

$$= -\sqrt{6}, \quad 2 \leq t < 4$$

$$\frac{1}{T} \int_0^T f^2(t) dt = \frac{1}{4} \left[ \int_0^2 (3t)^2 dt + \int_2^4 (-\sqrt{6})^2 dt \right] = \frac{1}{4} \left[ 9 \cdot \frac{t^3}{3} \Big|_0^2 + 6 \cdot 2 \right]$$


$$= \frac{1}{4} \left[ \frac{2 \cdot 8}{3} + 12 \right] = \frac{36}{4} = 9$$

$$\boxed{V_{RMS} = 3V}$$
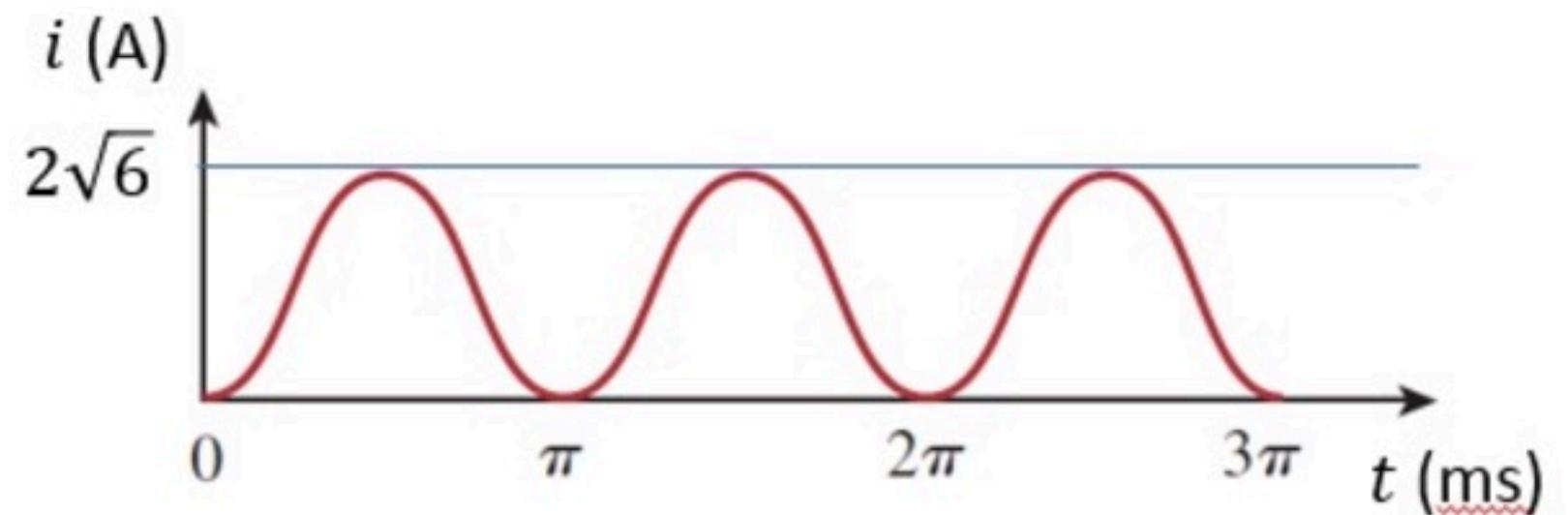
# PP AC power 005

Unlimited Attempts.

Find  $I_{rms}$  for this waveform (it is a sine wave that has an offset, i.e., it is shifted up).



Given Variables:

. . .

Calculate the following:

$I_{rms}$  (A) :

3



Hint: Utilize the fact that you know the  $I_{rms}$  for a sine wave.

$$i = \sqrt{6} - \sqrt{6} \cos(\omega t) = \sqrt{6}(1 - \cos(\omega t))$$

$$i^2 = 6(1 - \cos(\omega t))^2$$

$$\begin{aligned} A &= \frac{1}{T} \int_0^T i^2 dt = \frac{6}{T} \int_0^T [1 - 2\cos(\omega t) + \cos^2(\omega t)] dt \\ &= \frac{6}{T} \int_0^T dt - \frac{12}{T} \int_0^T \cos(\omega t) dt + \frac{6}{T} \int_0^T \cos^2(\omega t) dt \\ &= \frac{6}{T} \cdot T - \frac{12}{T} \cdot 0 + 6 \cdot \frac{1}{2} \end{aligned}$$

$\hookrightarrow$  WE KNOW FOR A COS

$$I_{RMS} = \frac{I_m}{\sqrt{2}} \Rightarrow I_{RMS}^2 = \frac{I_m^2}{2}$$

$$I_{RMS}^2 = \frac{I_m^2}{T} \int_0^T \cos^2(\omega t) dt$$

$$\Rightarrow \frac{1}{T} \int_0^T \cos^2(\omega t) dt = \frac{1}{2}$$

$$A = 6 + \frac{6}{2} = 9$$

$$I_{RMS} = \sqrt{A} \Rightarrow \boxed{I_{RMS} = 3A}$$

# PP AC power 006

Unlimited Attempts.

$$v_S(t) = 10\sqrt{2} \cdot \cos\left(10^6 t + \frac{\pi}{6}\right) V$$


Find the average power  $P_1$  supplied by the source  $v_S$ .

Find the average power  $P_2$  received by the  $5 \Omega$  resistor.

Find the average power  $P_3$  received by the  $4 \Omega$  resistor.

Find the average power  $P_4$  received by the capacitor.

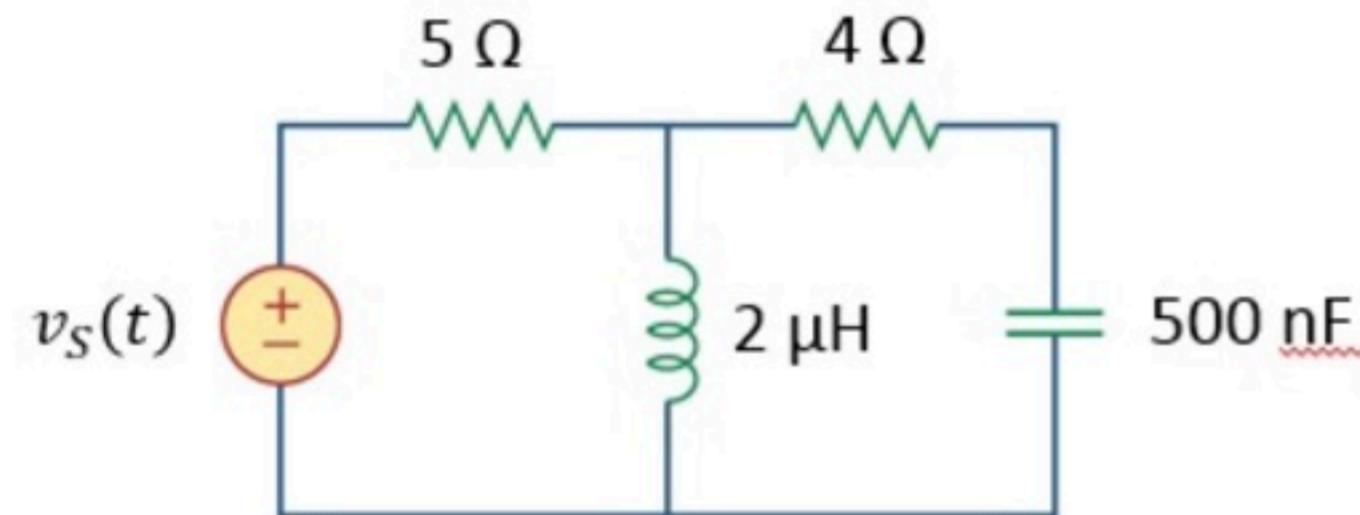Find the average power  $P_5$  received by the inductor.



Given Variables:

...

Calculate the following:

P1 (W) :

15



P2 (W) :

12.5



P3 (W) :

2.5



P4 (W) :

0




P5 (W) :

0



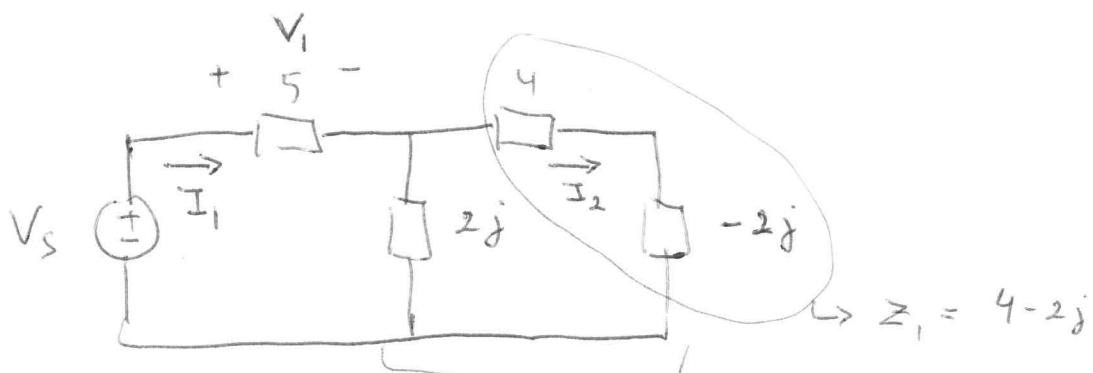Hint: Find S first for each element. Keep Vs algebraic. Can you predict P for the cap and inductor? Check.



$$\hookrightarrow Z_2 = \frac{1}{\frac{1}{2j} + \frac{1}{4-2j}} = \frac{2j(4-2j)}{4-2j+2j} = j(2-j) = 1+2j$$

$$I_1 = \frac{V_s}{5 + Z_2} = \frac{V_s}{6+2j}$$

$$\textcircled{1} \quad S_1 = \frac{1}{2} V_s \cdot I_1^* \quad (\text{SUPPLIED!}) \quad V_s \perp \uparrow I_1$$

$$= \frac{1}{2} V_s \frac{|V_s|^2}{6+2j} = \frac{|V_s|^2}{2} \cdot \frac{6+2j}{40} = \frac{100 \cdot 2}{2} \left( \frac{6+2j}{40} \right) \quad P_1 = \text{Re}[S_1]$$

$$\boxed{P_1 = 15W}$$

$$\textcircled{2} \quad S_2 = \frac{1}{2} V_1 I_1^* = \frac{1}{2} \cdot Z_{5\Omega} \cdot I_1 \cdot I_1^* = \frac{1}{2} Z_{5\Omega} |I_1|^2$$

$$S_2 = \frac{1}{2} \cdot 5 \cdot \frac{|V_s|^2}{|6+2j|^2} = \frac{5}{2} \cdot \frac{100 \cdot 2}{40} = 12.5$$

$$\boxed{P_2 = 12.5W}$$

$$\textcircled{3} \quad I_2 = I_1 \cdot \frac{2j}{2j + Z_1} = I_1 \cdot \frac{2j}{2j + 4 - 2j} = I_1 \cdot \frac{2j}{4} = I_1 \cdot \frac{j}{2}$$

$$S_3 = \frac{1}{2} Z_{4\Omega} |I_2|^2 = \frac{1}{2} \cdot 4 \cdot |I_1|^2 \cdot \frac{|j|^2}{4} = \frac{|I_1|^2}{2} = \frac{1}{2} \cdot \frac{|V_s|^2}{|6+2j|^2}$$

$$= \frac{1}{2} \cdot \frac{100 \cdot 2}{40} = 2.5$$

$$\boxed{P_3 = 2.5W}$$

WE KNOW A CAPACITOR AND INDUCTOR ONLY HAVE REACTIVE POWER  $\Rightarrow \boxed{P_4 = P_5 = 0}$

CHECK:  $P_{\text{REC.}} = P_{\text{SUPPLIED}} \Rightarrow 12.5 + 2.5 = 15 \quad \underline{\text{OK}}$

# PP AC power 007

Unlimited Attempts.

$$i_S(t) = 2 \cdot \cos\left(10^3 t + \frac{\pi}{4}\right) \text{ A}$$

Find the complex power  $S_1 = a_1 + b_1j$  supplied by the source  $i_S$ .


Find the complex power  $S_2 = a_2 + b_2j$  received by the  $10 \Omega$  resistor.

Find the complex power  $S_3 = a_3 + b_3j$  received by the  $2 \Omega$  resistor.

Find the complex power  $S_4 = a_4 + b_4j$  received by the CCVS.

Find the complex power  $S_5 = a_5 + b_5j$  received by the inductor.

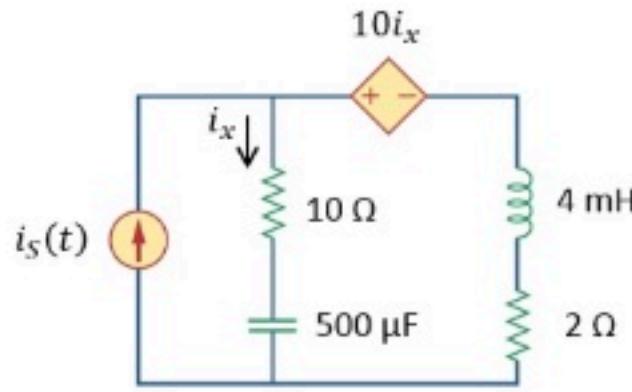Find the complex power  $S_6 = a_6 + b_6j$  received by the capacitor.



Given Variables:

...

Calculate the following:

a1 (W) :

32



b1 (VAR) :

4



a2 (W) :

50



b2 (VAR) :

0



a3 (W) :

2



b3 (VAR) :

0



a4 (W) :

-20



b4 (VAR) :

10



a5 (W) :

0



b5 (VAR) :

4



a6 (W) :


0



b6 (VAR) :

-10



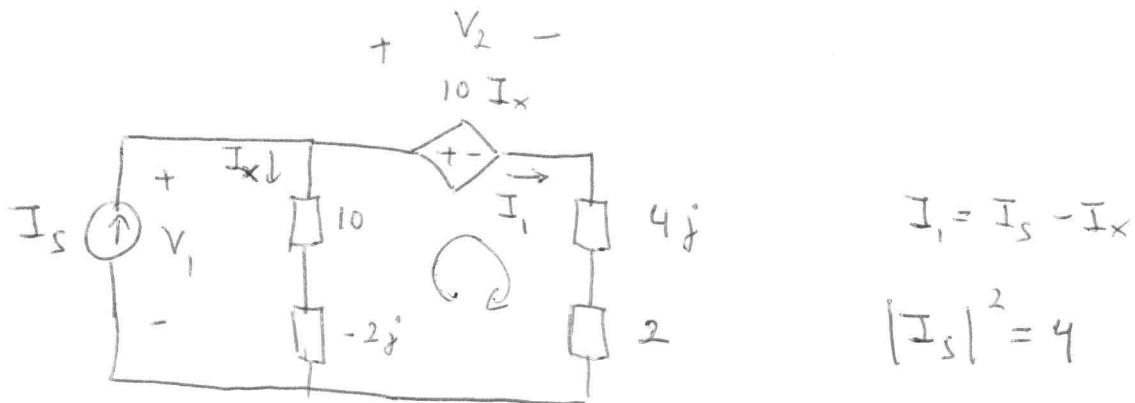

$$I_1 = I_s - I_x$$

$$|I_s|^2 = 4$$

KVL:  $I_x (10 - 2j) = 10 I_x + (2 + 4j) I_1$

$$= 10 I_x + (2 + 4j)(I_s - I_x)$$

$$I_x (10 - 2j - 10 + 2 + 4j) = (2 + 4j) I_s$$

$$I_x (2 + 2j) = I_s (2 + 4j) \Rightarrow I_x = I_s \frac{(1 + 2j)}{(1 + j)} = I_s \frac{(3 + j)}{2}$$

①  $V_1 = I_x (10 - 2j) = I_s \frac{(3 + j)(10 - 2j)}{2} = I_s (16 + 2j)$

NOTE DIRECTION OPPOSITE PASSIVE SIGN CONVENTION  $S_1 = \frac{1}{2} V_1 \cdot I_s^* = \frac{1}{2} I_s (16 + 2j) I_s^* = |I_s|^2 (8 + j) \Rightarrow S_1 = 32 + 4j$

②  $S_2 = \frac{1}{2} Z_{10,2} |I_x|^2 = \frac{1}{2} \cdot 10 \cdot |I_s|^2 \cdot \frac{10}{4} \Rightarrow S_2 = 50 + 0j$

③  $I_1 = I_s - I_x = I_s \left(1 - \frac{(3+j)}{2}\right) = I_s \frac{(-1-j)}{2}$  EXPECTED ↑

$$S_3 = \frac{1}{2} Z_{2,2} |I_1|^2 = \frac{1}{2} \cdot 2 |I_s|^2 \cdot \frac{|-1-j|^2}{4} = \frac{|I_s|^2}{4} \cdot 2 \Rightarrow S_3 = 2 + 0j$$

④  $S_4 = \frac{1}{2} V_2 I_1^* = \frac{1}{2} \cdot 10 I_x \cdot I_1^* = 5 \cdot I_s \frac{(3+j)}{2} \cdot I_s^* \frac{(-1+j)}{2} = |I_s|^2 \cdot \frac{5}{4} (-4 + 2j)$

$$\Rightarrow S_4 = -20 + 10j$$
 RECEIVED SINCE WE USED PASSIVE SIGN CONVENTION

⑤  $S_5 = \frac{1}{2} Z_L |I_1|^2 = \frac{1}{2} \cdot 4j |I_s|^2 \cdot \frac{|-1-j|^2}{4} = 2j \cdot 4 \cdot \frac{1}{4} \Rightarrow S_5 = 0 + 4j$  AS EXPECTED ↑

⑥  $S_6 = \frac{1}{2} Z_C |I_x|^2 = \frac{1}{2} (-2j) |I_s|^2 \frac{|3+j|^2}{4} = -j \cdot 4 \cdot \frac{10}{4} \Rightarrow S_6 = 0 - 10j$

CHECK:  $\sum P_{REC} = \sum P_{SUPPL} \Rightarrow 50 + 2 - 20 = 32 \quad OK$


$$\sum Q_{REC} = \sum Q_{SUPPL} \Rightarrow 10 + 4 - 10 = 4 \quad OK$$

# PP AC power 008

Unlimited Attempts.

Find the value of  $Z_L = a + jb$  that will receive the maximum amount of power

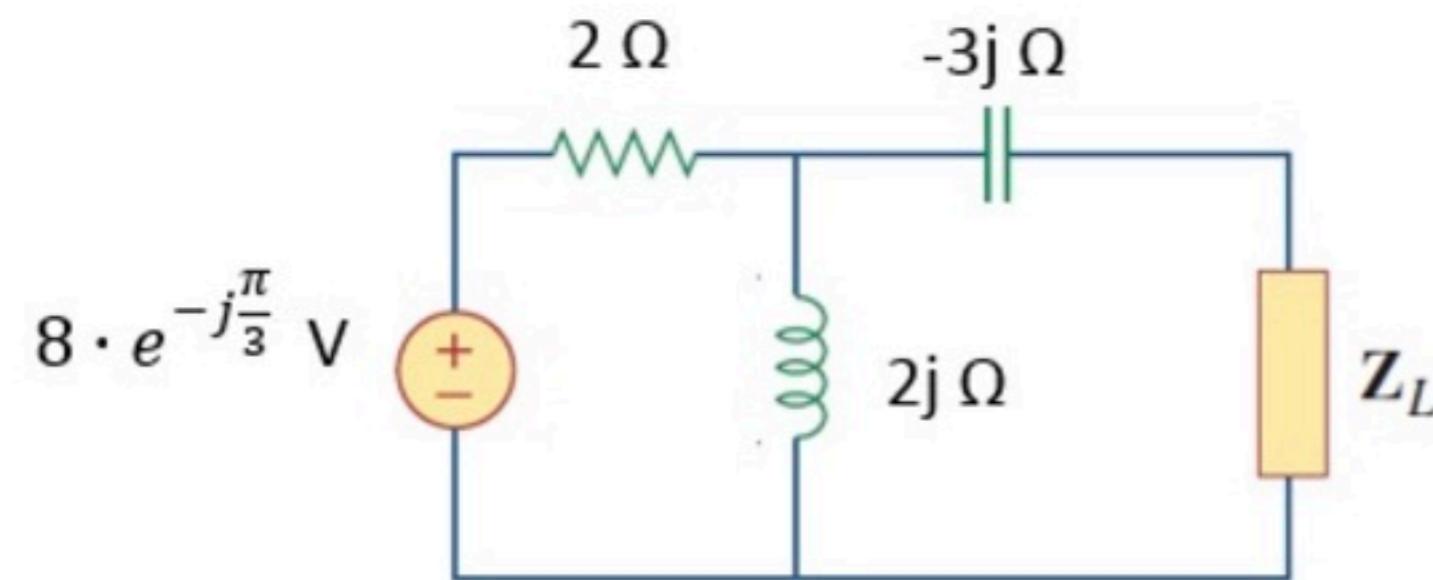Find the resulting complex power  $S = c + jd$  received by the load.



Given Variables:

...

Calculate the following:

a (ohm) :

1



b (ohm) :

2



c (W) :

4




d (VAR) :

8



Hint: Set the independent source to zero. Find Zth.

①

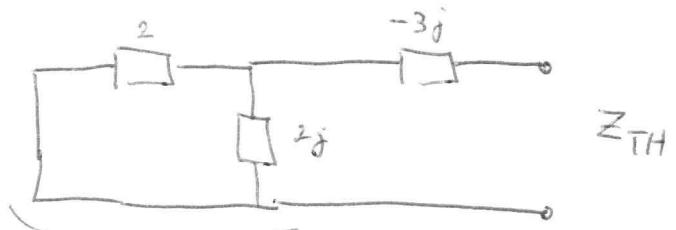


$$\hookrightarrow z_1 = \frac{1}{\frac{1}{2} + \frac{1}{2j}} = \frac{4j}{2+2j} = \frac{2j}{1+j} = \frac{2j(1-j)}{2} = 1+2j$$

$$\Rightarrow Z_{TH} = z_1 - 3j = 1-2j$$

MAX POWER: 
$$Z_L = Z_{TH}^* = 1+2j$$

②

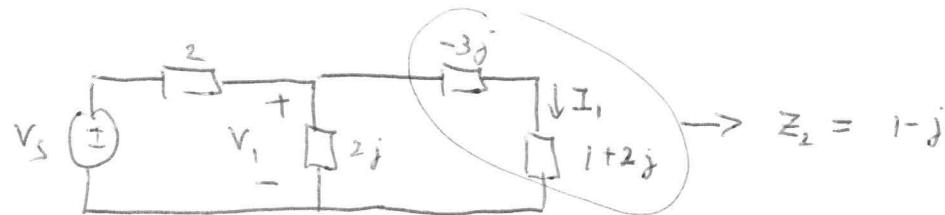OPTION 1:

$$\hookrightarrow z_2 = 1-j$$

$$\hookrightarrow z_3 = \frac{1}{\frac{1}{2j} + \frac{1}{1-j}} = \frac{2j(1-j)}{1-j+2j} = \frac{2j+2}{1+j} = 2$$


$$V_1 = V_s \cdot \frac{z_3}{z_3 + z_2} = \frac{V_s}{2}$$

$$I_1 = \frac{V_1}{z_2} \Rightarrow S_L = \frac{1}{2} z_2 \cdot |I_1|^2 = \frac{1}{2} (1+2j) \frac{|V_s|^2}{4} \cdot \frac{1}{|z_2|^2}$$

$$= \frac{1}{2} \cdot \frac{64}{4} \cdot \frac{1}{2} (1+2j)$$

$$S_L = 4 + 8j$$

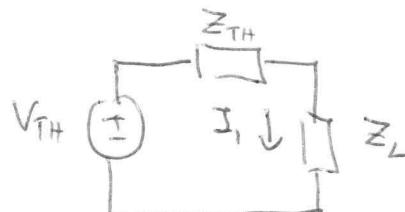OPTION 2: FIND  $V_{TH} \Rightarrow V_{OC} = V_s \cdot \frac{2j}{2+j} = V_s \cdot \frac{j}{1+j} = V_{TH}$



$$I_1 = \frac{V_{TH}}{z_{TH} + z_2} = \frac{V_{TH}}{(1-2j) + (1+2j)} = \frac{V_{TH}}{2}$$

AS EXPECTED


$$S_L = \frac{1}{2} z_2 |I_1|^2 = \frac{1}{2} (1+2j) \frac{|V_{TH}|^2}{4} = \frac{(1+2j)}{8} |V_s|^2 \frac{|j|^2}{|1+j|^2}$$

$$S_L = (1+2j) \cdot \frac{64}{8} \cdot \frac{1}{2} \Rightarrow S_L = 4 + 8j$$
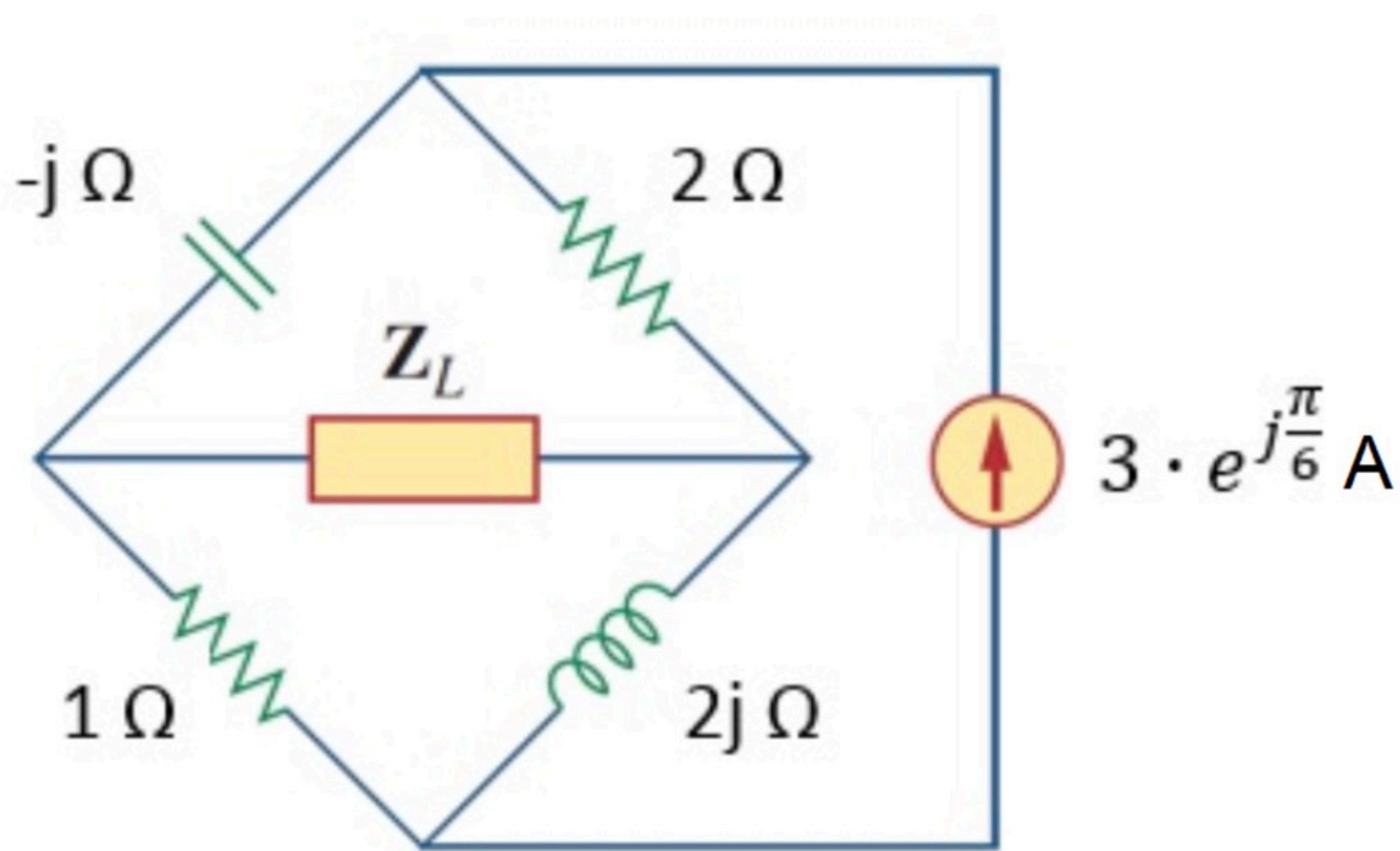
# PP AC power 009

Unlimited Attempts.

Find the value of  $Z_L = a + jb$  that will receive the maximum amount of power



Given Variables:

...

Calculate the following:

a (ohm) :


1.5



b (ohm) :

-0.5



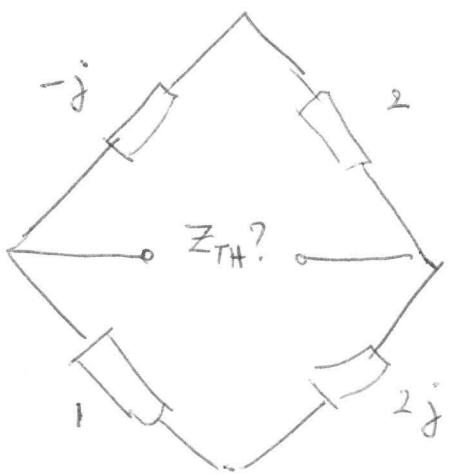

$$\begin{aligned}
 Z_{TH} &= (2-j) \parallel (1+2j) = \frac{1}{\frac{1}{2-j} + \frac{1}{1+2j}} \\
 &= \frac{(2-j)(1+2j)}{2-j + 1+2j} = \frac{2-j+4j+2}{3+j} \cdot \frac{3-j}{3-j} \\
 &= \frac{1}{10} \cdot (4+3j)(3-j) \\
 &= \frac{1}{10} (12+9j-4j+3) \\
 &= 1.5 + 0.5j
 \end{aligned}$$


$Z_L^*$  =  $Z_{TH}$  FOR MAX POWER

$Z_L = 1.5 - 0.5j$
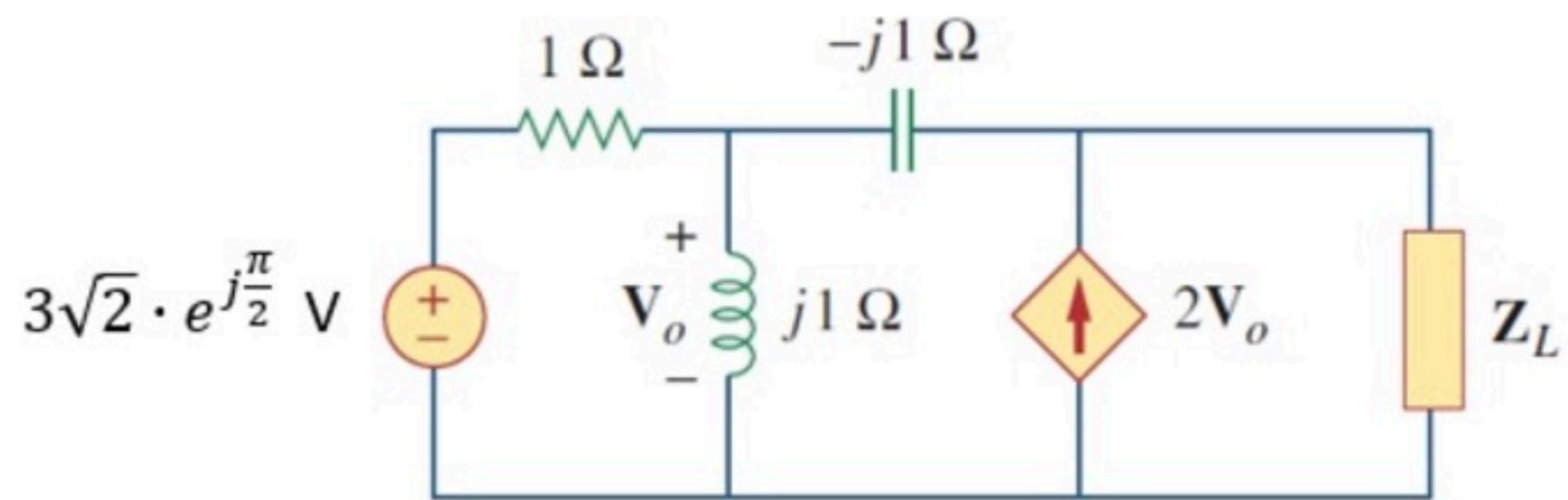
# PP AC power 010

Unlimited Attempts.

Find the value of  $\mathbf{Z}_L = a + jb$  that will receive the maximum amount of power



Given Variables:

...

Calculate the following:

a (ohm) :

0.5




b (ohm) :

-0.5



Hint: Use a test source to find the ZTh.

FIND  $Z_{TH}$ :

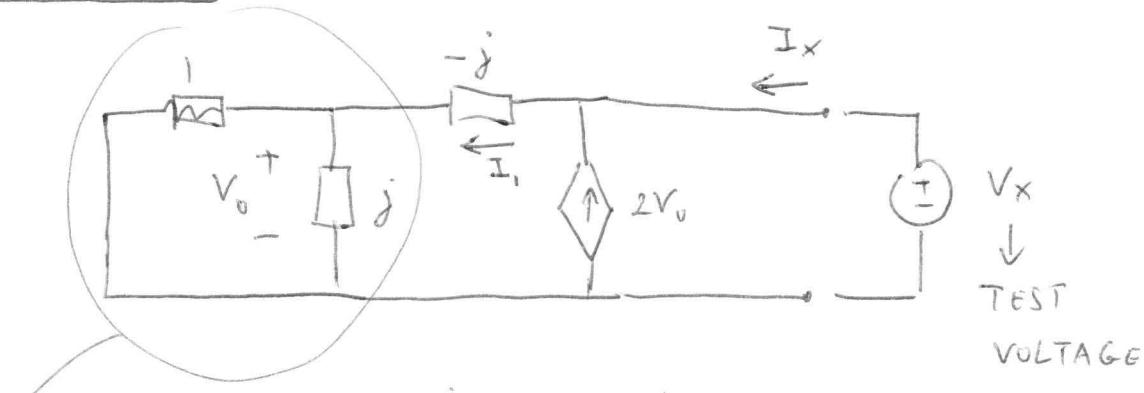

$$\rightarrow Z_1 = \frac{1}{\frac{1}{1+j} + \frac{1}{j}} = \frac{j}{1+j} = \frac{j(1-j)}{2} = \frac{1+j}{2}$$

$$I_1 = \frac{V_x}{Z_1 - j} = \frac{V_x}{\frac{1-j}{2}}$$

$$V_o = V_x \cdot \frac{Z_1}{Z_1 - j} = V_x \frac{(1+j)}{(1-j)}$$

$$I_x = I_1 - 2V_o = \frac{2V_x}{1-j} - 2V_x \frac{(1+j)}{1-j} = V_x \frac{(-2j)}{1-j}$$

~~$$Z_{TH} = \frac{V_x}{I_x} = \frac{V_x (1-j)}{V_x (-2j)} = \frac{1-j}{-2j} = \frac{(1-j) \cdot j}{2} = \frac{1+j}{2}$$~~

MAX POWER:  $Z_L = Z_{TH}^*$

$$Z_L = 0.5 - 0.5j$$