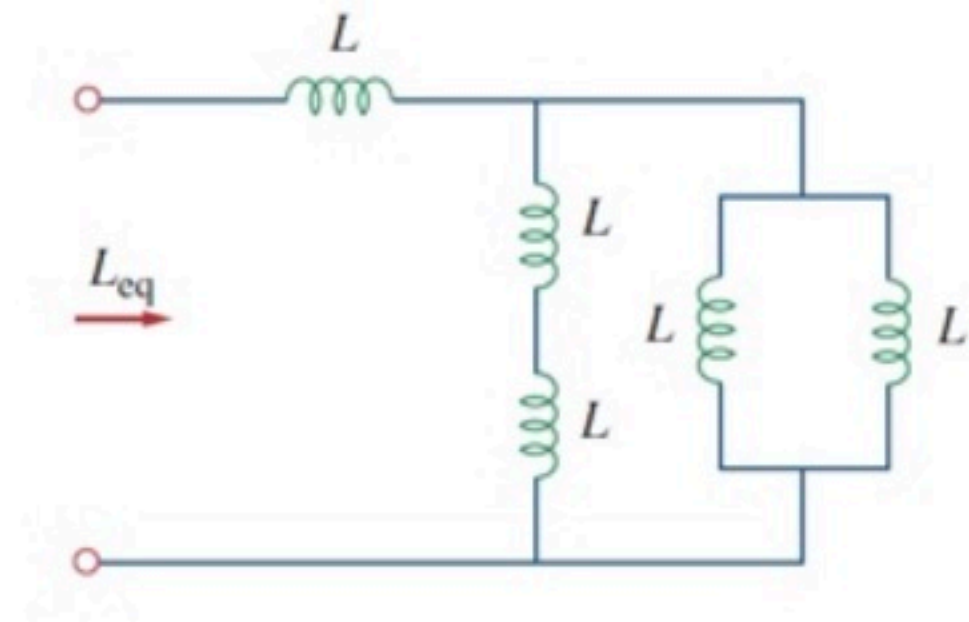


PP Capacitors Inductors 007

Unlimited Attempts.

Find $X = \frac{L_{eq}}{L}$.



Given Variables:

$\therefore \dots$

Calculate the following:

X (H/H) :

1.4



Hint: Series and parallel connection of inductors