
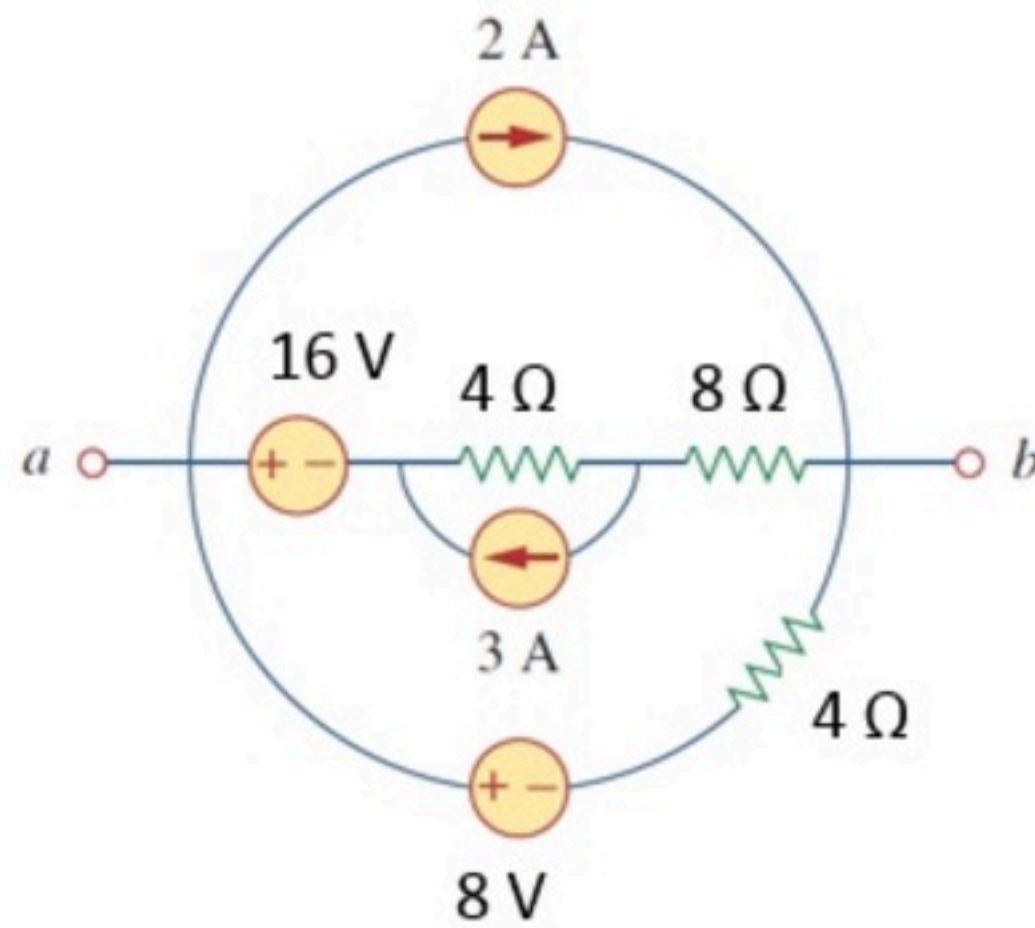


PP Circuit theorems 017

Unlimited Attempts.

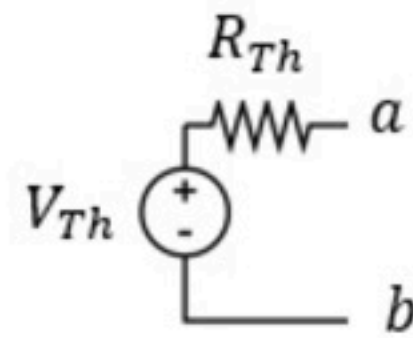Find the Thevenin equivalent model of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

V_{th} (V) :

7



R_{th} (ohm) :

3



Hint: Use superposition to find V_{oc} .