
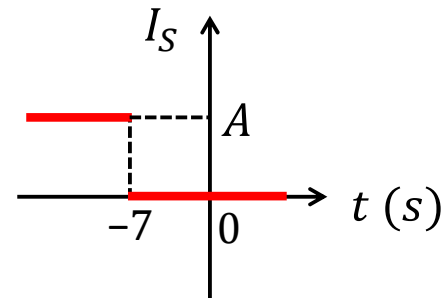


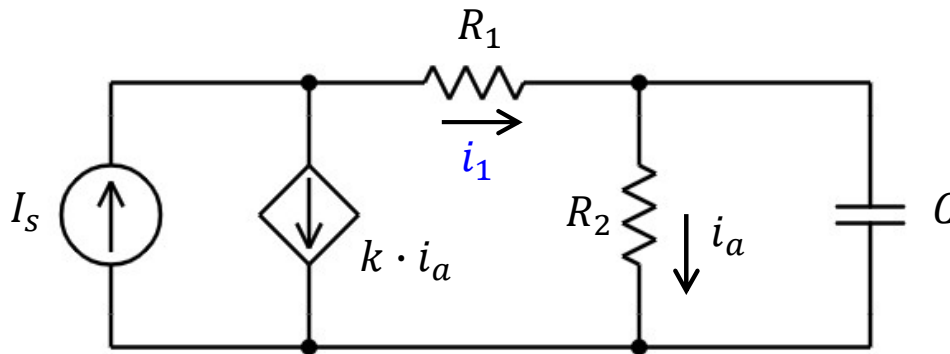The current source I_s changes from A to 0 at $t = -7$ s, as shown on the right. For $t < -7$ s, you may assume the system has reached steady state.



- (a) Find $i_1(-7^- \text{ s})$. (Note: we are asking for i_1 , not i_a)
- (b) Find $i_1(t)$ for $t > -7$ s. Write the equation.


R1: 2Ω
R2: 3Ω
A: 6 A
k: 2 A/A
C: 2 nF



For $t < \frac{\pi}{40}$ s, the switch is open and you may assume the system has reached steady state. The switch closes at $t = \frac{\pi}{40}$ s and remains closed.

(a) Find $v_x \left(\frac{\pi^-}{40} \text{ s} \right)$ (i.e., just before the switch closes)

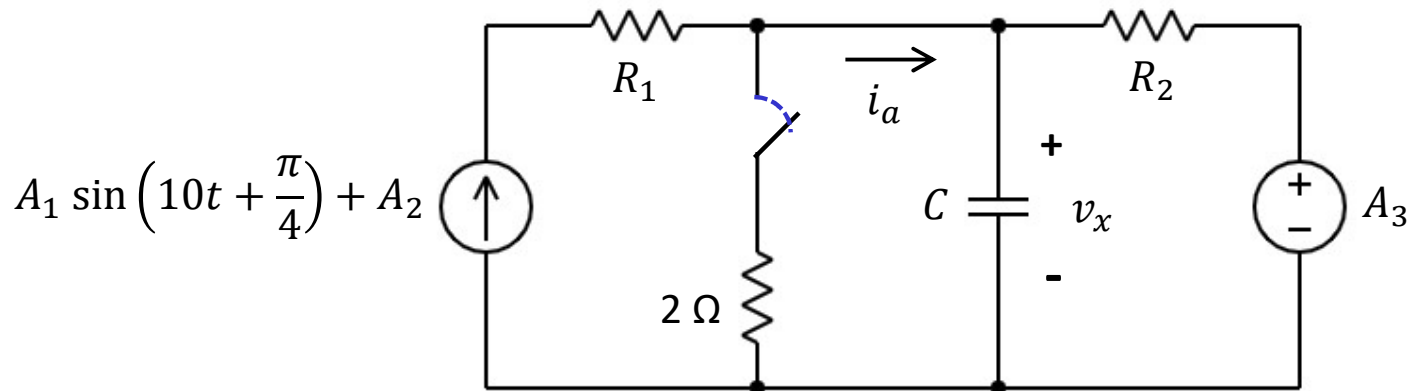(b) Find $i_a \left(\frac{\pi^+}{40} \text{ s} \right)$ (i.e., right after the switch closes)





R1:	1 Ω
R2:	2 Ω
C:	50 mF
A1:	2 A
A2:	2 A
A3:	1 V

The AC circuit below has $\omega = 10 \text{ rad/s}$ and is in steady state. The phasor diagram shows the phasors of v_x and i_a . You are given the angle α and $|V_x|$. The element represented by the rectangular box is either an inductor or a capacitor but you are not told which.

You are also told this piece of information: $v_s = A \sin(\omega t)$ with some unknown value of A (positive or negative).

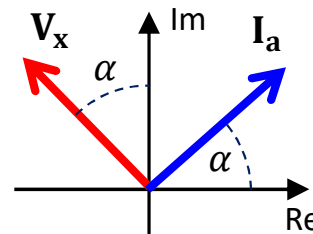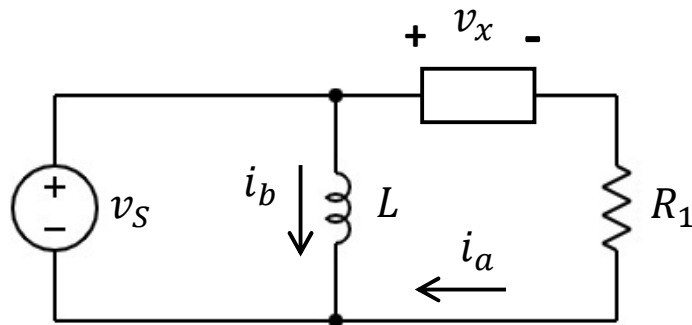- At what time t_0 does the waveform of v_x reach its maximum value? (if there are multiple such times, giving one of them is sufficient).
- What is the mystery element (capacitor or inductor) and why?
- What is the value of i_b at time $T/8$ (with T the period)?



$ V_x $:	3 V
alpha:	60 degrees
R1:	3 Ω
L:	2 H