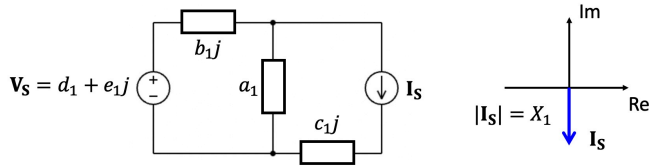


The circuit below represents an AC circuit in steady-state in the phasor domain (for the complex numbers, you may assume units are V, A, Ω , etc. as appropriate). Both sources in the circuit have the same ω , but you are not told the value of ω . Each box represents the impedance of a single circuit element (a resistor, capacitor or inductor).

- What are the maximum value of $v_S(t)$ and $i_S(t)$, called v_{Smax} and i_{Smax} respectively? For v_{Smax} , find Y_1 such that $v_{Smax} = Y_1 \sqrt{2}$.
- We now double ω of both sources but keep everything else the same (such as the capacitor, inductor and resistor values; the amplitude and phase of the sources, etc.). Find the new value of all complex numbers in the circuit (the new value of a_1 is called a_2 , etc.) as well as the new magnitude of the current source $|I_S| = X_2$.



$$a_1 = 50$$

$$b_1 = -20$$

$$c_1 = 10$$

$$d_1 = 1$$

$$e_1 = 1$$

$$X_1 = 5A$$

a. The max value of a sinusoidal waveform is its amplitude

$$v_{S,max} = |V_S| = \sqrt{d_1^2 + e_1^2} = \sqrt{1^2 + 1^2} = \sqrt{2} \Rightarrow Y_1 = 1$$

$$i_{S,max} = |I_S| = X_1 \Rightarrow \boxed{i_{S,max} = 5A}$$

b. Analyze which elements have a dependence on ω

a_1 is the impedance of a resistor $\Rightarrow Z_R = 50$, this has no dependence on ω so if $\omega \rightarrow 2\omega$, $50 \rightarrow 50 \Rightarrow \boxed{a_2 = 50}$

$b_1j \Rightarrow -20j$ is the impedance of a capacitor

$$Z_C = \frac{1}{j\omega C} \Rightarrow \text{if } \omega \rightarrow 2\omega, \text{ then } \frac{1}{j2\omega C} = \frac{1}{2(j\omega C)} = \frac{1}{2} \cdot \frac{1}{j\omega C} = \frac{1}{2} Z_C$$

$$\text{if } \omega \rightarrow 2\omega, \text{ then } -20j \rightarrow \frac{1}{2}(-20j) = -10j \Rightarrow \boxed{b_2 = -10}$$

$c_1j \Rightarrow 10j$ is the impedance of an inductor

$$Z_L = j\omega L \Rightarrow \text{if } \omega \rightarrow 2\omega, \text{ then } j2\omega L = 2(j\omega L) = 2Z_L$$

$$\text{if } \omega \rightarrow 2\omega, \text{ then } 10j \rightarrow 2(10j) = 20j \Rightarrow \boxed{c_2 = 20}$$

$V_S = d_1 + e_1j = 1 + j$ is the phasor for a source $v_S(t) = \frac{\sqrt{2}}{2} \cos(\omega t + \frac{\pi}{4})$

$$\text{if } \omega \rightarrow 2\omega, \text{ then } v_S(t) = \frac{\sqrt{2}}{2} \cos(2\omega t + \frac{\pi}{4}) \Rightarrow V_S = \frac{\sqrt{2}}{2} e^{j\pi/4} = 1 + j \Rightarrow$$

$$\boxed{\begin{matrix} d_2 = 1 \\ e_2 = 1 \end{matrix}}$$

\Rightarrow the phasor for a voltage waveform does not depend on ω

$$\text{Similarly, } i_S(t) = 5 \cos(\omega t - \frac{\pi}{2}) \quad \text{if } \omega \rightarrow 2\omega, i_S(t) = 5 \cos(2\omega t - \frac{\pi}{2}) \Rightarrow \boxed{X_2 = 5A}$$