(a)
$$V_{5} \stackrel{?}{=} \frac{1}{120} = \frac{1}{120}$$

$$V_{ab} = V_{s} \frac{z_{1}}{z_{1+3}} \cdot \frac{-\delta}{2\delta - \delta} = V_{s} \cdot \frac{6j}{6j+3(6+\delta)} \frac{-j}{\delta} = -V_{s} \frac{6j}{18+9j}$$

$$= -\frac{6e^{\frac{3\pi}{2}} \cdot 6j}{9(2+i)} \frac{(2-j)}{(2-\delta)} = \frac{-6j \cdot 6j}{9} \frac{(2-j)}{(4+i)} = \frac{36}{9} \cdot \frac{2-j}{5} = \frac{4}{5}(2-j)$$

$$V_{TH} = V_{ab} = \frac{8}{5} - \frac{4}{5}j$$
 $a = 1.6V$ $b = -0.8V$

(1)
$$\frac{3}{16} = \frac{1}{1+\frac{1}{4}} = \frac{6}{3} = 2-2$$

$$\mathbf{Z}_{TH} = \frac{(2+2j)/(-j)}{(2+2j)/(-j)} = \frac{1}{\frac{1}{2+2j} + \frac{1}{-j}} = \frac{-j(2+2j)}{-j+2+2j} = \frac{2-2j}{2+j}$$

$$= \frac{(2-2j)(2-j)}{(2+j)(2-j)} = \frac{(4-2j-4j-2)}{5} = \frac{2}{5} - \frac{6}{5}j$$

$$Z_{TH} = \frac{2}{5} - \frac{6}{5}i$$
 $C = 0.4 \Omega$ $d = -1.2 \Omega$